Australia $1.25 New Zealand $1.30 Malaysia $4.50

PRACTICAL ELECTRONICS

JULY 1981

65p

1·25

PE QUASAR AM/FM STEREO TUNER

FREE SUPPLEMENT!

Over 20 CIRCUITS TO BUILD

Plus...
DIGITAL PRECISION LIGHT, NOISE and CAPACITANCE METERS

CASE COUPON & DPM OFFER...INSIDE!

Unique in concept—the home computer that grows as you do!

The Acorn Atom

£120

plus VAT and p&p

Also available ready-built

£150

plus VAT and p&p

● The picture shows mixed graphics and characters in three colours

Special features include

- * FULL SIZED KEYBOARD
- * ASSEMBLER AND BASIC
- * TOP QUALITY MOULDED CASE HIGH RESOLUTION COLOUR GRAPHICS*

* optional

The Acorn Atom is a definitive personal computer. Simple to build, simple to operate. A powerful, full facility computer with all the features you would expect.
Just connect the assembled computer to any domestic TV and power source and you are ready to begin. (Power requirement: 8V at 800mA). There is an ATOM power unit available – see the coupon below.

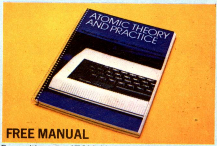

FREE MANUAL

Free with every ATOM, kit or built, is a computer manual. The first section explains and teaches you BASIC, the language that most personal computers and the ATOM operate in. The instructions are simple and learning quickly becomes a pleasure. You'll soon be writing your own programs. The second section is a reference manual giving a full description of the ATOM's facilities and how to use them. Both sections are fully illustrated with example programs.

The standard ATOM includes:

HARDWARE

● Full-sized QWERTY keyboard ● 6502 Microprocessor ● Rugged injection-moulded case ● 2K RAM ● 8K HYPER-ROM ● 23 integrated circuits and sockets ● Audio cassette interface ● UHF TV output ● Full assembly instructions

SOFTWARE

● 32-bit arithmetic (±2,000,000,000) ● High speed execution ● 43 standard/extended BASIC commands ● Variable length strings (up to 256 characters) ● String manipulation functions ● 27 x 32 bit integer variables ● 27 additional arrays ● Random number function ● PUT and GET byte ● WAIT command for timing ● DO-UNTIL construction ● Logical operators (AND, OR, EX-OR) ● Link to machine – code routines ● PLOT commands, DRAW and MOVE

The ATOM modular concept

The ATOM has been designed to grow with you. As you build confidence and knowledge you can add more components. For instance the next stage might be to increase the ROM and RAM on the basic ATOM from 8K + 2K to 12K + 12K respectively. This will give you a direct printer drive, floating point mathematics, scientific and trigonometric functions, high resolution graphics.

From there you can expand indefinitely. Acorn have produced an enormous range of compatible PCB's which can be added to your original computer. For instance: ● A module to give red, green and blue colour signals ● Teletext VDU card (for Prestel and Ceefax information) ● An in-board connector for a communications loop interface – any number of ATOMs may be linked to each other or to a master system with mass storage/hard copy facility ● Floppy disk controller card. For details of these and other additions write to the address below.

ACORN COMPUTER

4a Market Hill,
CAMBRIDGE CB2 3NJ

Your ACORN ATOM may qualify as a business expense. To order complete the coupon below and post to Acorn Computer for delivery within 28 days. Return as received within 14 days for full money refund if not completely satisfied. **All components are guaranteed with full service/repair facility available.**

Please send me the following items:

Quantity	Item		Item price inc. VAT+p&p	TOTALS
	ATOM KIT – 8K ROM + 2K RAM (MIN)		@ £140.00	
	ATOM ASSEMBLED–8K ROM+2K RAM (MIN)		@ £174.50	
	ATOM KIT – 12K ROM + 12K RAM (MAX)		@ £255.00	
	ATOM ASSEMBLED–12K ROM+12K RAM (MAX)		@ £289.50	
	1K RAM SETS		@ £11.22	
	4K FLOATING POINT ROM (inc in 12K Version)		@ £23.30	
	PRINTER DRIVE (inc in 12K version)	6522 VIA	@ £10.35	
		LS244 Buffer	@ £3.17	
	MAINS POWER SUPPLY (1.3 amps)		@ £10.20	
			TOTAL	

To: Acorn Computer Ltd., 4a Market Hill, CAMBRIDGE CB2 3NJ
I enclose cheque/postal order for £
Please debit my Access/Barclaycard No.
Signature
Name (Please print)
Address

Telephone No.
Registered No: 1403810. VAT No: 215 400 220

PE/ /81

BARCLAYCARD VISA

PRACTICAL
ELECTRONICS
VOLUME 17 No. 7 JULY 1981

CONSTRUCTIONAL PROJECTS

PE QUASAR 26
Stereo AM/FM Tuner
CAPACITANCE METER *by Martin Kent* 34
Ranges from 1p to 20µ
LIGHT METER *by Martin Kent* 46
A general purpose instrument with applications in photography, chemistry, medicine and pollution control
NOISE METER *by Martin Kent* 50
Indicates ambient noise levels in the range 60–110dB
INTERFACING COMPUKIT Part 7 *by D. E. Graham* 62
Conclusion

GENERAL FEATURES

COMMUNICATION BY FIBRE OPTICS *by Gary Gardner* 38
A bright future for telephones and TV
SEMICONDUCTOR UPDATE *by R. W. Coles* 42
Featuring iAPX432 U410B
MICROPROMPT 54
Cream of idea soup

NEWS AND COMMENT

EDITORIAL 17
NEWS & MARKET PLACE 18
Including Countdown and Points Arising
INDUSTRY NOTEBOOK *by Nexus* 23
Slimming for health
CB PROPOSALS 24
The low-down from the Home Office
SPECIAL OFFER — DIGITAL PANEL METER 45
For use with all our free case projects
EXTRA CASE COUPON 57
To save you money on another case
PATENTS REVIEW 58
We look at the second of the controversial Carver ideas
READOUT 59
American advice
SPACEWATCH *by Frank W. Hyde* 61
Our resident stargazer celebrates a bi-centenary and the success of the Space Shuttle

SPECIAL 12 PAGE SUPPLEMENT

CIRCUITS SUPPLEMENT
22 designs of diverse appeal (between pages 42 & 43)

OUR AUGUST ISSUE WILL BE ON SALE FRIDAY, 10 JULY 1981
(for details of contents see page 43)

© IPC Magazines Limited 1981. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS, ENGLAND
Tel. Watford (0923) 40588. Telex: 8956095

ALL DEVICES BRAND NEW. FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED (TELEPHONE ORDERS BY ACCESS NOW ACCEPTED Minimum £10·00 please). TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 50p TO ALL ORDERS UNDER £10·00. OVERSEAS ORDERS POSTAGE AT COST.

VAT **Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost incl. p&p.**

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m.–6 p.m. Ample Free Car Parking space available.

POLYESTER CAPACITORS: (Axial Lead type)
400V: 1nF, 1n5, 2n2, 3n3, 4n7, 6n8 **11p;** 10n, 15n, 18n, 22 **12p;** 33n, 47n, 68n **16p;** 100n, 150n **20p;** 220n **30p;** 330n **42p;** 470n **52p;** 680n **60p;** 1µF **68p;** 2µ2, 4µ7 **85p.**
160V: 10nF, 12n, 100n **11p;** 150n, 220n **17p;** 330n, 470n **30p;** 680n **38p;** 1µF **42p;** 1µ5 **45p;** 2µ2 **48p;** 4µ7 **58p.**
1000V: 1nF **17p;** 10nF **30p;** 15n **40p;** 22n **36p;** 33n **42p;** 47n, 100n **50p;** 470n **99p.**

POLYESTER RADIAL LEAD CAPACITORS: 250V;
10n, 15n, 22n, 27n **6p;** 33n, 47n, 68n, 100n **7p;** 150n, 220n **10p;** 330n, 470n **13p;** 680n **19p;** 1µ **23p;** 1µ5 **40p;** 2µ2 **46p.**

ULTRASONIC TRANSDUCERS
40KHz **395p pr.**

ELECTROLYTIC CAPACITORS (Values in µF). **500V:** 10 **52p;** 47 **78p; 250V:** 100 **65p; 63V:** 0·47, 1·0, 1·5, 2·2, 3·3, **8p;** 4·7 **9p;** 6·8, 10 **10p;** 15, 22 **12p;** 33 **15p;** 47 **12p;** 100 **19p;** 1000 **70p; 50V:** 47 **12p;** 68 **20p;** 220 **24p;** 470 **32p;** 2200 **90p; 40V:** 4·7, 15, 22, **9p;** 330 **90p;** 4700 **120p; 25V:** 1·5, 6·8, 10, 22 **8p;** 33 **9p;** 47 **8p;** 100 **11p;** 150 **12p;** 220 **15p;** 330; **22p;** 470 **25p;** 680, 1000 **34p;** 2200 **50p;** 3300 **76p;** 4700 **92p; 16V:** 40, 47, 100 **9p;** 125 **12p;** 220 **13p;** 470 **20p;** 680 **34p;** 1000 **27p;** 1500 **31p;** 2200 **36p;** 3300 **74p;** 4700 **79p.**
TAG-END TYPE: 450V: 100µF **65p; 70V:** 4700 **245p; 64V:** 3300 **198p;** 2200 **139p; 50V:** 3300 **154p;** 2200 **110p; 40V:** 4700 **160p; 25V:** 10,000 **320p;** 15,000 **345p.**

TANTALUM BEAD CAPACITORS:
35V: 0·1µ, 0·22, 0·33 **15p;** 0·47, 0·68, 1·0, 1·5 **16p;** 2·2, 3·3 **18p;** 4·7, 6·8 **22p;** 10 **28p; 16V:** 2·2, 3·3,**16p;** 4·7, 6·8, 10 **18p;** 15 **36p;** 22 **30p;** 33, 47 **40p;** 100 **75p; 10V:** 15, 22 **26p;** 33, 47 **35p;** 100 **55p.**

MYLAR FILM CAPACITORS:
100V: 1nF, 2n, 4n, 4n7, 10 **6p;** 15nF, 22n, 30n, 40, 47 **7p;** 56, 100n, 200 **9p;** 470n/**50V: 12p.**

CERAMIC CAPACITORS: (50V)

Range: 0·5pf to 10nF	**4p**
15nF, 22nF, 33nF, 47nF	**5p**
100nF/30V **7p;** 220nF/6V	**8p**

POLYSTYRENE CAPACITORS:
10pF to 1nF **8p** 1·5nF to 12nF **10p.**

POTENTIOMETERS: Carbon Track, 0·25W Log & Linear Values.

500Ω, 1K & 2K (LIN ONLY) Single	**29p**
5KΩ-2MΩ single gang	**29p**
5KΩ-2MΩ single gang D/P switch	**78p**
5KΩ-2MΩ dual gang stereo	**88p**
1W Wire-wound 50Ω-20K	**115p**

SLIDER POTENTIOMETERS
0·25W log and linear values 60mm track

5KΩ, 500KΩ Single gang	**70p**
10KΩ, 500KΩ Dual gang	**110p**
Self-Stick graduated Alum. Bezels	**36p**

PRESET POTENTIOMETERS

0·1W 50Ω-2·2M Mini Vert. & Horiz.	**7p**
0·25W 100Ω-3·3MΩ Horiz. larger	**10p**
0·25W 250Ω-4·7MΩ Vert.	**10p**
Precision Cermet 1W 100Ω-100K	**90p**

SILVER MICA (pF)

2, 3·3, 4·7, 6·8, 8·2, 10, 12, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180	**15p**
220, 250, 270, 330, 360, 390, 470, 600, 800 & 820pF	**21p**
1000, 1200, 1800	**30p**
3300, 4700	**60p**

TRIMMERS miniature

2-6pF, 2-10pF	**22p**
2-25pF, 5-56pF	**30p**
10-88pF	**35p**

COMPRESSION

3-40pF, 10-80pF	**20p**
20-250pF	**28p**
100-580pF	**39p**
400-1250pF	**48p**

RESISTORS—Erie make 5% carbon Miniature High Stability, Low Noise.

	RANGE	Val.	1-99	100+
0·25W	2Ω2-4·M7	E24	**2p**	**1p**
0·5W	2Ω2-4·M7	E12	**2p**	**1p**
1W	2Ω2-10M	E12	**5p**	**3p**
2% Metal Film 10Ω-1M			**6p**	**4p**
1% 0·5W 51Ω-1M24			**8p**	**6p**

100+ price applies to Resistors of each type not mixed values.

TRANSISTORS

AC107	**35**
AC125	**35**
AC126	**25**
AC127/8	**25**
AC141	**30**
AC142	**30**
AC176	**28**
AC187	**28**
AC188	**30**
ACY17	**70**
ACY18	**70**
ACY19	**75**
ACY20	**75**
ACY21	**75**
ACY22	**60**
ACY28	**75**
AD149	**79**
AD161/2	**42**
AF118	**95**
AF139	**40**
AF178	**75**
BC107	**10**
BC107B	**12**
BC108	**10**
BC108B	**12**
BC108C	**12**
BC109	**10**
BC109B	**12**
BC109C	**12**
BC117/8	**20**
BC140	**30**
BC142	**30**
BC143	**30**
BC147	**9**
BC147B	**10**
BC148	**9**
BC148B	**10**
BC148C	**10**
BC149	**9**
BC149C	**12**
BC153/4	**27**
BC157/8	**10**
BC159	**11**
BC160	**45**
BC167A	**10**
BC168C	**10**
BC169C	**10**
BC170	**15**
BC171/2	**11**
BC173	**11**
BC177/8	**20**
BC179	**20**
BC181	**20**
BC182/3	**10**
BC184	**10**
BC182L	**10**
BC183L	**10**
BC184L	**10**
BC187	**26**
BC212	**10**
BC212L	**10**
BC213	**10**
BC213L	**10**
BC214	**10**
BC214L	**10**
BC237/8	**14**
BC307B	**14**
BC308B	**16**
BC327	**15**
BC328	**15**
BC337/8	**15**
BC441	**34**
BC461	**34**
BC477/8	**40**
BC516	**40**
BC517	**40**
BC547/8	**14**
BC549C	**14**
BC556/7	**15**
BC558/9	**15**
BCY70	**16**
BCY71	**18**
BCY72	**20**
BD121	**95**
BD124	**115**
BD131	**48**
BD132	**48**
BD133	**60**
BD135	**45**
BD136/7	**40**
BD138/9	**40**
BD140	**40**
BD144	**198**
BD205	**110**
BD245	**45**
BD378	**70**
BD434	**55**
BD517	**75**
BD695A	**85**
BD696A	**85**
BDY56	**180**
BDY60	**160**
BF115	**35**
BF167	**29**
BF173	**27**
BF177	**25**
BF178	**30**
BF179	**35**
BF180	**38**
BF194/5	**12**
BF196/7	**12**
BF198	**16**
BF199	**18**
BF200	**30**
BF224	**25**
BF244A	**28**
BF244B	**29**
BF256B	**35**
BF257/8	**32**
BF259	**35**
BF274	**42**
BF336	**40**
BF451	**35**
BF594	**30**
BF595	**39**
BF910	**95**
BFR39	**23**
BFR40	**23**
BFR41	**23**
BFR79	**23**
BFR80	**25**
BFR81	**25**
BFR98	**105**
BFX29	**28**
BFX84	**26**
BFX85/86	**28**
BFX87/88	**28**
BFY50	**23**
BFY51	**23**
BFY52	**23**
BFY56	**32**
BFY64	**35**
BFY81	**120**
BFY90	**80**
BRY39	**40**
BSX20	**20**
BSX29	**34**
BSY95A	**25**
BU105	**170**
BU108	**240**
BU109	**210**
BU205	**190**
BU206	**200**
BU208	**200**
E421	**250**
MD8001	**250**
MJ2955	**90**
MJE340	**54**
MJE370	**100**
MJE371	**100**
MJE520	**95**
MJE2955	**99**
MJE3055	**70**
MPF102	**66**
MPF103	**36**
MPF104	**36**
MPF105	**36**
MPF106	**40**
MPSA05	**25**
MPSA06	**25**
MPSA12	**32**
MPSA55	**30**
MPSA56	**30**
MPSA70	**30**
MPSU02	**58**
MPSU05	**55**
MPSU06	**55**
MPSU52	**65**
MPSU55	**60**
MPSU56	**60**
OC23/26	**170**
OC28	**130**
OC36	**120**
OC41/42	**120**
OC44	**120**
OC45	**40**
OC70	**40**
OC71	**40**
OC72	**40**
OC76	**50**
OC81	**50**
OC82	**50**
OC83	**40**
OC84	**40**
OC170	**85**
OC171	**85**
OC200	**85**
TIP29A	**36**
TIP29B	**56**
TIP29C	**60**
TIP30A	**48**
TIP30B	**50**
TIP30C	**58**
TIP31A	**45**
TIP31C	**55**
TIP32A	**48**
TIP32C	**60**
TIP33A	**65**
TIP33C	**78**
TIP34A	**74**
TIP34C	**88**
TIP35A	**160**
TIP35C	**185**
TIP36A	**170**
TIP36C	**199**
TIP41A	**55**
TIP41B	**60**
TIP42A	**60**
TIP42B	**75**
TIP120	**90**
TIP121	**99**
TIP141	**120**
TIP142	**120**
TIP147	**120**
TIP2955	**60**
TIP3055	**60**
TIS43	**32**
TIS44	**45**
TIS45	**45**
TIS48	**50**
TIS88A	**50**
TIS90	**30**
TIS91	**32**
TIS93	**32**
UC734	**65**
ZTX107	**11**
ZTX108	**11**
ZTX109	**12**
ZTX212	**28**
ZTX300	**13**
ZTX301	**16**
ZTX302	**16**
ZTX303	**25**
ZTX304	**17**
ZTX314	**25**
ZTX320	**30**
ZTX326	**30**
ZTX341	**30**
ZTX500	**14**
ZTX501	**15**
ZTX502	**15**
ZTX503	**18**
ZTX504	**25**
ZTX531	**25**
ZTX550	**25**
2N696	**30**
2N697	**23**
2N698	**40**
2N699	**48**
2N706A	**19**
2N708	**19**
2N914/5	**32**
2N918	**35**
2N930	**20**
2N1131/2	**24**
2N1303	**60**
2N1304	**65**
2N1305	**60**
2N1307	**65**
2N1308	**68**
2N1613	**30**
2N1671B	**160**
2N2160	**295**
2N2219A	**28**
2N2220A	**26**
2N2221A	**26**
2N2222A	**25**
2N2369A	**18**
2N2646	**45**
2N2846	**80**
2N2904	**28**
2N2905A	**26**
2N2906	**26**
2N2907A	**26**
2N2926G	**10**
2N3053	**26**
2N3054	**58**
2N3055	**48**
2N3442	**140**
2N3565	**15**
2N3614	**199**
2N3615	**199**
2N3663	**15**
2N3702/3	**10**
2N3704/5	**10**
2N3706/7	**10**
2N3708/9	**10**
2N3710	**10**
2N3711	**10**
2N3771	**179**
2N3772	**195**
2N3773	**270**
2N3819	**22**
2N3820	**45**
2N3822/3	**65**
2N3866	**90**
2N3903/4	**18**
2N3905	**15**
2N3906	**17**
2N4037	**46**
2N4058	**10**
2N4061	**10**
2N4062	**10**
2N4069	**45**
2N4427	**80**
2N4859	**78**
2N4871	**55**
2N5135/6	**20**
2N5138	**18**
2N5172	**18**
2N5179	**45**
2N5180	**45**
2N5191	**75**
2N5194	**80**
2N5305	**24**
2N5457	**36**
2N5458	**36**
2N5459	**36**
2N5485	**36**
2N5777	**45**
2N6027	**32**
2N6109	**60**
2N6290	**70**
2SA715	**60**
2SC495	**70**
2SC496	**70**
2SC1096	**85**
2SC1173	**125**
2SC1306	**150**
2SC1307	**220**
2SC1449	**85**
2SC1678	**140**
2SC1923	**50**
2SC1945	**225**
2SC1953	**90**
2SC1957	**90**
2SC1969	**198**
2SC2028	**85**
2SC2029	**180**
2SC2078	**155**
2SC2091	**85**
2SC2314	**85**
2SC2166	**165**
2SC1679	**190**
2SD234	**75**
3N128	**112**
3N140	**112**
40250	**85**
40251	**97**
40311	**60**
40313	**130**
40315	**60**
40316	**95**
40317	**60**
40320	**60**
40360	**40**
40361	**50**
40362	**50**
40406	**75**
40407	**60**
40408	**70**
40411	**285**
40412	**65**
40467	**130**
40468	**85**
40594	**105**
40595	**110**
40603	**110**
40636	**175**
40673	**95**

ANTEX
Solderin
Irons

C15W	3
CX17W	3
CCN15W	3
X25W	3
Spare bits	
Elements	1
Iron stand	1

DIL SOCKETS (TEXAS) Low profile

8 pin	**8p**
14 pin	**10p**
16 pin	**10p**
18 pin	**16p**
20 pin	**22p**
22 pin	**25p**
24 pin	**25p**
28 pin	**35p**
36 pin	—
40 pin	**30p**

SPECIAL OF

	1+
741	**15p**
NE555	**18p**
2114L-3	**135p**
2114L-2	**150p**
2532	**£8**
2708	**250p**
2716	**295p**
4116	**150p**
2114-45	**125p**
4027	**250p**

Access

LINEAR IC's

702	**75**
709C 8 pin	**35**
710	**67**
741	**15**
747C 14 pin	**78**
748C 8 pin	**36**
753 8 pin	**185**
810	**159**
9400CJ	**350**
AY-1-0212	**675**
AY-1-1313A	**660**
AY-1-1320	**225**
AY-1-5050	**99**
AY-1-5051	**160**
AY-3-1270	**840**
AY-3-8500	**390**
AY-3-8910	**770**
AY-3-8912	**650**
AY-5-1224A	**235**
AY-5-1230	**450**
AY-5-1317A	**630**
AY-5-8100	**775**
CA3011	**110**
CA3012	**175**
CA3014	**157**
CA3019	**70**
CA3020	**186**
CA3023	**191**
CA3028A	**80**
CA3035	**235**
CA3036	**115**
CA3043	**275**
CA3045	**365**
CA3046	**70**
CA3048	**214**
CA3059	**195**
CA3075	**213**
CA3080E	**65**
CA3081	**190**
CA3089E	**215**
CA3090AQ	**375**
CA3123	**150**
CA3130	**90**
CA3140	**48**
CA3160	**95**
CA3189	**295**
ICL7106	**795**
ICL7107	**975**
ICL8038CC	**340**
ICL8211	**150**
ICM7205	**1150**
ICM7207	**475**
ICM7215	**1050**
ICM7216A	**1950**
ICM7216B	**1950**
ICM7217A	**790**
ICM7224	**785**
LD130	**452**
ICM7555	**85**
LF351	**48**
LF356	**90**
LM10	**395**
LM301A	**26**
LM308	**95**
LM311	**70**
LM318	**200**
LM324	**50**
LM339	**68**
LM348	**90**
LM349	**115**
LM358	**50**
LM379	**415**
LM380	**80**
LM381N	**145**
LM382	**125**
LM384	**140**
LM386	**99**
LM387	**120**
LM389	**99**
LM733	**75**
LM2917	**195**
LM3900	**60**
LM3909	**70**
LM3911	**125**
LM3914	**240**
LM3915	**240**
LM3916	**255**
LM13600	**135**
LS7220	**280**
M252AA	**625**
M253AA	**1150**
MC1303	**88**
MC1304P	**260**
MC1310P	**150**
MC1445	**150**
MC1458	**45**
MC1494	**694**
MC1495	**350**
MC1496L	**92**
MC1596	**225**
MC1648	**290**
MC1709G	**90**
MC1710	**79**
MC3302	**150**
MC3340P	**120**
MC3360P	**120**
MC3401	**52**
MC3403	**135**
MC3405	**150**
MFC6040	**97**
MK50398	**635**
MM5303	**635**
MM5307	**1275**
MM57160	**575**
MSM5526	**820**
NE529	**225**
NE543	**210**
NE544	**185**
NE555	**18**
NE556DB	**55**
NE560	**325**
NE561	**395**
NE562B	**410**
NE564	**435**
NE565A	**120**
NE566	**180**
NE567	**170**
NE570	**450**
NE571	**420**
RC4136D	**69**
S566B	**265**
SAB3209	**425**
SAB3210	**275**
SG3402	**295**
SN76003N	**240**
SN76013N	**170**
SN76018	**148**
SN76023N	**170**
SN76033N	**195**
SN76115N	**215**
SN76131	**125**
SN76227N	**95**
SN76477	**175**
SP8629	**299**
TAA621AX1	**250**
TAA661A	**155**
TAD100	**159**
TBA120S	**70**
TBA550Q	**330**
TBA641-A12/ BX1 or BX11	**250**
TBA651	**190**
TBA800	**90**
TBA810S	**95**
TBA820	**70**
TBA920Q	**260**
TCA965	**120**
TDA1004	**290**
TDA1008	**310**
TDA1022	**575**
TDA1024	**105**
TDA1490	**290**
TDA2020	**320**
TDA2030	**300**
TL061	**46**
TL064CN	**159**
TL071CP	**45**
TL072CP	**70**
TL074CN	**125**
TL081CP	**42**
TL083CP	**95**
TL084CP	**105**
UAA170	**170**
UAA180	**170**
XR2206	**320**
XR2211	**575**
XR2266	**750**
ZN414	**95**
ZN423	**195**
ZN424E	**130**
ZN425E	**350**
ZN427	**625**
ZN1034E	**200**
ZN1040E	**685p**

COMPUTER IC's

2114-450	**125**
2114L-300n	**135**
2114L-200n	**150**
2532-32K	**£8**
2708	**250**
2716-5V	**300**
2732-450n	**£8**
4116	**140**
6502	**550**
6503	**850**
6505	**795**
6520	**325**
6522	**570**
6532	**795**
6545	**1450**
6551	**785**
6592	**£27**
6800	**375**
6802	**550**
6809	**1475**
6810	**175**
6821	**190**
6840	**470**
6850	**190**
6852	**390**
8080A	**450**
8085A	**990**
81LS95	**99**
81LS96	**99**
81LS97	**99**
8212	**210**
8214	**425**
8216	**200**
8251	**475**
8253	**899**
8255	**425**
8257	**800**
8T26A	**150**
8T28A	**150**
8T31	**350**
8T95N	**160**
8T97N	**150**
AY-3-1015	**395**
AY-5-1013	**375**
AY-5-2376	**750**
MC1488	**75**
MC1489	**75**
MC14411	**950**
MC14412	**1100**
RO-3-2513U	**600**
SFF96364E	**950**
SFC71301	**820**
TMS2716-3V	**1050**
TMS4027	**250**
TMS6011	**365**
Z80CPU 2·5	**525**
Z80ACPU 4M	**650**
Z80 P10	**475**
Z80A P10	**550**
Z80 CTC	**475**
Z80A CTC	**550**
Z80S10–1	**£19**
Z80AS10	**£24**
Z80 DART	**£12**
Z80A DART	**£15**
74S132	**138**
74S138	**240**
74S188	**210**
74S189	**158**
74S194	**360**
74S241	**540**
74S262	**850**
74S287	**325**
74S288	**210**
74S470	**325**
74S472	**1150**
74S475	**825**
75150	**140**
75154	**150**
75450	**95**
75451/2	**70**
75454	**225**
75491/2	**89**

TTL 74
(TEXAS)

7400	**11**
7401	**11**
7402	**11**
7403	**14**
7404	**14**
7405	**18**
7406	**36**
7407	**36**
7408	**17**
7409	**20**
7410	**17**
7411	**25**
7412	**20**
7413	**32**
7414	**38**
7416	**30**
7417	**30**
7420	**19**
7421	**38**
7422	**25**
7423	**28**
7425	**28**
7426	**43**
7427	**32**
7428	**35**
7430	**19**
7432	**27**
7433	**36**
7437	**35**
7438	**32**
7440	**20**
7441	**68**
7442	**58**
7443	**120**
7444	**116**
7445	**105**
7446	**132**
7447	**72**
7448	**75**
7450	**20**
7451	**20**
7453	**20**
7454	**20**
7460	**20**
7470	**40**
7472	**30**
7473	**35**
7474	**34**
7475	**56**
7476	**40**
7480	**52**
7481	**120**
7482	**75**
7483	**90**
7484	**99**
7485	**105**
7486	**33**
7489	**205**
7490	**42**
7491	**84**
7492	**50**
7493	**57**
7494	**85**
7495	**70**
7496	**80**
7497	**176**
74100	**130**
74104	**62**
74105	**62**
74107	**34**
74109	**60**
74110	**54**
74111	**68**
74112	**170**
74116	**170**
74118	**85**
74119	**120**
74120	**75**
74121	**35**
74122	**50**
74123	**65**
74125	**50**
74126	**45**
74128	**45**
74132	**55**
74136	**55**
74141	**75**
74142	**185**
74143	**250**
74144	**250**
74145	**90**
74147	**150**
74148	**125**
74150	**130**
74151	**70**
74153	**70**
74154	**120**
74155	**75**
74156	**75**
74157	**70**
74159	**165**
74160	**99**
74161	**99**
74162	**99**
74163	**99**
74164	**120**
74165	**120**
74166	**130**
74167	**205**
74170	**205**
74172	**375**
74173	**110**
74174	**100**
74175	**82**
74176	**80**
74177	**85**
74178	**110**
74179	**150**
74180	**90**
74181	**280**
74182	**85**
74184	**130**
74185	**130**
74188	**310**
74190	**130**
74191	**120**
74192	**120**
74193	**120**
74194	**102**
74195	**75**
74196	**99**
74197	**88**
74198	**160**
74199	**150**
74221	**150**
74246	**150**
74247	**151**
74248	**189**
74249	**189**
74251	**110**
74265	**66**
74273	**267**
74278	**249**
74279	**99**
74283	**149**
74284	**350**
74285	**350**
74290	**107**
74293	**135**
74297	**236**
74298	**185**
74365	**95**
74366	**95**
74367	**95**
74368	**95**
74390	**185**
74393	**185**
74490	**185**

74LS

LS00	**13**
LS01	**13**
LS02	**15**
LS03	**15**
LS04	**16**
LS05	**23**
LS08	**22**
LS09	**23**
LS10	**20**
LS11	**32**
LS12	**32**
LS13	**40**
LS14	**60**
LS15	**40**
LS20	**21**
LS21	**32**
LS22	**35**
LS26	**44**
LS27	**35**
LS28	**35**
LS30	**20**
LS32	**25**
LS33	**35**
LS37	**30**
LS38	**35**
LS40	**28**
LS42	**66**
LS47	**85**
LS48	**105**
LS49	**105**
LS51	**25**
LS54	**30**
LS55	**30**
LS63	**150**
LS73	**45**
LS74	**35**
LS75	**45**
LS76	**45**
LS78	**50**
LS83	**105**
LS85	**80**
LS86	**38**
LS90	**50**
LS91	**125**
LS92	**75**
LS93	**60**
LS95	**115**
LS96	**120**
LS107	**45**
LS109	**75**
LS112	**40**
LS113	**75**
LS114	**40**
LS122	**70**
LS123	**75**
LS124	**180**
LS125	**45**
LS126	**45**
LS132	**60**
LS133	**35**
LS136	**55**
LS138	**62**
LS139	**70**
LS145	**120**
LS147	**210**
LS148	**170**
LS151	**90**
LS153	**85**
LS154	**200**
LS155	**75**
LS157	**70**
LS158	**70**
LS160	**90**
LS161	**98**
LS162	**110**
LS163	**95**
LS164	**115**
LS165	**145**
LS166	**175**
LS168	**210**
LS169	**210**
LS170	**288**
LS173	**105**
LS174	**110**
LS175	**110**
LS181	**295**
LS183	**298**
LS189	**128**
LS190	**95**
LS191	**95**
LS192	**95**
LS193	**99**
LS194	**125**
LS195	**130**
LS196	**120**
LS197	**85**
LS200	**345**
LS202	**345**
LS221	**120**
LS240	**165**
LS241	**165**
LS242	**165**
LS243	**165**
LS244	**150**
LS245	**145**
LS247	**135**
LS248	**135**
LS249	**135**
LS251	**130**
LS253	**95**
LS257	**95**
LS258	**120**
LS259	**160**
LS261	**450**
LS266	**75**
LS273	**180**
LS275	**320**
LS279	**88**
LS280	**250**
LS283	**90**
LS290	**130**
LS295	**215**
LS298	**130**
LS299	**420**
LS300	**175**
LS302	**175**
LS323	**270**
LS321	**450**
LS324	**200**
LS325	**320**
LS326	**330**
LS327	**315**
LS346	**185**
LS347	**150**
LS348	**190**
LS352	**185**
LS353	**185**
LS365	**65**
LS366	**65**
LS367	**65**
LS368	**90**
LS373	**150**
LS374	**150**
LS375	**150**
LS377	**199**
LS378	**140**
LS379	**215**
LS384	**250**
LS385	**420**
LS386	**85**
LS390	**140**
LS393	**140**
LS395	**210**
LS396	**199**
LS398	**275**
LS399	**230**
LS445	**140**
LS447	**195**
LS490	**245**
LS668	**105**
LS669	**105**
LS670	**270**
LS673	**750**
LS674	**850**

CMOS

4000	**14**
4001	**14**
4002	**15**
4006	**86**
4007	**19**
4008	**76**
4009	**46**
4010	**50**
4011	**18**
4012	**24**
4013	**43**
4014	**80**
4015	**82**
4016	**35**
4017	**70**
4018	**76**
4019	**42**
4020	**85**
4021	**90**
4022	**85**
4023	**24**
4024	**60**
4025	**24**
4026	**170**
4027	**45**
4028	**92**
4029	**98**
4030	**55**
4031	**185**
4032	**125**
4033	**175**
4034	**213**
4035	**95**
4036	**275**
4037	**115**
4038	**110**
4039	**299**
4040	**85**
4041	**80**
4042	**70**
4043	**80**
4044	**80**
4045	**175**
4046	**96**
4047	**98**
4048	**65**
4049	**35**
4050	**38**
4051	**86**
4052	**86**
4053	**86**
4054	**130**
4055	**130**
4056	**135**
4059	**575**
4060	**110**
4061	**1225**
4062	**995**
4063	**120**
4066	**46**
4067	**430**
4068	**26**
4069	**22**
4070	**25**
4071	**25**
4072	**25**
4073	**25**
4075	**23**
4076	**85**
4077	**30**
4078	**28**
4081	**26**
4082	**25**
4085	**90**
4086	**90**
4089	**150**

CMOS (CONT.)

4093
4094
4095
4096
4097
4098
4099
4160
4161
4162
4163
4174
4175
4194
4408
4409
4410
4411
4412F
4415F
4419
4422
4432
4433
4435
4440
4450
4451
4452
4490
4500
4501
4502
4503
4506
4507
4508
4510
4511
4512
4513
4514
4515
4516
4517
4518
4519
4520
4521
4522
4526
4527
4528
4529
4530
4531
4532
4534
4536
4538
4539
4541
4543
4549
4553
4554
4555
4556
4557
4558
4559
4560
4561
4562
4566
4568
4569
4572
4580
4581
4582
4583
4584
4585
4599
40097
40106
40161
40174
40193

15
15
24
12
12
250
40
12
12
15
15
8
8
8
8
8
4
5
2 5
6
5 6
7 7
4
15
16
17
19
9
9
40
50
65

rs
OV 32
58
70
38
40
48
60
95
V 78
V 95
V188
150
180
38
24
29
35
32
38
130

Insertion Force SOCKETS
£6.50; 28 way **£8.20;** 40 way **£9.75**

BRIDGE RECTIFIERS
(plastic case)

1A/50V	**20**
1A/100V	**22**
1A/400V	**29**
1A/600V	**34**
2A/50V	**35**
2A/200V	**40**
2A/400V	**46**
2A/600V	**65**
6A/100V	**83**
6A/400V	**95**
6A/600V	**125**
10A/200V	**215**
10A/600V	**350**
25A/200V	**240**
25A/600V	**395**
BY164	**56**
VM18	**50**

ZENERS
Range: 2V7 to 39V 400mW **8p each**
Range: 3V3 to 33V 1·3W **15p each**

VARICAPS

MVAM2	**165**
MVAM115	**158**
BA102	**30**
BB105B	**40**
BB106	**40**

Noise Diode
Z5J **195**

TRIACS

3A/100V	**48**
3A/400V	**56**
3A/800V	**85**
8A/100V	**60**
8A/400V	**69**
8A/800V	**115**
12A/100V	**78**
12A/400V	**82**
12A/800V	**135**
16A/100V	**103**
16A/400V	**105**
16A/800V	**220**
25A/400V	**185**
25A/800V	**295**
25A/1000V	**480**
30A/400V	**525**
T2800D	**120**

DIAC
ST2 **25**

SPEAKERS

8Ω 0·3W 2"; 2¼"; 2½"; 3"	**80**
40Ω 2·5"	**80**
64Ω 2·5"	**80**
80Ω 2·5"	**80**
8×5" 8Ω 6W HF Cone	**425**

Piezo Tweeters Xovers etc. available.

ALUM.BOXES

3×2×1"	**65**
4×2½×2"	**85**
4×2¾×2½"	**103**
5×4×2	**105**
5×2¾×1½"	**90**
5×2¾×2½"	**130**
5×4×1½"	**99**
5×4×2½"	**120**
6×4×2"	**120**
7×5×3"	**180**
8×6×3"	**210**
10×7×3"	**275**
12×5×3"	**260**
12×8×3"	**295**

OPTO ELECTRONICS
LEDS including Clips

TIL209 Red 125"	**13**
TIL211 Green 125"	**18**
TIL212 Yellow	**18**
TIL220 ·2" Red	**15**
0·2" Yel, Grn, Amber	**18**
Red, Green and Yellow Rectangular LEDS.	**29**
Triangular LEDs R&G	**18**
0·2" Flashing LED Red	**55**
0·2" Red/green LED	**65**
0·2" Red High Bright	**59**
2N5777 **45;** OCP71	**120**
ORP12	**86**
LD271 Infra Red (emit)	**46**
TIL32 Infra Red (emit)	**58**
SFH205 (detector)	**91**
TIL78 (detector)	**60**

7 Segment Displays

TIL321 ·5" C.An	**115**
TIL322 ·5" C.th	**115**
DL704 ·3" C.Cth	**99**
DL707 ·3" C.Anod	**99**
DL747 ·6" C.Cathod.	**180**
·8" Orange C.A.	**250**
FND357 or 500	**120**
·3" Green C.A.	**140**
±1·3" Red or Green	**150**
Bargraph 10 seg. Red	**225**

Liquid Crystal Display
3½ digit **675p;** 4 digit **750p**
6 Digit LCD **850p**

VEROBOARDS 0·1"

	Clad	Plain
2½×3¾"	**73p**	**52p**
2½×5"	**83p**	—
3¾×3¾"	**83p**	—
3¾×5"	**95p**	**79p**
3¾×17"	**326p**	**211p**
4¾×18"	**426p**	—
Pkt. of 100 pins		**50p**
Spot Face Cutter		**118p**
Pin Insertion Tool		**162p**

'VQ' Board	**150p**
'DIP' Board	**330p**
Vero Strip	**144p**
S100 Board	**£14**

PROTO-DECs

Veroblock	**375p**
S-Dec	**350p**
Eurobreadboard	**520p**
Bimboard 1	**785p**
Superstrip SS2	**998p**

VERO WIRING PEN and Spool **310p**
Spare Wire (Spool) **75p;** Combs **6p** ea.

FERRIC CHLORIDE
1 lb bag Anhydrous
195p + 50p p&p

DALO ETCH RESIST
Pen + Spare tip **90p**

ALFAC TRANSFERS
Etch Resist.
Full range available:
35p a sheet

COPPER CLAD BOARDS

Fibre Glass	Single-sided	Double-sided	SRBP 9·5"×8·5"
6"×6"	**90p**	**110p**	**95p**
6"×12"	**150p**	**196p**	

SOLDERCON PINS
100 pins **60p** 500 pins **275p**

VOLTAGE REGULATORS

1A	T03	+ve		−ve	
5V	7805	**145p**		7905	**220p**
12V	7812	**145p**		7912	**220p**
15V	7815	**145p**		7915	**220p**
18V	7818	**150p**			—
1A	T0220 Plastic Casing				
5V	7805	**60p**		7905	**65p**
12V	7812	**60p**		7912	**65p**
15V	7815	**60p**		7915	**65p**
18V	7818	**60p**		7918	**65p**
24V	7824	**60p**			
100mA	T092 Plastic Casing				
5V	78L05	**30p**		79L05	**65p**
6V	78L62	**30p**			—
8V	78L82	**30p**			—
12V	78L12	**30p**		79L12	**65p**
15V	78L15	**30p**		79L15	**65p**

CA3085	**95**
LM300H	**170**
LM304H	**160**
LM305H	**140**
78H05 5V/5A	**550p**
78HG+5 to +24V 5A	**650p**
79HG −2.25V to −24V 5A	**850p**

LM309K	**135**
LM317H	**240**
LM317K	**350**
LM323K	**625**
LM325N	**240**
LM326N	**240**
LM327N	**270**
LM723	**35**
TBA625B	**75**

SWITCHES

SLIDE 250V

1A DPDT	**14**
1A DPDT C/OFF	**15**
½A DP on/on/on	**40**

TOGGLE 2A 250V

SPST	**33**
DPDT	**44**
4 pole on off	**54**

PUSH BUTTON
Spring loaded
Latching or Momentary 6A

SPDT c/over	**99**
DPDT c/over	**145**

MINIATURE
Non Locking

Push to make	**15p**
Push break	**25p**

SUB-MIN TOGGLE

SP changeover	**60**
SPST on off	**54**
SPDT c/off	**85**
SPDT Biased	**105**
DPDT 6 tags	**75**
DPDT C/OFF	**88**
DPDT Biased	**145**
3 pole c/over	**205**

ROCKER: 5A, 250V, SPST **28p**
ROCKER: (white) 10A 250V SPDT changeover **38p**
ROCKER: With neon lights red when on. 10A 250V, DPST **85p**
ROCKER: (White) 10A/250V DPDT **72p**

ROTARY: "Make-A-Switch" Make your own multiway Switch as required. Shafting assembly has adjustable stop.
Accommodates up to 6 Wafers **90p**
Break before make Wafers. Silver contacts. 1 pole/12 way; 2 pole/6 way; 3 pole/4 way; 4 pole/3 way; 6 pole/2 way **65p**
Mains DPST Switch to fit **45p**
Screen & Spacers **6p**

ROTARY: (Adjustable Stop Type)
1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way **45p**

ROTARY: Mains 250V AC, 4 Amp **56p**

CRYSTALS

100KHz	**300**
455KHz	**370**
1MHz	**295**
1·008M	**295**
1·8432M	**300**
2·0MHz	**305**
2·4576M	**305**
3·2768M	**290**
3·57954M	**150**
4·0MHz	**290**
4·032M	**290**
4·194304M	**270**
4·433619M	**150**
5·0MHz	**290**
5·185M	**300**
5·24288M	**390**
6·0MHz	**290**
6·144M	**295**
6·5536M	**290**
7·168M	**290**
7·68MHz	**300**
8·0MHz	**290**
8·867237MHz	**270**
10·0MHz	**290**
10·7MHz	**270**
12·0MHz	**290**
14·31818M	**320**
16·0MHz	**290**
18·0MHz	**290**
18·432M	**290**
26·69M	**290**
27·648M	**330**
38·66667MHz	**290**
48·0MHz	**270**
100·0MHz	**375**

COMPUTER CORNER

- **SUPERBOARD II:** (Series II New Version) Ready-built and tested; 50Hz. **Only £149**
- **PSU** 5V/3A for above **£18**
- **Plastic Case for Superboard,** fits UK101, NASCOM etc. **£25**
- **Space Invaders for Superboard** (4K) **£5**
- **UK101 New Issue Compukit.** Complete kit **Only £149**
- **4K Memory** (8×2114) **£10**
- **SEIKOSHA GP80A.** Unihammer, 80 column impact matrix printer. Light weight (2·5Kgs) Now being offered at a rediculously low price of **Only £195**
- **EPSON TX80** 80 column dot matrix printer available in tractor feed or friction feed. **£235**
- **VIDEO GENIE** based on TRS80 16K RAM NEW VERSION **Only: £289**
- **SOFTY.** Intelligent EPROM Programmer Kit **£99**
  Ready-Built & Tested **£120**
  PSU for above (Built) **£20**
- **TEX UV EPROM** Eraser. Erases up to 32 ICs in 15-30 min. **£33**
- **UHF MODULATOR** 6MHz **280p**
  UHF MODULATOR 8MHz **450p**
- **KEYPADS** 4×4 matrix **350p**
- **Model 756 ASCII** Keyboard **£40**
- **10×C12 Cassettes** in stockable racks **£5.50**

p+p extra on all the above items.

We stock a wide selection of Computer Books.

DIL PLUGS (Headers)
14 pin **44p;** 24 pin **88p**
16 pin **49p;** 40 pin **255p**
(DIL Sockets on opp. page)

'D' CONNECTORS
(Cannon type)

	Plugs	**Sockets**	**Covers plastic**
9 way	**95p**	**125p**	—
15 way	**135p**	**198p**	**150p**
25 way	**198p**	**284p**	**170p**
37 way	**290p**	**398p**	**185p**

AMPHENOL PLUGS
IEEE **475p,** Centronics // **575p**

DIL switches (SPST)

4 way	**80p**
6 way	**98p**
8 way	**105p**
10 way	**175p**

(SPDT)

4 way	**190p**

EDGE CONNECTORS
double type

	·1	·156
2×10 way	—	**82p**
2×15 way	—	**98p**
2×18 way	**140p**	**120p**
2×22 way	**150p**	**125p**
2×25 way	**165p**	**160p**
2×30 way	**188p**	—
2×36 way	**197p**	—
2×40 way	**205p**	—
2×43 way	**250p**	—

TRANSFORMERS (mains Prim. 220-240V)
6-0-6V 100mA; 9-0-9V 75mA; 12-0-12V 75mA **98p**
8VA type: 6V-·5A 6V-·5A; 9V-·4A 9V-·4A; 12V-·3A 12V-·3A; 15V-·25A 15V-·25A **220p**
12VA: 4·5-1·3A 4·5V-1·3A; 6V-1·2, 6V-1·2A 12V-·5A 12V-·5A **250p** (30p p&p)
24VA: 6V-1·5A 6V-1·5A; 9V-1·2A 9V-1·2A; 12V-1A 12V-1A; 15-·8A 15-·8A; 20V-·6A 20V-·6A **320p** (44p p&p)
50VA: 6V-4A 6V-4A; 9V-2·5A 9V-2·5A; 12V-2A 12V-2A; 15V-1·5A 15V-1·5A; 20V-1·2A 20V-1·2A; 25V-1A 25V-1A; 30V-·8A 30V-·8A **365p** (60p p&p)
100VA: 12V-4A 12V-4A; 15V-3A 15V-3A; 20V-2·5A 20V-2·5A; 30V-1·5A 30V-1·5A; 40V-1·25A 40V-1·25A; 50V-1A 50V-1A **820p** (60p p&p)

JUMPER LEADS Ribbon Cable Assembly
Single ended DIP, 24" length Cable
14 pin **145p** 16 pin **165p;**
24 pin **240p;** 40 pin **380p.**
Double ended DIP

Length	14 pin	16 pin	24 pin	40 pin
6"	**185p**	**205p**	**300p**	**465p**
12"	**195p**	**215p**	**315p**	**490p**
36"	**230p**	**250p**	**375p**	**595p**

WEMON

A 4k monitor specially designed to produce the best from your

Superboard, Superboard Series 2, UK101 or Enhanced System.

Look at these superb facilities:

- Full screen editing.
- Home cursor/screen clear facility.
- True insert/delete.
- Fully programmable cursor control with meaningful symbols on screen.
- Single key Basic
- True ASCII keyboard routine.
- Auto remote control of tape recorder (requires only a relay).
- Open line facility.
- Named tape files.
- Two key video swap (Series 2 only).
- Bell (Series 2 only).
- Cursor indication of quotes mode.
- User definable flashing cursor character.
- User controllable command vectoring for your own machine code routines.
- Full or partial scroll-up or scroll-down (callable by program).
- Auto list on error (displays faulty line upon carriage return).
- Single command save (automatically returns "list").
- Centronics compatible printer driver.

Monitor functions include:

- Scrolling list in data mode.
- Warm restart vector.
- Fill memory.
- Search memory.
- Two save and three load routines.
- Floppy disc vector.
- Break handling routine.
- Tabular display of memory.

All this for only £19·95
+ 50p P&P + VAT.

WATFORD'S BOOKSHOP CORNER

Personal Computer Book	**630p**
Illustrating BASIC	**390p**
BASIC with Style	**490p**
A Bit of BASIC	**540p**
Advanced BASIC	**750p**
BASIC Computer Games	**550p**
More BASIC Computer Games	**550p**
Some Common BASIC Progrms	**1050p**
Practical BASIC Programs	**1100p**
6502 Software Design	**900p**
6502 Application Book	**890p**
Programming the 6502 (C202)	**1050p**
Programming & Interfacing the 6502	**1050p**
6502 Assembly Language Programming	**1290p**
6800 Assembly Language Programming	**1100p**
6809 Assembly Language Programming	**1350p**
Practical Intro to PASCAL	**500p**
Using CP/M: A self teaching guide	**690p**
8080A/8085 Assembly Lang. Programming	**1100p**
Z80 Instruction Handbook	**350p**
Z80/8080 Assembly Lang. Programming	**650p**
Z80 Microcomputer Handbook	**750p**
8080/Z80 Assembly Lang. Techniques	**840p**
Programming the Z80 (C280)	**1060p**
Z80 Assembly Language Programming	**1290p**
Intro to TRS-80 Graphics	**690p**
TRS80 BASIC – A self teaching guide	**720p**
ZX80 Pocket Book	**500p**
30 programs for the Sinclair ZX80	**700p**
Making the most of your ZX80	**790p**
32 BASIC Programs for PET Computer	**1050p**
PET and the IEEE 488 Bus (GP1B)	**1100p**
PET Graphics	**1000p**

Please add 55p P&P charge on books.

WATFORD ELECTRONICS
33/35 CARDIFF ROAD, WATFORD, HERTS.
Telephone 40588

We're giving away this soldering iron worth over £10.

Choose any of 10 selected kits from the Heathkit catalogue as your first order, and we'll give you a superb soldering iron worth over £10. Plus a 10% discount!

These kits have been specially designed with first-time kit builders in mind. So even if you've never built an electronic kit before you won't find it difficult. In fact, the simple to follow step-by-step instructions make it easy to build any Heathkit kit.

And with your special offer discount you can afford to see just how easy it is.

Full details of this FREE offer are available in the Heathkit 48 page catalogue. So send the coupon for your copy now.

To: Heath Electronics (UK) Limited. Dept. (PE7). Bristol Road, Gloucester. GL2 6EE.

Please send me a copy of the Heathkit catalogue. I enclose 28p in stamps.

Name ______________________________

Address ______________________________

____

____

NB: If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.

HEATHKIT HEATH ZENITH

OHIO SCIENTIFIC COMPUTERS

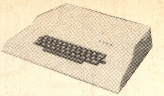

Superboard 3 **£159.** Power supply kit **£11.95.** Modulator **£3.50.** Guard band kit **£10** (converts the display to 32×32, gives 1200 and 300 Baud tape speeds, increases computing speed by 50% and converts to 50Hz). **Special offer:** Superboard 3 + power supply and modulator kit + guard band kit ONLY £172. 4K extra ram **£15.60.** Case **£27.** Cassette recorder **£18.** Cegmon improved monitor rom **£29.50.** Assembler/Editor tape **£25.** Word processor program **£10.** Display expansion kit 30 lines × 54 characters for Superboard 2 (Not 3) **£14.** Cheapo memory expansion offer:- Buy a 610 expansion board with 8K ram on board and space for another 16K for **£159** and get a free 5V 3A power kit and any extra ram you want for **£3/K.** Buy a minifloppy disc drive + case + power supply + DOS for **£275** and we will do the extra ram for **£2/K** (Max 16K). Wemon Improved monitor rom **£19.95.** Centronics Printer Driver kit **£10.** New Series 2 Challenger C1P:- cheapo 4K version **£212** + £4.50 Post.

PRINTERS

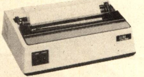

Buy any of the below and get a free interface kit and word processor program for UK101 or Superboard 2:- OKI Microline 80 (Illustrated) **£299.** Seikosha GP80 **£225.** Epson MX80 tractor **£359.** Epson MX80 tractor + friction **£399.** Epson MX70 **£259.** Epson TX80 **£295.**

MEMORY CHIPS
2114 450ns **£1.95.** 4116 200ns **£1.99.** 4027 **£1.30.** All low current.

SINCLAIR PRODUCTS•
Sinclair products only are all post free. SC110 Oscilloscope **£139,** Adaptor **£4,** Rechargeable batteries **£7.95,** ×1 probe **£8.05,** ×10 probe **£8.86,** Carry case **£8.80.** PFM200 **£52.40,** Adaptor **£4,** Case **£1.73,** connector kit **£11.27.** PDM35 **£32.95,** adaptor **£4,** case **£1.73.** DM235 **£56.50,** DM350 **£78,** DM450 **£107,** adaptor **£4,** case **£8.80,** rechargeable batts **£7.95.** Microvision TV **£69.** Adaptor **£6.95.**

BATTERY ELIMINATORS•
3-way type 6/7½/9V 300ma **£3.50.** 100ma radio types with press studs 9V **£4.95.** 9+9V **£6.25.** Car convertor 12V input, output 3/4½/6/7½/9V 800ma **£3.04.**

BATTERY ELIMINATOR KITS•
100ma radio types with press-studs 9V **£1.79,** 9+9V **£2.50.** Stabilized 8-way types 3/4½/6/7½/9/12/15/18V 100ma **£3.12,** 1 Amp **£8.50.** Stabilized power kits 2-18V 100ma **£3.12,** 1-30V 1A **£8.50,** 1-30V 2A **£15.30.** TTL and computer supplies 5V stabilized 1½A **£9,** 3A **£14,** 6A **£20.** 12V car convertors 6/7½/9V 1A **£1.62.**

TV GAMES•
AY-3-8600 + kit **£12.98.** AY-3-8550 + kit **£9.26.**

PRINTED CIRCUIT MATERIALS•
PC etching kit:- economy **£3.42,** standard **£5.76.** 40 sq ins pcb **50p.** 1 lb FeCl **£2.20.** Etch resist pens:- economy **50p,** dalo **90p.** Drill bits 1/32" or 1mm **35p.** Etching dish **92p.** Laminate cutter **£1.30.**

BI-PAK AUDIO MODULES•
AL30A **£4.53.** PA12 **£9.31.** PS12 **£1.75.** T538 **£2.90.** S450 **£27.90.** AL60 **£5.62.** PA100 **£19.24.** SPM80 **£5.26.** BMT80 **£6.36.** Stereo 30 **£24.14.** AL80 **£8.56.**

COMPONENTS•
1N4148 **£1.5p.** 1N4002 **3.7p.** NE555 8 dil **26p.** 741 8 dil **20p.** bc182, bc184, bc212, bc214, bc547, bc549 **6.1p.** Resistors 5% ¼W E12 10R to 10M **1.5p, 0.8p** for 50+ of one value. Polyester capacitors 160V .015, .068mf **2.9p,** .047, .1mf **4.4p,** .01mf **3.3p,** .022, .033mf **3.7p,** .15, .22, .33mf **5.4p,** .47mf **6.6p.** Polystyrene capacitors E12 63V 10 to 1000pf **4p,** 1n2 to 10n **5p.** Ceramic capacitors 50V E6 22pf to 47n **2.5p.** Electrolytic capacitors 50V .5, 1, 2mf **6p,** 25V 5, 10mf **6p,** 16V 22, 33mf **6p,** 47mf **5p,** 100mf **7p,** 330, 470mf **9p.** Zeners 400mW E24 2v7 to 33V **7p.** Preset pots subminiature 0.1W horiz or vert 100 to 2M2 **8p.** IC sockets 8 dil **8.7p,** 14 dil **10.1p,** 16 dil **12p.**

SWANLEY ELECTRONICS

Dept. PE, 32 Goldsel Road, Swanley, Kent BR8 8EZ.

Postage £3.50 on Superboard, £4.50 on printers and 45p on other orders. Lists 27p post free. Please add VAT to all prices except those sections marked with a • which already include it at the old 15% rate. Overseas and credit orders welcome. ZX81 part exchange possible.

TRAIN AT HOME

Be an ELECTRONIC ENGINEER

Do something PRACTICAL about your future.

Firms all over Britain are crying out for qualified people. With the right training, *you* could take your pick of these jobs.

Now, the British Institute of Engineering Technology will train you in your spare time to be an Electrical Engineer.

You risk nothing! **We promise to get you through your chosen course–or, refund your fee!**

So, join the thousands who have built a new future through home study Engineering courses.

Courses in
C & G Elect. Technicians
C & G Elect. Installations
Telecomms. Technicians Exams
Television Servicing
Radio Maint. & Repairs (BIET)
Pract. Radio & Electronics
Plus over 60 other home study courses.

POST COUPON FOR FREE 44 PAGE GUIDE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Aldermaston Court, Dept TPE13, Reading RG7 4PF.

NAME (Block capitals please) ______________________________

ADDRESS ______________________________

______________________________ POSTCODE ______________________________

Other Subjects ______________________________ AGE ______

Accredited by CACC Member of ABCC

You can't beat The System.

The Experimentor System™—a quicker transition from imagination through experimentation to realization.

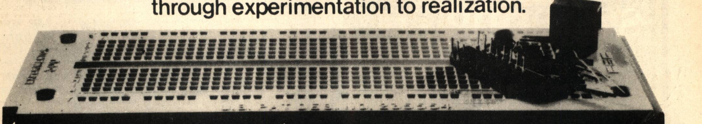

Experimentor solderless breadboard.

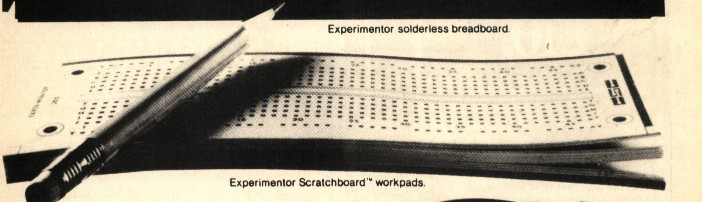

Experimentor Scratchboard™ workpads.

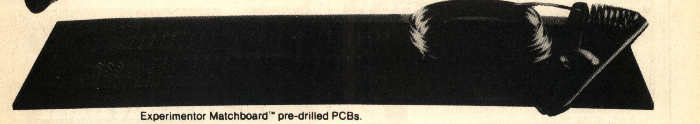

Experimentor Matchboard™ pre-drilled PCBs.

When you have a circuit idea that you want to make happen, we have a system to make it happen quicker and easier than ever before: The Experimentor System.

You already know how big a help our Experimentor solderless breadboards can be. Now we've taken our good idea two steps further.

We've added Experimentor Scratchboard workpads, with our breadboard hole-and-connection pattern printed in light blue ink. To let you sketch up a layout you already have working so you can reproduce it later.

With Experimentor Matchboard you can go from breadboard to the finished product nonstop! We've matched our breadboard pattern again, this time on a printed circuit board, finished and ready to build on. All for about £1.20

There's even a letter-and-number index for each hole, so you can move from breadboard (where they're moulded) to ScratchboardTM (where they're printed) to MatchboardTM (where they're silkscreened onto the component side) and always know where you are.

When you want to save time and energy, you can't beat The Experimentor System.

1. EXP-300PC, which includes one item. A Matchboard pre-drilled PCB. **£1.20**	**2.** EXP-302, which includes three items. Three 50-sheet Scratchboard workpads **£1.50**	**3.** EXP-303, which includes three items. Two Matchboards and an EXP-300 solderless breadboard **£7.60**	**4.** EXP-304, which includes four items. Two Matchboards, an EXP-300 breadboard and a Scratchboard workpad **£8.70**

GLOBAL SPECIALTIES CORPORATION

GSC

G.S.C. (UK) Limited, Dept.5W
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex. CB11 3AQ.
Telephone: Saffron Walden (0799) 21682
Telex: 817477

GLOBAL SPECIALTIES CORPORATION. DEPT.5W
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex.

Name ____________________

Address ____________________

Inc P&P and 15% VAT

1.EXP 300PC **£2.25**	Qnty.Reqd.	2.EXP 302 **£2.58**	Qnty.Reqd.
3. EXP 303 **£9.40**	Qnty.Reqd.	4. EXP 304 **£11.15**	Qnty.Reqd.

FREE Catalogue tick box ☐

I enclose cheque/ PO for

£ ____________________

Phone your order with Access, Barclaycard or American Express

Card No. ____________________ Expiry date ____________________

CHROMASONIC electronics

DEPT P.E. 48 JUNCTION ROAD, ARCHWAY, LONDON N19 5RD
TELEPHONE 01-263 9493 01-263 9495
100 YDS FROM ARCHWAY STATION & 9 BUS ROUT

YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPONENTS AND COMPUTER

UK101

£149 IN KIT FORM
£199 READY BUILT & TESTED
£225 COMPLETE IN CASE

4K Expansion (8x2114) NOW ONLY £14.00

No extras required
- ★ Free sampler tape
- ★ Full Qwerty keyboard
- ★ 8K basic incl garbage collection routine
- ★ Ram expandable to 8K on board (4K inc)
- ★ Kansas City tape interface
- ★ NEW MONITOR ALLOWS FULL EDITING & CURSOR CONTROL **NOW INCLUDED IN KIT**

CASES

Available for U.K. 101, Superboard Nascom, Appx. DIM. 17″ × 15″ 435 × 384 mm.

PRICE £24.50
Post + Packing £1.50

UK101 MEMORY BOARD

★ On board power supply (uses the UK101 transformer). ★ Facility for 4K eprom expansion. ★ Fully buffered for expansion via 40 pin socket ★ 40 pin header & 8T28's included.

8K Kit (inc. 16K skts) **£79.95.** 16K Kit **£106.95**
Printed circuit board **£29.95**

PARALLEL PERIPHERAL INTERFACE

UK101 AND SUPERBOARD COMPATIBLE.
Interfaces to GP80, MX80 series, TX80, centronics P1, etc printers. Can operate relays, motors, various other peripherals. LED binary display. Plugs into ACIA socket. Fully documented.

Built and tested. ONLY **£29.95**

PRINTERS

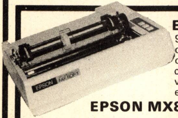

EPSON MX80 £359
9 × 9 dot matrix, 80 c.p.s. True descenders, various print densities up to 132 columns, tab controls both horizontal & vertical, bold expanded condensed printing, bidirectional.

EPSON MX80 FT/1 £399
Dual single sheet friction and continuous tractor feed, 9 wire head, true descenders.

EPSON MX80 FT/2 £449
Additional feature to FT/1 is high resolution graphics.

EPSON MX70 £259
Tractor feed, 7 wire head, high resolution graphics.

SEIKOSHA GP80A £199
Dot matrix 5 × 7, 80 columns, 30 cps, graphics, double width characters.

VIDEO GENIE

VIDEO GENIE based on TRS80

Utilises Z80, 12K level II Basic, Integral Cassette Deck, UHF O/P, 16K RAM, all TRS80 features. Simply plugs into monitor or UHF TV with VU meter.

£289

	£
Expansion Box	185.00
Expansion Box (RS232)	215.00
16K Ram Card	94.00
32K Ram Card	129.00
Single Disk Drive (35 track)	215.00
Dual Disk Drive (40 track)	410.00
Parallel Printer Cable	17.00
Disk Drive Cable (4 drives)	32.00
Dual Disc Drive Cable	17.00
Parallel Printer Cable for Unexpanded V.G.	33.00
Sound Kit (fitting extra)	7.00
Lower Case Kit (fitting extra)	27.50
Video Genie Technical Manual	£5.00

UK101 SOUND

Sound generator and combined parallell in out port kit containing P.C.B., AY-3-8910, 6520 PIA, fully documented and demo tape.

£29.95

AY-3-8910 **£8.50**

UK101 COLOUR BOARD

A U.K. PRODUCT

AT LAST!!

Designed to simply plug into your computer and any standard colour television in

"8" GLORIOUS **COLOURS**

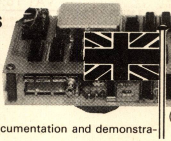

KIT (Uncased)

Includes full documentation and demonstration tape.

UK101, Superboard **£84.95**
Available for Pet **£98.95**

Send for further details.

MONITORS

EG100 12″ Black & White	**£65**
Moni 9″ (illust) B&W	**£82**
Hitachi Professional Monitors	
9″ Black & White	**£99.95**
12″ Black & White	**£149**

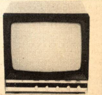

BARCLAYCARD VISA

Please add VAT 15% to all prices. Postage on computers, printers and cassette decks charged at cost, all other items, P&P 30p. Place your order using your Access or Barclaycard (Min. tel order £5). Trade and export enquiries welcome. Official orders welcome.

Access

PET

4008 8K RAM
4016 16K RAM
4032 32K RAM
4040 Dual Disk Drive

The new PET printer. 4022 80 column tractor feed. 3023 80 column friction feed. C2N Cassette Unit. For the business man we stock the 8000 range inc. 8032 and 8050 with daisy wheel printers coming soon.

COMPLETE 32K SYSTEM

PHONE FOR MOST COMPETITIVE PRICES

APPLE

APPLE II PLUS

THISTRIE COMPLETE SYSTEMS AVAILABLE
Complete Systems
16K Machines
32K Machines
48K Machines.
Disk Drive with/without Controller.
Printers – Monitors – Graphics Tablet All Available

Apple II plus

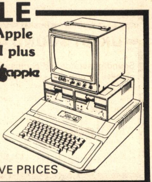

PHONE FOR MOST COMPETITIVE PRICES

PRESTEL BY TANTEL

The greatest thing since television and telephones. Communication at your fingertips for business and home. Up to date info. 180,000 pages of information on Travel, News, Investment, Holidays, Hotels, etc. etc.

Ask Prestel a question and you have your answer in seconds in full colour on you own TV. Only requires a telephone jack socket available from the PO.

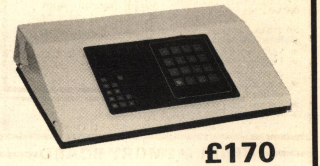

£170

Tantel is Post Office approved.
Send for details.

TRANSFORMERS

CONTINUOUS RATINGS

All voltages are at full load.

+ VAT 15%

30 VOLT RANGE (2x15V SECS)

Pri 0-220-240V Sec Volts available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12-0-12V or 15-0-15V.

Ref.	Amps 30V	Amps 15V	Price	P&P
112	.5	1	**2.90**	1.00
79	1	2	**3.93**	1.00
3	2	4	**6.35**	1.20
20	3	6	**7.39**	1.44
21	4	8	**8.79**	1.60
51	5	10	**10.86**	1.60
117	6	12	**12.29**	1.72
88	8	16	**16.45**	1.96
89	10	20	**18.89**	1.84
90	12	24	**21.09**	O.A.
91	15	30	**24.18**	O.A.
92	20	40	**32.40**	O.A.

50 VOLT RANGE (2x25V SECS)

Pri 220/240V, Volts out 5, 7, 8, 10, 13, 15, 17, 20, 33, 40V or 20-0-20V or 25-0-25V.

Ref.	Amps 50V	Amps 25V	Price	P&P
102	.5	1	**3.75**	1.20
103	1	2	**4.57**	1.20
104	2	4	**7.88**	1.44
105	3	6	**9.42**	1.60
106	4	8	**12.82**	1.72
107	6	12	**16.37**	1.84
118	8	16	**22.29**	2.20
119	10	20	**27.48**	O.A.
109	12	24	32.88	O.A.

60 VOLT RANGE (Split Sec)

Pri 220/240V Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24-0-24V or 30V-0-30V.

Ref.	Amps 60V	Amps 30V	Price	P&P
124	.5	1	**4.27**	1.20
126	1	2	**6.50**	1.20
127	2	4	**8.36**	1.60
125	3	6	**12.10**	1.72
123	4	8	**13.77**	1.96
40	5	10	**17.42**	1.84
120	6	12	**19.87**	2.04
121	8	16	**27.92**	O.A.
122	10	20	**32.51**	O.A.
189	12	24	**37.47**	O.A.

CASED AUTO TRANSFORMERS

240V cable in 115V USA flat pin outlet.

VA	Price	P&P	Ref
20	**6·55**	0.95	**56W**
75	**8·50**	1.20	**64W**
150	**11·00**	1.44	**4W**
250	**13·39**	1.44	69W
500	**20·13**	2.04	67W
1000	**30·67**	2.20	84W

12 OR 24V OR 12-0-12V

Pri 220-240 volts

Ref	Amps 12V	Amps 24V	Price	P&P
111	0·5	0·25	**2·42**	0.95
213	1·0	0·5	**2·90**	1.00
71	2	1	**3·86**	1.00
18	4	2	**4·46**	1.20
85	5	2 5	**6·16**	1.20
70	6	3	**6·99**	1.20
108	8	4	**8·16**	1.44
72	10	5	**8·93**	1.60
116	12	6	**9·89**	1.60
17	16	8	**11·79**	1.72
115	20	10	**15·37**	1.84
187	30	15	**19·72**	2.04
226	60	30	**40·41**	O.A.

SPLIT BOBBIN Pri 0.240-Sec.

12-15-20-24-30V Outputs available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12-0-12 or 15-0-15V.
Ref 009 – 1 Amp **£2·98.** P. & P. £1·10.
Ref 010 – 2 Amp **£4·65.** P. & P. £1·10
'open' frame fixing. Other types available.

AUTO TRANSFORMERS

Voltages available 105, 115, 190, 200, 210, 220, 230, 240.

Ref.	VA	£	P&P
113*	80	**2·73**	1.00
64	75	**4·41**	1.20
4	150	**5·89**	1.20
53	350	**10·08**	1.44
67	500	**12·09**	1.84
84	1000	**20·64**	2.20
93	1500	**25·61**	O.A.
95	2000	**38·31**	O.A.
73	3000	**65·13**	O.A.
80S	4000	**84·55**	O.A.
57S	5000	**98·45**	O.A.

*0, 115, 220, 240.

15V CT Range (7.5v-0-7.5v)

			P&P
171	500mA	**2·30**	0 52
172	1A	**3·26**	0 92
173	2A	**3·95**	0·90
174	3A	**4·13**	0 99
175	4A	**6·30**	1 10

MAINS ISOLATORS (SCREENED)

Pri 0-120; 0-100-120V (120, 220, 240V) Sec 60-55-0-55-60V twice to give 55, 60, 110, 115, 120, 125, 175, 180, 220, 225, 230, 235, 240V.

Ref	VA	Price	P&P
*07	20	**4·84**	1.20
149	60	**7·37**	1.20
150	100	**8·38**	1.44
151	200	**12·28**	1.72
152	250	**14·61**	2.04
154	500	**22·52**	2.20
155	750	**32·03**	O.A.
156	1000	**40·92**	O.A.
157	1500	**56·52**	O.A.
158	2000	**67·99**	O.A.
159	3000	**95·33**	O.A.

*Pri 0-240V Sec 115 or 240V
State sec volts required.

SCREENED MINIATURES

Ref	mA	Volts	£	P&P
238	200	3-0-3	**2·83**	0.50
212	1A. 1A	0-6. 0-6	**3·14**	1.00
13	100	9-0-9	**2·35**	0.50
235	330. 330	0-9. 0-9	**2·19**	0.60
207	500. 500	0-8-9. 0-8-9	**3·05**	0.95
208	1A. 1A	0-8-9. 0-8-9	**3·88**	1.20
236	200. 200	0-15. 0-15	**2·19**	0.60
214	300. 300	0-20. 0-20	**3·08**	1.00
221	700(DC)	20-12-0-12-20	**3·75**	1.00
206	1A. 1A	0-15-20 twice	**5·09**	1.20
203	500. 500	0-15-27 twice	**4·39**	1.20
204	1A. 1A	0-15-27-0 twice	**6·64**	1.20
239	50	12-0-12	**2·88**	0.50
234	500	6-0-6	**2·19**	0 44

– NEW –
Constant Voltage Transformers (1%)

For "clean" mains to computers or peripherals.

250 VA	**£98.00**
500 VA	**£129.00**
1000 VA	**£149.00**

Appointed distributors of Galatrek stabilisers.

UK Postage only. Overseas post extra.

AVO METERS & MEGGERS

Avo 8 MK5 latest model	**£116.40**
Avo 71 Electronics &	**£45.40**
Avo 73 TV Service	**£63.90**
Avo MM5 minor	**£40.50**
Avo EM272 316KΩV input Z	**£67.10**
Avo DA116 LCD Digital	**£121.70**
Avo DA211 LCD Digital (hand	**£57.00**
Avo DA212 LCD Digital held)	**£74.00**
Battery Megger BM7/500V	**£65.30**
Wee Megger hand crank	**£97.20**

Plus P&P £1.32 + VAT 15%
All Avos Meggers & accessories available.

OTHER PRODUCTS

100W Solder Gun includes bulb for spot-on joints **£5.39** + VAT.

Jewellers Screwdriver Set
£2.00 + VAT. P&P 40p + VAT.

SPECIAL OFFER Multimeter (20KΩ/V) with combined audio/I.F. test oscillator at 1KHz. and 465 KHZ. AC/DC to 1000 volts. DC current to 500 MA resistance to 1M size 160×97×40mm **£8·50.** P&P £1·00, VAT 15%

ABS Plastic Boxes: inset brass nuts, slots to take P.C. cards (boards) flush fitting lid.

PBI – 80mm × 62 × 40 **80p**
PB2 – 100mm × 75 × 40 **90p**
PB3 – 120mm × 100 × 45 **£1.04**
PB4 – 215mm × 130 × 85 **£2.68**

P&P 50p + VAT

Bridge Rectifiers

100V	25A	**£1.80**
100V	50A	**£2.20**
200V	2A	**.52**
200V	4A	**.75**
400V	1A	**.25**
400V	4A	**.98**
400V	6A	**£1.44**
500V	12A	**£3.60**

P&P 20p VAT 15%

NEW RANGE TRANSFORMERS

0-36-48 twice to give 36-0-36 48-0-48V, 60V, 72V, 84V, 96V.

Amps	Ref	Price	P.&P.
0·5	430	**4·88**	0·76
1	431	**8·12**	0·99
2	432	**13·35**	1·31
3	433	**16·17**	1·40
4	434	**20·65**	2·11
5	435	**29·30**	2·47
6	436	**36·69**	O.A.
8	437	**40·03**	O.A.

Antex Soldering Irons 15W (CN240) & 25W **£4.58** + 60p P&P + VAT.
Safety stand for above **£1.75** + P&P 30p + VAT.

Soldering Iron – 25W to BS spec. **£1.75** + 30p P&P + VAT.

De-solder Pumps – Spring loaded with quick action button release for one handed working. **Large £5.10** + P&P 35p + VAT. **Small £4.75** + P&P 30p + VAT.
Replacement tips. **Small 65p** + VAT. **Large 86p** + VAT.

METAL OXIDE RESISTORS £1.00/100 (Electrosil) TR4 5% 47Ω/95Ω/180Ω/360Ω/390Ω/430Ω/470Ω/510Ω/560Ω/820Ω/1K/1K1/1K2/1K3/1K6/1K8/2K4/3K/16K/20K/22K/24K/47K/82K/100K/110K/120K/130K/180K/220K/270K/300K.
P&P 50p + VAT.

BATTERY ELIMINATORS
Plugs into 13A socket 3, 6, 7·5, 9, 12V DC @ 300 mA output **£5.10** or 3, 6, 9V **£4.60** P&P 60p + VAT.

TELEPHONES — Latest model 746, boxed, 2 tone grey **£11.50** + VAT. Ivory **£12.50** + VAT P&P £1.20 + VAT.

PANEL METERS

43 x 43mm		82mm · 78mm	
0-50μA	**6.20**	0-50μA	**6.70**
0-500μA	**6.70**	0-500μA	**6.70**
0-1mA	**6.70**	0-1mA	**6.70**
0-30V	**6.70**	0.30V	**6.70**

VU ind. Panel 48mm × 45mm or 40mm × 40mm 250 A fsd or Edge-type centre zero 39 × 18mm **£2.60.** Carriage 76p. VAT 15%

Send 20p for catalogue Prices correct 1/1/81

SPECIAL OFFER
25W Soldering Iron to BS Spec. **£1.75**
P&P 30p + VAT 15%

"Educational" Meters (Moving coil) 0-10A, 0-15V, 0-30V.
Free standing large scale easily read meters with top screw terminals for quick connections. Size 75 × 78mm scale **£4·50** P&P 66p + VAT.

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01–488 3316/7/8
NEAREST TUBE STATIONS ALDGATE & LIVERPOOL ST

Rapid Electronics

Hillcroft House
Station Road
Eynsford Kent

COMPONENTS KITS

¼W Resistor Kit. Contains 10 of each value from 4.7Ω to 1M (total of 650 resistors). **480p each**

Ceramic capacitor kit. Contains 5 of each value from 22pF to 0.01uF (total 135 caps.). **370p each.**

Polyester Capacitor Kit. Contains 5 of each value from 0.01 to 1uF (total 65 capacitors). **575p each.**

Nut and Bolt Kit. Total of 300 items. **140p each.**

25 6BA ¼" bolts
25 6BA ½" bolts
50 6BA nuts
50 6BA washers
25 4BA ¼" bolts
25 4BA ½" bolts
50 4BA nuts
50 4BA washers

RESISTORS

Carbon film ¼W 5% 4.7Ω to 10M. Sold in packs of 10 per value. **10p per pack.**

Potentiometers

Preset miniature horizontal 100Ω to 1M.	**7p**
Rotary pot. 5K-1M Log or Lin	**32p**
Slide pots. 5K-500K Log or Lin. 60mm travel	**63p**
Mixer type control knobs to suit above pots. Available in red, black, green, grey, yellow and blue. For rotary pots.	**16p**
Slide pots.	**12p**

CAPACITORS

Polyester. Radial leads. 250V. C280 type.
0.01, 0.015, 0.022, 0.033, **6p;** 0.047, 0.068, 0.1, **7p;** 0.15, 0.22, **9p;** 0.33, 0.47, **13p;** 0.68, **20p;** 1.0uF, **23p.**
Electrolytic Radial leads.
0.47/63V, 1/63V, 2.2/63V, 4.7/63V, 4.7/63V, 10/25V, **7p;** 22/25V, 47/25V, **8p;** 100/25V, **9p;** 220/25V, **14p;** 470/25V, **22p;** 1000/25V, **30p.**
Tantalum bead.
0.1/35V, 0.22/35V, 0.33/35V, 0.47/35V, 1/35V, **12p;** 2.2/25V, 4.7/25V, 10/25V, **20p;** 22/16V, 47/6V, **27p.**
Ceramic disc type. Sold in packs of 5 per value.
15p per pack. 22pF to 0.01uF.

CABLES

20 metre pack of connecting cable stranded 2m each of 10 different colours **75p each.**

	per metre
Speaker cable	**10p**
Lightweight screened	**12p**
4 core screened	**45p**
Standard screened	**16p**
Stereo screened	**24p**
Min. mains 3 core	**23p**

OPTO

3mm red	**9p**
3mm green	**14p**
3mm yell.	**14p**
5mm red	**9p**
5mm green	**14p**
5mm yell.	**14p**
10 3mm or 5mm clips	**30p**
FND500	**90p**

CONNECTORS

DIN	Plug	Socket
2 pin	**9p**	**9p**
3 pin	**12p**	**10p**
5 pin 180°	**13p**	**11p**
Phono	**10p**	**12p**

Jack	Plug	Socket
2.5mm	**10p**	**10p**
3.5mm	**10p**	**9p**
Standard	**16p**	**20p**
Stereo	**24p**	**25p**

DIODES

1N4001 **4p**
1N4002 **5p**
1N4006 **7p**
1N4148 **3p**

400mW zeners **8p ea.**

VEROBOARD

Size 0.1 matrix

2.5" ×1"	**22p**
2.5"×3.75"	**75p**
2.5"×5"	**85p**
3.75"×5"	**95p**
VQ board	**160p**
Veropins per 100	
Single sided	**50p**
Double sided	**60p**
Spot face cutter	**105p**

HARDWARE

5 PP3 battery connectors	**30p**
5 Red or black croc clips	**30p**
22mm solid alum. knob	**36p**
28mm solid alum. knob	**48p**
Red or black probe clip	**35p**
Magnetic earphone · plug	**18p**
Crystal earphone · plug	**44p**
Ultrasonic transducers	**350p**
Red or amber neon	**45p**
20 way ribbon cable	**120p/m.**
T05 or T018 heatsink	**15p**
T0220 heatsink	**28p**
4mm plug (var. colours)	**18p**
4mm skt (var. colours)	**17p**
20mm panel fuseholder	**25p**
606 100mA transformer	**100p**
Dalo pen	**100p**
10 metres 22swg solder	**100p**
64mm 64 ohm speaker	**100p**
64mm 8 ohm speaker	**100p**

LS TTL

LS00	**16**	LS14	**60**	LS75	**45**	LS123	**75**	LS161	**105**
LS01	**16**	LS20	**22**	LS76	**50**	LS125	**60**	LS164	**110**
LS02	**16**	LS30	**22**	LS78	**50**	LS132	**65**	LS174	**110**
LS04	**18**	LS32	**28**	LS83	**90**	LS136	**60**	LS244	**170**
LS08	**25**	LS42	**70**	LS86	**45**	LS138	**75**	LS365	**70**
LS10	**20**	LS73	**50**	LS90	**50**	LS139	**75**	LS366	**70**
LS13	**40**	LS74	**35**	LS93	**65**	LS157	**75**	LS367	**70**

SOCKETS

Texas	
8 pin	**9p**
14 pin	**10p**
16 pin	**12p**
100 Soldercon pins	**60p**
TO5 or TO18 skt.	**15p**

REGULATORS

78L05	**30**	7905	**65**
78L12	**30**	7912	**65**
78L15	**30**	7915	**65**
7805	**60**	LM723	**40**
7812	**60**	LM317T	**180**
7815	**60**	LM323K	**500**

LINEAR CIRCUITS

		LM301A	**30**	LM3900	**50**	SN76477	**170**
741	**18**	LM318	**85**	LM3909	**70**	TBA800	**80**
CA3080	**70**	LM324	**45**	LM3911	**120**	TBA810	**95**
CA3130	**90**	LM339	**50**	LM3914	**260**	TL081	**40**
CA3140	**45**	LM380	**80**	LM3915	**260**	TL082	**70**
ICM7555	**90**	LM381	**120**	LM13600	**120**	TL084	**110**
LF351	**45**	LM382	**120**	NE555	**23**	XR2206	**300**
LF353	**85**	LM387	**120**	NE556	**55**	ZN414	**100**
LF356	**90**	LM1458	**40**	RC4136	**85**	ZN425E	**390**

CMOS

4001	**22**	4016	**35**	4028	**80**	4066	**40**	4082	**25**
4002	**25**	4017	**70**	4040	**85**	4068	**25**	4093	**55**
4007	**25**	4020	**85**	4046	**100**	4069	**22**	4510	**85**
4008	**80**	4023	**25**	4047	**100**	4070	**25**	4518	**90**
4011	**22**	4024	**60**	4049	**35**	4071	**25**	4520	**100**
4013	**45**	4025	**25**	4050	**40**	4072	**25**	4528	**100**
4015	**80**	4027	**40**	4060	**105**	4081	**25**	4532	**120**

TRANSISTORS

AC128	**25**	BC182L	**10**	BF244B	**30**	ZTX108	**12**
AC176	**25**	BC184L	**10**	BFX29	**25**	ZTX300	**14**
AD161	**40**	BC212L	**10**	BFY50	**23**	2N2369	**17**
AD162	**40**	BC214L	**10**	BFY51	**23**	2N2646	**45**
BC107	**10**	BC478	**30**	MJ2955	**100**	2N3053	**23**
BC108	**10**	BC547	**10**	TIP31A	**45**	2N3055	**50**
BC108C	**12**	BC548	**10**	TIP32A	**45**	2N3702	**9**
BC109	**10**	BC549	**10**	TIP41A	**60**	2N3704	**9**
BC109C	**12**	BD131	**35**	TIP42A	**60**	2N3819	**20**
BC148	**8**	BD132	**35**	TIP2955	**60**	2N3904	**10**
BC178	**18**	BD139	**35**	TIP3055	**55**	2N3905	**10**
BC179	**18**	BD140	**35**	ZTX107	**12**	2N5459	**30**

NEW CAT

New 28 page Catalogue
–vastly extended range.
Please send 28p in stamps.
FREE with orders over £5.

OUT NOW

Please add 50p P&P on orders under £20. Please add VAT at 15% to total order value. Official orders welcome from schools, colleges etc.

The Rapid Guarantee ★ Same day despatch ★ Competitive prices ★ Top quality components ★ In-depth stock

---

Conquer the chip.

Be it a career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

MASTER ELECTRONICS

LEARN THE PRACTICAL WAY BY SEEING AND DOING

- Building an oscilloscope.
- Recognition of components.
- Understanding circuit diagrams.
- Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.

MASTER COMPUTERS

LEARN HOW TO REALLY UNDERSTAND COMPUTERS, HOW THEY WORK – THEIR 'LANGUAGE' AND HOW TO DO PROGRAMS.

- Complete Home Study library.
- Special educational Mini-Computer supplied ready for use.
- Self Test program exercise.
- Services of skilled tutor available.

MASTER THE REST

- Radio Amateurs Licence.
- Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators – Digital Meters etc.

FREE

Please send your FREE brochure without obligation to:

Name __________

Address __________

____

(Block Caps please)

I am interested in
PRACTICAL ELECTRONICS _____
COMPUTER TECHNOLOGY _____
OTHER SUBJECTS (please state your interests) _____

PE/7/813

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,
4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS.

REMOTE CONTROL COMPONENTS AND KITS

LD271 IR Emitting diode	.36
SFH205 Photodiode Detector	.90
SL480 IC Pulse Amp.	1.70
SL490 32 Command Encoder/ transmitter	2.40
ML922 10-channel receiver + 3 analogue outputs	4.20
ML926 16-channel receiver 4 momentary binary outputs	1.40
ML928 16-channel receiver, 4 latched binary outputs	1.40
ML929 16-channel receiver, 4 latched binary outputs	1.40
Clip-on Plastic Reflector for IR LEDs, increases range	.20

ML925. A decoder designed for model/toy control, providing a 2-speed drive motor and three position latched steering system or a vehicle with momentary action steering and a third motor, eg. gun turret, winch, etc. Outputs also available for other facilities such as horn, turn indicators, headlights, etc. **2.10**

To make things EVEN EASIER, we have designed several new kits:—

MK6 – Simple Infra Red TRANSMITTER. A Pulsed infra red source which comes complete with a hand held plastic box. Requires a 9V battery. **4.20**

MK7 – Infra Red RECEIVER. Single channel, range approximately 20 ft. Mains powered with a triac output to switch loads up to 500W at 240V ac, but can be modified for use with 5 to 15V dc supplies and transistor or relay outputs. **9.00**

•Special Price •MK6 and MK7 together. Order as RC500K. 12.50

MK8 – Coded Infra Red TRANSMITTER. Based on the SL490, the kit includes 2 IR LEDs, measures only 8×2×1.3 cms. and requires a 9V (PP3) battery. **5.90**

MK9 – 4 Way KEYBOARD. For use with the MK8 kit, to make a 4-channel remote control transmitter. **1.90**

MK10 – 16-Way KEYBOARD. For use with the MK8 kit, to generate 16 different codes for decoding by the ML928 or ML926 receiver (MK12) Kit. **5.40**

MK11 – 10 On-Off Channel IR RECEIVER with 3 analogue outputs 0-10V) for controlling such functions as lamp brightness, volume, tone, etc. Other functions include an on/standby output and a toggle output, which may be used for sound muting. Based on ML922 decoder IC. Includes its own mains supply. **12.00**

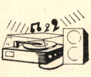

MK12 – 16 Channel IR RECEIVER. For use with the MK8 kit with 16 on/off outputs which with further interface circuitry, such as relays or triacs, will switch up to 16 items of equipment on or off remotely. Outputs may be latched or momentary, depending on whether the ML926 or ML928 is specified. Includes its own mains supply. **11.95**

MK13 – 11-Way KEYBOARD. For use with MK8 and MK11 kits. Transmits programme step + and –, analogue + and – (3), mute normalise analogue outputs, and on/standby. **4.35**

ARE YOU SITTING COMFORTABLY?

Our new TDR300K Touch Dimmer Kit will ensure that you are. Based on our highly successful TD300K touch controlled dimmer kit, the TDR300K incorporates an infra red receiver, enabling the lamp brightness to be varied and switched on or off by touch or remotely by means of a small hand held transmitter. The complete kit, which includes easy to follow instructions, will fit into a plaster depth box and the plastic front plate has no metal pads to touch, ensuring complete safety. Even a neon is included to help you locate the switch in the dark.

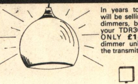

In years to come everyone will be selling remote control dimmers, but you can have your TDR300K kit now for ONLY **£14.30** for the dimmer unit and **£4.20** for the transmitter.

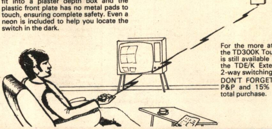

For the more athletic of you the TD300K Touchdimmer kit is still available at **£6.50** and the TDE/K Extension kit, for 2-way switching etc., is **£2.**

DON'T FORGET to add 50p P&P and 15% VAT to your total purchase.

24 HOUR CLOCK/APPLIANCE TIMER KIT

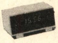

Switches any appliance up to 1KW on and off at preset times once per day. Kit contains: AY-5-1230 IC, 0.5″ LED display, mains supply, display drivers, switches, LEDs, triac, PCBs & full instructions.

CT1000K Basic Kit	£14.90
CT1000KB with white box (56/131×71mm)	£17.40
Ready Built	£22.50

DIGITAL VOLTMETER/ THERMOMETER KIT

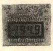

£19.50

Digital Voltmeter

Based on the ICL 7106. This kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5″ liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V supply (PP3 battery).

DISCO LIGHTING KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto isolated audio input.

DL1000K

This kit features a bidirecitonal sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorproates meter dimming control. **£14.60**

DLZ1000K

A lower cost version of the above, featuring undirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. **£8.00**

Optional Opto Input DLA1 **60p**

INTEGRATED CIRCUITS

555 Timer	21p
741 Op Amp	19p
AY-5-1224 Clock	£2.60
AY-5-1230 Clock/Timer	£4.50
AY-3-1270 Thermometer	£8.20
CA3080 Transconductance Op. Amp.	72p
CA3130 CMOS Op. Amp.	75p
ICL7106 DVM (LCD Drive)	£7.00
LM377 Dual 2W Amp.	£1.45
LM379S Dual 6W Amp.	£3.50
LM380 2W Audio Amp.	80p
LM382 Dual low noise re amp.	£1.00
LM386 250mW low voltage amp.	75p
LM1830 Fluid level Detector	£1.50
LM2917 F/V Converter (14 pin)	£1.60
LM3909 LED Flasher/oscillator	60p
LM3911 Thermometer	£1.20
LM3914 Dot/Bar Driver (linear)	£2.10
LM3915 Dot/Bar Driver (log.)	£2.20
MM74C911 4-digit Display Controller	£6.50
MM74C926 4-digit counter with segment output	£4.50
S566B Touchdimmer	£2.50
SL440 AC Power Control	£1.75
SN76477 Complex Sound Generator	£2.52
TBA800 5W Audio Amp.	68p
TBA810AS 7W Audio Amp.	£1.00
TCM7555 CMOS 555 Timer	79p
TDA1024 Zero Voltage Switch	£1.20
TDA2020 20W Audio Amp.	£2.85
TL081 J-FET Op. Amp.	37p
TL082 Dual J-FET Op. Amp.	60p
TMS1121 Clock/7 day timer	£8.50
ZN1034E Timer	£1.80

All ICs supplied with Data Sheets.

Data Sheets only – per device **10p**

EVERY DOOR SHOULD HAVE ONE

Whatever kind of door you have, our New Electronic Combination Lock will enable you to open it easily but make things very difficult for unwelcome visitors. The unit, which comes complete with a 10-way keypad, requires an easily remembered four digit code to be entered before the door can be opened, while the intruder has over 5,000 combinations to choose from. The code can be easily changed by means of a pre-wired plug and a momentary or latched output version can be made. The kit has even more uses in a car where it may be used to disable the ignition. Another useful feature is the Save Button. This stores the combination number, enabling the car to be used by authorised persons such as garage personnel without disclosing the code. The complete kit measures 7×6×3 cms. deep and consumes a mere 40uA when not in use, and will drive a 5V to 15V (750mA) solenoid or relay coil (not supplied) directly. So why not treat your door to a new lock for **ONLY £10.50** and think about all the keys you can lose or forget without ever locking yourself out. **(As featured in P.E. May '81.)**

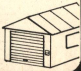

CMOS

4000	17p	4019	42p	4069	19p
4001	18p	4023	22p	4070	19p
4002	18p	4025	21p	4071	18p
4007	17p	4026	£1.30	4077	26p
4011	19p	4027	40p	4081	20p
4012	17p	4028	50p	4093	54p
4013	38p	4040	80p	4501	24p
4015	75p	4049	38p	4511	90p
4016	35p	4050	40p	4514	£1.80
4017	70p	4060	£1.08	4516	£1.80

CAPACITORS

Polyester 250V

0.01	6p	0.22	12p
0.002	6p	0.33	12p
0.033	7p	0.47	15p
0.047	7p	0.68	18p
0.068	7p	1.0	24p
0.1	7p	1.5	27p
0.15	12p	2.2	31p

Electrolytics A Axial R Radial

63V	1.0	R	5p	16V	10	R	5p
	2.2	R	5p		22	R	5p
	4.7	R	6p		33	R	5p
	10	R	7p		47	R	6p
	47	R	12p		100	R	8p
25V	22	A	8p		220	R	11p
	47	A	10p		470	R	14p
	100	A	14p		1000	R	20p
	110	A	15p	10V	47	A	8p
	470	A	24p		100	A	8p
	1000	A	34p		220	A	12p

Tantalum (bead)

35V	0.1	9p	10V	22	20p
	0.22	9p	6.3V	33	20p
	0.47	9p		47	27p
	1.0	9p	3V	100	27p
25V	2.2	10p			
	4.7	14p			
	10	20p			

Ceramic 50V

		1,000pF	4p
100pF	4p	2,200pF	4p
220pF	4p	4.700pF	5p
470pF	4p	10,000pF	5p

TRIACS

400V Plastic Case (Texas)

3A TIC206D	49p
8A TIC226D	58p
12A TIC236D	85p
16A TIC246D	96p
25A TIC263D	190p
6A with trigger Q4006LT	80p
8A isolated tab TXAL226B	65p
Diac	18p

VOLTAGE REGULATORS

Available in 5V, 12V, & 15V versions.

78L series 100mA pos.	26p
79L series 100mA neg.	60p
78 series 1A pos.	52p
79 series 1A neg. 5V.	75p
LM317T adjustable 1.2V-37V 1.5A	£1.80

MINI TRANSFORMERS

Standard mains primaries 240V a.c. 100mA secondaries

6-0-6V	80p
9-0-9V	85p
12-0-12V	90p

Opto Isolated Triac

MOC3020 0·6A/ 400V **£1.10**

LEDs

0.1″ Red	9p
0.1″ Green	12p
0.1″ Yellow	12p
0.2″ Red	9p
0.2″ Green	12p
0.2″ Yellow	12p
0.2″ clips	3p
Rectangular Red	16p
Rectangular Green	17p
Rectangular Yellow	17p

Flat Face rectangular, Triangular, Arrowhead or Square

Red	17p
Green	20p
Rec. Yellow	20p

RECTIFIERS

1N4001 1A/50V	4p
1N4004 1A/400V	6p
1N5401 3A/50V	8p
1N5404 3A/400V	10p
1A 50V Bridge	19p
1A 400V Bridge	22p
3A 50V Bridge	48p
3A 400V Bridge	58p

(Bridge rectifiers are miniature PCB mounting types)

DISPLAYS

FND504 Red 0·5″ c.c. pin compatible with DL504	75p
DL307 Red 0.3″ c.a. pin compatible with DL707	75p
DL727 Dual 0.5″ c.a. Red	£1.50
MP463 0.5″ c.c. Red, four digit multiplexed	£2.20
DL 34M 0·1″ Bubble magnified 4 digit c.c. multiplexed 14 pin DIL package. Red	£4.50

MINI KITS

These kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB, short instructions and all components.

MK1 TEMPERATURE CONTROLLER/ THERMOSTAT

Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater. 1KW **£4**

MK2 SOLID STATE RELAY

Ideal for switching motors, lights, heaters, etc. from logic. Opto-isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. **£2.60**

MK3 BAR/DOT DISPLAY

Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. **£4.75**

MK4 PROPORTIONAL TEMPERATURE CONTROLLER

Based on the TDA 1024 Zero voltage switch, this kit may be wired to form a "burst fire" power controller enabling the temperature of an enclosure to be maintained to within 0-5°C. 3KW **£5.55**

MK5 MAINS TIMER

Based on the ZN1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load 1KW. **£4.50**

BOXES

Moulded in high impact ABS. Supplied with lids and screws. Black.

B1	75×6×35mm	65p
B2	95×71×35mm	85p
B3	115×95×37mm	95p

VMOS POWER FETS

VN10KM 0 5A/60V (TO92)	52p
VN66AF 2A/60V (TO220)	88p

TRANSISTORS

BC108	8p	BFY50	20p
BC182	8p	TIP31A	40p
BC182L	8p	TIP32A	40p
BC212	9p	2N3055	45p
BC212L	9p	2N3442	90p
BC337	16p	2N3819	20p

D.I.L. I.C. SOCKETS

8 pin	8p	18 pin	17p
14 pin	12p	28 pin	24p
16 pin	14p	40 pin	36p
Soldercon Pins			50p/100

ZENER DIODES

400mW3 3V-30V	8p
1 3W 7.5-27V	15p

RESISTORS

¼W 10 ohm-10M. E12 series.

Pack of 10 (one value)	10p
10 packs (10 values)	80p

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD 50p P&P and 15% VAT TO TOTAL. OVERSEAS CUSTOMERS ADD £1.50 (Europe). £4 (elsewhere) for P&P. Send sae for price list and with all enquiries. Callers welcome 9.30 5.00 (Mon Fri) 10.00 4.00 (Sat.)

TK Electronics
(PE7), 11 BOSTON ROAD
LONDON W7 3SJ. 01-579 9794

New! Sinclair ZX81 Personal Computer.

Kit: £49.95 complete

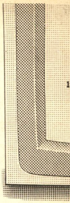

Built: £69.95 complete

Reach advanced computer comprehension in a few absorbing hours

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. At £99.95, the ZX80 offered a specification unchallenged at the price.

Over 50,000 were sold, and the ZX80 won virtually universal praise from computer professionals.

Now the Sinclair lead is increased: for just £69.95, the new Sinclair ZX81 offers even more advanced computer facilities at an even lower price. And the ZX81 kit means an even bigger saving. At £49.95 it costs almost 40% less than the ZX80 kit!

Lower price: higher capability
With the ZX81, it's just as simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, or to select a program off a cassette through the keyboard.

Higher specification, lower price – how's it done?
Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

Kit or built – it's up to you!

The picture shows dramatically how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.

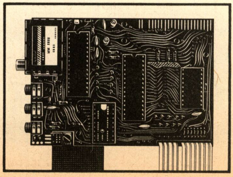

Proven micro-processor, new 8K BASIC ROM, RAM – and unique new master chip.

New Sinclair teach-yourself BASIC manual

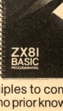

Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to con programs. You need no prior know – children from 12 upwards soon become familiar with computer operation.

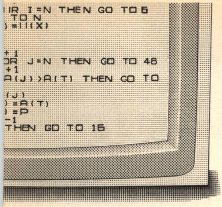

```
IIR I=N THEN GO TO 6
 TO N
)=II(X)

+1
OR J=N THEN GO TO 46
+1
A(J)>A(T) THEN GO TO

(J)
)=A(T)
)=P
-1
THEN GO TO 16
```

v, improved specification

30A micro-processor – new faster
sion of the famous Z80 chip, widely
recognised as the best ever made.

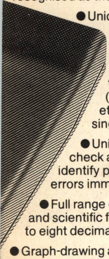

- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and merical arrays.

Jp to 26 FOR/NEXT loops.

Randomise function – useful for games well as serious applications.

Cassette LOAD and SAVE with med programs.

K-byte RAM expandable to 16K tes with Sinclair RAM pack.

Able to drive the new Sinclair printer ot available yet – but coming soon!)

Advanced 4-chip design: micro-ocessor, ROM, RAM, plus master chip nique, custom-built chip replacing ZX80 chips.

sinclair ZX81

inclair Research Ltd,
Kings Parade, Cambridge, Cambs.,
32 1SN. Tel: 0276 66104.
eg. no: 214 4630 00

If you own a Sinclair ZX80...

The new 8K BASIC ROM used in the Sinclair ZX81 is available to ZX80 owners as a drop-in replacement chip. (Complete with new keyboard template and operating manual.)

With the exception of animated graphics, all the advanced features of the ZX81 are now available on your ZX80 – including the ability to drive the Sinclair ZX Printer.

Coming soon– the ZX Printer.

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alphanumerics across 32 columns, *and* highly sophisticated graphics. Special features include COPY, which prints out exactly what is on the whole TV screen without the need for further instructions. The ZX Printer will be available in Summer 1981, at around £50 – watch this space!

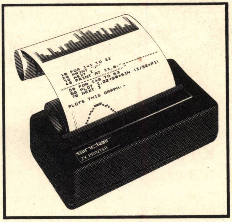

16K-BYTE RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.

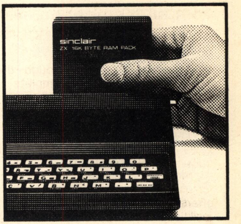

How to order your ZX81

BY PHONE – Access or Barclaycard holders can call 01-200 0200 for personal attention 24 hours a day, every day.
BY FREEPOST – use the no-stamp-needed coupon below. You can pay by cheque, postal order, Access or Barclaycard.
EITHER WAY – please allow up to 28 days for delivery. And there's a 14-day money-back option, of course. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST 7, Cambridge, CB2 1YY. **Order**

Qty	Item	Code	Item price £	Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack(s).	18	49.95	
	8K BASIC ROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95

TOTAL £ ______

Please tick if you require a VAT receipt ☐
*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £ ______
*Please charge to my Access/Barclaycard account no. ______

*Please delete/complete as applicable. Please print.

Name: Mr/Mrs/Miss ______

Address ______

FREEPOST – no stamp needed. **PRE07**

DIGITAL THERMOMETER

This is one of our range of PROJECT KITS. The kit includes all the parts required to complete the project, including the case and battery. Calibration is simple and an accuracy of up to 1% can be obtained.

The instrument covers the range −50°C to +150°C. Read-out is on an LCD display. Powered by a 9V battery it is an ideal instrument for home or laboratory.

Full building instructions included.

PROJECT KIT 800104 £26.50

£3 off

SPECIAL SUMMER OFFER!!!

THIS KIT IS NOW ONLY **£23.50**

IF ORDERED BEFORE SEPT 30TH 1981

■ PROJECT PACKS

These PROJECT PACKS include PCB, Components and data.

AERIAL AMPLIFIER
Up to 20DB of gain on your TV or FM radio signal. Order TV or FM (VHF) version. (80022) **£5.45**

DISCO LIGHT DISPLAY
Three lamps controlled by a audio filter/triac circuit. Ideal for discos and parties. **£5.80**

DRILL SPEED CONTROLLER
Controls the revs on your mains electric drill. **£4.80**

LOGIC ANALYSER
The first Analyser for the home constructor. Useful to track down problems in digital systems. Send for full specification. (81094) **£87.25**

HIGH COM NOISE REDUCTION SYSTEM
Performs better than other tape noise reduction systems. Developed by Telefunken. Pack contains pre-built and tested modules. (81117) **£49.55**

IONISER
Generates negative Ions for a real healthy atmosphere. Easy to build. (9823) **£10.50**

SOUND EFFECTS GENERATOR
An experimental circuit that produces train, motorbike, and space noises. Lots of fun. (81112) **£8.30**

PROGRAMMABLE SLIDE FADER
Uses computer techniques for you to program, on tape, a slide show for two projectors. Fades and changes are reproduced automatically. (81002) **£46.50**

TALK FUNNY
Simple Ring Modulator circuit that distorts your voice, or musical instrument. (80052) **£10.00**

MINIMIXER
Mixer on a single PCB for two microphones, tape and two turntables. Ideal for Discos etc. (81068) **£37.50**

NEW SUMMER 1981 CATALOGUE

NOW AVAILABLE

Send a 14p stamp for your copy. Over 70 projects for you to build. Our comprehensive ranges of high quality components, integrated circuits and hardware are listed. Lots of ideas for your hobby in 44 pages of information. SEND FOR YOUR COPY NOW

HOW TO ORDER

Send a cheque or postal order to DORAM ELECTRONICS LTD. or write or phone your ACCESS account number. Please add 40p for postage and packing in the UK. All our prices include VAT. A telephone answering service is available outside our office hours.

DORAM ELECTRONICS LTD.
FITZROY HOUSE, MARKET PLACE, SWAFFHAM, PE37 7QH.

☎ (0760) 21627

Access

DORAM
ELECTRONICS LTD

---

3 CHANNEL SOUND/LIGHT CHASER

LB31000SLC **£32.70**

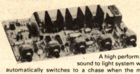

A high performance sound to light system which automatically switches to a chase when the music ceases. Super sensitive with an anti interference circuit, the unit will operate from practically any amp and control up to 1,000W/channel, 5Hz to 70K. Controls: bass/mid/treble/master sensitivity/chase speed.

3 CHANNEL SOUND/LIGHT

LB31000SL

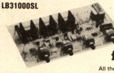

£22.70

All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.

2/4/8 CHANNEL CHASER

LB81000LC

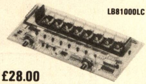

£28.00

An all logic chaser system for use with up to 8 channels at 1,000 watts each. Facilities include footswitch trigger and module cascading (16, 24, 32 channel, etc.), chase speed and re-cycle delay.

4 CHANNEL SEQUENCER

LB41000LS

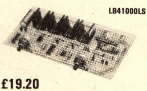

£19.20

A 4 channel sequence generator for banks of lamps up to 1,000W per channel. Two speed controls, cross effect to provide settings between seconds and rapid burst.

1 AND 3 CHANNEL DIMMERS

LB31000LD

LB31000LD **£16.20**

Single channel version

LB11000LD **£7.20**

Power dimmer units for theatre/stage applications up to 1,000W per channel, with on board suppressing. The unit is also available without rotary pots for use with sliders —

LB31000LD (no pots) **£15.00** Sliders **75p** each.

ROPE LIGHTS/DRIVER

LB41000LC-S

£24.20

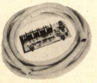

4 colour **ROPES** (6 metre) **£36.50**

A four channel chaser up to 1,000W per channel, with a sound trigger facility. The music input signal modulates the speed of the chase giving an excellent sound/light effect. The unit will control up to 10 ropes with chase speed and trigger level control

STEREO DISCO MIXER/PREAMP

LBPA3
M – Magnetic
C – Ceramic

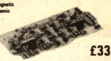

£33.70

Magnetic or ceramic deck versions – please state

All the requirements of a stereo disco preamp on one board, left and right deck mixers/tone controls/mic. mixer/tones/mic. auto fade over decks/and P.F.L. The unit can be used with either LB100/150/250.

Full set of pots — **£8.63**

LBPA2

£17.20

A four channel mixer and tone stage for mics, guitars, etc. Can be used with any LB amps. Set of pots **£2.74.**

LBPA1

£19.50

A stereo hi-fi preamp and tone stage for mag. p.u./tape/tuner, etc. Set of pots **£3.27.**

3-WAY ACTIVE CROSSOVER

LBAC01

£17.90

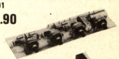

LBPSU1

£7.20

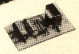

Bass/mid/treble active crossover with stage booster! Available with crossover points of 200 or 300Hz, and 2K or 3KHz (please specify) LBPSU1 supply for LBAC01. (1 or 2).

POWER AMPLIFIERS

Tough dealing power amps for use in sound systems. Open/short circuit protection and fused. Heavy gauge heatsinks and rugged o/p devices (all operate down to 4 ohms).

25W R.M.S.	110W R.M.S.	160W R.M.S.	270W R.M.S.
20Hz to 60K 0.07% THD 96DB S/N LB25	5Hz to 25K 0.1% THD 110DB S/N LB100	5Hz to 25K 0.1% THD 110DB S/N LB150	5Hz to 25K 0.1% THD 110DB S/N LB250
£11.20	**£19.70**	**£29.20**	**£43.50**

Note all models are available with either 500mV or 775mV sensitivity. Please state when ordering.

LBRLD1

£6.20

A de-thump unit for use with any LB power amps.

POWER AMP POWER SUPPLIES

LB25PS	LB100PS	LB150PS	LB250PS
£11.20	**£16.20**	**£19.00**	**£26.50**
P/P £1.20	P/P £1.40	P/P £1.40	P/P £1.70

FOR GUITARS, P.A. AND DISCO.

PIEZO HORNS

£5.75

P/P 50p

CELESTION LOUDSPEAKERS

(ALL STANDARD CONE 8 OHMS)

G10-50 (10 inch 50W)	G12-65 (12 inch 65W)	G12-100 (12 inch 100W)	G15-100 (15 inch 100W) Cambric Edge
£14.70	**£20.70**	**£26.45**	**£36.45**
P/P £1.70	P/P £1.70	P/P £1.70	P/P £2.00

NEW — MINI MODULES — NEW

Ingeniously designed mini pre-amplifier 'building blocks' for use in music and P.A. applications. You choose the type and number of units you require for your particular system and mount each module via its control direct onto your panel.

LBMM1 Pre-amp for mics, guitars etc.
LBMM2 Mixer for up to 6 LBMM1/2/3/4/5
LBMM3 Bass/boost/cut for either LBMM1/2/3/4/5
LBMM4 Mid-boost/cut for either LBMM1/2/3/4/5
LBMM5 Treble boost/cut for either LBMM1/2/3/4/5
LBPSU1 ± 15V supply for up to **12 modules**
LBPSU ± 15V regulated for up to 50 modules

MM1 £4.50; MM2 £5.20; MM3 £5.70; MM4 £5.70; MM5 £5.70; PSU1 £7.20; RPSU £14.50.

Discount on MM1/2/3/4/5 10 to 24 – 20%, 25+ – 30%

Buy it with Access

L & B

ELECTRONIC MODULES

PROFESSIONAL ENGINEERING BY PROFESSIONALS

45 Wortley Road, West Croydon, Surrey
CR0 3EB. Tel. 01-689 4138

Each module is manufactured from the highest quality components, fully tested, supplied with a connection and circuit diagram and guaranteed for twelve months.

All prices shown are **VAT** inclusive. Please include **50p** post/packing except where individually stated. To mail order send cheque/P.O./registered cash or Access number. C.O.D. service £1 extra. For our catalogue/specifications send 50p.

PLEASE NOTE THIS COMPANY HAS NO CONNECTION WITH LB ELECTRONICS OF HILLINGDON

BI-PAK

SEMICONDUCTORS
DEPT. PE7, PO Box 6, WARE, HERTS.
Visit our Shop at: 3 Baldock Street, Ware, Herts.

GIRO NO. 388 7006
TEL: 0920 3182
TELEX: 817861

PLUGS AND SOCKETS

1625	2mm Plug RED	£0·16
1626	2mm Plug BLACK	£0·16
1628	2mm Socket RED	£0·16
1629	2mm Socket BLACK	£0·16
1634	4mm Plug BLACK	£0·16
1637	4mm Plug RED	£0·16
1640	4mm Socket BLACK	£0·16
1643	4mm Socket RED	£0·16
1652	2 Pin DIN Chassis Socket	£0·08
1654	5 Pin 180° DIN Chassis Socket	£0·12
1655	5 Pin 240° DIN Chassis Socket	£0·12
1656	2·5mm Chassis Socket	£0·10
1657	3·5mm Chassis Socket	£0·10
1658	Metal Std. Jack Chassis Socket (mono)	£0·18
1659	Metal Std. Jack Chassis Socket (stereo)	£0·24
1660	Single Phono socket	£0·09
1661	Double Phono Socket	£0·12
1662	Coax surface socket	£0·22
1663	Coax Flush Socket	£0·22
1664	Plastic Std. Jack Socket (mono)	£0·20
1665	Plastic Std, Jack Socket (stereo) for headphones	£0·32
1666	Car Aerial Chassis Socket	£0·18
1667	AC Chassis Socket	£0·16
1668	4 Way Phono Chassis Socket	£0·22
1669	Plastic Std. Jack Chassis socket stereo switched	£0·32
1670	AC switched non rev. socket	£0·32
1672	2 Pin DIN line socket	£0·10
1674	5 Pin 180° DIN line socket	£0·17
1675	5 Pin 240° DIN line socket	£0·20
1676	2·5mm Plastic line socket	£0·12
1677	3·5mm Plastic line socket	£0·12
1678	Std. jack plastic line socket (mono)	£0·17
1679	Std. jack metal line socket (mono)	£0·30
1680	Std. jack plastic line socket (stereo)	£0·22
1681	Std. jack metal line socket (stereo)	£0·38
1682	Phono lin line metal socket	£0·16
1684	Coax line socket	£0·34
1685	Coas back-back socket	£0·14
1686	AC linesocket (2 pin USA Type)	£0·18
1687	Phono in line plastic socket	£0·12
1688	Phono back-back socket	£0·20
1689	2 Pin DIN plug	£0·10
1692	5 Pin 180° DIN plug	£0·14
1693	5 Pin 240° DIN plug	£0·14
1696	2·5mm Plug (Metal)	£0·15
1697	3·5mm Plug (Plastic)	£0·12
1698	3·5mm Plug (Metal)	£0·16
1699	Std. Plastic Jack Plug (Mono)	£0·16
1700	Std. Metal Jack Plug (Mono)	£0·30
1701	Std. Metal Jack Plug (Stereo)	£0·35
1702	Plastic Phono Plug	£0·11
1703	Car Aerial Plug	£0·24
1704	Coax TV Plug	£0·22
1705	Right Angle Jack Plug (Mono)	£0·20
1706	2·5mm Plastic Plug	£0·12
1707	Std. Plastic Jack Plug (Stereo)	£0·22
1708	Metal Phono Plug	£0·14
1709	2·1mm DC Plug	£0·12
1710	2·5mm DN Plug	£0·12
1711	AC Plug (2 pin USA Type)	£0·16
1712	AM Aerial Plug	£0·17
1713	Cassette AC Input Plug	£0·15
1714	FM Aerial Plug	£0·13
1715	PL259 Plug	£0·40
1716	SO239 Socket 4 hole fixing	£0·38
1717	SO239 Socket single hole fixing	£0·40
1718	PL258 Double Ended Female Coupler	£0·40
1719	NC555 Reducer for PL259 (Small)	£0·16
1720	NC556 Reducer for PL259 (Large)	£0·16
1721	M359 Right Angle Coupler PL259 SO239	£0·75
1722	M358 T Connector Female-Male-Female	£0·85
1723	NC563 Inline Coupler PL259 × 2	£0·60
1724	BNC15 50 ohm standard plug	£0·64
1725	BNC 1502 Chassis mounting socket	£0·75
1726	BNC1503 Chassis mounting socket single hole fixing	£0·70
1727	BNC1520 BNC male to SO239 female	£0·85
1728	BNC1521 BNC female to PL259 male	£0·85
1729	Junction Box on in two out	£0·80
1730	Low loss splitter	£1·00

AERIALS

105	Adjustable Aerial Gutter Mount	£3·00
106	C.B. Mobile Antenna	£9·50
107	FM Indoor Ribbon Aerial	£0·50
108	4 Section Car Aerial (Stainless)	£2·16
109	4 Section Car Aerial (Chrome)	£1·80
110	8 Section 1200mm Telescopic Aerial	£2·00
111	8 Section 750mm Telescopic Aerial	£2·60
112	5 Section 570mm Telescopic Aerial	£2·64
113	Roof Mounting Aerial	£3·80

AUDIO LEADS

114	5 pin – 3·5mm 3 & 5 connected	£0·65
115	5 pin – 3·5mm 1 & 4 connected	£0·65
116	Car Aerial Ext Lead	£1·00
117	Mains Cassette Lead	£0·48
119	2 × 2 pin Plug in In Line Stereo Jack Socket	£0·74
120	Universal Car Adaptor Plug	£0·52
123	20ft. Coiled Guitar Lead	£1·50
125	5 pin to 5 pin DIN	£0·65
126	5 pin to DIN to open ends	£0·65
127	5 pin to DIN to 4 Phono Plugs	£1·00
128	5 pin Plug to 5 pin socket	£0·75
129	5 pin to 5 pin Plug (Mirror image)	£0·72
130	2 pin Plug to 2 pin Line Socket 5 mtrs	£0·55
132	2 pin Plug to 2 pin Line Socket 10 mtrs	£0·85
133	5 pin Plug to Phono Plug	£0·65
136	Headphones ext lead 6mtrs	£1·50

DON'T FORGET
YOUR NEW BI-PAK
CATALOGUE!
OUT NOW!
ONLY 75p
PLUS 25p p & p

COMPONENT PACKS

C26	300 Performed carbon resistors mixed ¼-½w	£1·00
C27	50 2-10 watt wire wound resistors mixed	£1·00
C28	300 Approx Resistors mixed values (count by weight)	£1·00
C29	200 Approx Capacitors mixed values and types (count by weight)	£1·00
C30	60 Precision Resistors 1-5% tol.	£1·00
C31	100 Approx 1/8 watt min Resistors mixed values	£1·00
C32	6 Pieces Ferrite Rods	£1·00
C33	60 Metres Single strand wire assorted colours	£1·00
C34	15 Reed switches glass type	£1·00
C35	5 Micro switches assorted types including min.	£1·00
C36	6 Assorted Audio jack sockets and plugs	£1·00
C37	100 Disc ceramic caps mixed values	£1·00
C38	20 Assorted pots	£1·00
C39	40 C280 type capacitors metal foil	£1·00
C40	60 Electrolytics assorted	£1·00
C41	50 Assorted polyestor/polystyrene	£1·00
C42	60 Low voltage Electrolytics mixed values up to 10v.	£1·00
C43	15 Assorted slider pots	£1·00
C44	10 Dual gang pots log and in assorted	£1·00
C45	1 Pack assorted Handware nuts/bolts etc.	£1·00
C46	10 Assorted switches slide/rocker/mains	£1·00
C47	3 Relays 24v coil	£1·00
C48	20 Assorted knobs push, screw and slider types	£1·00
C49	20 Assorted Tag strips and panels	£1·00
C50	4 Wave change switches rotary	£1·00
C51	1 Pack of assorted PVC sleeving and markers	£1·00
C52	100 ⅓ watt resistors mixed values	£1·00
C53	35 Presets assorted type and values	£1·00
C54	40 Metres stranded wire assorted colours	£1·00
C55	10 Assorted Din/sockets/Coax/speakers/phono	£1·00
C56	10 Assorted plugs Din/coax/speakers/etc.	£1·00
C57	10 Metres assorted cable. Mains/speaker/coax/microphone	£1·00
C58	100 sq in copper clad board single side paper	£1·00
C59	75 sq in copper clad fibreglass board	£1·00

BABANI BOOKS

No.	TITLE	PRICE
BP160	Coil Design and Construction Manual	£1·25
BP202	Handbook of Integrated Circuits (IC's) Equivalents & Substitutes	£1·45
BP205	First Book of Hi-Fi Loudspeaker Enclosures	£0·95
BP207	Practical Electronics Science Projects	£0·75
BP208	Practical Stereo and Quadrophony Handbook	£0·75
BP211	First Book of Diode Characteristics Equivalents and Substitutes	£1·25
BP213	Electronic Circuits for Model Railways	£1·00
BP214	Audio Enthusiasts Handbook	£0·85
BP218	Build Your Own Electronic Experiments Laboratory	£0·85
BP219	Solid State Novelty Projects	£0·85
BP220	Build Your Own Solid State Hi-Fi and Audio Accessories	£0·85
BP221	28 Tested Transistor Projects	£1·25
BP222	Solid State Short Wave Receivers for Beginners	£1·25
BP223	50 Projects Using IC CA3 130	£1·25
BP224	50 CMOS IC Projects	£1·25
BP225	A Practical introduction to Digital IC's	£1·25
BP226	How to Build Advanced Short Wave Receivers	£1·20
BP227	Beginners Guide to Building Electronic Projects	£1·25
BP228	Essential Theory for the Electronics Hobbyist	£1·25
BP6	Engineers and Machinists Reference Tables	£0·70
BP7	Radio and Electronic Colour Codes and Data Chart	£0·35
BP14	Second Book of Transistor Equivalents and Substitutes	£1·10
BP23	First Book of Practical Electronic Projects	£0·75
BP24	52 Projects Using IC41	£0·95
BP27	Giant Chart of Radio Electronic Semiconductor and Logic Symbols	£0·60
BP28	Resistor Selection Handbook (International Edition)	£0·60
BP29	Major Solid State Audio Hi-Fi Construction Projects	£0·85
BP32	How to Build Your own Metal and Treasure Locators	£1·35
BP33	Electronic Calculator Users Handbook	£1·25
BP34	Practical Repair and Renovation of Colour TVs	£1·25
BP35	Handbook of IC Audio Preamplifier & Power Amplifier Construction	£1·25
BP36	50 Circuits Using Germanium, Silicon and Zener Diodes	£0·75
BP37	50 Projects Using Relays. SCR,s and TRIACs	£1·25
BP38	Fun and Games with Your Electronic Calculator	£0·75
BP39	50 (FET) Field Effect Transistor Projects	£1·50
BP40	Digital IC Equivalents and Pin Connections	£2·50
BP41	Linear IC Equivalents and Pin Connections	£2·75
BP42	50 Simple L.E.D. Circuits	£0·95
BP43	How to Make Walkie-Talkies	£1·50
BP44	IC555 Projects	£1·75
BP45	Projects in Opto-Electronics	£1·25
BP46	Radio Circuits Using IC's	£1·35
BP47	Mobile Discotheque Handbook	£1·35
BP48	Electronic Projects for Beginners	£1·35
BP49	Popular Electronic Projects	£1·45
BP50	IC LM3900 Projects	£1·35
BP51	Electronic Music and Creative Tape Recording	£1·25
BP52	Long Distance Television Reception (TV-DX) for the Enthusiast	£1·95
BP53	Practical Electronic Calculations and Formulae	£2·25
BP54	Your Electronic Calculator and Your Money	£1·35
BP55	Radio Stations Guide	£1·75
BP56	Electronic Security Devices	£1·45
BP57	How to Build Your Own Solid State Oscilloscope	£1·50
BP58	50 Circuits Using 7400 Series IC's	£1·35
BP59	Second Book of CMOS IC Projects	£1·50
BP60	Practical Construction of Pre-amps. Tone Controls, Filters & Attn.	£1·45
BP61	Beginners Guide to Digital Techniques	£0·95
BP62	Elements of Electronics – Book 1	£2·25
BP63	Elements of Electronics – Book 2	£2·25
BP64	Elements of Electronics – Book 3	£2·25
BP65	Single IC Projects	£1·50
BP66	Beginners Guide to Microprocessors and Computing	£1·75
BP67	Counter, Driver and Numeral Display Projects	£1·75
BP68	Choosing and Using your Hi-Fi	£1·65
BP69	Electronic Games	£1·75
BP70	Transistor Radio Fault-Finding Chart	£0·50
BP71	Electronic Household Projects	£1·75
BP72	A Microprocessor Primer	£1·75
BP73	Remote Control Projects	£1·95
BP74	Electronic Music Projects	£1·75
BP75	Electronic Test Equipment Construction	£1·75
BP76	Power Supply Projects	£1·75
BP77	Elements of Electronics – Book 4	£2·95
BP78	Practical Computer Experiments	£1·75
BP79	Radio Control for Beginners	£1·75
BP80	Popular Electronic Circuits – Book 1	£1·95

BUDGET STEREO HEADPHONES

BLACK WITH PADDED EARCUPS
IMPEDANCE 8 ohms
FREQUENCY RESPONSE
30-18,000 HZ
WEIGHT 300gms
£4·20 O/No 885

GOOD QUALITY STEREO HEADPHONES

DOUBLE PADDED HEAD BAND
CIRCULAR VENTED PADDED PIECES
BLACK AND ALUMINIUM FINISH
IMPEDANCE 8 ohms
FREQUENCY RESPONSE
20-19,000 HZ
WEIGHT 350gms
£8·25 O/No 884

SUPERIOR QUALITY STEREO HEADPHONES

WIDE BLACK PADDED HEAD BAND WITH PADDED MATT ALUMINIUM EARCUPS
IMPEDANCE 8 ohms
FREQUENCY RESPONSE
15-25,000 HZ
WEIGHT 290 gms
£15·85 O/No 883

ENAM. COPPER WIRE

		2oz
365	40 swg	£1·00
366	38 swg	£0·88
367	36 swg	£0·90
368	34 swg	£0·82
369	32 swg	£0·80
370	30 swg	£0·80
371	28 swg	£0·76
372	26 swg	£0·74
373	24 swg	£0·66
374	22 swg	£0·62
375	20 swg	£0·60
376	18 swg	£0·60
377	16 swg	£0·52
378	14 swg	£0·52

TINNED COP. WIRE 4oz

379	24 swg	£0·94
380	22 swg	£0·83
381	20 swg	£0·88
382	18 swg	£0·90
383	16 swg	£0·78

HARDWARE IN PACKS OF 25

839	OBA 1″ Bolt	£0·70
840	OBA ½″ Bolt	£0·40
842	2BA 1″ Bolt	£0·35
843	2BA ½″ Bolt	£0·30
844	2BA ¼″ Bolt	£0·32
845	4BA 1″ Bolt	£0·28
846	4BA ½″ Bolt	£0·20
847	4BA ¼″ Bolt	£0·18
848	6BA 1″ Bolt	£0·24
849	6BA ½″ Bolt	£0·18
850	6BA ¼″ Bolt	£0·20
851	OBA Solder Tags	£0·20
852	2BA Solder Tags	£0·16
853	4BA Solder Tags	£0·14
854	6BA Solder Tags	£0·12
855	OBA Full Nut	£0·42
856	2BA Full Nut	£0·26
857	4BA Full Nut	£0·18
858	6BA Full Nut	£0·18
859	OBA Washer	£0·12
860	2BA Washer	£0·09
861	4BA Washer	£0·09
862	6BA Washer	£0·09

FUSE HOLDERS

506	20mm Chassis Fuse Holder	£0·14
507	1¼″ Chassis Fuse Holder	£0·14
508	1¼″ Car in line Fuse Holder	£0·12
509	20mm Panel Fuse Holder	£0·26
510	1¼″ Panel Fuse Holder	£0·32

TRANSFORMERS

2021	6-0-6v 100mA	£0·90
2022	9-0-9v 75mA	£0·90
2023	12-0-12v 100mA	£1·15
2024	0-6v 0-6v 280mA	£1·60
2025	0-12v 0-12v 150mA	£1·80
2026	6-0-6v 1 Amp	£2·40
2027	9-0-9v 75mA	£2·00
2028	12-0-12v 1 Amp	£2·50
2029	15-0-15v 1 Amp	£2·75
2031	Multi tap ½ Amp	£3·40
2032	Multi tap 1 Amp	£4·80
2033	Multi tap 2 Amp	£6·40
2034	0-35v 1 7 Amp	£4·90
2035	0-55v 2 Amp	£6·65
2036	0-17v 750mA	£2·85
2037	Min audio output	£0·25
2038	min audio driver	£0·36
2040	0-45-55v 1·5 Amps	£6·45
2041	0-55-65v 2 Amp	£8·45
2042	0-25v 2 Amps	£4·50
2043	15-0-15 150mA	£2·40

Access and Barclaycards accepted - just telephone our Orderline - Ware (STD 0920) 3182. Add 15% V.A.T., and 50p postage per order. Terms: C.W.O., cheques, Postal Orders payable to Bi-Pak.

If you're into MICROPROCESSORS then they should be into an M P UroBreadBoard

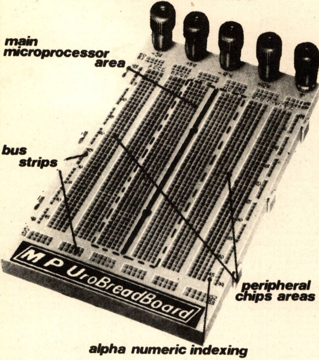

- * MPU Section accepts 24, 28, 40 & 64 pin DIL microprocessors
- * Auxiliary Areas accept any .3" or .6" RAM, ROM or peripheral chip
- * Power Bus Strips on all sides
- * 5 incoming turret Power Terminals
- * Component Support Bracket included
- * Over 1400 contact points
- * Alpha-Numeric column and row indexing
- * Eurocard size (160mm x 100mm)
- * Slots onto all BIMBOARDS
- * Non-Slip rubber backing
- * Ideal for schools and colleges
- * Long life, <10m.ohms, nickel silver contacts

The PROFESSIONALS breadboard that BEGINNERS can start on

BOSS *INDUSTRIAL MOULDINGS LTD*

2 Herne Hill Rd, London SE24 0AU, England
Telephone 01-737 2383 Telex 919693
Cables & Telegrams: LITZEN LONDON SE24

Please send me . . . . MPUroBreadBoard(s) @ £18.
This price includes VAT & PP, is applicable from Mar. 1, '81, but please add 15% for Overseas Orders, make cheques/P.O. payable to BOSS Industrial Mouldings Ltd and allow 10 days for order processing and cheque clearance etc.

I enclose a cheque/P.O. to the value of £..........................

Name . . . .
Company . . . .
Address . . . .
. . . .
. . . .
Telephone Number PE/7/81

Mullard Modules

LP1171	LP1179	LP1186	LP1157
IF. Strip	AM.FM Front end	varicap	Med & Long tuner
Pair £5.75		£5.00	£2.50

Complete with Data

Foster Dynamic Microphones
200 ohm impedence: £1.75 Pair
Moving coil Complete on Chassis

Ultra Sonic Transducers 40KC/S
Complete on 18" Screened cable £1.75 each
Pairs £2.95

Ultra sonic Transmitter
Complete unit (uncased requires 1.5V) £3.25

Stereo Cassette Tape Heads
Quality replacement for most recorders with mounting plate. Record/Replay £2.80

Hewlett – Packard Displays (5082-7650) HIGH EFFICIENCY & VERY BRIGHT

Half inch red common anode definitely the brightest will replace (DL707)

Excellent character appearance, evenly lighted segments, wide viewing angle, body colour improves 'Off' segment contrast. Categorized for luminous intensity, use of like categories yields a uniform display. Consumption as low as 3mA per segment, designed for multiplex operation. Standard 14 pin dual-in-line package configuration.

ONLY £1.00 each Set of 6 for **£5**

Vero Computer Frames
19×8" with 64 runners & guides.
List price £43. Our price £17.95.

National 4116 Dynamic (16K RAM)
200 N/Seconds £1.95
Less 10% per 4. 15% per 8.

All items new stock – delivery by return post
All items inclusive of VAT & Post Paid. **Quantity Discounts** 15% per 10. 20% per 50.

SCOOP ONLY £29.95 +V.A.T.

Professional *ASCII* Keyboards

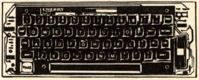

The 'CHERRY' Computer Keyboard

BRITISH MADE

- 52 KEY 7 BIT ASCII CODED
- POSITIVE STROBE. +5V - 12V.
- FULL ASCII CHARACTERS
- PARALLEL OUTPUT WITH STROBE
- POWER LIGHT ON CONTROL
- CHIP BY GENERAL INSTRUMENT (G.I.) TTL OUTPUT
- SUPERBLY MADE SIZE 13 x 5.5 x 1.5 ins.
- BLACK KEYS WITH WHITE LEDGENS
- ESCAPE. SHIFT. RETURN & RESET KEYS
- CONTROL. REPEAT & BELL

Complete with DATA

Ideal for use with **TANGERINE, TRITON, TUSCAN, APPLE and most computers.** Ex-Stock from HENRY'S

This is definitely the BEST BUY. FULLY GUARANTEED. Supplied BRAND NEW in manufacturers original packing. Just post remittance total £35.95 (incl. V.A.T. & Post)

HENRY'S

404 Edgware Road,
London, W2, England 01-402 6822

4¼in x 3¼in **METER.** 30μA, 50μA or 100μA, **£5.10.** 50p P. & P.

MICROPHONES FOR TAPE RECORDERS

DM228R 200 ohm with 3·5 and 2·5mm Jack Plugs	**£1.70**
DM229R 50K with 3·5 and 2·5mm Jack Plugs	**£2.25**
DM18D 200 ohm with 5 and 3 pin Din Plugs	**£1.99**

Postage on above microphones 17p

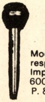

CARDIOID DYNAMIC MICROPHONE

Model UD-130 Frequency response 50–15,000c/s. Impedance Dual 50K and 600 ohms. **£8.02.** 50p P. & P.

2in x 2in meters 500μA, **£4.14** 17p P.& P.

60 x 45mm meters 50μA, 100μA, 500μA and 1mA VU meter, **£4.00.** 26p P. & P.

6V BUZZERS. 50mm diameter 30mm high, **52p.** 15p. P. & P.

MULTI- METER

7N 360TR
20,000 ohm/volt
RESISTANCE RANGES
X1, X10, X1K, X10K
£13.30
P.&P. 75p

LP30 LOW PASS FILTER
Cut off frequency 30MHz
£3.50 post 75p

SWR9-SWR & FS METER
£10.20 Post 75p

CX3 CO-AX SWITCH
For one transceiver to 3 aerials or 3 aerials to one transceiver. 150 watt **£5.65** Post 75p

PL259 Plug **33p;** Socket **33p;** PL259/SO239 Angled Connector **70p;** 1 watt dummy lead **95p;** 2m Rubber Neck Aerial with PL259 Plug **£3.30.** POST ON ABOVE ITEMS 14p.

All above prices include V.A.T. Send 50p for new 1980 fully illustrated catalogue, S.A.E. with all enquiries. Special prices for quantity quoted on request.

M. DZIUBAS
158 Bradshawgate · Bolton · Lancs. BL2 1BA

MC Micro Circuits Prime components~Low prices.

Dept. PE7, Unit 9/10, 1st Floor, East Block, 38 Mount Pleasant, London WC1X 0AP. Tel: 01-837 1165, 01-278 7369. Telex: 8953084 Maclin G.

All our microchips are at micro prices. Don't be fooled by low prices. We do not offer for sale surplus, sub-spec or rebranded devices. All our parts are quaranteed new, first quality, factory prime, full spec devices. It is also our policy to offer you the best of new devices that become available and these are featured regularly. Prices are exclusive of p&p and VAT – please refer to "Ordering Information" before ordering. Official orders from schools, colleges, universities and Gov. authorities accepted.

NEW, LOW, LOW PRICES ON MEMORIES

Compare our prices before you buy elsewhere! All devices are brand new, factory prime, full spec. and fully guaranteed!
All prices exclude P&P and VAT.

Please refer to Ordering Information before ordering.

STATIC RAMS	**1-24**	**25-99**	**100+**
2114L 200 NS Lower Power	1.75	1.60	1.45
4118 250 NS 8K	6.95	6.25	5.95
DYNAMIC RAMS	**1-24**	**25-99**	**100+**
4116 150NS	2.50	2.25	1.95
4116 Ceramic Package Goldplated 200 NS	1.50	1.30	1.20
HM4864 64K (65Kx1) Single 5V 200 NS	14.95	10.95	9.95
CMOS RAMS	**1-24**	**25-99**	**100+**
TC5514P 4K(1K x 4) or equivalent 450NS	3.95	3.50	2.95
HM6116 16K (2K x 8) 150 NS	15.95	14.95	13.95
EPROMS	**1-24**	**25-99**	**100+**
2708 450 NS	2.95	2.75	2.50
2716 5V 450 NS	3.25	2.95	2.75
2532 5V 450 NS	10.95	9.95	8.95

Ordering information: Unless otherwise stated, for orders under £50 add 50p p&p. Add 15% VAT to total (no VAT on books). All devices are brand new, factory prime and full spec and subject to prior sales and availability. Prices subject to change without notice. Minimum telephone order using ACCESS is £10. If ordering by post with ACCESS, include name, address and card no. written clearly. Please allow 4/6 weeks delivery on books.

NEW

SENSATIONAL LOW PRICE ON

64K DYNAMIC RAMS ONLY £9.95

Minimum order (10 pcs (Total price £115 inc. P&P 50p & VAT)
(for quantity 1-9, £14.95 + P&P + VAT)
Ex-STOCK WHILE SUPPLY LASTS!
From HITACHI. HM4864-3 (65K × 1) 200NS, Single +5V Supply, 16 pin. Complete with data sheet and cross reference list.

DTL

830	55p
935	65p
937	55p
944	65p
946	55p
947	55p
962	55p
9099	90p

7400

7400	11p
7401	12p
7402	12p
7403	13p
7404	17p
7405	18p
7408	17p
7409	18p
7410	18p
7412	18p
7413	32p
7414	38p
7513	28p
7420	16p
7427	32p
7430	18p
7432	25p
7440	16p
7442	68p
7447	72p
7448	75p
7473	32p
7474	32p
7475	40p
7476	40p
7485	105p
7486	33p
7490	35p
7491	84p
7492	50p
7493	50p
7496	45p
74121	35p
74123	45p
74126	45p
74132	55p
74141	75p
74148	125p
74150	130p
74154	90p
74157	55p
74161	99p
74165	120p
74174	100p
74122	45p
74125	50p
74190	130p
74192	120p
74193	120p
74194	102p
74195	100p
74196	100p
74197	88p
74283	140p
74290	120p
74365	90p
74366	95p

74LS

74LS00	12p
74LS01	12p
74LS02	13p
74LS03	13p
74LS04	13p
74LS08	20p
74LS10	19p
74LS11	20p
74LS12	30p
74LS13	35p
74LS14	60p
74LS15	38p
74LS20	18p
74LS21	30p
74LS22	38p
74LS26	45p
74LS27	45p
74LS30	18p
74LS32	23p
74LS37	35p
74LS38	35p
74LS40	25p
74LS42	56p
74LS47	78p
74LS48	85p
74LS49	99p
74LS73	30p
74LS74	30p
74LS75	42p
74LS85	98p
74LS86	39p
74LS90	35p
74LS93	70p
74LS96	150p
74LS107	40p
74LS112	75p
74LS123	63p
74LS125	50p
74LS126	50p
74LS132	70p
74LS138	69p
74LS139	75p
74LS148	170p
74LS151	75p
74LS153	75p
74LS155	65p
74LS157	74p
74LS160	115p
74LS161	78p
74LS163	90p
74LS164	90p
74LS165	150p
74LS168	190p
74LS173	100p
74LS174	99p
74LS175	99p
74LS181	280p
74LS190	110p
74LS195	87p
74LS196	100p
74LS221	110p
74LS240	210p
74LS241	200p
74LS242	220p
74LS244	175p
74LS245	220p
74LS251	120p
74LS253	120p
74LS257	110p
74LS260	90p
74LS273	175p
74LS290	95p
74LS293	120p
74LS365	57p
74LS373	170p
74LS374	170p
74LS375	140p
74LS393	135p
74LS490	140p
74LS670	260p

LOW PROFILE SOCKETS BY TEXAS

	SALE
8 pin	7p
14 pin	9p
16 pin	10p
18 pin	15p
20 pin	18p
22 pin	22p
24 pin	22p
28 pin	25p
40 pin	28p

CMOS

4001	19p
4002	19p
4006	75p
4007	19p
4008	80p
4009	35p
4010	45p
4011	24p
4012	24p
4013	38p
4014	70p
4015	75p
4016	35p
4017	75p
4018	76p
4019	42p
4020	88p
4021	100p
4022	88p
4023	22p
4024	50p
4025	20p
4026	130p
4027	45p
4028	75p
4029	80p
4030	50p
4031	195p
4033	145p
4035	104p
4036	290p
4037	105p
4038	110p
4039	290p
4040	99p
4041	75p
4042	73p
4043	86p
4044	88p
4045	160p
4047	99p
4048	56p
4049	38p
4050	40p
4051	69p
4052	75p
4053	73p
4054	111p
4055	121p
4056	121p
4059	560p
4060	112p
4063	112p
4066	56p
4067	422p
4068	19p
4069	19p
4070	28p
4071	25p
4072	25p
4075	20p
4076	88p
4077	23p
4078	29p
4081	23p
4082	25p
4085	86p
4086	68p
4089	130p
4093	68p
4094	225p
4095	99p
4096	325p
4098	110p
4099	180p
4501	25p
4502	112p
4503	68p
4507	52p
4508	288p
4510	76p
4511	125p
4512	75p
4514	250p
4515	290p
4516	109p
4518	99p
4520	99p
4521	230p
4526	105p
4527	130p
4528	99p
4529	140p
4531	150p
4532	125p
4538	150p
4543	160p
4556	70p
4560	225p
4569	240p
4572	46p
4584	79p
4585	125p

74C

74C20	30p
74C76	60p
74C85	145p
74C97	125p
74C98	125p
74C107	100p
74C160	110p
74C161	145p
74C162	145p
74C163	145p
74C192	175p
74C193	175p
74C194	175p
74C195	175p
74C903	45p

KEYBOARD ENCODER	
AY-5-2376	795p

SUPPORT DEVICES	
6520	325p
6522	625p
6532	825p
6551	825p
6810	350p
6820	360p
6821	325p
6845	£23.50
6850	295p
6852	350p
8212	210p
8214	450p
8216	210p
8224	275p
8226	225p
8288	425p
8251	475p
8253	995p
8255	445p
8257	895p
8259	950p
MC144 12VL	797p
Z80 PT0	595p
Z80 CTC	595p
Z80A PI0	695p
Z80A CTC	695p
Z80 DMA	£19.95p
Z80A DMA	£24.95p
Z80 SI0/0	£29.95p
Z80A SI0/0	£34.95p
Z80 SI0/1	£29.95p
Z80A SI0/1	£34.95p
Z80 SI0/2	£29.95p
Z80A SI0/2	£34.95p

DIL SWITCHES	
4 pole	99p
6 pole	115p
8 pole	140p
10 pole	175p

LINEAR IC s

AY 3 1350	795p
AY 3 8910	825p
709	30p
723	33p
741	18p
ICL7106	575p
ICL7107	695p
ICL8038	295p
ICM7216A	1875p
ICM7216B	1675p
ICM7555	80p
LM301AM	30p
LM311	50p
LM318	75p
LM324	45p
LM339	45p
LM380	65p
LM1496	65p
LM1871	550p
LM1872	550p
LM3900	50p
LM3914	225p
LM3915	225p
LM13600	125p
NE555	18p
NE556	50p
RC4136	85p
SN76477N	175p
TBA810DAS	85p
TL071	55p
TL074	130p
TL082	75p
TL084	110p
TL490	175p
XR2206	325p
XR2207	375p

VOLTAGE REGULATORS	
7805/7812	50p
7905/7912	80p
78HO5SC	575p
78GHKC	625p

EPROMS	
2708 450 NS	**295p**
2716 5V 450 NS	**325p**
2532 32K 450 NS	**£10.95**
2732 Intel type 450 NS	**£14.95**
2564 NS (8Kx8) 450NS 28 pin **NEW!**	**£99**

UARTS	
AY5 1013A	325p
AY3 1015D	398p
IM6402 1PL	325p

CPU'S	
6502	625p
6504	750p
6505	750p
6800	645p
6802	925p
6809	£19
8080A	425p
8085A	£10.95
Z80	700p
Z80A	900p
Z8001	£125
Z8002	£95

3½ Digit LCD display with "Lo BAT" sign LCD 106 £5.95

INTERFACE LINEAR	
MC1488	90p
MC1489	90p
DM123	125p
75150	125p
75154	125p
75182	195p
75322	250p
75324	325p
75325	325p
75361	350p
75365	295p
75451	50p
75491/2	75p
8T26	155p
8T28	175p
8T95	175p
8T97	155p

LEDs	
TIL209	9p
TIL211	13p
TIL212	15p
TIL220	12p
TIL222	15p
TIL224	18p

DISPLAYS	
FND500	80p
FND510	80p
FND567	125p
DL704	85p
DL707	85p
MV57164	225p

ISOLATORS	
ILD74	120p
ILQ74	325p
MCT6	90p
TIL111	75p

FLOPPY DISC CONTROLLERS	
FD1771 B-01 S/D Inverted Bus	£21.95
FD 1791 B-01 D/D Inverted Bus	£34.95

NOW LONDON~BASED FOR EVEN FASTER SERVICE!

See new address above

NEW SUPER MUSIC MACHINE KIT!

AT LAST – an affordable kit that can be PROGRAMMED TO PLAY ANY SONG OR GROUP OF SONGS! Instead of a nightmare of numerous ICs and special expensive Bipolar ROMs, the SUPER MUSIC MACHINE uses a SPECIAL MASK PROGRAMMED COMPUTER CHIP, one CMOS gate and the most popular erasable EPROM, the 2708/2706 series. BASIC KIT includes drilled, plated and screened PC board and ALL components except the EPROM and 12V transformer. The basic kit will play short renditions of 25 tunes through its 7 WATT AMPLIFIER SECTION. Add an optional ROM and any tune programmed will be played. If you have the equipment to program 2708 EPROMs, we supply full information on programming your own music!

FEATURES

- Basic kit contains 25 short tunes in the main IC!
- Will address external ROM for up to 1,000 MORE NOTES per ROM! (ROM is not included.)
- Operates on 12V AC or 12V DC at 500mA. (Using unit on 12V DC and with optional ROM requires 9V bias battery, not included.)
- **7 watts of audio power** will drive 8 or 16 ohm speakers or horn speakers (not included).
- DIP switches not included.
- 'NEXT TUNE' provision steps sequentially through all tunes.
- Tune address can be wire jumper selected or board is designed to take DIP switches.
- PITCH, VOLUME and TEMPO are all adjustable.
- SPECIAL 'CHIME' SEQUENCES can be activated regardless of tune address to provide for multiple doorbell applications.
- All tunes consist of electronic musical notes played one at a time. There are no chords or harmony sound to the music.
- STEP-BY-STEP ASSEMBLY INSTRUCTIONS provided.
- Large number of PREPROGRAMMED ROMS with popular and classical tunes readily available. Send sae for list and prices.

ONLY £16.75 for basic kit (plus p&p 60p).

SE 01 Sound Effects Kit

The SE 01 is a complete kit that contains all the parts to build a programmable effects generator. Designed around the new **Texas Instruments SN 76477** Sound Chip, the board provides banks of MINI DIP switches and pots to program the various combinations of the SLF Oscillator. VCO Noises. One Shot and Envelope Controls A Quad Op Amp IC is used to implement and Adjustable Pulse Generator. Level Comparator and Multiplex Oscillator for even more versatility. The 3¼" × 3" PC Board features a prototype area to allow for user added circuitry. Easily programmed to duplicate Explosion. Phaser Guns, Steam Trains, or almost an infinite number of other sounds. The unit has a multiple of applications. The low price includes all parts, assembly manual, programming charts and detailed 76477 chip specifications. It runs on a 9V battery (not included). On board 100MV amp will drive a small speaker directly, or the unit can be connected to your stereo with incredible results! (Speaker not included). **COMPLETE KIT ONLY £14.99** P&P 67p VAT.

BOOKS BY HOWARD W. SAMS INC. SALE!

(Please order books by reference number *and* title. Please add 75p P&P per book. No VAT)

REF	**TITLE**	**NORMAL PRICE**	**SALE PRICE**
21168	Active Filter Cookbook	£10.95	**£7.75**
21440	Aviation Electronics	£6.75	**£5.75**
21558	Audio IC OP Amp Application	£5.95	**£4.75**
21586	Basic Programming Primer	£6.50	**£4.75**
21554	Boolean Algebra for Computer Logic	£4.50	**£3.75**
21447	The 8080A Bugbook Microcomputer Interfacing & Programming	£5.04	**£3.75**
21465	Building and Installing Electronics Intrusion Alarms	£3.95	**£2.75**
21524	The Cheap Video Cookbook	£4.50	**£3.75**
21398	CMOS Cookbook	£7.75	**£6.75**
21652	Computer Dictionary 3rd Ed	£8.95	**£7.75**
21693	Computers & Programming Guides for Scientists & Engineers	£11.95	**£8.75**
21697	8085A Cookbook	£7.50	**£5.75**
21539	Design of Active Filters with Experiments	£5.95	**£4.75**
21536	DBUG An 8080 Interpretive Debugger	£3.75	**£2.75**
21537	Design of Op Amp Circuits with Experiments	£5.95	**£4.75**
21686	Design of VMOS Circuits with Experiments	£5.95	**£3.75**
21550	Introductory Experiments in Digital Electronics & 8080A Microcomputer Programming & Interfacing Book 1	£9.95	**£7.75**
21551	Introductory Experiments in Digital Electronics & 8080A Microcomputer Programming & Interfacing Book 2	£9.95	**£7.75**
21351	How to Buy and Use Minicomputers and Microcomputers	£7.50	**£5.75**
21684	How to Program & Interface the 6800	£10.50	**£7.75**
21459	How to Program Microcomputers	£6.75	**£4.75**
21127	How to Read Schematic Diagrams	£4.25	**£3.75**
21613	How to Use Integrated Circuits Logic Elements	£4.50	**£3.75**
21527	IC Converter Cookbook	£10.50	**£8.75**

6809 S-100 SINGLE-BOARD COMPUTER

- Meets IEEE S-100 Standard!
- Uses Motorola's Powerful MC6809 CPU!
- 4K, 8K, 16K ROM!
- 2K RAM!
- RS – 232 Handshake!
- Selectable BAUD Rates!
- Manual includes: 11"×7" Schematic, Parts List, User Notes Software Listings and MORE!
- ACIA, PIA, 8080 Simulated I/O! **Bareboard only £49!** (plus £1 p&p)

CPU (6809) **£19**! ADSMON; Monitor (2716) **£25! COMPLETE BOARD ASSEMBLED AND TESTED, ONLY £250**! (plus £2 p&p)

Kaise Autoranging Auto Unit Display 3½ digit DMMs from ONLY £39.96 exc VAT.

6200, as itemised. ONLY **£39.96** exc VAT
6220, as 6200, plus 10Amp AC/DC measurement ONLY **£48.65** exc VAT
6110 with 10Amp AC/DC measurement AND Continuity Check!
ONLY **£74.74** exc. VAT   Optional vinyl carry case **£2.30** exc. VAT

- ★ **1mV 100μA and 0.1Ω resolution!**
- ★ **Measures AC voltage to 600V!**
- ★ **Measures DC voltage to 1000V!**
- ★ **Measures resistance to 2 Megohms!**
- ★ **Low power Ohm ranges!**
- ★ **Displays mV, V and mA!**
- ★ **0.8% accuracy!**
- ★ **Zero adjustment!**
- ★ **3 other models too!**

NEW EXCITING, ENTERTAINING SOFTWARE FOR THE APPLE II and APPLE II PLUS!! **ASTEROIDS IN SPACE!!!!**

If you liked 'Invaders' you'll love ASTEROIDS IN SPACE by Bruce Wallace! Your spaceship is travelling in the middle of a shower of asteroids. Blast the asteroids with lasers, but beware – BIG ASTEROIDS FRAGMENT INTO SMALL ASTEROIDS! The Apple game paddles allow you to rotate your spaceship, fire its laser gun, and give it thrust to propel it through endless space. From time to time, too, you'll encounter an alien spaceship whose mission is to DESTROY YOU, so you'd better destroy it first! High resolution graphics and sound effects add to the arcade-like excitement this program generates. RUNS ON ANY APPLE II WITH AT LEAST 32K AND ONE DISK DRIVE!
ON DISKETTE
ONLY £14.95

UNIVERSAL SCR

C106D 400V/5A Sale **30p**

THE NEW GI COMPUTER SOUND CHIP

The amazing AY-3-8910 is a fantastically powerful sound and music generator, perfect for use with any 8-bit micro processor. Contains 3 tone channels, noise generator, 3 channels of amplitude controls, 16 bit envelope period control, 2 parallel I/O, 3D/A converters plus much more. All in 40 pin DIP Super easy to interface to the S 100 or other Busses. ONLY £8.50 + VAT, including FREE reprint of BYTE 79 article! Also, add £2.25 for 60-page data manual.
"Perhaps the next famous composer will not direct a 150-piece orchestra but rather a trio of microcomputers controlling a bank of AY-3-8910s." BYTE July '79.

NEW

PRACTICAL ELECTRONICS

STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July Issue).
For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF. System.

.**Features**
VHF - M.W. - L.W. Bands. Interstation muting and A.F.C. on VHF.
Tuning Meter. Two back printed P.C.B's. Ready made chassis and scale.
Aerial: AM - Ferrite Rod, FM - 75 or 300 ohms.
Stabilized power supply with "C" core mains transformer.
All components supplied are to P.E. strict specification.
Front scale size 10½" x 2½" approx.

Complete with circuit diagrams and instructions. -

INTRODUCTORY DRICE-ONLY

£17.95
plus £2.50 p&p

PRACTICAL ELECTRONICS CAR RADIO KIT (Constructors pack 7)

2 WAVE BAND MW LW
• Easy to build • 5 push button tuning
• Modern styling design • All new unused components
• 6 watt output • Ready etched & punched P.C.B.
• Incorporates suppression circuits • Now with tape input socket

All the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. Features: Pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia.
The P.E. Traveller has a 6 watts output, neg ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The radio fits easily in or under dashboards.
Complete with instructions.

£10.50
plus £2.00 p&p

CONSTRUCTORS PACK 7A

Suitable stainless steel fully retractable locking aerial and speaker (approx. 6" x 4") is available as a kit complete **£1.95** per pack, p&p £1.15

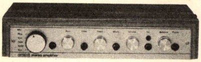

30 + 30 WATT STEREO AMPLIFIER BUILT AND TESTED

Viscount IV unit in teak simulate cabinet silver finished rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder. DIN speaker and input socket 30 + 30 watts. RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14¾" x 10" approx.

READY TO PLAY £32.90 plus £3.80 p&p

HI FI STEREO AMPLIFIER MODULES

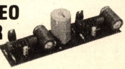

- Mullard LP1183 built preamplifier suitable for ceramic and auxiliary inputs. **£1.95** plus 70p p&p.
- Mullard LP1184 built preamplifier suitable for magnetic/ceramic and auxiliary inputs. **£4.95** plus 80p p&p
- Matching I.C. 10 + 10 Stereo Power amplifier kit. **£3.95** plus £1.15 p&p
- Matching power supply kit with transformer. **£3.00** plus £1.96 p&p
- Matching set of 4 slider controls complete with knobs for bass, treble and volumes. **£1.70** plus 80p p&p.
- Complete with application notes.

£14.95
plus £2.90 p&p

10+10 WATT STEREO AMPLIFIER KIT

- Featuring latest SGS/ATES TDA 2006 10 watt output I.C.'s with in-built thermal and short circuit protection.
- Mullard Stereo Preamplifier module.
- Attractive black vinyl finish cabinet. Size 9" x 8⅜" x 3⅝" approx.
- Converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disc amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amplifier assembly kit and mains power supply. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs and contrasting ready made black vinyl finish cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit.

SPECIFICATIONS

Suitable for 4 to 8 ohms speakers

Frequency responce	40Hz — 20KHz
Input Sensitivity	P.U. 150mV Aux. 200mV Mic. 1.5mV
Tone controls	Bass ± 12db @ 60Hz Treble ± 12db @ 10KHz
Distortion	·1% typically @ 4 watts
Mains supply	220-250 volts 50Hz

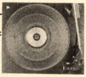

BSR chassis record deck with manual set down and return, complete with stereo ceramic cartridge. :**£8.50** plus £3.15 p&p when purchased with amplifier.
Available separately **£10.50** plus £3.16 p&p.

8" SPEAKER KIT 2 8" approx. twin cone domestic use speakers. **£4.75** per stereo pair plus £1.70 p&p when purchased with amplifier. Available separately **£6.75** plus £1.70 p&p.

STEREO MAGNETIC PRE-AMP CONVERSION KIT. All components including P.C.B. to convert your ceramic input on the 10+10 amp to magnetic. **£2.00** when purchased with kit featured above. **£4.00** separately inc. p&p.

RTVC

323 EDGWARE ROAD, LONDON W2
21B HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only, No callers
ALL PRICES INCLUDE VAT AT 15%
All items subject to availability. Price correct at and subject to change without notice.
For further information send for instructions 20p plus stamped addressed envelope.
NOTE: Goods despatched to mainland and N. Ireland only.
Persons under 16 years not served without parent's authorisation.
R TVC LTD. reserve the right to alter, update or improve their products without notice.

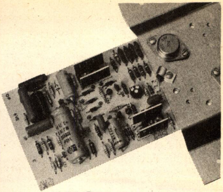

HIGH POWER MODULE KITS

125 WATT MODEL £10.50 plus £1.15 p&p (Illus)
200 WATT MODEL £14.95 plus £1.15 p&p

SPECIFICATIONS

Max. Output power	125 watt RMS
Operating voltage (DC)	50-80 Max.
Loads	4-16 ohms
Frequency response measured at 100 watts	25Hz-20KHz
Sensitivity for 100 watts	400mV @ 47K
Typical T.H.D. @ 50 watts 4 ohms load	0.1%
Dimensions	205 x 90 and 190 x 36 mm

The power amp kit is a module for high power applications—disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC Board is backprinted, etched and ready to drill for ease of construction, and the aluminium chasis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES

Suitable LS coupling electrolytic for 125W model	**£1.00** plus 25p p&p.
Suitable LS coupling electrolytic for 200W model	**£1.25** plus 25p p&p.
Suitable Mains Power Supply Unit for 125W model	**£7.50** plus £3.15 p&p.
Suitable Twin Transformer Power Supply for 200W model	**£13.95** plus £4.00 p&p

MULLARD LP1183 STEREO PREAMP

FREE!

Original listed price over £5.00. Suitable for ceramic and auxiliary inputs, when you purchase 2 power module kits.

50 WATT MONO MIXER AMPLIFIER

Six individually mixed inputs for two pick ups (Cer. or Mag.), two moving coil microphones and two auxiliary for tape, tuner, organs etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic and aux. inputs.
Power output 50 watt R.M.S. (continuous) for use with 4 to 8 ohms speakers. Finish: Attractively styled black vinyl case, with matching fascia and knobs. Complete and ready for use.

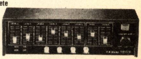

£39.95
plus £3.70 p&p

100 WATT MONO DISCO AMPLIFIER

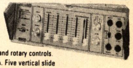

Brushed aluminium fascia and rotary controls. Size approx 14" x 4" x 10¼. Five vertical slide controls, master volume, tape leverl, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level controls (PRL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak.

£76.00
plus £4.60 p&p

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday ACTON: Mail Order only. No callers GOODS DESPATCHED TO MAINLAND AND N. IRELAND ONLY

PE VOLUME 17 No. 7 JULY 1981

THE END OF THE TUNNEL?

THERE have been one or two comments recently that the light at the end of the depression is just beginning to show and, although many component retailers are still finding the going a bit tough, there have been a couple of announcements recently that give rise to hope.

The main announcement was the draft specification on CB from the Home Office. Since its publication there has been plenty of discussion on how it meets the aspirations of the present illegal users, which of course it never could unless it allowed the American standard equipment. We believe the proposals are basically generous and the "U" turn made by HM Government in allowing the use of 27MHz is probably the best way out of the mess created by the delayed legalisation of a CB frequency. The proposals should give rise to a worthwhile system, probably giving better performance than the present a.m. CB. The Home Office announcement is covered on page 24 in this issue, PE will be publishing more on CB in the September issue and we will make our announcement next month.

Let us hope that British manufacturers will capitalize on the need for new sets, accessories and for modification of the old transceivers — though it may be expensive to get many of them to meet the Home Office requirements. We look forward to mass use of the system by a wide cross section of the community and we hope that most of the jargon now in use will not continue on the new band. One young lady (Editor's wife!) proclaimed that there was no way she was going to talk about "rubber apples and yellow ducks", when it was suggested that CB could be a great assistance in the home, car and office. This view is typical of many who are frightened off CB by all the "in talk" so let's see straightforward use by everyone, old and young.

COMPUTER PRESERVATION

The second announcement that shows problems can be overcome in these difficult times came from Lucas. They have now bought the old Nascom company which has been living "hand to mouth" under the receiver for some time. The Nascom products were basically good and their computers have always been in great demand by the hobbyist. Lucas Logic propose to improve some of the present products, introduce a "Nascom case" and are talking about the launch of a new system before too long. Although the company is now owned by Lucas the Nascom name will be retained.

This must be a triumph for all concerned with Nascom during its recent problems. It is remarkable that by careful handling and great efforts by all concerned production has continued and every new unit has been eagerly snapped up. When many companies are struggling for survival this preservation is truly noteworthy.

On another happy note Inmos have received the first Tobie award for "Research Achievement" on its 16K static RAM. The product has taken some time to appear but it looks good and should become the 16K industry standard. The Electronics Industry (or Tobie) Awards were organised in conjunction with the All Electronics/ECIF Show.

Mike Kenward

EDITOR
Mike Kenward
Gordon Godbold ASSISTANT EDITOR
Mike Abbott TECHNICAL EDITOR
David Shortland PROJECTS EDITOR
Jasper Scott PRODUCTION EDITOR
Jack Pountney ART EDITOR
Keith Woodruff ASSISTANT ART EDITOR
John Pickering SEN. TECH. ILLUSTRATOR
Isabelle Greenaway TECH. ILLUSTRATOR
Colette McKenzie SECRETARY

ADVERTISEMENT MANAGER **D. W. B. Tilleard** } **01-261 6676**
SECRETARY **Christine Pocknell** }
AD. SALES EXEC. **Alfred Tonge 01-261 6819**
CLASSIFIED MANAGER **Colin Brown 01-261 5762**

Editorial Offices:
Practical Electronics,
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG
Phone: *Editorial* Poole 71191

We regret that lengthy technical enquiries cannot be answered over the telephone (see below).

Advertising Offices:
Practical Electronics Advertisements,
King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Telex: 915748 MAGDIV-G

Make Up/Copy Dept.: 01-261 6601

Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in Practical Electronics.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to **one published project only.**

Components and p.c.b.s are usually available from advertisers; where we anticipate difficulties a source will be suggested.

Back Numbers

Copies of some of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 95p each including Inland/Overseas p&p.

Binders

Binders for PE are available from the same address as back numbers at £4·30 each to UK or overseas addresses, including postage and packing, and VAT where appropriate. Orders should state the year and volume required.

Subscriptions

Copies of PE are available by post, inland or overseas, for £11·80 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH. Cheques and postal orders should be made payable to IPC Magazines Limited.

...NEWS &

Edited by David Shortland & Jasper Scott

TXs get Teletext

Thorn Consumer Electronics who recently won a Queen's Award for Technological Achievement with their Ferguson TX colour television range have now released three new Teletext models.

Both the TX 9 chassis (14 to 22in) and the TX 10 chassis (22 to 26in) were designed from the outset to incorporate remote control and Teletext functions without the need for component or circuit changes to the chassis.

Thorn now believe that many of the colour sets bought during the boom period in the early and mid seventies will be replaced with remote control sets incorporating Teletext.

Nigel Schofield, Thorn's market analyst, said recently, "Almost half of all the 22in sets now incorporate a remote control facility, while the figure for 26in sets is almost 70 per cent. The consumer desirability of remote control is evident, and full remote models, including those with Teletext, outnumber simple remotes by two to one. Towards the luxury end of the colour market, Teletext already accounts for over 20 per cent of 26in deliveries to the trade, and the current market projection is for 175,000 consumer sets this year, which entails a tripling of last year's volume, which had itself shown a 200 per cent increase on the previous year."

Another reason Thorn are confident Teletext will become a major force in TV sales is that the cost of providing a Teletext facility to a remote control TX set is about £90 and this figure is expected to drop even further as the demand for sets increases.

Three screen sizes are available in the Teletext range: a 20in model (TX 9) and two TX 10 models (22in and 26in). The sets are designed around the Mullard decoder module with full infra-red remote control for all picture adjustments, channel selection and Teletext functions.

Ferguson have also released three add-on accessories for their range of TX models, all of which can be quickly fitted by a qualified dealer. The isolated chassis of the TX 10 makes it simple to feed signals in and out without the need for isolating components.

The TA120 enables the audio signal from the TV to be connected to a hi-fi system via a DIN socket without the loss of sound quality. As an extension of the TA120 Ferguson have introduced a loud speaker which enhances the television sound and is controlled by the TV's remote control. The speaker has been designed to be placed alongside or under the television and to prevent the loss of colour purity which occurs when conventional hi-fi speakers are similarly placed the drive units incorporate low leakage field magnets.

For those who wish to use their TVs for video recording or for encoded video from a video camera then the TA124 incorporates high performance buffer amplifiers for two-way video and sound signals. The TA124 enables recorded material to be replayed via a video input socket instead of the usual aerial socket.

A battery adaptor (TA92) is also available for the TX 9 range of portable TVs which will give up to five hours' viewing with an automatic cut-out to prevent excess battery drain.

Dansette to be resurrected

J. J. Silber, who have recently been in the news having acquired the brand name of Murphy, have announced that they have also purchased the Dansette name.

Many readers will no doubt remember Dansette record players and portable radios, though the name has disappeared in recent years.

Silber, who believe that Dansette was known as a name synonomous with good quality budget equipment, feel that there is room for a 'a high volume, low priced, quality product,' and that prospective purchasers will be encouraged by the Dansette name.

There are already plans for the introduction of a new range of stereo radio/record players. They will be introduced to the market during the middle of this year and if all goes according to plan they will have a substantial price advantage over other products in this field, and, claim Silber, will incorporate refinements normally associated with products in higher priced markets.

No figures for the purchase have been disclosed, but it has been described as 'a very reasonable sum'.

CLASSY BREADBOARD

The Verobloc laboratory module is Vero's latest solderless breadboard product and has been developed to simplify breadboard work. It features a large breadboard area and has a fully regulated three rail power supply (5V d.c. at 750mA, ±9V, ±12V, ±15V at 250mA) which is ideal for both TTL and CMOS.

The system which accepts most sizes of d.i.l. packages, diodes, resistors, capacitors, transistors and wire links comes ready assembled, complete with four Veroblocs and two pre-pierced front panels for mounting fuseholders, switches, trimpots etc. The d.c. voltage supplies may be picked up via 2mm jack sockets and toggle switches are provided for voltage selection.

The Verobloc which features tin copper nickle alloy contacts has bus strips for power distribution on both X and Y axes. All the contact positions are identified by moulded alpha numeric grid references.

The price of the Verobloc module (184–22880J) is £84·00 excluding VAT and p&p. For further details contact Vero Electronics Limited, Industrial Estate, Chandler's Ford, Hants.

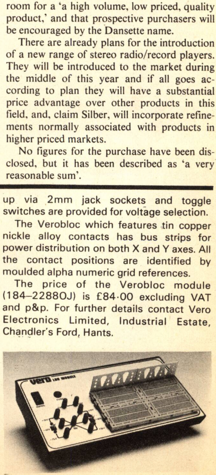

MARKET PLACE

Items mentioned are available through normal retail outlets unless otherwise specified. Prices correct at time of going to press.

MOVING COIL 'BREAKTHROUGH'

The introduction of the MC88E moving coil cartridge is the culmination of an intensive product and manufacturing development by Coral. Its high output voltage of 2·5mV does away with the need for a head amplifier or a step up device and this has been achieved by using a miniaturised armature, a unique coil winding technique and a compact magnet which generates a high magnetic flux density.

A low impedance has been obtained which is less than 1/20th of a regular moving coil cartridge weight. This ensures flat, stabilised electrical characteristics over the total audio range.

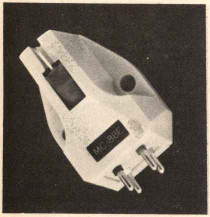

Coral's one point suspension system in which the centre of each armature is fully supported, effectively checks harmonic and intermodulation distortions and accomplishes excellent localisation for natural stereo.

The cartridge's very light weight of only 5grms will enable optimum balancing with most lightweight tone arms.

The MC88E is available for £29·95 from Videotone Ltd., 98 Crofton Park Road, London SE4 (01-690 8511).

A GRAND PAIR...

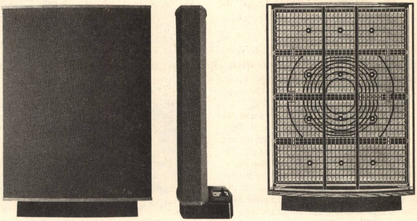

Quad have finally released a successor to their electrostatic loudspeaker which has been a standard in the hi-fi field for twenty-five years.

The Quad ELS63 which measures 925 × 66 ×27mm has an input impedance of 8Ω (largely resistive) and is suitable for use with amplifiers that have an output rating of 40V peak (100W into 8Ω). Amplifiers which are not short circuit protected should not be used with the ELS63.

The speaker is fitted with two protection circuits: one limits the maximum input voltage applied and the other detects fault conditions and shorts the applied signal. Although it is impossible to damage the speaker elements, the input voltage limiter can be damaged by persistent overdriving.

A small word of warning from Quad, however, to all those hi-fi buffs who *can* afford the £1000 price tag for a pair of ELS63's. Quad say that although the ELS63 will give a more realistic picture of an acoustic event than has ever before been possible, the real excellence of the speakers will only be fully realised if the very best source material is used and that ELS63's are very good at revealing any recording faults.

Quad Electroacoustics Ltd., Huntingdon, Cambs. (0480 52561).

CABINET KITS

For the loudspeaker constructor who wants a professional finish, Wilmslow Audio now stock a range of flat-pack cabinet kits for many popular designs including the new Wharfedale E50, E70 and E90 kits. All panels are accurately cut to size, and baffle boards have the necessary apertures cut and rebated if required.

When assembled, the cabinets may be painted, stained, or finished with iron-on veneer.

Wilmslow Audio Ltd., 35-39 Church Street, Wilmslow, Cheshire, SK9 1AS (0625 529599).

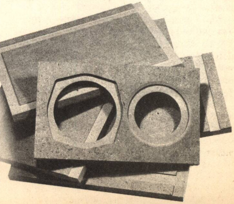

MAIL ORDER

The latest 24 page catalogue from Rapid Electronics shows a large increase in their range of components and hardware. Rapid have also increased their stockholding so that they are able to offer a return of post service with an immediate refund made against any item out of stock.

The catalogue is available upon receipt of two 14p stamps. Rapid Electronics Ltd., Hillcroft House, Station Road, Eynsford, Kent (0322 863494).

A leaflet is available from Cotswold Electronics Ltd., describing their "budget range" of toroidal transformers in 30, 60, 100, 160, 230, 330 and 530VA sizes and at prices ranging from £4·55 to £15·80.

Cotswold will accept "freepost" cheques, P.O.'s, money orders, Access and Barclaycard, and will accept credit card orders on a 24 hour answering service. All the customer needs to do is quote a type number, mains voltage, secondary voltage, VA rating and quantity required.

All types are normally supplied with 240, 110 or 220V primary windings but special windings can be supplied on request. Dual secondary windings from 6 + 6V to 50 + 50V are available and the choice is determined by the VA rating. The secondary windings can be operated in series, parallel or independently.

Cotswold Electronics Ltd., Unit T1, Kingsville Road, Kingsditch Trading Estate, Cheltenham (0242 41313).

VERSATILE MULTIMETER

The latest multimeter from Thurlby is the 1503 DMM which offers the bonus of a built-in frequency meter. Frequencies up to 3999·9kHz can be measured directly with a resolution of 100Hz. Accuracy is ±1 digit over a 10°C–30°C temperature range and is defined by a 6MHz crystal timebase. A movable decimal point allows for external pre-scaling by those wishing to extend the measurement range to 40MHz or 400MHz.

In normal multimeter mode, the instrument has a high resolution $4\frac{3}{4}$ *digit scale length and sensitivity figures of 10µV, 10mΩ and 1nA. There are 32 ranges provided enabling measurement of a.c. and d.c. voltage, resistance, diode test, and a.c. and d.c. current up to 25 amps.*

The 1503 which is priced at £139 plus VAT has a liquid crystal display and can be powered from internal batteries or from the mains.

Thurlby Electronics Ltd., Office Suite 1, Coach Mews, The Broadway, St. Ives, Huntingdon, Cambs (0480 63570).

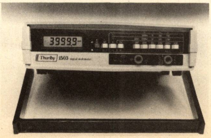

BASICALLY BRITISH

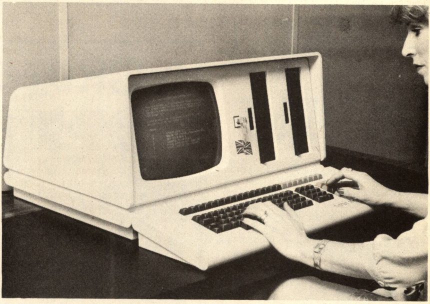

A British company, LSI Computers Ltd, have launched into the personal/small business computer market with the introduction of their M Three system. According to LSI, M Three, which has been developed with the help of a 25 per cent government grant, offers more ability, storage and user satisfaction than any comparable machine at present on the market.

In its basic form, M Three consists of a Zilog Z80 chip surrounded by 64K of RAM, two double-density mini-floppy disc drives, LSI's own VDU with 1920 character green phosphor display and a full functional keyboard. In addition to the normal QWERTY layout, the keyboard has editing keys, cursor control, numeric pad and fourteen programmable function keys.

It comes equipped with a CPM operating system and is programmable by users in high level languages such as BASIC, COBOL, etc. Applications software is also available from LSI including accounting, payroll, and stock control.

Prices for M Three range from £3000 to £4000. LSI can also supply suitable printers and other hardware.

POINTS ARISING . . .

POSITIVE IMPEDANCE CONVERTORS (June '81)

The tables mentioned in the worked examples of filter design can be found in 'Simplified Modern Filter Design' by Philip Gaffe, published by Iliffe.

ENLARGER TIMER (March '80)

Here, switches S4, 5, 6, 11, should be push-button normally off types. ICs 14, 15, 16 shown in Fig. 1 should be decoupled, that is, have 100n capacitors connected between +5V and 0V.

MARKET PLACE

NEW DEGREE

North Cheshire College have recently announced the launching of a new Bachelor of Education degree entitled "Computers in Industrial Society", which will be validated by the University of Manchester. The first student entry will be in September this year.

The degree has been planned to suit students with an arts background as well as those with a background in science, and it covers not only the technical aspects of microelectronics, but also the implications for industry and society in general.

In addition to periods of practical experience in schools, students will spend some time with an industrial or commercial organisation. This will be of particular value to those students not wishing to become teachers.

For further information, contact: Admissions (C.I.S.), North Cheshire College, Padgate Campus, Fearnhead, Warrington WA2 0DB (0925 814343 Ext. 6).

INSTANT ROM

A new programming aid for users of microcomputers (particularly the Commodore PET) has recently been announced by Greenwich Instruments Ltd.

Instant ROM is a CMOS memory package (2 or 4K) with battery back-up which plugs into any standard ROM/EPROM socket, or into the ROM expansion sockets of the PET and similar microcomputers. It can be treated as RAM, and machine code programs can be written into it. What makes Instant ROM unique is that the programs remain after the power has been switched off. It therefore behaves exactly like a ROM. Programs can be edited or altered immediately without erasure problems, yet the program is permanent.

When used with personal computers such as the PET, Instant ROM enables the user to write security and utility programs quickly, run and debug them, and then finally consign the correct program to EPROM. However, as the battery life is typically 6 years, it is also possible to ship a system with Instant ROM and to supply the ROM later.

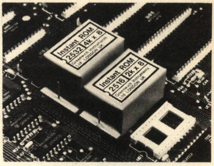
Instant ROM 2532 4k x 8
Greenwich Instruments Ltd LONDON UK
Instant ROM 2516 2k x 8
Greenwich Instruments Ltd LONDON UK

Prices, exclusive of VAT, are as follows: 2K devices: 2516 (for PET) and 2716—£39 inc. p&p; 4K devices: 2532 (for PET) and 2732—£56 inc. p&p. For further information contact Greenwich Instruments Ltd., 22 Bardsley Lane, Greenwich, London SE10 9RF (01-853 0868).

Countdown . . .

Please check dates before setting out, as we cannot *guarantee* the accuracy of the information presented below.

Transducer/Tempcon June 9–11. Wembley Conference Centre, London. **T**
Components June 9–12. Earls Court, London. **I**
Pet Computer Show June 18–20. West Centre Hotel, London. **B8**
Compec North June 23–25. Belle Vue Hotel, Manchester. **Z1**
International Word Processing Exhibition & Conference June 23–26. Wembley Conference Centre, London. **Z**
BEX Salisbury June 24–25. City Hall. **K**
Leeds Electronics Show June 30–July 2. University of Leeds **E**
National Education & Training (Exhibition & Conference) July 2–4. NEC, Birmingham. **B2**
BEX Portsmouth July 15–16. Centre Hotel. **K**
BAEC Amateur Electronics Exhibition July 18–26. The Shelter, Penarth Esplanade, S. Glam. **B9**
Microcomputer Show (& Seminars) July 29–31. Wembley Conference Centre. **O**
Solar Energy Exhibition Aug. 23–28. Brighton. **M**
Harrogate Int. Fest. of Sound Aug. 15–18. Royal Hall Exhibition Centre & Hotels. **X**
BEX Cardiff Sept. 3–4. Centre Hotel. **K**
Business & Light Aviation Sept. 3–5. Cranfield Airport. **Z1**
Microprocessor Workshop Sept. 7–8. University of Liverpool. **D**
Laboratory Sept. 8–10. Grosvenor House, Park Lane, London. **I**
Personal Computer World Show Sept. 10–12. Cunard Hotel, London. **M**
West of England Electronics Show Sept. 15–17. Bristol Exhibition Centre. **Q**
Business Telecoms & Electronic Office Sept. 23–25. Royal Lancaster Hotel. **O**
BEX Edinburgh Sept. 30–Oct. 1. Assembly Rooms. **K**
Viewdata Oct. 6–8. Wembley Conference Centre, London. **O**
BEX Bristol Oct. 14–15. Exhibition Centre. **K**
Video Show Oct. 16–18. West Centre Hotel, London. **Z1**
International Business Show Oct. 20–29. NE Conference, Birmingham. **A2**
Testmex Oct. 27–29. Wembley Conference Centre, London. **T**
Computer Graphics (Exhibition & Conference) Oct. 27–29. **O**
BEX Southampton Nov. 4–5. Polygon Hotel. **K**
Viewdata & TV User Nov. 4–6. West Centre Hotel, London. **Z1**
IFSEC (Fire & Security) Nov. 17–19. RDS, Dublin. **V**
Compec Nov. 17–20. Olympia, London. **Z1**
BEX Plymouth Nov. 18–19. Holiday Inn. **K**
INTRON Nov. 24–26. RDS. Dublin. **V**
There are **Continuous Events and Permanent Exhibition** at the National Micro & Electronics Centre. **L1**

A1	Inst. Electronics, Rochdale, Lancs.
A2	Hart Browne & Curtis ☎ 01-439 8556
A3	Sybex, 18 Rue Planchat, F-75020 Paris
B2	Brintex ☎ 01-637 2400
B5	Robin Bradbeer, N. London Polytechnic
B7	Modmags ☎ 01-437 1002
B8	Baroness International ☎ 01-734 2907
B9	BAEC, Penarth, S. Glam. ☎ 0222 707813
C	Barry College Radio Soc. ☎ 0222 565656
D	Liverpool Univ., Brownlow Hill, PO Box 147
D1	Infopress, 58 Fleet St. London
E	Evan Steadman, Saffron Walden ☎ 0799 22612
F1	ARS Electronica, 34 High St., Saffron Walden
I	ITF, Solihull ☎ 021-705 6707
K	Douglas Temple, Bournemouth ☎ 0202 20533
L1	World Trade Centre ☎ 01-488 2400
M	Montbuild Exhibitions ☎ 01-486 1951
O	Online, Northwood, Middx. ☎ 09274 28211
Q	Exhibitions For Industry ☎ 0883 34371
T	Trident, Tavistock ☎ 0822 4671
V	SDL ☎ Dublin 763871
V1	Jack Tootill, Ipswich ☎ 0473 44047
X	Exhibition & Conference, Harrogate ☎ 0423 62677
Z	BETA Exhibitions ☎ 01-405 6233
Z1	IPC Exhibitions, Sutton ☎ 01-643 8040

From HAMEG...

HM307

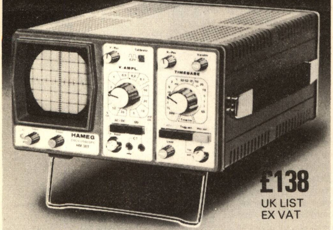

£138
UK LIST
EX VAT

The first portable scope with a component tester.

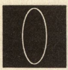

Capacitor 33uF

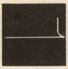

Transistor E-C

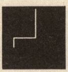

Transistor B-E

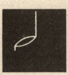

B-E 1uF + 68ohms

Oscilloscope Specifications:

Y Deflection

Bandwidth: DC - 10 MHz (-3dB)
Overshoot: Less than 1%
Sensitivity: 5 mV - 20 V/cm
Input Imp: 1 M ohm // 25pf

X Deflection

Timebase: 0.2s - 0.2 µs/cm
Triggering: 2 Hz - 30 MHz (3mm)
Auto + level control
Bandwidth: 2Hz - 1 MHz

General Information

Component Tester:	For single components and **in circuit**
Calibrator:	0.2V ± 1% for probe alignment
Power Supplies:	Regulated including high voltage
A.C. Input:	110, 127, 220, 237, V.A.C., 50 - 60 Hz
Weight:	8-¼ Lbs.
Size:	4-½"H × 8-3/8"W × 10-7/16"D

For further information on HAMEG's full range of top performance oscilloscopes, contact:

HAMEG LTD.
74-78 Collingdon Street, Luton, Beds. LU1 1RX
Tel: (0582) 413174

MICROCOMPUTER COMPONENTS

LOWEST PRICES — FASTEST DELIVERY

DEVICE	PRICE
CPU's	
6502	5.50
6800	3.82
6802	5.74
6803	14.53
6809	12.00
8085A	8.02
Z80 CPU	4.00
Z80A CPU	5.92
SUPPORT CHIPS	
6520	3.15
6522	5.60
6532	7.75
6821	1.93
6840	5.87
6850	1.95
6862	7.09
6871A1T	20.90
6880	1.07
6887	0.80
8212	2.25
8216	1.95
8224	2.50
8228	4.20
8251	4.75
8253	10.00
8255	4.20
Z80 CTC	4.00
Z80A CTC	4.90
Z80 DMA	11.52
Z80A DMA	17.25
Z80 DART	7.20
Z80A DART	7.67
Z80 P10	4.00
Z80A P10	4.40
Z80 S10-0	20.11
Z80 S10-1	20.11
Z80 S10-2	20.11
Z80A S10-0	24.17
Z80A S10-1	24.17
Z80A S10-2	24.17
MEMORIES	
2101	3.68
2102	2.54
2114 200ns low power	1.35
2708	1.73
2716 (5v)	2.67
2732 2532 (specify)	7.59
4116 150ns	1.25
4116 200ns	1.20
REGULATORS	
7805	0.55
7812	0.55
7905	0.65
7912	0.65
CRT CONTROLLERS	
9364AP	8.64
6845	11.72
BUFFERS	
81LS95	1.20
81LS96	1.25
81LS97	1.20
81LS98	1.25
8T26A	1.50
8T28A	1.50
8T95N	1.50
8T97N	1.50
8T98	1.50
MISC. SUPPORT CHIPS	
AY-3-1015 (or equiv.)	4.29
AY-5-1013 (or equiv.)	4.29
AY-5-2376 (or equiv.)	7.00
MC1488	0.75
MC1489	0.75
MC14411	8.75
MC14412	8.75
RO-3-2513L	7.82
RO-3-2513U	7.82
DATA CONVERTERS	
ZN425E	3.50
ZN426E	3.00
ZN427E	6.28
ZN428E	4.78
ZN429E	2.10
ZN432	28.09
ZN433	22.59
Data converter Handbook	1.00
74LS SERIES	
74LS00	0.14
74LS01	0.15
74LS02	0.14
74LS03	0.14
74LS04	0.15
74LS05	0.15
74LS08	0.14
74LS09	0.15
74LS10	0.14
74LS11	0.15
74LS12	0.15
74LS13	0.29
74LS14	0.51
74LS15	0.15
74LS20	0.14
74LS21	0.15
74LS22	0.15
74LS26	0.19
74LS27	0.15
74LS28	0.17
74LS30	0.14
74LS32	0.14
74LS33	0.17
74LS37	0.17
74LS38	0.17
74LS40	0.14
74LS42	0.40
74LS47	0.42
74LS48	0.70
74LS49	0.62
74LS51	0.14
74LS54	0.15
74LS55	0.15
74LS73	0.22
74LS74	0.19
74LS75	0.30
74LS76	0.22
74LS78	0.25
74LS83	0.54
74LS85	0.77
74LS86	0.18
74LS90	0.36
74LS91	0.81
74LS92	0.40
74LS93	0.39
74LS95	0.48
74LS109	0.26
74LS112	0.26
74LS113	0.26
74LS114	0.26
74LS122	0.45
74LS123	0.57
74LS124	1.07
74LS125	0.29
74LS126	0.29
74LS132	0.51
74LS136	0.29
74LS138	0.40
74LS139	0.40
74LS145	0.78
74LS148	1.13
74LS151	0.35
74LS153	0.35
74LS155	0.50
74LS156	0.50
74LS157	0.36
74LS158	0.40
74LS160	0.43
74LS161	0.43
74LS162	0.43
74LS163	0.43
74LS164	0.51
74LS166	0.37
74LS173	0.77
74LS174	0.78
74LS175	0.60
74LS181	1.50
74LS190	0.61
74LS191	0.61
74LS192	0.69
74LS193	0.69
74LS194	0.42
74LS195	0.42
74LS196	0.68
74LS197	0.68
74LS221	0.64
74LS240	1.01
74LS241	1.15
74LS242	0.85
74LS243	0.85
74LS244	0.84
74LS245	1.21
74LS247	0.41
74LS248	0.74
74LS249	0.74
74LS251	0.46
74LS253	0.46
74LS257	0.57
74LS258	0.40
74LS259	1.15
74LS261	3.12
74LS266	0.25
74LS273	0.97
74LS279	0.37
74LS283	0.45
74LS290	0.60
74LS293	0.53
74LS365	0.39
74LS366	0.38
74LS367	0.38
74LS368	0.38
74LS373	0.79
74LS374	0.79
74LS375	0.50
74LS377	0.97
74LS378	0.73
74LS379	0.56
74LS386	0.29
74LS390	0.68
74LS393	0.61
CMOS	
4000	0.14
4001	0.14
4002	0.14
4006	0.85
4007	0.18
4008	0.75
4009	0.39
4010	0.47
4011	0.17
4012	0.23
4013	0.42
4014	0.78
4015	0.80
4016	0.34
4017	0.68
4018	0.75
4019	0.44
4020	0.82
4021	0.88
4022	0.84
4023	0.23
4024	0.49
4025	0.19
4026	1,28
4027	0.44
4028	0.80
4031	1.85
4033	1.70
4034	1.99
4035	1.05
4036	2.75
4039	2.95
4040	0.83
4041	0.80
4042	0.68
4043	0.78
4044	0.78
4045	1.70
4046	0.95
4047	0.98
4048	0.54
4049	0.34
4050	0.37
4051	0.78
4052	0.78
4053	0.78
4054	1.28
4055	1.23
4060	1.08
4063	1.18
4066	0.46
4067	4.25
4068	0.25
4069	0.19
4070	0.29
4071	0.24
4072	0.24
4073	0.24
4075	0.24
4076	0.83
4077	0.29
4078	0.26
4081	0.24
4082	0.24
4085	0.57
4086	0.70
4093	0.53
4502	0.99
4507	0.45
4508	2.75
4510	0.83
4511	0.63
4512	0.79
4514	1.93
4515	2.98
4516	0.89
4518	0.89
4519	0.68
4520	0.89
4521	2.05
4522	1.45
4526	0.95
4527	1.20
4528	0.99
4532	1.15
4541	1.45
4543	1.45
4553	3.10
4555	0.50
4556	0.59
4566	1.90
4585	1.35
CRYSTALS	
4MHz	1.80

E. & O.E.

OFFICIAL ORDERS WELCOME – QUANTITY DISCOUNTS AVAILABLE

Midwich Computer Co., Ltd.,
(Dept. PE).,

Hewitt House, Northgate Street,
Bury St. Edmunds, Suffolk IP33 1HQ.
Telephone: (0284) 701321
Telex: 817682 MIDCOM G

All prices exclude post and packing on orders under £10 (50p) and VAT (15%).

ALL ORDERS DESPATCHED ON DAY OF RECEIPT WITH FULL REFUND FOR OUT OF STOCK ITEMS IF REQUESTED.

24 hour Telephone Credit Card Orders
Telephone: (0284) 701321.

CREDIT CARD ORDERS WELCOME

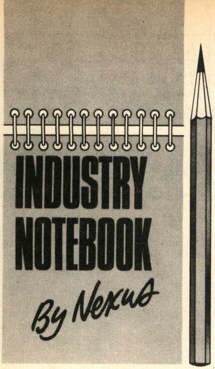

INDUSTRY NOTEBOOK

By Nexus

Scenarios

Imagine an industry once employing 505,000 regular whole-time workers now reduced to about 185,000. A dramatic decline by any standards and unquestionably qualifying for the use of words and phrases such as decimation, massacre, crucifixion or, at the very least, an obscenity or a national scandal. I choose the words, almost at random, from the current vocabulary of political hyperbole endlessly chanted in Westminster and the media. One might also expect a scream of anguish with over 300,000 honest and hardworking citizens 'thrown on the scrap heap'.

And yet this particular industry invites not a word of criticism and is not only admired but publicly highly praised. I refer to British agriculture, often described as the envy of the world and rightly so, with this comparatively tiny workforce producing 70 per cent in value of the food consumed by the nation's 56 million people and with a good export record as well.

Of course employment in agriculture has been declining over a long period. In 1801 it employed 36 per cent of the working population. By 1901 the figure had dropped to 9 per cent. But the figures quoted in my opening sentence are recent history, the period from 1960–1980. In 1960 the average wage of the half-million workers was £10·58. In 1980 the slimmed-down workforce was averaging close on £80 a week.

A similar scenario is now being enacted in manufacturing industry. Here again, slimming down has been taking place over many years but during the last decade was artificially delayed. The present phase of catching up (the alternative to going broke) is the natural and foreseeable result, with severe dislocation compounded by the general recession in trade.

The electronics industry with but few exceptions (e.g. ICL) has not only survived but prospered during the past two difficult years. It had, and still has, everything in its favour. It is a growth industry, it is highly innovative and, above all, it is still a young industry unhampered by traditional work practices which have proved such a curse in, for example, shipbuilding and steel. There are few industrial problems in introducing new processes and methods and in fact most of them originated in the industry itself. Computer-aided design (CAD), automatic component insertion, computer-aided manufacture (CAM) and, at the end of the line, automatic test equipment (ATE). No wonder output doubles and doubles again.

Even in electronics it is not an easy ride, particularly in the depressed areas of consumer electronics struggling against the flood of imports from the Far East. But UK manufacturers are grasping the nettle with products like the Ferguson TX TV, and Fidelity's new colour TV, the design of which cuts component count by 40 percent. In capital goods the outlook remains buoyant and morale is high.

Will the older industries follow the example of electronics with get-up-and-go? Let's look at BSC's Llanwern steelworks in South Wales. This modern plant was plagued by industrial disputes in which one or other of 17 unions was generally involved. Both productivity and morale were low. The 14-week steel strike in the spring of 1980 was a catalyst which helped changed attitudes. The realisation came that you had to feed the cow before you could milk it.

In just one year from the strike, Llanwern has doubled productivity and has now almost reached the productivity levels of the best in Europe. Demarcation has all but disappeared, absenteeism is all but absent, inter-union squabbles are forgiven and forgotten. Manning levels have been reduced by 60 per cent and everybody at Llanwern is much happier than in the past, especially so since production is to increase beyond that in the original slimming-down programme. Success has replaced failure, optimism has replaced despair.

It is now clear that Llanwern and its sister plants are not isolated exceptions. Textiles, one of the hardest hit industries, is now showing signs of recovery. Uncertainty in recent months is turning to confidence with investors returning to buy company shares and the recession 'bottoming out'.

Inmos

Inmos is thankfully now showing positive signs of life. This is the controversial VLSI company formed with financial backing from the British taxpayer and promising to establish large production facilities (for 4,000 people) in the UK. I was reporting this news in the November 1978 issue of PE, together with news of a 50/50 GEC/Fairchild project which I forecast would be in production ahead of Inmos.

Well, I was wrong in respect of GEC/Fairchild. The idea was dropped when Fairchild was acquired by Schlumberger and GEC has since taken a different path.

Inmos, however, continued in business, first absorbing £25 million of start-up cash and then a further £25 million. A pilot production plant was set-up, not in a depressed area of the UK, but in Colorado Springs, USA. So far as extra employment in the UK has been created, there is almost a nil return except for a handful of experienced people who would have had no difficulty in finding employment anyway.

The good news is that Inmos now has some semiconductor products to sell and has started setting up a distribution chain in the UK and the rest of Europe. Dr. Richard Petritz, the American president, chief executive and co-founder of Inmos, is not promising instant success. He accepts that the coming year is full of risk with spending continuing at a high rate and sales still very small.

While wishing Inmos every success I remain sceptical that there will be any serious production in the UK, at least for a number of years. And it takes a good deal of imagination to believe that Inmos will ever employ 4,000 people in the UK in four factories. In fact only one is in construction. But Inmos has an imaginative outlook and the dream could still come true!

Shuttle

The spectacular success of NASA's Space Shuttle is wonderful news for all technologically based industries if only in re-establishing confidence and redressing the balance with the ecology and anti-nuclear lobbies. They have had considerable success in their knocking campaigns with the implication that all technology is harmful, its application shameful. Yet, these same lobbyists shamelessly use cars (responsible for more casualties than war), exploit television for propaganda, and some occasionally enjoy a hot bath by courtesy of atomic energy.

HF Radio

Twenty years ago as communication satellites started going into orbit there was much talk of the death of HF radio and submarine cables, the historical methods of long-distance communication. The 'experts' were wrong on both predictions. Submarine cables have prospered mightily, aided by new technology. And if HF radio today carries a less percentage of total traffic it still carries more than in the past.

Far from being in a terminal condition, HF radio has been honoured with two Queen's Awards: Marconi Communications for technological achievement with their fast-tuning techniques launched in 1976 and now in a second generation, and Racal Communications for export achievement with a trebling of overseas business in the past three years.

Redifon has also introduced a new professional quality HF receiver, the R500, company-funded, which adds weight to the proposition that HF radio will remain a valuable asset in the communications business to the end of the century and beyond.

CB Proposals...

27MHz and 934MHz F.M.

As most readers will by now be aware the Home Office have issued a Draft Performance Specification on CB to be operated on 27MHz and 934MHz f.m. The draft is in our view generous in its outline of 40 and 20 channel systems respectively with effective radiated powers of 2W—on 27MHz—and 3W (integral aerial!) or 25W on 934MHz.

Perhaps the only criticism that CB enthusiasts will level at it is that the selected frequencies are not compatible with those of any other country, but since there is little "legal" compatibility between most of the other systems anyway, the problems may not be too great. This would however limit the sale of UK-made equipment.

One point that the spec. does make very clear is that no equipment with the ability to transmit an a.m. signal will be permitted. Present sets will remain illegal, they may be converted to f.m. but they will have to conform to the spec. in every way, and will need to be marked with the official mark to show that they do.

At the time of writing, the Home Office expect to publish the final spec. through HMSO at or near the end of May and presumably the Control of Manufacture and Importation order 1968 will be amended soon after to enable sets to be made, etc.

We publish here the letter we received from the Home Office, the 27MHz forward (934MHz is virtually the same) and section 1 of the 27MHz draft (General) plus the differences in the 934MHz draft.

The full drafts run for 25 and 22 A4 size pages.

CITIZENS BAND RADIO SPECIFICATIONS

Thanks for your enquiry about the technical specification for authorised citizens band radio equipment.

It is hoped that a legal system of citizens band radio will be introduced later in the year. This will operate in the 27MHz band and the 934MHz band and as promised I enclose a copy of the draft specifications for each of these.

These draft specifications will be considered by a land mobile radio specification committee whose normal membership of UK manufacturing interests has been slightly augmented in this case. This committee is scheduled to hold its first meeting on the 24th April and if you have any comments on the specification I would be grateful if you would let me have them in writing prior to that date so that they may be taken into account.

The technical standards set out in the specifications will be reflected in regulations under Part II of the Wireless Telegraphy Act, 1949. These will set standards for equipment to which manufacturers, importers or assemblers will have to conform; they will also contain a requirement for conformity to be certified by the manufacturer, importer or assembler.

The Radiotelephonic Transmitters (Control of Manufacture and Importation) Order 1968 (SI 1968/61) prohibited the importation and manufacture of citizens band equipment. The Order remains in force and covers equipment capable of transmitting on any frequency between 26·1MHz and 29·7MHz, but in due course provision will be made for manufacture and importation of equipment which meets the technical requirements as they are finally established.

Citizens' band equipment operating with amplitude modulation will remain illegal under the new facility. Sets may be converted, provided that they then conform *in all respects* with the authorised technical standards.

Home Office
27.4.81

FOREWORD

1. Citizens Band Radio, a personal two-way radio system, is available for use throughout the United Kingdom. It operates in the 27MHz waveband and the 930MHz waveband.

2. The Wireless Telegraphy Act 1949 provides that no radio equipment may be installed or used except under the authority of the Secretary of State. All citizens band radio equipment, whether hand held, mobile or base station, must be covered by a licence; it is a condition of this that the apparatus fulfils, and is maintained to, certain minimum technical standards. This specification sets out these standards for 27MHz f.m. equipment; 934MHz f.m. equipment is subject to a separate specification.

3. The manufacturer, assembler, or importer of citizens band equipment is responsible for ensuring that the apparatus conforms with the specification; and any additional requirements imposed by regulations under the Wireless Telegraphy Act 1949. Conformity with the required standards may be established by tests carried out by the manufacturer, assembler or importer, or by a reputable test establishment acting on his behalf, but in either case conformity with the specification will remain the responsibility of the manufacturer, assembler or importer.

1 GENERAL

1.1 Scope of specification

This specification covers the minimum performance requirements for angle modulated radio equipments, comprising base station, mobile and hand-held transmitters and receivers or receivers only and additionally any accessories e.g. attenuators, power amplifiers, vehicle adaptors for optional use with the above for use in the Citizens Band Radio service.

For all equipments covered by this specification, the nominal separation between adjacent channel carrier frequencies is 10kHz.

1.2 Permitted effective radiated power

The output radio frequency power of the equipment is limited to 4W. With the antenna permitted for use with the equipment this gives an effective radiated power of 2W.

If an antenna is mounted at a height exceeding 10m the licence will require a reduction in transmitter power of 10dB.

To enable the user to accomplish this easily the equipment manufacturer should provide as a standard accessory an attenuator having a nominal attenuation of 10dB, which may be purchased by the licensee.

1.3 Operating frequencies

The equipment shall provide for transmission and reception only of frequency modulated emissions on one or more of the following radio frequency channels:

Channel 1	27·60125MHz	Channel 21	27·80125MHz
Channel 2	27·61125MHz	Channel 22	27·81125MHz
Channel 3	27·62125MHz	Channel 23	27·82125MHz
Channel 4	27·63125MHz	Channel 24	27·83125MHz
Channel 5	27·64125MHz	Channel 25	27·84125MHz
Channel 6	27·65125MHz	Channel 26	27·85125MHz
Channel 7	27·66125MHz	Channel 27	27·86125MHz
Channel 8	27·67125MHz	Channel 28	27·87125MHz
Channel 9	27·68125MHz	Channel 29	27·88125MHz
Channel 10	27·69125MHz	Channel 30	27·89125MHz
Channel 11	27·70125MHz	Channel 31	27·90125MHz
Channel 12	27·71123MHz	Channel 32	27·91125MHz
Channel 13	27·72125MHz	Channel 33	27·92125MHz
Channel 14	27·73125MHz	Channel 34	27·93125MHz
Channel 15	27·74125MHz	Channel 35	27·94125MHz
Channel 16	27·75125MHz	Channel 36	27·95125MHz
Channel 17	27·76125MHz	Channel 37	27·96125MHz
Channel 18	27·77125MHz	Channel 38	27·97125MHz
Channel 19	27·78125MHz	Channel 39	27·98125MHz
Channel 20	27·79125MHz	Channel 40	27·99125MHz

Citizens Band Radio equipment shall not contain facilities for transmission of radio frequencies other than those listed above, and those contained in MPT. *(this specification—Ed.)*

Single channel equipment may be tested on any one of the approved channels. Multi-channel equipment shall be equipped to operate at the centre, and the upper and lower limits of the frequency range over which channel switching is possible.

1.4 Permitted modulation

Only equipment which employs frequency or phase modulation and has no facilities for any other form of modulation will meet the requirements of this specification.

1.5 Labelling

The equipment shall be provided with a clear indication of the type number and name of the manufacturer.

1.6 Certification of compliance

Compliance with this specification shall be indicated by an authorised mark stamped or engraved on the front panel of the equipment.

The mark used to indicate compliance shall be as shown in Fig. 1.

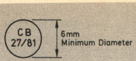

Fig. 1: Letter and figure height not less than 1 mm

1.7 Controls

Those controls, which if maladjusted might increase the interfering potentialities of the equipment, shall not be easily accessible.

934MHz VARIATIONS

1 GENERAL

1.1 Scope of specification

This specification covers the minimum performance requirements for angle modulated radio equipments, comprising base station, mobile and hand-held transmitters and receivers or receivers only and additionally any accessories, for example power amplifiers, attenuators, vehicle adaptors for optional use with the above for use in the Citizens' Band Radio service.

For all equipments covered by this specification the nominal separation between adjacent channel carrier frequencies is 25kHz.

1.2 Permitted effective radiated power

The output radio frequency power of the equipment is limited to 8W for equipments which has terminals for connexion of a separate antenna. With the antenna permitted for use with this equipment this gives a maximum effective radiated power of 25W.

For equipment with an integral antenna the effective radiated power is limited to 3W.

1.3 Operating frequencies

The equipment shall provide for transmission and reception or reception only of frequency modulated emissions on one or more of the following radio frequency channels:

Channel 1	934·025MHz	Channel 11	934·525MHz
Channel 2	934·075MHz	Channel 12	934·575MHz
Channel 3	934·125MHz	Channel 13	934·625MHz
Channel 4	934·175MHz	Channel 14	934·675MHz
Channel 5	934·225MHz	Channel 15	934·725MHz
Channel 6	934·275MHz	Channel 16	934·775MHz
Channel 7	934·325MHz	Channel 17	934·825MHz
Channel 8	934·375MHz	Channel 18	934·875MHz
Channel 9	934·425MHz	Channel 19	934·925MHz
Channel 10	934·475MHz	Channel 20	934·975MHz

(Although the specification quotes 25kHz separation the allocated channels are at 50kHz spacing—we are informed that this will be clarified at a later date—Ed.)

The separation between the "27MHz" frequencies now being used illegally and these proposals will obviously make the task of restricting any continuing illegal use that much more easy. It should also mean that, providing illegal use can be stopped, the radio control modellers should be free of interference from British CB.

It is anticipated that these proposals are realistic enough to encourage widespread use of the new service (hopefully without all the codes and jargon) and thus encourage illegal users to convert.

We do not yet know the restrictions and cost of a licence or (at the time of writing) the date of the introduction of the service—our guess is early September, but it is a guess.

ANNOUNCEMENT

PE will be publishing more on CB in the September issue. A full announcement will be made next month, when all will be revealed!

PE QUASAR
AM/FM STEREO TUNER

THE PE Quasar is an AM/FM stereo tuner which incorporates three ready-built and aligned modules: FM tuner (LP1179), r.f.-i.f. amplifier (LP1181) and a frequency multiplexed stereo decoder (LP1401). The design of the Quasar enables the completed tuner to be easily aligned using just a multimeter and a screwdriver.

CIRCUIT DESCRIPTION

The main circuit diagram of the PE Quasar is shown in Fig. 1.

The FM tuner is a ready-built and aligned VHF module (LP1179) with 75 and 300 ohms aerial inputs which has capacitance tuning for AM. Frequency drift on the FM waveband is counteracted by a built-in varicap diode across the oscillator circuit which facilitates the use of automatic frequency correction (a.f.c.) with a variation of ±0·5V (ref. zero) equalling a frequency shift of ±100kHz. The output from the tuner is connected to the i.f. circuit via a 10·7MHz ceramic filter (XLI). The output signal from the filter only becomes significant when the input signal corresponds to 10·7MHz. The filter then acts as a high Q tuned circuit.

The i.f. signal from the front end is matched to the ceramic filter and is applied to IC1 via pin 1. IC1 is a TDA1200. This i.c. integrates i.f. amplification and limiting (three stages with a level detector for each stage) with a balanced quadrature FM detector, an audio amplifier with a muting facility and a voltage regulator.

The complete system includes such features as an a.f.c. drive circuit and tuning meter drive. The a.f.c. output on pin 7 is reference to +5·6V and because the tuner module's a.f.c. is designed to operate with reference to zero volts, it is necessary to apply a stabilised voltage of approximately −4V. Providing L2 is correctly adjusted, VR1 can be set to obtain the necessary zero volts at the junction of R2 and R4.

INTERSTATION MUTING

Because of the high overall gain of the FM tuner a high level of noise can occur when tuning between stations. This noise can be reduced by interstation muting which keeps the audio stages inactive until a signal of pre-determined strength is received. The muting level in the Quasar can be altered by changing R13. A higher value reduces the muting whilst a lower value increases it.

STEREO DECODER

A block diagram of the LP1401, which is a ready-built and aligned frequency multiplexed stereo decoder, is shown in Fig. 2.

The multiplexed stereo output from pin 6 of IC1 is fed via R5 and C6 to the decoder where a splitter circuit extracts the stereo and mono signals. De-emphasis is applied to both

SPECIFICATION

MW520 to 1640kHz sensitivity 400μVm for 15dB s/n ratio
LW150 to 265kHz sensitivity 900μVm for 15dB s/n ratio
IF470kHz
VHF88 to 104MHz sensitivity 8μV for 30dB s/n ratio
Limiting 10mV or better
AFC ±100kHz
IF 10·7MHz
IF rejection 40dB min
Image rejection 40dB min
Stereo separation 38dB at 1kHz

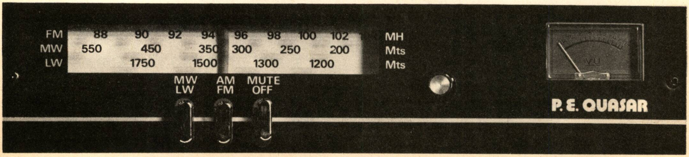
FM 88 90 92 94 96 98 100 102 MH
MW 550 450 350 300 250 200 Mts
LW 1750 1500 1300 1200 Mts
MW LW
AM FM
MUTE OFF
VU
P.E. QUASAR

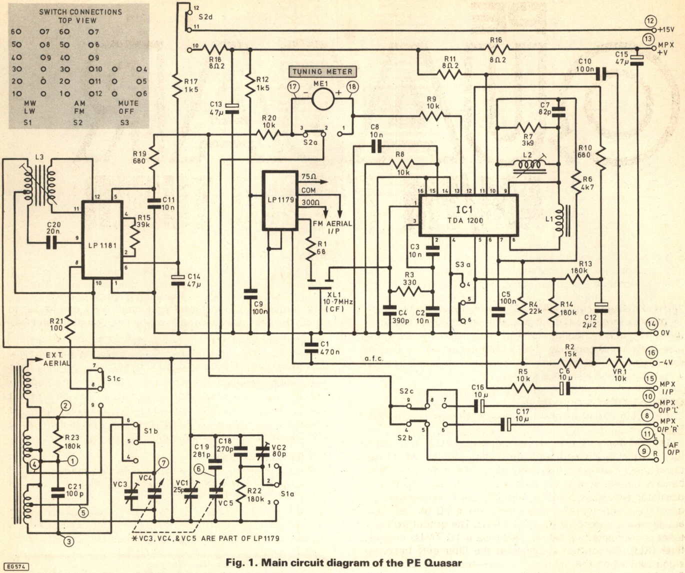

Fig. 1. Main circuit diagram of the PE Quasar

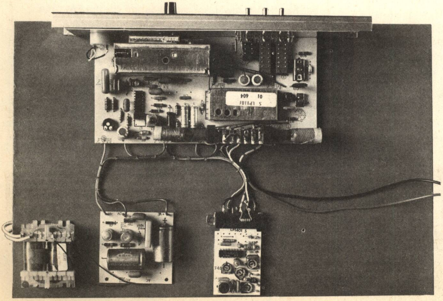

Photograph of the Quasar system

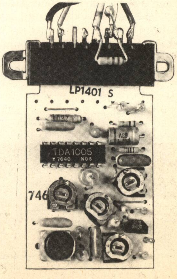

Stereo decoder and SK1

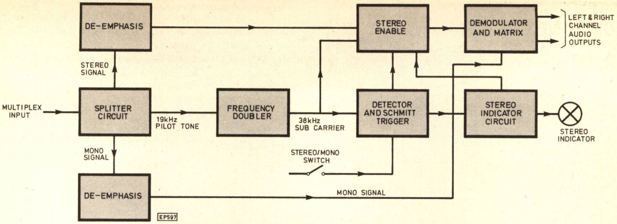

Fig. 2. Block diagram of the LP1401 stereo decoder

signals to improve the signal to noise ratio by attenuating the background noise whilst equalising the signal. The 19kHz pilot tone is also extracted and the 38kHz sub carrier, which was suppressed in the transmitted signal, is regenerated by a frequency doubler which is also amplitude limited to reduce noise. The sub carrier is then added in correct phase to the stereo signal and fed to the matrix where the original left and right channel signals are retrieved.

In the mono state the Schmitt trigger, stereo indicator lamp and the stereo on/off gate are all inactive. Only the mono signal is passed through the matrix to each channel.

The stereo enable switch is triggered by the 19kHz pilot tone. For good reception the strength of the stereo signal has to be high; a poor stereo signal would sound better in mono. The level of the pilot tone is monitored and for the Quasar to switch to the stereo mode the pilot tone signal must be higher than 15mV r.m.s.

When the stereo switch is operated a d.c. output from the detector circuit operates the Schmitt trigger which switches on the stereo indicator lamp and the demodulator.

The use of a manual mono/stereo switch enables the mono mode to be selected when a stereo signal is being received.

AM I.F. MIXER

The MW/LW ferrite rod aerial affords adequate sensitivity to all but the weaker signals. However, an extra winding is provided for an external aerial. Signals from the ferrite aerial are fed to the input of the LP1181. This module, which is pre-aligned, performs the functions of a local oscillator/mixer, i.f. amplification, detection and a.g.c. Resistor R20 acts as the "diode load" and tuning meter drive.

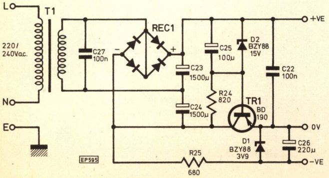

Fig. 3. Circuit diagram of the power supply unit

POWER SUPPLY

The circuit diagram of the power supply is shown in Fig. 3. The power supply is a voltage doubler circuit. The unregulated supply appears across the positive terminal of C23 and the negative terminal of C24. The design is unconventional only as far as the negative line is regulated and designated as 0V with the −4V negative supply rail derived via R25. This voltage which is Zener stabilised and decoupled by C26 is used for a.f.c. offset.

CONSTRUCTION

The p.c.b. design for the main board of the Quasar is shown in Fig. 4 with the component layout shown in Fig. 5. Before fitting the FM tuner (LP1179) the AM oscillator trimmer screw on the tuner should be removed (Fig. 6). Carefully check the orientation of IC1 and the AM module (LP1181) before soldering. Also note the position of the fixed coil L1 which is used in place of a variable inductor. The MW/LW aerial assembly should be soldered last as shown in Fig. 7. After soldering the aerial assembly should be glued to the p.c.b.

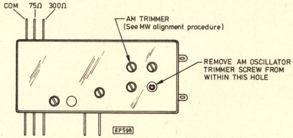
COM
75Ω
300Ω
AM TRIMMER (See MW alignment procedure)
REMOVE AM OSCILLATOR TRIMMER SCREW FROM WITHIN THIS HOLE
EP598

Fig. 6. AM oscillator modification for the FM tuner

The power supply p.c.b. design is shown in Fig. 8 with the component layout shown in Fig. 9. After these two p.c.b.s have been soldered, carefully check the orientation of all the components and that none of the tracks are shorted out by slivers of solder.

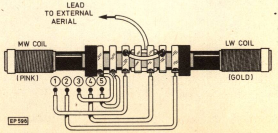

Fig. 7. Wiring details for the aerial assembly

COMPONENTS . . .

Resistors

R1	68
R2	15k
R3	330
R4	22k
R5,R8,R9,R20	10k (4 off)
R6	4k7
R7	3k9
R10,R19,R25	680 (3 off)
R11,R16,R18	8Ω2 (3 off)
R12,R17	1k5 (2 off)
R13,R14,R22,R23	180k (4 off)
R15	39k
R21	100
R24	820
*R26,R27	2k2 (2 off)

All resistors $\frac{1}{4}$ to $\frac{1}{2}$W 10%

Potentiometers

VR1	10k preset

Capacitors

C1	470n
C2,C3,C8,C11	10n (4 off) polyester
C4	390p polystyrene
C5,C9,C10,C22,C27	100n (5 off)
C6,C16,C17	10μ 25V (3 off) elect.
C7	82p polystyrene
C12	2μ2 63V elect
C13,C14,C15	47μ 25V elect (3 off)
C18	270p polystyrene
C19	281p 2%
C20	20n polyester
C21	100p 5% polystyrene
C23,C24	1500μ to 3300μ16V elect (2 off)
C25	100μ 16V elect
C26	220μ 16V elect
VC1	25p (max) trimmer
VC2	80p (max) trimmer

Semiconductors

D1	3·9V 300mW Zener
D2	15V 300mW Zener
REC1	
TR1	BD190
IC1	TDA 1200

Inductors

L1	220 KE (22μH)
L2	L101 (2·2μH)
L3	AM Osc coil (42276)

Miscellaneous

- 10·7 MHz filter
- LP1181
- LP1401
- FM Tuner front end LP1179
- VU meter
- Ferrite rod assembly
- Mains transformer
- Chassis
- p.c.b.s.
- Drive cord and guides. S1, S2, S3.

*See Fig. 10.

Note the p.c.b.s supplied in the kit are not drilled.

Constructor's Note

A kit of parts for the Quasar (minus the stereo enable and stereo indicator modifications) is available from **RT&VC, 21B High Street, Acton W3 6NG.** (Price £17·95 plus £2·50 p&p.)

The front panel should be assembled next. If a stereo indicator and an enable switch (Fig. 10) are to be fitted, then the mounting holes for these should be drilled first. The front panel legend can then be fixed using either double sided tape or non plastic solvent glue. The mounting holes can then be cut out in the legend using a sharp knife. The tuning meter can then be fitted to the back plate using double sided tape. Before the back plate is fitted to the main p.c.b. the three grommets should be fitted into the mounting holes for the LP1179 tuner. The three tuning drive cord guides should be inserted into the back plate and peened over using a hammer.

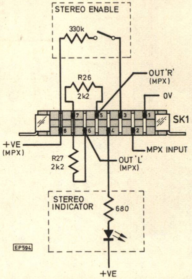

Fig. 10. Connection diagram for SK1

The two wires for the tuning meter should be soldered before the back plate is fitted. After mounting the back plate onto the p.c.b. the drive tuning cord should be fitted following the diagram in Fig. 11. The tuning indicator was formed using a piece of copper wire and length of p.v.c. sleeve. To improve the definition of the tuning needle a piece of white p.v.c. tape was fitted behind the tuning display. Do not fit the front panel into position until after the tuner has been aligned.

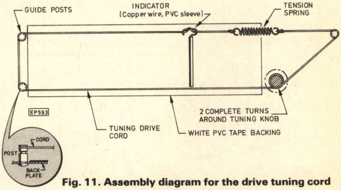

Fig. 11. Assembly diagram for the drive tuning cord

The LP1401 stereo decoder, which is supplied assembled and tested, plugs into SK1 and before any interboard wiring is carried out the two resistors should be soldered to SK1 (Fig. 10). With all the boards and SK1 assembled the interboard wiring should be carried out as shown in Fig. 12.

FM ALIGNMENT

After the Quasar has been assembled and wired it can be switched on and the voltage supplies checked. It should then be connected to a suitable amplifier and speaker system. To

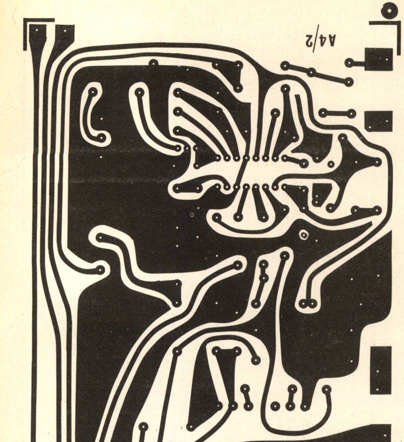

Fig. 4. P.c.b. design for the main board

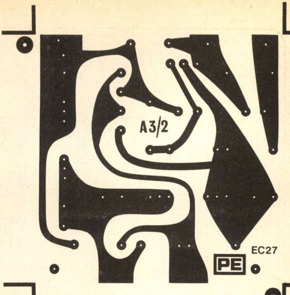

Fig. 8. P.c.b. design for the p.s.u.

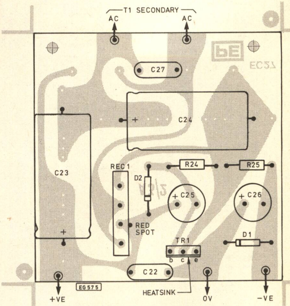

Fig. 9. Component layout for the p.s.u.

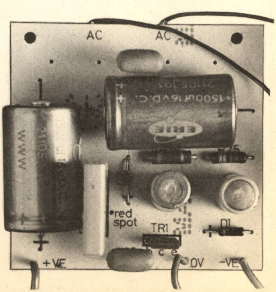

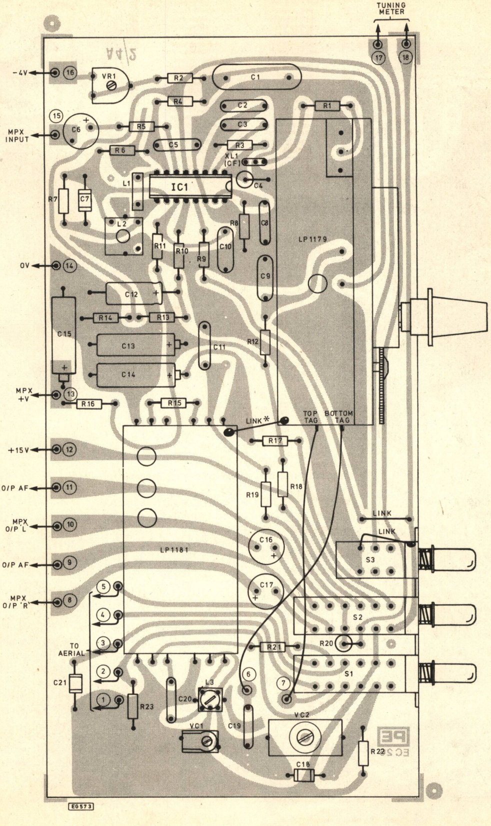

Fig. 5. Component layout for the main board. *Note this link is soldered to the case of each module

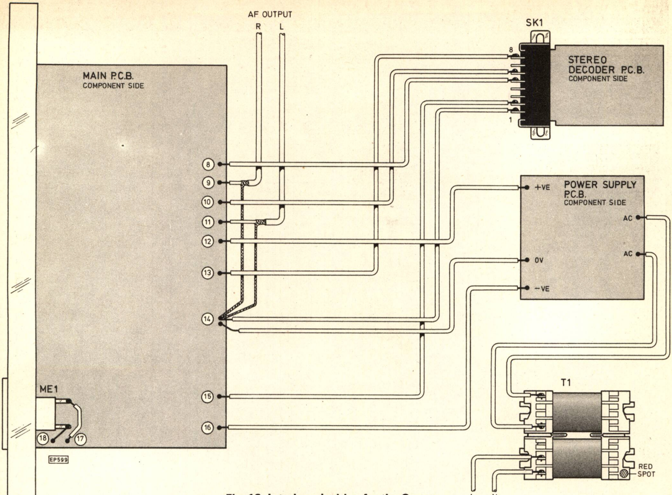

Fig. 12. Interboard wiring for the Quasar

align the FM band the following procedure should be carried out:
a) Cancel the AFC by shorting C1.
b) Press the AM/FM and Mute/Off switches in.
c) Connect an aerial to tuner (75 or 300Ω).
d) Unscrew the core of L2 so that it is approximately 4 to 6mm proud of the can. If the construction is correct the Quasar will operate.
e) Adjust L2 for maximum undistorted audio output and maximum meter deflection.
f) Remove the link across C1.
g) Short the junction of R1 and XL1 to earth.
h) Adjust VR1 for zero volts across C1 and remove the link between R1/XL1 and earth.

This completes the FM alignment and the core of L2 should be sealed with candle wax.

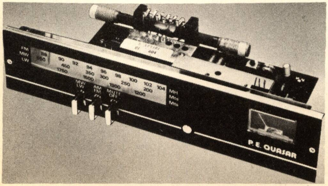

AM MEDIUM WAVE

The medium wave band can be aligned using the following procedure:

a) Put the AM/FM and the MW/LW buttons in the out position and place the aerial coils flush with the end of the ferrite rod.
b) Tune the set to approximately 433M and adjust L3 to receive Radio 2. If this is not available set the tuner to any other known wavelength at the extreme LF end and tune L3 to receive that station.
c) Set the tuner to 247M and adjust VC1 to receive Radio 3.
d) Repeat steps (b) and (c) until the two extreme stations correspond to the scale.
e) Tune the set to a weak station at the extreme LF end and adjust the medium wave coil L3 for maximum output.
f) Tune the set to a weak station on the HF end and adjust the AM trimmer on the tuner for maximum output.
g) Repeat steps (d) and (f) for best results.

AM LONGWAVE

The longwave band can be aligned using the following procedure:

a) Press the MW/LW button in and set the pointer to 1500M.
b) Adjust VC2 to receive Radio 4.
c) Set the LW ferrite coil for maximum output. Both the aerial coils can now be sealed with candle wax. ★

VIDEOTONE

BUY DIRECT FROM US AND GET THE SAME HIGH QUALITY AT LOW PRICES!

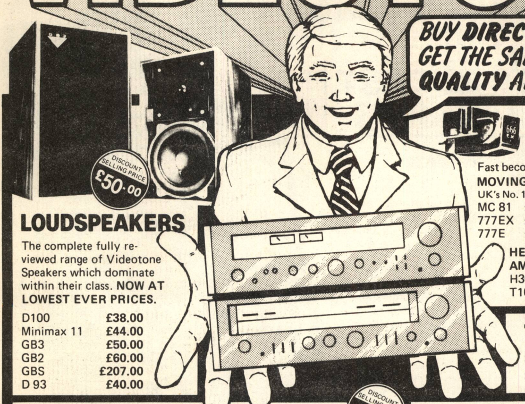

LOUDSPEAKERS

The complete fully reviewed range of Videotone Speakers which dominate within their class. **NOW AT LOWEST EVER PRICES.**

D100	£38.00
Minimax 11	£44.00
GB3	£50.00
GB2	£60.00
GBS	£207.00
D 93	£40.00

CORAL CARTRIDGES

Fast becoming one of the top names

MOVING COIL UK's No. 1 Cartridge		MOVING MAGNET	
MC 81	£48.87	555SX	£7.28
777EX	£35.00	555E	£14.22
777E	£25.00	666E	£32.48

HEAD AMP		HEADSHELLS	
H300	£51.75	S100	£6.00
T100	£24.75	S101	£7.00
		S200	£4.00

TURNTABLES

Sansui SR222 Mk2	£69.00
Sansui P50S	£69.00

AMPS- TUNER-CASSETTE

DISCOUNT SELLING PRICE £68·00

DISCOUNT SELLING PRICE £75·00

30 watt amp MC input SA4 130	£75.00
Stereo Tuner ST 4120	£68.00
Cassette full features SC 4200	£95.00
50 watt amplifier WA7700	£77.00
20 watt amplifier LA2020	£58.00

This new range of Electronics from Videotone redefines the words quality and value for money to a new high.

MICROPHONES

MU 105-22	£29.30
MU 105-12	£22.25
MU 25 C	£17.39

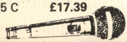

HEADPHONES

Superbly made with top flight performance

HP90	£12.65
HP80	£9.69

* A MESSAGE FROM VIDEOTONE *

Dear Customer

You will find that the products advertised on this page are the best possible value for money. They are only low in price because we have eliminated large amounts of selling costs that other brands have to suffer. These savings are passed directly onto you. We have full brochures on any specific item you may be interested in and a competent realistic staff of engineers at our London Showrooms to help you in your choice. Our consumer protection packages are comprehensive and we offer every form of financing you may require. We carry out our own servicing and are dedicated to giving **Value for Money.** We are confident our products are unbeatable. You may purchase with confidence because our Engineers have specially selected them from competitive sources throughout the world and we import them directly ourselves. **Remember, you have 21 days trial period on all products. That is the measure of our confidence.**

C Hardcastle

Cliff Hardcastle, Managing Director.

Quality plus value ~ always

VIDEOTONE

ALL PRICES INCLUDE VAT

ALL PRODUCTS ON DISPLAY & CONTINUOUS DEMONSTRATIONS

98 CROFTON
PARK ROAD
LONDON SE4
TEL: 01-690 8511/2

SEND FOR OUR LATEST FREE BROCHURE
AND DETAIL LIST OF LOCAL SALES OUTLETS IN THE U.K.

NAME ____________________

ADDRESS ____________________

____

PE

Capacitance METER

MARTIN KENT

FREE CASE PROJECT

DP600 Capacitance Meter

CAPACITANCE measurement is a frequent requirement of professional engineers and hobbyists alike. In these times of rising prices, hobbyists are obliged to keep a store of used components which may be useful in future circuits. Component markings gradually disappear with time and capacitor markings seem to disappear most quickly. How frustrating it can be to be faced with a box of unmarked capacitors and a circuit requiring completion.

Matching of capacitor values is often required and apart from its primary function of testing components, a capacitance meter may also be used for a wide variety of tests including cable length, cable capacitance, p.c.b. track capacitance and it is a very useful development tool.

The DP600 Capacitance Meter provides quick and accurate capacitance measurement between 1p and 19·99µ at low cost.

CAPACITANCE MEASUREMENT

There are a large number of methods in use for the measurement of capacitance and the cost of embodying many of these techniques is out of all proportion to the accuracy and usefulness of the instrument. Among the aims in the design of the meter has been the provision of a low cost instrument, with good accuracy, covering a wide range of measurement, with low power consumption and ease of use.

The traditional method of measurement is to use a bridge arrangement with a.c. energisation, and adjusting for null indication. This method can be expensive and requires careful adjustment by the operator.

Rate of charge can be useful for capacitor measurements but is exponential, although, if a constant current source is used instead of a voltage source, good linearity can be achieved. If the constant current source is turned on for an accurately defined time, then the charge on the capacitor at the end of this time will be proportional to the capacitance. A considerable amount of circuitry is required to use such a technique in a repetitive mode, rather than a single-shot mode.

Ideally, once the capacitor to be measured is connected to the instrument, the measurement should be updated automatically as it enables circuit adjustments to be carried out simultaneously and changes in capacitance to be monitored.

The heart of the DP600 is a CMOS monostable which requires very little supply current and operates at low supply voltages; the block diagram of the instrument is shown in Fig. 1.

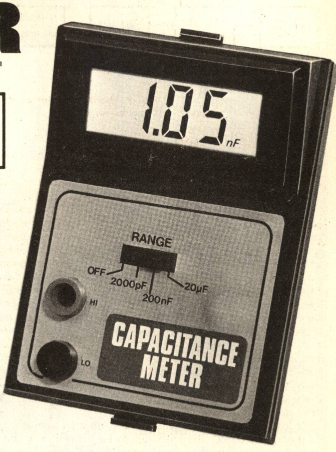

When triggered by an input pulse, the monostable produces an output pulse of duration proportional to R and C; accurate decade resistors are therefore suitable for setting the range of measurement, and C is the capacitor to be measured. A system suited to use of standard resistors for range switching results in much lower cost than instruments requiring standard capacitors. The monostable is triggered by a constant frequency source and the constant amplitude pulses are averaged by an RC integrator. The output voltage is now proportional to the applied capacitor and provides a direct readout on the LE DPM200 panel meter. Measurements are automatically updated by the frequency source.

An ideal capacitor is composed of two parallel plates with a dielectric of infinite resistance between the plates. However, practical capacitors have a parallel loss resistance which will shunt the capacitor and reduce the monostable pulse width slightly. The effect will only be noticeable for capacitors with very low parallel resistance, or high leakage.

SPECIFICATION

RANGE	RESOLUTION	ACCURACY
2000pF	1pF	0·75% ±3 digits
200nF	0·1nF	
20µF	0·01µF	

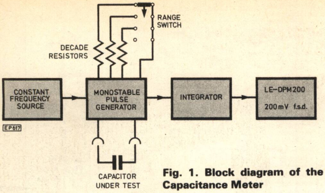

Fig. 1. Block diagram of the Capacitance Meter

CIRCUIT DESCRIPTION

The circuit diagram of the Capacitance Meter is shown in Fig. 2. Panel Meter ME1 provides a complete analogue-to-digital convertor with ultra-low power consumption and calibrated 200mV full scale.

CMOS timer IC1 operates between V+ and COM, which is typically 2·8V. Switch S1d selects the appropriate decade resistor for the range of measurement. Accuracy of measurement is dependent upon the monostable output pulses being of constant amplitude. The COM pin of ME1 has good stability with temperature but the change in current drawn through it by the lower value resistor, R8, on the top range can reduce the Common voltage by about 2%, which would be directly indicated in range accuracy. Each range could be individually calibrated, but it is desirable to use only one adjustment. To provide good amplitude stability R9 and IC2 are used, which is a bandgap reference integrated circuit with typically 1·2V output. Resistors R6–R8 should be high stability metal film types as they directly influence measurement accuracy. Pulse averaging is carried out by R10 and C3 with calibration by VR1.

To optimise measurement accuracy, an offset control is incorporated. Before the capacitor to be measured is connected to the instrument, the effects of stray capacitance may be eliminated by adjusting VR2. Provision of the offset control also enables measurements to be made of capacitors situated at the end of long cables by eliminating the cable capacitance.

The LE DPM200 panel meter includes a dual-slope integration A to D convertor which contains an RC oscillator for control of the integrator timing cycle. To reduce the cost of the instrument, the frequency source required to trigger the CMOS monostable may be derived from the panel meter. The oscillator has a nominal frequency of 48kHz which is divided down to perform the various timing functions. The backplane signal for the LCD is set at a frequency of *clock divided by 800,* or nominally 60Hz. The maximum pulse width output from IC1 is 1k × 20μ or 20ms. The period of the triggering waveform must be greater than the monostable period otherwise the monostable would be retriggered during a measurement cycle, instead of at the end of the cycle, resulting in erroneous readings. To slow down the internal clock frequency slightly C4 is added between CLK (oscillator) and TEST (digital ground).

The backplane signal is a nominal 5V amplitude with respect to TEST, but is +2·5V/–2·5V with respect to Analogue Common. Level shifting is provided by TR1.

IC1 requires a narrow trigger pulse which should return to the high state before the end of the output pulse. TR2 and associated circuitry produces a narrow negative-going pulse, of typically 50μs, for each positive-going edge of the backplane signal.

The timing waveforms of the circuit are shown in Fig. 3.

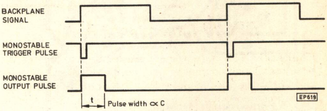

Fig. 3. Timing waveforms

Another advantage of using the internal oscillator is that the system is synchronised to the measurement cycle of the A to D convertor to reduce the display jitter which would otherwise result from the charging and discharging of C3. The R10/C3 time constant could be lengthened but this would reduce the response time of the instrument to change in applied capacitance. The display drive circuitry within ME1 is switched to the required decimal point by S1b.

ASSEMBLY AND TESTING

Assembly of the p.c.b. is very straightforward as the use of the self-contained panel meter greatly reduces the component count. The panel meter is connected to the p.c.b. via ribbon cable and the assembly should be tested before fixing into the case.

When the unit is switched on, the display should be able to be adjusted for zero reading by VR2 on each range. To calibrate the instrument it is preferable to use a standard capacitor, alternatively comparison may be made with another capacitance meter. Calibration should be carried out at mid-range, using either a 1000p, 100n, or 10μ standard capacitor. With VR1 adjusted accordingly on one range, the metal film resistors R6–R8 will ensure accurate measurement on the other ranges.

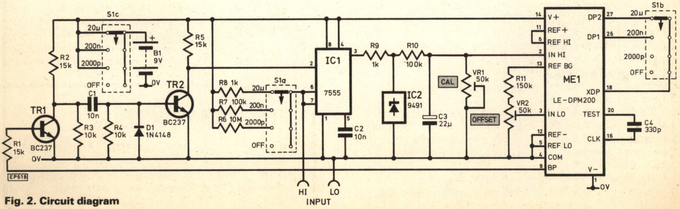

Fig. 2. Circuit diagram

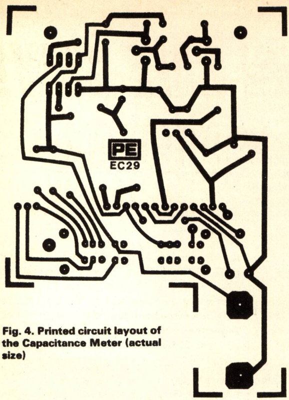

Fig. 4. Printed circuit layout of the Capacitance Meter (actual size)

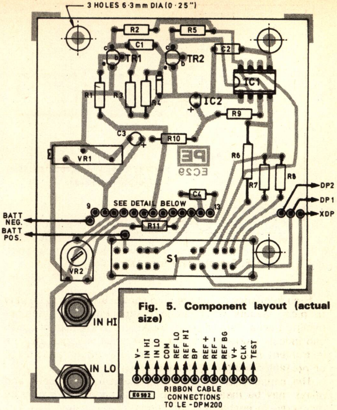

Fig. 5. Component layout (actual size)

If a capacitor of over-range value is connected to the instrument, the standard over-range warning should be indicated whereby a 1 will show in the leading digit with the other digits blanked.

APPLICATIONS

The Capacitance Meter may be used to measure a wide range of capacitors including electrolytic types.

Cable capacitance can be an important factor in signal distribution systems and this may easily be measured with the instrument. Total capacitance may be measured, alternatively the capacitance per unit length is often required and may be established using a one foot or one metre length.

If the capacitance per unit length is known or can be measured, then the length of cables may be measured using the DP600.

COMPONENTS . . .

Resistors

R1	15k	Carbon film 5%
R2	15k	„ „ „
R3	10k	„ „ „
R4	10k	„ „ „
R5	15k	„ „ „
R6	10M	Metal film 0·5%
R7	100k	„ „ „
R8	1k	„ „ „
R9	1k	Carbon film 5%
R10	100k	„ „ „
R11	150k	„ „ „

Variable Resistors

VR1	50k	Multiturn preset
VR2	50k	

Capacitors

C1	10n	Polyester
C2	10n	„
C3	22μF	Tantalum bead 16V
C4	330pF	Polystyrene

Semiconductors

D1	IN4148
TR1	BC237
TR2	BC237
IC1	ICM7555
IC2	Teledyne 9491/Intersil 8069

Miscellaneous

ME1 LE DPM200 (see special offer)
Instrument case
P.c.b.
Ribbon cable
4P4T Slide switch
PP3 Battery connector
4mm p.c.b. mounting terminals (2 off)

A kit of components (excluding the DPM200 and case) is available at £12.95 inc. VAT from **Lascar Electronics Ltd., Unit 1, Thomasin Road, Basildon, Essex SS13 1LH.**

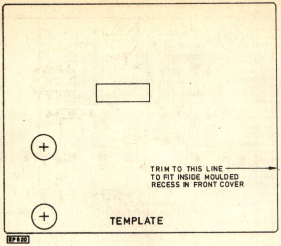

Fig. 6. Template for front panel drillings

High frequency circuits require careful attention to be paid to p.c.b. layouts when siting components and interconnecting tracks. Parallel p.c.b. tracks act as capacitors which can induce spurious oscillation and noise voltages and the instrument may be used to detect unwanted capacitance before fault-finding in systems is required.

The capacitance of components such as switches and relays may be measured, also crystal capacitance may be measured to enable the conditions for resonance in a particular oscillator circuit to be established. ★

ON SALE NOW!

PE POPULAR PROJECTS...

Our book *PE Popular Projects* containing a selection of 19 popular projects is now on sale at newsagents and components stores. The book costs £1·25 from retail outlets and is also available for £1·50, UK post paid, or £1·80 overseas surface post paid, from Post Sales Department (PE Popular Projects), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

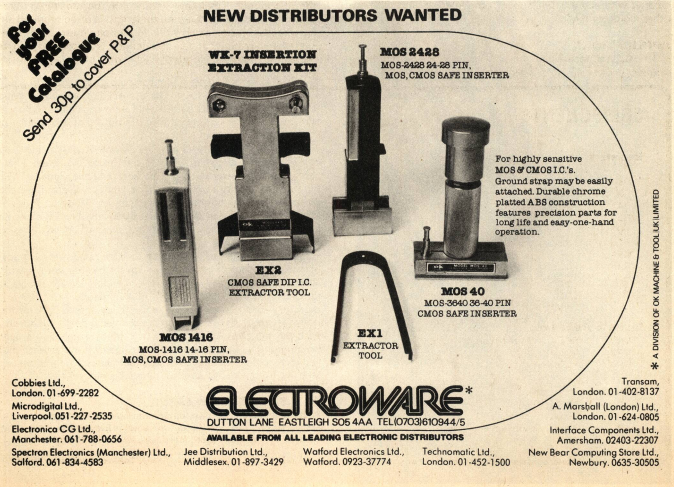
NEW DISTRIBUTORS WANTED

For your FREE Catalogue
Send 30p to cover P&P

WK-7 INSERTION EXTRACTION KIT

MOS 2428
MOS-2428 24-28 PIN,
MOS, CMOS SAFE INSERTER

For highly sensitive MOS & CMOS I.C.'s. Ground strap may be easily attached. Durable chrome platted ABS construction features precision parts for long life and easy-one-hand operation.

EX2
CMOS SAFE DIP I.C.
EXTRACTOR TOOL

MOS 40
MOS-3640 36-40 PIN
CMOS SAFE INSERTER

MOS 1416
MOS-1416 14-16 PIN,
MOS, CMOS SAFE INSERTER

EX1
EXTRACTOR
TOOL

ELECTROWARE*
DUTTON LANE EASTLEIGH SO5 4AA TEL(0703)610944/5

* A DIVISION OF OK MACHINE & TOOL (UK) LIMITED

AVAILABLE FROM ALL LEADING ELECTRONIC DISTRIBUTORS

Cobbies Ltd.,
London. 01-699-2282
Microdigital Ltd.,
Liverpool. 051-227-2535
Electronica CG Ltd.,
Manchester. 061-788-0656
Spectron Electronics (Manchester) Ltd.,
Salford. 061-834-4583
Jee Distribution Ltd.,
Middlesex. 01-897-3429
Watford Electronics Ltd.,
Watford. 0923-37774
Technomatic Ltd.,
London. 01-452-1500
Transam,
London. 01-402-8137
A. Marshall (London) Ltd.,
London. 01-624-0805
Interface Components Ltd.,
Amersham. 02403-22307
New Bear Computing Store Ltd.,
Newbury. 0635-30505

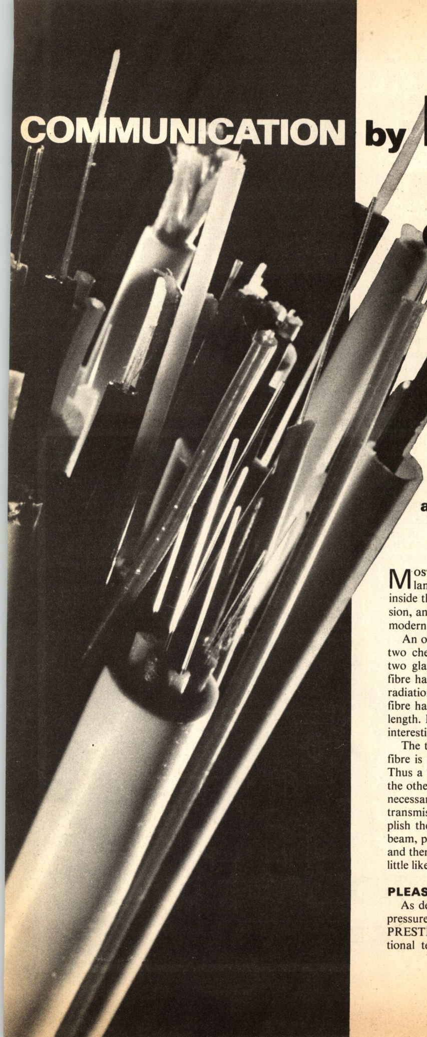

COMMUNICATION by FIBRE OPTICS

Gary Gardner

Fibre optics are now in use as communications links. This article describes what they are and how they are made and used.

MOST of us are by now familiar with decorative fibre optic lamps on coffee tables. The use of fibre optics for seeing inside the body has been shown on TV on more than one occasion, and one may have good cause to marvel at this wonder of modern science.

An optical fibre consists of a fine strand of glass made from two chemically dissimilar glasses, one inside the other. These two glasses are referred to as the core and the cladding. The fibre has the ability to act as a wave guide to electro-magnetic radiation, such as ordinary visible light, or infra red. Thus the fibre has the unique ability to bend light, and direct it along its length. It is this property that makes the use of optical fibres so interesting.

The transmission of visible light or infra red down an optical fibre is analogous to an electrical current passing down a wire. Thus a "signal" introduced at one end should ideally emerge at the other end unchanged in shape and amplitude. Why then is it necessary for us to advocate the use of an optical fibre for the transmission of signal, if an ordinary coaxial cable will accomplish the same result? To convert electrical signals into a light beam, pass this down the optical fibre, detect it at the other end, and then convert the light back again into an electrical signal is a little like using a sledge-hammer to crack a nut, isn't it?

PLEASE TRY AGAIN LATER . . .

As demand for telecommunications services increases, so the pressure on our telephone system grows. The advent of PRESTEL, viewphone, and computer data through conventional telephone cables can and will crowd out the ordinary telephone conversations that also have to be carried. By the use of optical fibre communication systems the capacity for carrying signals is increased by tens of thousands. The reason for this is quite simple; the capacity of a carrier wave is related to its frequency. The frequency of light is many thousand times that of ordinary radio waves.

With optical fibres, the possibility of "crossed lines" will be reduced, because of the total lack of crosstalk between adjacent fibres. For military applications, such as onboard ship, communication cannot be jammed or interfered with, which is a major benefit for military use. Because of their smaller physical size, the existing underground trunking system used for the interconnection of telephone subscribers to the exchanges needs little if any modification to accommodate the new cable.

To the motorist, if nothing else, the lack of the familiar road-up signs will bring a sigh of relief. In oil refineries and other petrochemical plants, the risks of sparks causing fire or explosion are almost completely eliminated by use of fibre optic data links. The basic raw materials are commercially available today and, although the prices are high at present, these will fall dramatically when volume production gets under way.

MANUFACTURE

There are two major processes used for the manufacture of optical fibres. The British Post Office (now renamed British Telecom) have developed a glass-making process called the Double Crucible process. In this process, glasses of dissimilar composition are produced by melting extremely pure ingredients in a coaxial crucible. Once molten, the two glasses are drawn simultaneously from the bottom of the crucible to form a glass rod. As previously described, this rod consists of a central core encased in another glass, which forms the cladding.

The reason the ingredients have to be so pure, is that any impurities cut down the transmission properties of the glass. Looking at an ordinary glass shelf edge on, shows the glass to be green in colour; an optical fibre exhibiting similar properties would be useless as a transmission medium. An optical fibre has to appear as transparent as an open window, yet is equivalent to a pane of glass about a mile in thickness. To achieve this, the basic chemicals have to be purified to an extraordinary high level, and must only contain a total metal impurity of a few parts in a thousand million!

The glass rod so formed (called the preform) is then reheated until plastic, and carefully drawn into a fibre of a thickness which is comparable to that of a human hair. The fibre is protected by applying a silicone resin and polypropylene, which adds mechanical strength. A number of these conductors are then positioned around a steel strength member, and sheathed in polythene. Fibres of this type are now being manufacturered by British Telecom licencees, both in this country and abroad. GEC will shortly be producing fibres for the telephone network in this country, and Erricson likewise in Sweden.

The alternative method of production, which makes fibres of a different type, is called the Chemical Vapour Deposition method, and relies upon a glass-like layer (usually a phosphosilicate) being deposited on the inside of a quartz tube. After such a layer has been deposited, the tube is heated strongly, whilst it is rotated in a special lathe. This has the effect of collapsing the walls of the tube, resulting in the formation of a solid glass rod, which can then be reheated and drawn into a fibre, consisting of a narrow core—the deposited layer—surrounded by the cladding—the quartz tube. Again, British Telecom have a development programme for this type of fibre, and volume production is being carried out in this country by such companies as STC and GEC.

BICC and Pirelli also have small development production of fibres of this type, which will in all probability expand in the not too distant future when the demand justifies. Pilkington Ltd has two production sites producing fibres called "Hytran". One method is a modification of the double crucible, the other is by a process called "phase separable" glass.

LIGHT SOURCE

All the signals carried along optical fibres are in the form of light waves in the infra red part of the electromagnetic spectrum. These can be generated either by using a miniature laser or by using a light emitting diode. The high radiance l.e.d. is unfortunately restricted to low bandwidth short distance operations. By low bandwidth we mean a data rate of about 35Mbit/s. The alternative approach is to use a Gallium Arsenide laser which has a higher output, and is more suitable for operation over longer distances. It also has the ability to handle much higher data rate which are typically 140Mbit/s. Unfortunately, these tiny lasers are expensive (about £500 each), but it is confidently predicted that the price will dramatically fall in the future.

On the other end of the optical fibre, we have the light detector, which can be either a PIN diode or an avalanche diode. Unfortunately, the received infra red signal is very low (often less than 100nW), and it is important that the detector gathers most of the received power, and efficiently converts it. The silicon PIN diode meets these criteria at an economic cost. The alternative use of the avalanche photodiode provides a higher sensitivity than the PIN diode, but is only superior at higher data rates above 1Mbit/s.

WHEN?

We already use, albeit in a limited way, fibre optic systems for the transmission of telephone conversations. By the end of 1977, several of the British interested parties had demonstrated the feasibility of optical fibres in operating systems, and the Post Office had run its systems operating at both 8Mbit/s and 140Mbit/s. After the initial demonstration systems, it was found necessary to follow these up with production systems. The main reasons for this was for the Post Office to gain manufacturing and installation and operational experience.

In practice, 18 possible routes were chosen, and put out to tender. In April 1979 orders were placed to the value of £6M for a total of 34 systems on 15 routes located throughout the British Isles. The total length of the routes is 450km, giving a total fibre requirement of 3,600km. Thus orders have been awarded to STC, GEC and Plessey for the supply and installation of optical fibre transmission systems—both cables and equipment—for the expansion of the telecommunications network.

Optical fibre receivers, transmitters, l.e.d.s and avalanche photodiodes (*Pilkington Ltd*).

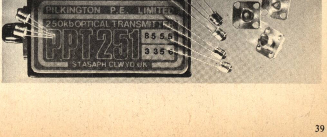

TRANSMISSION SYSTEMS

The transmission system is categorised by the data transmission rate, which can be 2–8–34–140Mbit/s. These, with the exception of 2Mbit/s, will all be used in the digital network being developed by British Telecom, and together with the system exchanges, lead to the Integrated Services Digital Network. The 140Mbit/s (equivalent to 1,920 telephone channels) systems will be used in the trunk network. The typical route length will be 60km and will require repeaters located at 8km intervals. Six systems will be used on three routes.

The 34Mbit/s (equivalent to 480 telephone channels) will also be used in the trunk network. In this case the repeater spacings need only be at 10–11km spacings. Four systems of this type have been ordered for installation on two routes.

The 8Mbit/s (equivalent to 120 telephone channels) will be used for both the trunk and junction networks. In the former, the route length is typically 50km ("long haul") and for the latter the lengths are typically 10–20km. In all, 24 short haul systems of this type will be installed on nine routes. Because of their shorter lengths, they are usually located in urban areas. In practice, only a few of the systems will require repeaters, but where required, these will be housed in surface buildings with spacings of up to 12km.

STC and Plessey each intend to complete at least on 8Mbit/s by this time (Croydon—Vauxhall and Brownhills—Walsall, respectively). In addition, GEC expects to install part of a 140Mbit/s route (Chiswick—Faraday). The remaining systems will follow over the next two years, with all of them becoming operational by Autumn 1982. In addition to these inland routes, a 5 nautical mile loop of optical cable will be laid by a cableship in Lough Fyne. Later, two repeaters will be inserted, to provide an operational submarine system.

THE FUTURE?

In the immediate future, it is anticipated that optical fibres will be used extensively in the trunk (or main) network, as opposed to the junction or local networks. The use of optical fibre in the trunk network offers an economic alternative to coaxial cables currently in use.

Unfortunately, the situation is somewhat different when one considers the junction network, as the use of pulse code modulation on existing systems reduces the economic advantages of optical fibres. What is certain, however, is that the cost of fibres will ultimately fall and thus encourage their use and adoption in this network. With the local network, ultimately the use of optical fibre will permit the transmission of television, and to this end, British Telecom are actively considering its introduction—a pilot scheme is under way in Milton Keynes.

The use of fibre optical systems in submarine cables could certainly offer some benefits over the existing system. These benefits include dramatic cost savings (some sources quote a reduction of 75 per cent), smaller physical size (with corresponding comparative ease of handling), and of course, longer distances between repeaters, further reducing installation costs, and ultimately providing higher reliability.

Although the use of optical fibres for this application is some way off, there are many other lines of development taking place, which will enable cheaper fibre with lower signal attenuation to be manufactured reliably. The transmitters and receivers will be fabricated in a single chip, rather than from discrete components as at present.

Potentially, these developments could transform the cost effectiveness and practical application of optical fibres over a period of a few years. The prospect for optical fibre is that it could carry the programmes of all eleven Television Companies broadcasting in the UK, and future developments such as 3D television, videophones, personal computers all *down a single fibre!*

However, this *is* some way in the future, but nevertheless implications on how the new technology will ultimately change our lives are well established. All that remains is for these systems to be introduced on a national basis. Let the light shine on. ★

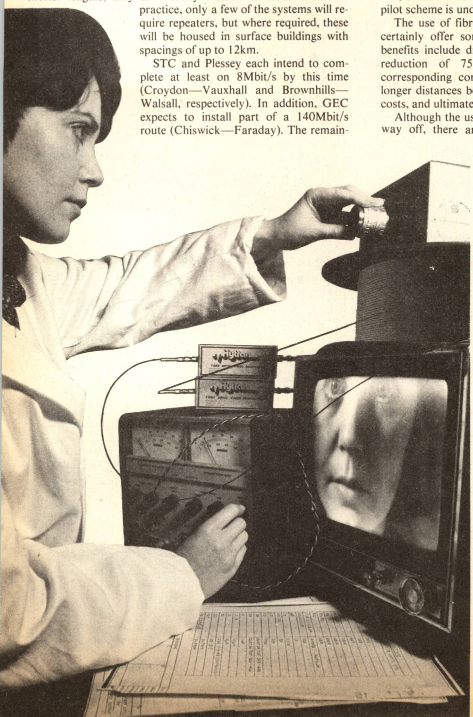

A video camera connected via a fibre optic link to a monitor. The reel holding the fibre optic element and the modems can be clearly seen. (*Pilkington Ltd.*)

THE PRINTER YOU THOUGHT YOU COULDN'T AFFORD....

FREE
2000 sheets
Tractor Paper
VALUE £20 inc VAT

The SEIKOSHA GP80 - 80 column impact matrix printer

£199*

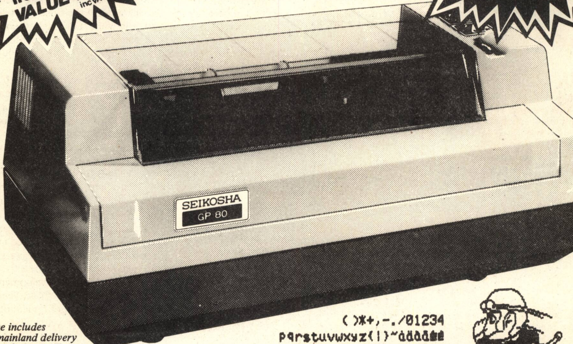

**price includes UK mainland delivery but excludes VAT.*

Standard Centronics interface makes it ideal for most hobby Micro's

```
( )*+,-./01234
pqrstuvwxyz{|}~äääää
ABCDEFGHIJKLMNOPQRSTL
öōÜüùū¥£¢$↑↓←→ !"#$%&
bcdefghijklmnopqrstuv
```

Printout sample of GP80

The GP-80 is a revolutionary new graphic printer with a difference, not only does it have an amazingly low price, but unlike its competitors the GP-80 uses a unique 'Uni-hammer' system and with a name like Seikosha behind it you can be sure of its quality, reliability and precision construction. The GP-80 is an ideal printer for your system or VDU, and it produces a top quality printout.*

*If you would like a GP-80, complete the order form or telephone today. (*part of the Seiko Watch Company).*

Allow 14 days delivery, subject to availability, full refund if goods returned within 14 days.

- ★ PRINT METHOD - Impact Dot Matrix
- ★ CHARACTER MATRIX - 5 x 7 Dot Matrix
- ★ CHARACTER SET - 128 characters
- ★ CHARACTER CODE - ASCII
- ★ PRINT SPEED - 30 characters/second
- ★ CHARACTERS/LINE - 80 or extended chs.
- ★ CHARACTERS/INCH - 12
- ★ LINES/INCH - 6 (9 for graphics)
- ★ LINES/SECOND - 5 (7.5 for graphics)
- ★ PAPER FEED - Pin Feed
- ★ PAPER/WIDTH - Up to 8" plain paper
- ★ COPIES - 3
- ★ RIBBON - Inkroller built in cassette type (1 colour)
- ★ POWER SUPPLY - 100/117/220 ± 10% 50/60 Hz
- ★ POWER CONSUMPTION - 15W(print) 5W (idling)
- ★ DIMENSIONS - 17.25 d x 32.8 w x 13.2 h cms
- ★ WEIGHT - 2.5 kg (5½ lb.)
- ★ NOISE LEVEL - Under 60 phon
- ★ INTERFACES - Centronics fitted as standard
- ★ WARRANTY – 12 months

Dealer Enquiries Welcome

Micro Peripherals

61 New Market Square,
Basingstoke, Hampshire.
RG21 1HW

Telephone: 0256 56468
(4 lines)

Telex: 858575

Seiko appointed importer and distributor

Order to: MICRO PERIPHERALS, 61 New Market Square,
Basingstoke, Hampshire RG21 1HW

Please supply:

Quantity	Description	Unit Price		Total
....	GP-80 Printer	£228.85	includes 15% VAT and P&P	....

I enclose my cheque/PO or debit my Access/Visa account £ ________

Access/Visa Account No. ....

Signed..

Name (please print)..

Address...

.... PE7

Semiconductor UPDATE...

FEATURING iAPX 432 U410B

R.W. Coles

THE SHAPE OF THINGS TO COME . . .

No doubt people who read this column regularly have become numbed by the endless stream of new microprocessor wonder-chips I keep raving on about. It wouldn't surprise me, I have become numbed myself by the relentless, almost boring, march of microprocessor technology towards the ever bigger ever faster and ever more capable digital processor. Well, relentless progress is one thing and a quantum jump is quite another, and this month I am glad to report a spectacular quantum jump in microprocessor technology, from Intel, who else?

The name tag "microprocessor" is rather inadequate to describe this new concept in silicon. Intel themselves call it a "micro-mainframe", and they aren't joking or shooting a line—the iAPX 432 will outperform many familiar mainframe processors such as the IBM 370—but it's not just a super souped up 8080, it's a whole new concept in digital processing on silicon which bears little relation to any of its microprocessor antecedents.

Yes, it's a 32-bit processor alright, and it has the party tricks you might expect. 32-bit integer multiply in 6·25 microseconds, 80 bit floating point multiply in 26·125 microseconds, address range of 2^{32} (over 4 billion bytes!), an 8 Megahertz clock rate, etc., etc. Amazing enough in themselves but they're not the most important features of the iAPX 432.

ADA

The new processor has been designed with the computer programmer and high level languages firmly in mind. No more electronics engineers with logic analysers trying to discover what is wrong with the software, no more tortuous assembly language programs, this machine will *always* be programmed in a high level language with all the increased programmer productivity that that brings, even for high speed "real-time" applications. If, for you, "high level language" means BASIC, forget it. The language to learn for the future is ADA, sponsored by the American Department of Defense and designed to incorporate all the best features of PASCAL but with enhancements to suit it for the real time applications which have traditionally had to be programmed in assembler.

ADA was developed quite separately to the iAPX 432, but the new processor grew from the same body of experience and academic research and it fits the new language exactly, to the extent that many ADA statements compile directly into 432 instructions. Even system programmers will use ADA, and recourse to assembly language will rarely, if ever, be needed.

The new processor was also designed from the start for multi-tasking and multi-processor operation. Extra processing power can be added to a 432 system in the form of "attached processors" and, even better, the presence or absence of these extra processors can be transparent to the programmer!

Finally, the 432 has extensive hardware checking facilities to detect any software errors (such as trying to access instructions as data) which manage to slip through the formidable checking process already carried out by an ADA compiler.

Descending from those dizzy heights to good old fashioned hardware, the iAPX 432 is actually a three chip set of unprecedented complexity. Two of the chips, the iAPX 43201 and the iAPX 43202, act as the CPU or "General Data Processor (GDP)" as Intel call it. Together these chips house no fewer than 160,000 separate transistors, and they each have so many interconnections that a special 64-pin QUIP (Quad Inline Package) has had to be designed for them. The third device, the iAPX 43203, is called an "Interface Processor (IP)" and is used as a post-box for all GDP peripheral data transfers to attached processors, bulk storage devices, high speed printers and so on. There can be several 43203s in a system.

Believe it or not the GDP pair dissipates less than 5 watts and all three devices will run from a single 5 volt supply. With this sort of power just around the corner, the home computers of today will soon appear to be as quaint as the cats whisker wireless!

DIDDY AMP

Being an electronics person of great antiquity, the term "audio-amplifier" still stirs within me memories of the marvellous Mullard 5-10 and the other warm and glowing "bottle-jobs" of my youth. All you newcomers to the gentle art of audio amplification have missed the best bit without a doubt, because now all you need to perform this trifling function is a tiny square of plastic with eight puny legs, like the U410B from AEG-TELEFUNKEN, a "diddy-amp" if ever I saw one. Within this ridiculously inexpensive mini-dip package lives an amplifier which has a 40dB closed loop gain and a 1W maximum output power. You would normally use these uninteresting objects in, say, toys, doorbells, CB radios, intercoms and so on, where you would be well advised to keep the power down to a quite adequate 50mW, because at this level the total harmonic distortion reaches 1 per cent. A companion device, the U411B, does the same job but condescendingly allows you to alter the gain by means of a single external resistor.

They're good—but they'll *never* replace the 5-10!

LED WARNING

Perhaps as a response to the Three Mile Island "incident", Siemens have produced a novel variation on the theme of seven segment l.e.d. numerical displays. When all is peaceful with the reactor, those in the control room will be reassured by rows of *green* numbers, indicating coolant temperature, reactor flux, and knocking-off time etc. If things start to get a bit hairy, those reassuring green digits will turn to a panic stricken *red* colour, and all concerned will be quickly informed of the impending melt-down so that they can finish the crossword or wave their colleagues goodbye or something.

"It can't be serious . . . the display's still green!"

The quick change act is made possible by constructing each segment from two l.e.d. chips of different colours wired in anti-parallel. When an external circuit senses that a reading is becoming dangerous, a quick change of drive polarity is all that's required to scare the hell out of everyone in eyeshot.

I don't have a part number for these saviours of the world, but they are part of the Siemens HD series of 10mm digits, and they could no doubt be used in many less worrying circumstances.

CIRCUITS SUPPLEMENT

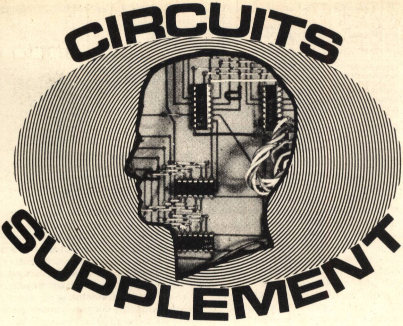

A selection of readers' original circuit ideas.

Why not submit *your* idea? Any idea published will be awarded payment according to its merits.

Each idea submitted must be accompanied by a declaration to the effect that it has been tried and tested, is the original work of the undersigned, and that it has not been offered or accepted for publication elsewhere. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

COMPUTER CASSETTE MOTOR CONTROL

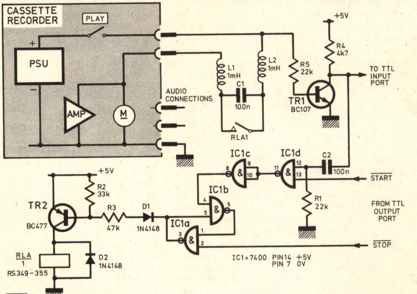

EP539

THE circuit shown is a motor control system for an unmodified domestic cassette recorder, as commonly used for program and data storage with a small computer. It is necessary for the computer to be able to start and stop the cassette motor as required. This is achieved with control pulses, taken from two spare bits of an output port. One bit, when strobed low, will stop the motor, the other will start it, provided that the 'Play' switch on the cassette recorder is depressed. The computer can optionally sense the status of this switch on a one bit input port, thus providing for helpful messages to the operator, such as 'Press play on the cassette recorder'. This input can also be used to commence the timing for a record operation, insuring that the data is not written when the tape is stationary.

The circuit also overcomes the annoying disadvantage inherent in most systems, whereby it is not possible to rewind a tape without some unplugging, because the motor does not start when the buttons are pressed.

IC1a and IC1b form a bistable, whose output is connected via TR2 to the reed relay RL1. The relay interrupts the motor current via the socket provided on most cassette recorders. L1 and L2 are small chokes incorporated to reduce the current surges near computer circuitry, but they could be omitted for simplicity. R1 and C2 detect switch closures, and automatically start the motor, unless the computer is permanently holding $\overline{\text{STOP}}$ low, thus overriding the operator's control. Should a cassette recorder not be wired as shown, it obviously does no harm to change the recorder's internal wiring for this system.

D. Greaves,
Romsey,
Hants.

ELECTRONIC AIR FRESHENER

YOU have no doubt noticed how muggy the air is before a storm and how fresh it can be when the storm is over, even if the temperature has not changed. Have you ever wondered what caused the difference? No, not humidity, but the balance between two types of charged particles in the air; charges due to the electrical discharges we call lightning. These particles are called ions, and come in two versions, positive and negative. When the balance between these two is not equalised, the air can feel heavy and humid, or fresh and light. With an excess of positive ions the air is oppressive; with an excess of negative ions it is invigorating. This same effect causes the difference between vitality-lowering jungle air, and invigorating Swiss mountain air. No one as yet can explain why we are effected in this way, but negative ions have been used experimentally with great temporary success to treat disorders such as asthma.

Your first step is to cut an aluminium cover for the machine and bend it as shown in the diagram. Drill three holes on each side to screw it to the wooden base. Now screw the ignition coil to the base so that it is central. If you intend to mount the dimmer on the base as I did it will be necessary to mount the coil at a third the distance from one edge to allow for the box. However, it would probably be neater to mount your control on the wall direct.

Now wire up according to the circuit. If you have the dimmer on the wall, connect the combination to a terminal block on the base board to anchor the wires as shown.

Now make a wick of wire wool and insert into the h.t. outlet at the top of the coil. Put on the aluminium cover you have made, connecting it to earth, and screw it down. You have now completed the working end of the negative ion generator.

A useful addition, for the sake of safety, is to fix a piece of zinc gauze across the top and bottom of the cover to allow free access of air, but which will keep inquisitive fingers away.

Now wire your terminal block to the light dimmer and switch on. If the dimmer has no mains switch, you will need to add one, but most now incorporate their own on/off switch. However, an extra switch in the line will add to safety as only you will now be able to switch the device on.

Having switched on you will be able to hear a high voltage discharge coming from the ignition coil. Now turn the dimmer *up* slowly till this discharge just ceases, and the air in your room will become like the Swiss Alps.

To understand the operation it is enough to know that a light dimmer contains a triac which is switched on part the way through each half cycle of the mains. The earlier during each half cycle it is switched on the more power it will pass.

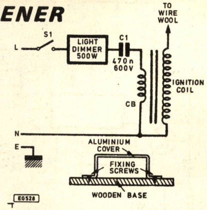

The capacitor in our circuit passes this rapid switching charge through to the ignition coil at 100 times per second for 50Hz mains, rather like the contact breaker on the car opening 100 times per second, while at the same time isolating the mains from being directly connected to the ignition coil. Therefore 100 high voltage pulses are produced per second, the amplitude of which are controlled by the dimmer setting.

To convert this high voltage to negative ions, a silent discharge of electrons is required from a pointed object. I first tried a bunch of needles, but later found that wire wool provided thousands of minute sharp points for the purpose.

Michael Farrington
Tunbridge Wells,
Kent.

SNAP

THIS simple 'Snap' circuit is built around one 7400 (Quad NAND) which makes it very simple and cheap to build. The first two gates are in an R.S. flip-flop configuration, but both their outputs are held at '1' by connecting both switched inputs to '0'.

As soon as one of the switches is thrown then the gate has two '1' inputs and so gives a '0' output, which is put into the other gate, and thus prevents it from giving anything but a '1' output. Thus, while the switch is held the other switch cannot affect the state of the flip-flop. When the first switch is set back to '0', then the circuit is reset to its original stable state. The two other NAND gates are wired to invert the outputs from the flip-flop. Thus, when the switches are at '0' the l.e.d.s are not lit, but the appropriate l.e.d. is lit by the first switch to be set at '1'.

If s.p.d.t. push-to-make switches are used then the circuit will provide a sensitive 'who pushed first' snap indicator which resets itself when both buttons are released.

J. Hobson,
Minister,
Sheppey,
Kent.

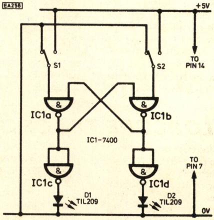

BURGLAR ALARM

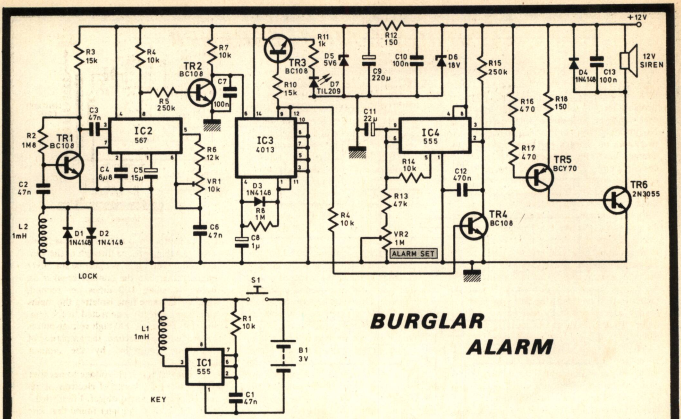

THIS consists of an astable multivibrator used as a key, and a lock circuit. This operates at a frequency of 3·2kHz and uses a 1mH choke as the load which acts as a primary of a transformer, when brought into close proximity to the lock.

The lock uses a r.f.c. (which has two diodes to prevent large voltages being induced onto it) to act as the secondary of a transformer picking up impulses from the key. These are amplified via TR1 to a large enough level to operate IC1, which is a phase locked loop tone decoder. The decoder output at pin 8 is high until the correct frequency is introduced to the i.c. This frequency is set by C6 and VR1 and R8 and adjusted to match the frequency of the key.

The output from the NE567 is buffered and inverted by TR2, the collector of which operates one half of a CD4013, which is wired as a monostable and used to make sure only one operation of the NE567 at a time is accepted before switching the other half of the CD4013 which is connected as a bistable.

The Q output of the bistable switches TR3 which lights the l.e.d. indicates when the lock has been operated to arm the alarm.

The alarm function uses a NE555 timer as a voltage sensing device. The trigger on pin 2 of the i.c. sets the internal RS bistable when the voltage across C12 is low before it is charged via R15. A voltage is tapped off pin 5 (the control voltage pin) and fed to the threshold pin 6 via a voltage divider. When the supply voltage falls due to an instantaneous drain on the battery (operation of the lights or courtesy light etc.) the voltage at pin 5 falls as well. If this level drops below the threshold voltage which is held there via C11, then the output resets and falls to a low state and stays there.

When this happens IC4 output switches on TR5 allowing TR6 to switch on and operate the siren. The internal bistable of the NE555 is not set if the Q output of the CD4013 bistable is high. If it is low, then the alarm is armed and TR4 is off and allows C12 to charge.

A stabilised supply is needed for the NE567 and CD4013 and is derived via R12 and D5 giving 5·1V. To suppress transients arriving from the car electrics a 18V. Zener and a 0·1μ capacitor are connected across the supply.

Peter Robinson
Tyldesley,
Manchester.

OSCILLOSCOPE TRACE DOUBLER

MOST designs for trace doublers work on the principle of switching, at some preset frequency, between two or more inputs and applying a d.c. level shift to separate the traces. This chopped effect can be most annoying especially when viewing digital waveforms. This circuit switches between inputs midway along each sweep and has the advantage that d.c. levels between inputs can be instantly compared.

The sweep or X output of the oscilloscope is applied to VR1 so that the input level can be adjusted to centralise the switching point. IC1 is arranged as a voltage comparator such that when the input voltage from VR1 exceeds the value set on the +ve input by R1 and R2 then the output goes low. This output is applied to the control input of IC2 which is a triple two input analogue gate.

The first half of the trace therefore contains information from input 1 and the second half from input 2. Pin 7 of IC2 is taken to a -ve supply in order to accommodate negative input signals.

R. Macfarlane,
Aberdeen,
Scotland.

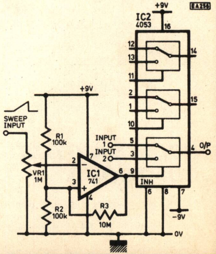

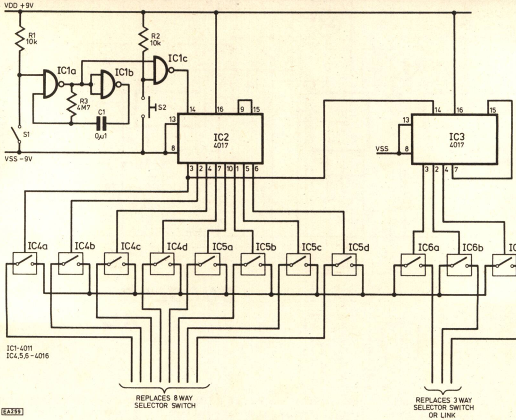

RANDOM TUNE SELECTOR UNIT

THIS simple add-on device converts these 24 tune doorbells to give a random selected tune each time the doorbell is pressed. The tune selection switches are replaced with CMOS switches.

In the random tune select mode S1 open circuit, the oscillator IC1 a,b continuously clocks the decade counters through the 24 switch positions. When the doorbell is pressed a tune is selected and plays through, regardless of the following changes in switch positions.

To select a particular tune S1 is closed and S2 pressed to clock through the decade counters until the desired tune is found.

The unit shares the doorbell's 18V power supply. This is the maximum voltage recommended for CMOS devices. The prototype worked on this, but some diodes in series with the supply lines could be used to reduce the supply to about 15V.

J.R. Scarborough,
Skellingthorpe,
Lincoln.

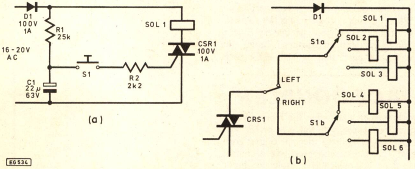

(a)

(b)

POINTS MOTOR CONTROL

THIS circuit was designed as a points motor control for use in model railway layouts. Normally 16–20V a.c. are applied directly to a coil, the resultant magnetic field attracting a solenoid with a brass pin attached to it. The brass pin in turn fits directly into the operating mechanism of the railway points. The disadvantage of such a simple system is that the solenoid may be burnt out if power is applied for too long, e.g. in the hands of a youngster.

Capacitor C1 charges via R1 from the half wave rectified output of D1. When switch S1 is closed, the voltage present on C1 is sufficient to fire thyristor CSR1. Resistor R2 limits the gate current to somewhere in the region 7–10mA. The thyristor now conducts and operates the points motor. Because C1 is now discharged and R1 is too large to maintain an adequate level of gate current, the thyristor will turn off when the half wave rectified voltage waveform falls to zero, thus preventing any excess current flowing through the coil, even if S1 is kept closed.

By suitable switching, the output of the unit can be routed to various parts of the model layout.

The unit should be fed from an a.c. source in order for the thyristor to turn off. A single pole two way switch is used to select left or right, then the appropriate points are selected on a 2 pole multiway rotary switch (maximum twelve ways with two single pole, twelve way wafers) and S1 is activated.

T. J. S. Mowat,
Kincardine o'Neil,
Aberdeenshire.

FREEZER ALARM

THE unit was designed for low cost of construction and to be unobtrustive when in use. Current consumption in the quiescent state is around 0·5 mA.

The temperature sensor is a rod thermistor whose resistance at −25°C is around 14k. Perhaps a bead type would be more sensitive (and more expensive) but hysteresis introduced by the relatively large thermal inertia of the rod allows the freezer to be open for several minutes for loading without triggering the alarm.

Super alpha pair, TR1 and TR2 provide a sharp trigger for IC1a. IC1a and 1b form a gated astable with a duty cycle between 2 and 4 seconds. The output pulses of IC1a and 1b gate a second astable formed by IC1c and 1d. This astable generates a pulsed output of several hundred hertz.

TR3 is driven via a 10k resistor by the output from IC1. The transducer is a telephone earpiece which is just as effective but much cheaper than a miniature loudspeaker.

The thermistor is located at the top of the freezing compartment and left to cool for an hour. VR1 is then adjusted so that the alarm is triggered by heat from a finger on TH1 for about 10 seconds.

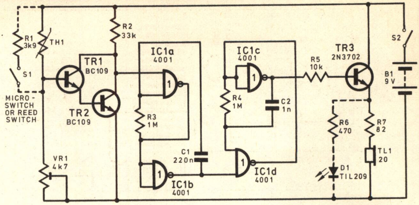

EG536

If the freezer is in a remote location such as a garage the transducer may be connected by twin flex to the house. The alarm unit should be located beside the freezer.

A burglar alarm facility (dashed) can be added by wiring a microswitch or magnet operated reed switch in parallel with the thermistor. This switch closes when the freezer top is opened.

The on/off switch is a shorting plug which is removed when the freezer is being defrosted. The plug is mounted on the top of the case to give a clear visual indication that the alarm is disabled. The plug would also be removed before loading or unloading when the freezer is located outside the house.

R. Mackay,
Grangemouth,
Scotland.

DIGITAL POTENTIOMETER

IT is useful on many occasions to be able to feed a value set on a variable resistor into a microcomputer. Examples of this include cursor and graphics control, games, servo position, and even speed control. The easiest way to do this is to feed a voltage output from the resistor to an A to D converter; but this does tend to be expensive if 8 bit resolution is required. The circuit presented here achieves 8 bit accuracy from 100k potentiometer at not very much cost.

Capacitor C1 charges up via VR1 until the threshold of the 3140 is reached. Obviously the setting of VR1 will influence the charge up time. The output of the 3140 changes and in so doing loads the two four bit latches, IC3 and 4, with the current count value on the outputs of IC5 (a 14 bit counter). This latched value will vary between 1 and 255 using the values shown, over the sweep of the potentiometer. The counter continues until Q9 goes high, corresponding to a count of 256. The output from pin 8 of the Schmitt trigger goes high very quickly after, resetting the counter and discharging C1 by means of the transistor. As the counter resets Q9 goes low, and capacitor C2 starts to charge slowly, until the threshold of the Schmitt is reached releasing the counter and stopping the discharge. This delay is necessary to ensure C1 has plenty of time to discharge. The main oscillator should be adjusted to give a count of 255 with the potentiometer fully open, this corresponds to 107kHz.

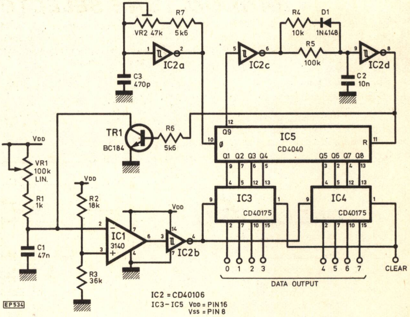

The data is continuously available at the latch outputs. If some form of Read/Clear is required the clear line should be connected to the processor port, otherwise it should be pulled up.

I. C. Lare,
Northwich,
Cheshire.

DELAYED SWITCH ON FOR SPEAKERS

THIS circuit connects the loudspeaker to a power amplifier a few seconds after the amplifier is switched on, thereby avoiding turn on 'thumps' and possible damage to the speaker.

When the power is switched off, the speaker will be disconnected when the rail voltage falls by about 30%; the time taken depending on whether the amplifier is handling a signal. This disconnection protects the speaker from the d.c. offsets at the output, and oscillations that occur in many power amplifiers a few moments after being switched off.

If the amplifiers form part of a large system driven at high levels, and a power failure occurs, then the speakers will be disconnected very rapidly. Even if the power is immediately reinstated, the connection of the speakers will be delayed, thus turn on 'thumps' from preamps, mixing desks, crossovers, etc, will cause no damage.

D1 sets up a reference voltage at pin 2 on the comparator (IC1). At the moment of turn on, the voltage at pin 3 is zero and the output voltage swings negative, hence TR1 and RLA remain off. C1 charges via R1 and when the voltage on pin 3 of IC1 exceeds the reference, the output (pin 7) swings positive, turns on TR2, which in turn connects the RLA and the speaker. When the power is disconnected, the supply rail falls rapidly (provided a speaker is being driven) and the relay will 'drop out' naturally when the supply rail falls to a fraction of its nominal value. In addition, C1 discharges via R2 and when the voltage on pin 3 of IC1 falls to some 70% of its original value, the comparator output will swing negative and turn off TR1, hence RLA and the speaker.

The voltage on pin 2 of IC1 is normally some 70% of that on pin 3 to allow for variations in the rail voltage which occur in the unstabilised power supplies common to all high quality audio power amplifiers.

Ben Duncan,
Tattershall,
Lincoln.

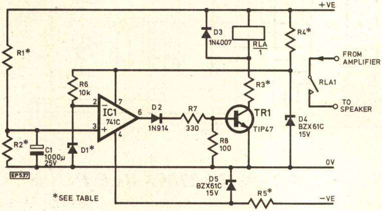

Power	Max. voltage	R1	R2	R3	R4	R5	RLA.	D1 (All BZX85 or BZX61c)
17w into 8Ω 35w into 4Ω	24V	10K	2K	Link across	47OR	1K2	24V	3V3
40w into 8Ω 80w into 4Ω	35V	10K	1K5	1 watt 220R	1 watt 1K	2K7	24V	3V3
80w into 8Ω 150w into 4Ω	47V	10K	1K	Link across	1 watt 1K6	4K3	48V	3V6
150w into 8Ω 250w into 4Ω	63V	1 watt 10K	1K	1 watt 560R	2 watt 2K2	1 watt 6K8	48V	4V7
250w into 8Ω 500w into 4Ω	85V	1 watt 10K	1K	2 watt 1K5	4 watt 3K3	1 watt 10K	48V	6V2

All Resistors $\frac{1}{2}$ watt unless otherwise indicated.

CABLE TESTER

A healthy cable is indicated by both green LEDs being lit and the red one extinguished. To give this indication, the voltages along the chain of LEDs must descend so that $Va > Vb$, $Vb \geqslant Vc$, and $Vc > Vd$. These voltages can only be maintained by currents flowing along each conductor as shown. Any single open or short circuit on the cable extinguishes one or both of the green LEDs. Multiple faults can result in the red LED paralleling the green ones and taking current from them.

J. A. Percival,
Clowne,
Derbyshire.

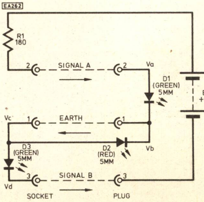

LEDS SHOULD BE OF THE SAME TYPE AND MANUFACTURE

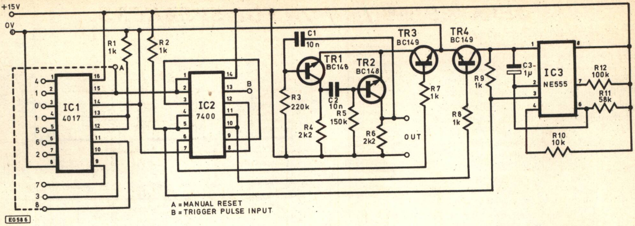

PROGRAMMABLE PULSE GENERATOR

THIS circuit describes a device which creates a series of audible signals each of which is about 0·25 second long with a gap of about the same length between each. It was originally designed to identify a number of remote sensors. Each remote would contain one of these circuits and be connected to a small radio transmitter. When triggered it would emit a specific number of 'bleeps' and then reset itself to await the next trigger. The idea being that each remote sensor would transmit a different number of 'bleeps' and so the master on receiving the signals would be able to identify which remote was triggered.

Pins 8–13 of IC2 are wired up to create a latch, when a trigger pulse is detected at pin 13 (B), a trigger pulse being logic 0, pins 10 and 11 go high and via TR4 an oscillator IC3, operating at approximately 4Hz, is switched on providing a clock pulse for IC1. Pins 1–11 of IC1 provide outputs which are normally low and go high when the corresponding number of pulses is provided at the clock input, e.g., when five pulses are sent to the clock input, output 5 (pin 5) will go high. When a clock pulse is provided by IC3 and sent to the clock input of IC1 it is also sent through an inverter, produced by pins 4, 5 and 6 on IC2. The output of the inverter (pin 6) is used to switch on and off an audio oscillator via TR3. The audio oscillator is produced by TR1 and TR2, and is a simple multivibrator. An output can be taken from both sides of R6 and can drive a small high impedance crystal transducer. This output is the final output and it is here that I connected the transmitter mentioned earlier. Every time the clock oscillator goes low a 'beep' will be heard in the transducer. The programmable part is achieved by creating a direct link from one of the numbered outputs to the reset pin (pin 15) on IC1 thus when a wire is connected as shown by the dotted line eight 'beeps' will be heard and then the circuit will reset itself. As the latch requires a low reset the pulse is first sent through an inverter produced by pins 1, 2 and 3 of IC2.

Other uses for this circuit could include an automatic telephone dialler or a simple remote control system. The number of 'beeps' can be increased by an indefinite degree by connecting another 4017 counter into the circuit. To do this simply disconnect pin 12 on the existing counter, from the resistor R1 and take it to the clock input (pin 14) on the next counter, all other pins should be connected as they are on the first counter; the output pins on counter two can then be checked to see how many pulses they produce.

J. Chalmers,
East Grinstead,
West Sussex.

VARIABLE LIGHT FLASHER

THIS circuit is for a simple light flasher that is for both domestic and disco use. It is built around a TTL SN7414N hex inverter Schmitt used as an oscillator. To obtain full lamp brilliance a triac is used, rather than a thyristor, and is driven by a BFY50 transistor. The output of the power supply is about 9V which is dropped to 5·1V, for the i.c., using a Zener diode.

The range of frequencies that the lamp will flash over is determined by C1, VR1 and R1. The formula for calculating the frequency is $f = 1/(R_1 + VR_1)C_1$ where f is in hertz, C is in farads, R is in ohms.

With the values shown in the diagram the lamp flashes about once every second to about 45 times a second. The lamp load that the circuit will drive is determined by the handling capability of the triac.

K. Badcock,
Kettering,
Northants.

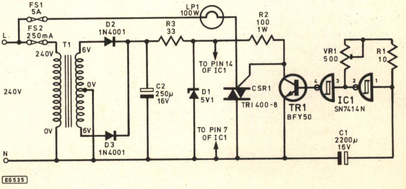

ELAPSED TIME METER

THE meter is connected across the mains supply to the device being timed, after any on/off switch or thermostat.

Because the display is only activated when a reading is required, and is not multiplexed, the circuit shows very little current consumed when counting, and a negligible amount on standby. It will run for at least a year on one PP3 battery.

The operation is as follows: when the device being timed is operating, 50Hz pulses are fed from T1 through D37 into IC1. The pulse level is limited to 9V by D38. IC1 is gated by IC2 to divide by 1800. The output of IC2 is stretched by R17 and C1 and clocks IC3a as well as resetting IC1. IC3a gives an output pulse every 0·1 hour, and these pulses are counted by IC3b and IC4, the count being displayed in BCD format when S1 is pressed.

The display l.e.d.s are shunted by diodes, and have other diodes in series, to prevent reverse voltages being applied to the l.e.d.s. The display brightness is kept low to enable the l.e.d.s to be driven directly by the 4518 ICs, and to reduce battery drain.

S2 resets the counters, and D40/D41 ensure that the output pulse from IC2 only resets IC1.

The counter gives a maximum count of 99·9 hours. If a larger count is required, a 4017 could be inserted between IC1 and IC3a, the latter being used for the first (tenths) display. The maximum count will then be 999·9 hours.

A. M. Tucker,
Charminster,
Dorchester.

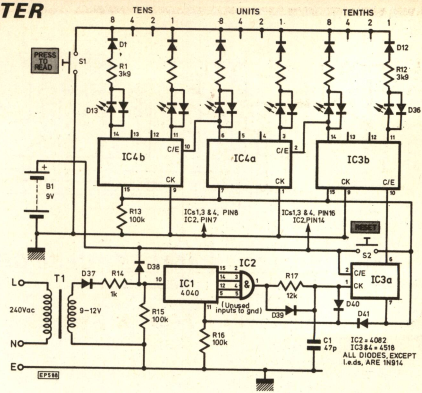

HEXADECIMAL DISPLAY UNIT

THIS circuit decodes a 4-bit binary number and displays the appropriate hexadecimal character (0–F) on a 7-segment display.

The diode matrix would normally use 78 diodes in a conventional system but this has been reduced to 34 by using diodes in the matrix to stop segments lighting. All segments light otherwise.

Two 7442s are used to produce a 1 to 16 output from the binary input because the 74154 could not pull the segment driver inputs low enough through the diode matrix.

The use of 7400s to drive the display allowed the unused input to be used for display blanking.

J. K. Semple,
Plaxted,
Kent.

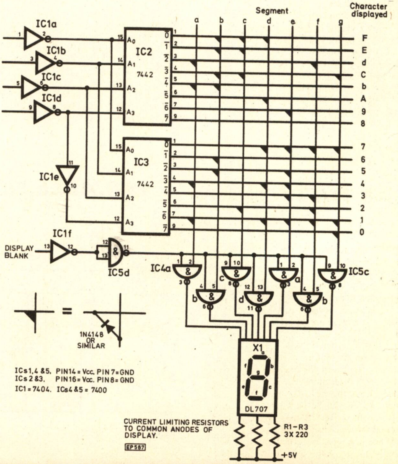
Segment
a b c d e f g
Character displayed
F E d C b A 9 8 7 6 5 4 3 2 1 0
IC1a
IC1b
IC1c
IC1d
IC1e
IC1f
IC2 7442
IC3 7442
A0 A1 A2 A3
DISPLAY BLANK
IC5d
IC4a
IC5c
1N4148 OR SIMILAR
ICs1,4 &5, PIN14 = Vcc, PIN 7 = GND
ICs 2 &3, PIN16 = Vcc, PIN 8 = GND
IC1 = 7404, ICs4 &5 = 7400
X1
DL707
CURRENT LIMITING RESISTORS TO COMMON ANODES OF DISPLAY.
R1–R3 3X 220
+5V
EP587

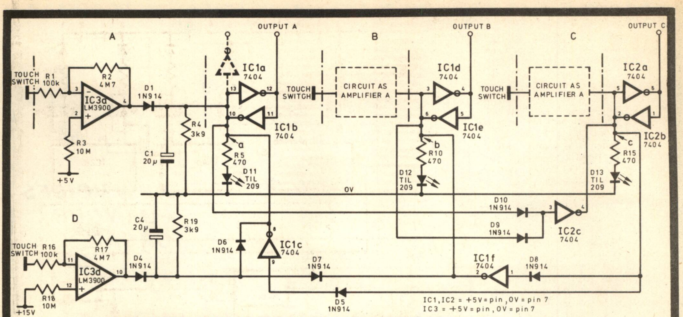

EG572

MULTI-WAY TOUCH SWITCH

THIS circuit has been developed to eliminate the possibility of activating the wrong combination of switches. Switch C can never be switched 'on' when either switches A or B or both are 'on'. Circuit D enables switches A and B to be switched 'on' simultaneously.

This circuit senses the 50Hz noise our body is always picking up and uses that as the control signal. IC3a is connected as a standard amplifier with a gain of about 50. When a finger touches the touch plate, the noise voltage on the touch plate is amplified and then rectified by D1 and filtered by C1 to provide a small voltage change across R4, providing a logic 1 pulse at IC1a. IC1a and IC1b acts as a memory. When the finger is removed, point a remains at logic 1. The output of switch A goes from logic 1 to logic 0. The l.e.d. D11 goes on when point a is at logic 1 and will remain so as long as it is at logic 1.

To enable switch C to be turned 'off' when switch A is 'on', point a is connected via an inverter to point c of switch C. This will result in the memory circuit of switch C being reset, and its output will go to logic 1 if it is at logic 0.

Switch B is wired similarly to switch C. Switch D is wired to switches A and B at point a and b respectively to enable switches A and B to be switched 'on' simultaneously.

Further stages can be added to this multi-way switch and different switching combinations can also be chosen.

Multi-pole function can be achieved by connecting an inverter to point a or its equivalent point in the other stages.

This unit was intended for direct interface with TTL, but the output could be used to drive a relay if heavier loads are required.

The knob of a door could be used as a touch plate, thus using the unit as a burglar alarm.

Yee Yew Khuan,
Selangor,
West Malaysia.

CAR THEFT ALARM

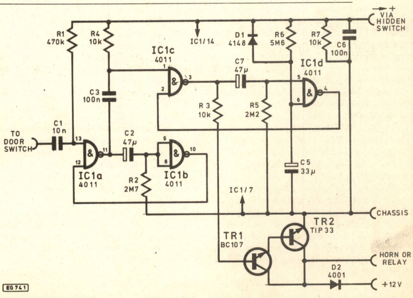

EG741

THIS alarm consists of two monostable multivibrators built around a single i.c., a two-transistor driver stage able to drive the car's horn or a relay, and a hidden switch to turn the unit on/off.

When the car's door is opened, the door contact will close and trigger the first multivibrator. If the unit isn't turned off before a certain time determined by R2 C2, the second multivibrator will be triggered, sounding the horn (or drawing the relay) for a time determined by R5 C7. To be able to leave the car without triggering the alarm, pin 6 will be held low for a time determined by R6 C5, making the second multivibrator insensitive to triggering.

When the unit is turned off, C5 will rapidly discharge through D1 R7 to make it possible to turn the unit on again immediately. With the values shown, the alarm will sound for about 2 minutes and you'll have about 20 seconds to turn the unit off after entering the car. These times can be changed by altering the RC-networks. If the diode D2 is connected directly across the horn (or relay) the + connection will not be necessary.

Anders Ljungfeldt,
Gothenburg,
Sweden.

NEW VOICES FOR YOUR ORGAN

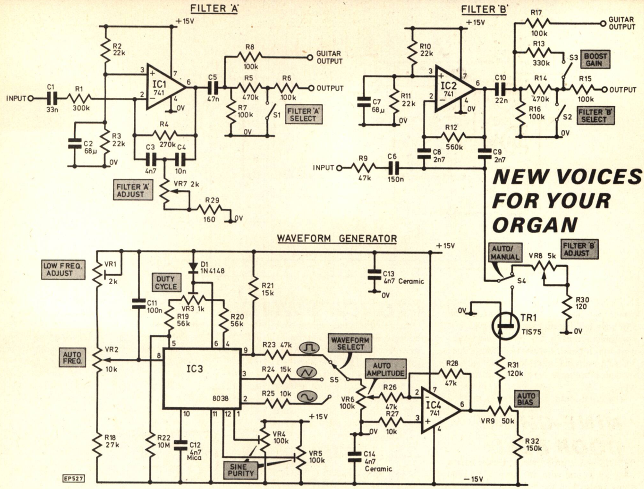

THE desirability of a large range of interesting voices is an indisputable requirement for all organists. This presents no problem when unlimited funds are available since the ubiquitous chip has provided the means to produce an almost infinite range of sounds controllable by tabs, drawbars, peddles, knee switches, etc. However, in the more modest range of organs, as few as three tabs only may be available on each manual, together with presets such as vibrato, wha, banjo, etc. This does allow a dozen or so combinations but it will soon become desirable to have more.

The new sounds are achieved by the use of two filter circuits either singly or in combination, both employing LM741 operational amplifiers to provide band pass characteristics. Both filters provide gain over a narrow band of frequencies but filter A has a gain of unity at low frequencies. By connecting adjusting resistors, the band pass frequency can be varied over a wide range whilst the band width remains constant.

Filter A will pass the fundamental frequency of the note played plus the harmonics which lie within the pass band. These harmonics being boosted by the gain in the pass band.

Filter B provides very similar boosting characteristics to the harmonics but does not pass the fundamental.

Use of filter A or both will provide a basic flute-like tone but with the addition of the selected higher harmonics. The effect will be to considerably brighten the tone and particularly to increase the attack on the leading edge of the envelope. The addition of the upper harmonics will not produce edgy string-like sounds since the width of the pass band is insufficient, the sound being more bell-like.

By setting S4 to auto, VR8 is replaced by a field effect transistor used as a variable resistor, so that voltage control of the pass band frequency can be achieved. This allows the use of a waveform generator to control the filter frequency and provide repetitive effects of almost infinite variety.

The waveform generator circuit is based on the 8038. It can provide sine, square, triangular and ramp-type waveforms over a frequency range of 0·1 to 100 Hz approximately.

The chosen waveform is applied to filter B via the f.e.t. TR1 together with a d.c. bias which sets the nominal pass band frequency. The amplitude control sets the extent of the frequency sweep. Many combinations of pass band frequency sweep amplitude and repetition rate are possible.

Using the filters with their nominal pass band frequencies set by VR7 and VR8 will provide very bright voices when used on their own or will brighten any combination of the organs existing voices. Vibrato will enhance all the voices as desired. If the waveform generator is used with a sine wave to drive filter B an effect similar to vibrato will occur but only on the upper harmonics. With very small amplitudes this can be a very subtle and musical effect, particularly when the sweep frequency is matched to the tempo of the music being played. Many other modern effects can be produced with large amplitudes of sweep frequency, for example, when matched to the beat of the music or when very slow, allowing the pass band to sweep the whole range.

Some combinations of the controls will not be musical but many new voices and combinations of effects will enhance the performance of your organ.

The complete unit should be installed in parallel with the existing organ filters. The bus bar connections should be made to the filter inputs with the outputs going to the summing amplifiers.

B. F. Smith,
Humberstone,
Leicester.

TERMINAL SOUND

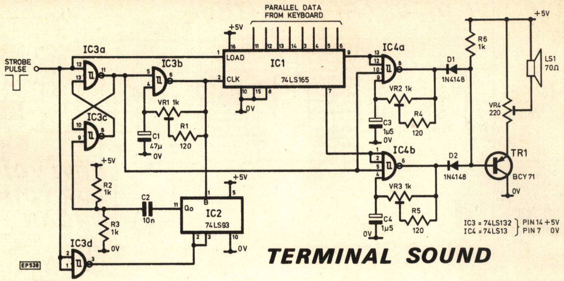

INTENDED as an addition to microprocessor or VDU keyboards, this produces a different pattern of high and low tones for each key on the keyboard. Although it is not necessary to learn these different patterns, after some use the tone generator becomes a real aid to accurate typing.

The 8-bit data from the keyboard is loaded into a shift register IC1, and latch IC3a,c is set, when a keyboard strobe pulse is produced. Pulses from the oscillator IC3b shifts the data so that the two tone oscillator IC4a,b produce a high tone for a 1 and a low tone for a 0. These tones are summed and fed to a small loudspeaker. Counter IC2 resets the latch after the last data bit is shifted out.

VR1 sets the speed of shifting, and VR2/VR3 adjust the high and low tones respectively. VR4 sets the volume. The circuit shown is for negative strobe pulses, but is easily rearranged for positive strobes.

T. P. Hopkins,
Didsbury,
Manchester.

NINE-CHIME DOOR BELL

THIS bell is programmed by the user to play a tune with anything up to nine notes. Instead of one oscillator playing the tune, two oscillators are used, which are tuned so as to give a chord on every note.

When the bell push is operated, the latch formed by IC2 is triggered and the decade counter IC3 is reset. The output of the latch operates a switching transistor. This applies the supply voltage to ICs 1, 3, 4, 5, and 6. At this point, a slow oscillator formed by IC1 is started, the output of which starts the counter counting. A tempo control is provided which speeds up or slows down the tune.

Each output of the counter goes via a preset and diode which are commoned and the output voltage from each note (which is programmed by adjusting the pre-sets), goes to two voltage controlled oscillators formed by IC4 and 5. Each VCO has its individually controllable tune preset. In practice these are set up so the notes produced form a melodic chord. The output from each VCO goes to a simple power amplifier formed by IC6. This is provided with a simple volume control which feeds a loudspeaker.

When the last note has played the counter is automatically reset and the latch also resets. The power is removed from all the i.c.s except IC2, which is always receiving power so the door chime may be triggered.

Graeme Durant,
Selby,
N. Yorkshire.

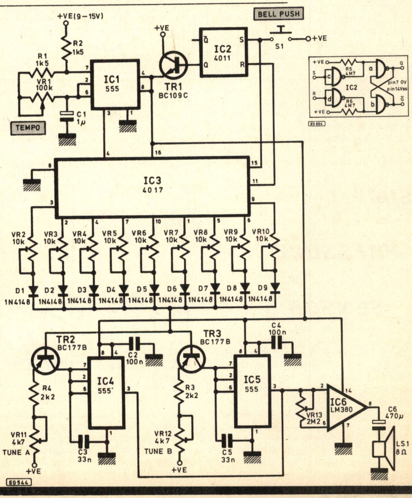

INDUCTIVE DISCHARGE IGNITION

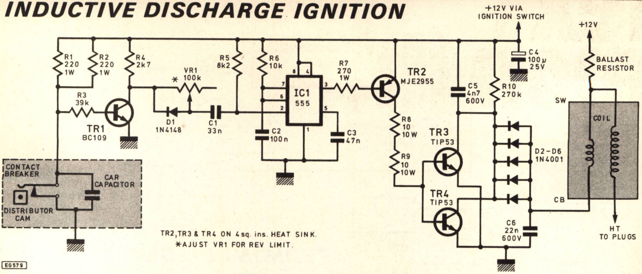

WITHOUT going into the controversy about the advantages of capacitor or inductive discharge ignition versus normal ignition, a circuit for inductive discharge ignition is presented here. It is a points assisted unit in which the coil load of 3·5 amps is removed to a switching transistor. Other features in the circuit are: rev limit, points bounce control, long dwell time, lower RFI than a CDI system.

Most ignition coils have a resistance (including ballast) of about 3·5 ohms and an inductance of some 11mH. A time constant of 3 milliseconds results and some 10 milliseconds are needed for the coil to saturate fully after switch-on. In the circuit presented the coil is switched on for most of the time (long dwell) and is only switched off to fire the plugs for about 1 millisecond. (For very high revs this time can be reduced to 500µs.)

IC1 acts as a 1ms monostable and with its output normally low TR2, TR3 and TR4 are switched on. When triggered IC1 output goes high for 1ms and switches TR2, TR3 and TR4 off for this period to fire the plugs. TR1 acts as an inverter to trigger the monostable and the circuitry around VR1, C1 and D1 act as a rev limiter and point bounce control. When the points open TR1 conducts and C1 is rapidly charged bringing pin 2 of IC1 low momentarily before C1 charges up again. This triggers IC1. When the points close again TR1 stops conducting and C1 discharges slowly through VR1. Points bounce occurs on closing and should a bounce occur a retrigger cannot occur because C1 has not yet fully discharged. Should the time constant of C1, VR1 be set very long then C1 may not have discharged when the next firing pulse is required. A misfire occurs and the revs are limited to the corresponding time constant set by VR1. In practice VR1 should be set at maximum safe engine revs for effective point bounce control.

TR3 and TR4 are high voltage switching transistors. Each can handle 3 amps but gain at this current is low. Parallel operation reduces individual current to a point where gain is higher requiring less base drive.

The circuitry around D2 to D6, C5, C6 is for surge control and to prevent high reverse voltages across TR3 and TR4. Note that C6 has a much lower value than a normal car capacitor and this can be varied to tune the coil for best output using a 'scope. The value shown however is a good average value for most coils.

R. Immelman,
Somerset West,
South Africa.

SIMPLE PRESSURE SENSOR

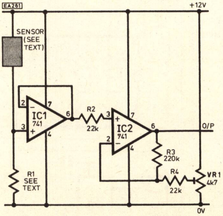

THIS unit was originally designed as part of a burglar alarm system, although, as it is capable of giving an output which is almost linearly proportional to pressure, it may find many other uses such as a tactile sensor in a robot.

The circuit shown is a linear reading pressure sensor. The voltage at the output of the potential divider formed by the sensor and R1 (which rises with increased pressure) is buffered by IC1 and fed to the amplification stage IC2—the resulting output is directly proportional to pressure. The preset VR1 is used to set the output voltage to a convenient level in the absence of an input. This output could then be fed into an A/D converter for use in a robotic system.

The sensor is a piece of conductive foam of the type with which CMOS i.c.s are supplied. As the foam is compressed its resistance decreases. In the prototype the foam was sandwiched between a piece of p.c.b. material with a wide strip of copper removed from the middle, and a piece of plain circuit board. Built in this way the foam bridges the gap on the p.c.b. although the foam could be sandwiched between two pieces of copper backed board with one terminal of the sensor being taken from each.

The resistor R1 should be approximately $\frac{1}{4}$ the value of the uncompressed resistance of the foam.

S. Draper,
Sudbrooke,
Lincoln.

next month...

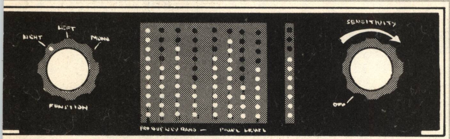

AUDIO ANALYSER

Ever wondered what effect your room furnishings have on the output of your hi-fi or if your amplifier delivers equal power over the audio spectrum? Now you can find out with our Audio Analyser. We will also describe a stereo microphone preamplifier and a noise source which can be used with it.

Model Train Controller

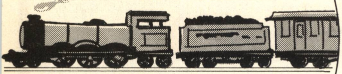

Adds realism to train movements by ensuring smooth starting, acceleration and gentle braking in a single control. An added feature is protection against track short circuits.

New Series... DIGITAL DESIGN

This is a new approach to the subject which brings together theory and practice and includes many useful tips and "standard circuits" etc. It comes complete with a wide range of useful projects which complement the theory.

PRACTICAL ELECTRONICS

OUR AUGUST ISSUE WILL BE ON SALE FRIDAY, 10 JULY 1981

LINEAR ICS

THE LOWEST PRICES FOR PRIME CMOS/TTL/74C IN THE UK

TRANSISTOR

TBA120S	1.00
L200	1.95
U237B	1.28
U247B	1.28
U257B	1.28
U267B	1.28
LM301H	0.67
LM301N	0.30
LM308TC	0.65
LM324	0.64
LM339N	0.66
LM348N	1.86
LF351N	0.49
LF353N	0.76
LM374N	3.75
LM380N-14	1.00
LM380N-8	1.00
LM381N	1.81
ZN419CE	1.98
NE544N	1.80
NE555N	0.30
NE556	0.50
NE560N	3.50
NE562N	4.05
NE564N	4.29
NE565N	1.00
NE566N	1.60
NE570N	3.85
SL624	3.28
TBA651	1.81
uA709HC	0.64
uA709PC	0.46
uA710HC	0.65
uA710PC	0.59
uA741CH	0.66
uA741CN	0.27
uA747CN	0.70
uA748CN	0.36
uA753	2.44
uA758	2.35
TBA820M	0.78
TCA940E	1.80
TDA1028	2.11
TDA1029	2.11
TDA1054	1.45
TDA1062	1.95
TDA1072	2.69
TDA1074A	5.04
TDA1083	1.95
TDA1090	3.05
HA1137	1.20
HA1196	2.00
HA1197	1.00
TDA1220	1.40
LM1303	0.99
LM1307	1.55
MC1310P	1.90
MC1330	1.20
MC1350	1.20
HA1370	1.90
HA1388	2.75
TDA1490	1.86
MC1496P	1.25

SL1610P	1.60
SL1611P	1.60
SL1612P	1.60
SL1613P	1.89
SL1620P	2.17
SL1621P	2.17
SL1623P	2.44
SL624C	3.28
SL1625P	2.17
SL1626P	2.44
SL1630P	1.62
SL1640P	1.89
SL1641P	1.89
TDA2002	1.25
ULN2242A	3.05
ULN2283B	1.00
CA3080E	0.70
CA3089E	1.84
CA3090AQ	3.35
CA3123E	1.40
CA3130E	0.80
CA3130T	0.90
CA3140E	0.46
CA3189E	2.20
CA3240	1.27
MC3357P	2.85
LM3900N	0.60
LM3909N	0.68
LM3914N	2.80
LM3915N	2.80
KB4400	0.80
KB4406	0.60
KB4412	1.95
KB4413	1.95
KB4417	1.80
KB4420B	1.09
TDA4420	2.65
KB4423	2.30
KB4424	1.65
KB4431	1.95
KB4432	1.95
KB4433	1.52
KB4436	2.53
KB4437	1.75
KB4438	2.22
KB4441	1.35
KB4445	1.29
KB4446	2.75
KB4448	1.65
NE5044N	2.26
NE5532N	1.85
SD6000	3.75
SL6270	2.03
SL6310	2.03
SL6600	3.75
SL6640	2.75
SL6440	POA
SL6690	3.20
SL6700	2.35
ICL8038CC	4.50
MSL9362	1.75
MSL9363	1.75
HA11211	1.95

HA11223	2.15
HA11225	1.45
HA12002	1.45
HA12017	0.80
HA12402	1.95
HA12411	1.20
HA12412	1.55
LF13741	0.33
SN76660N	0.80

FREQ. DISPLAY AND SYNTH. DEVICES

SAA1056	3.75
SAA1058	3.35
SAA1059	3.35
11C90DC	14.00
LN1232	19.00
LN1242	19.00
MSL2318	3.84
MSM5523	11.30
MSM5524	11.30
MSM5525	7.85
MSM5526	7.85
MSM5527	9.75
MSM55271	9.75
MSL2312	3.94
SP8629	3.85
SP8647	6.00
95H90PC	7.80
HD10551	2.45
HD44015	4.45
HD12009	6.00
HD44752	8.00
MC145151	12.45
MC145156	8.75

MISC

ICM7106CP	9.55
ICM7107CP	9.55
ICM7216BP	19.50
ICM7555	0.94

4000 series

4000	0.13
4001	0.13
4002	0.14
4007	0.19
4008	0.70
4009	0.30
4010	0.30
4011	0.24
4011	0.15
4012	0.20
4013	0.35
4015	0.70
4016	0.30
4017	0.65
4019	0.38
4020	0.68
4021	0.75
4022	0.68
4023	0.19
4024	0.45
4025	0.18
4026	1.05
4028	0.60
4029	0.75
4030	0.35
4035	0.75
4040	0.68
4042	0.65
4043	0.68
4043	0.93
4044	0.68
4946	0.69
4047	0.69
4049	0.30
4050	0.30
4051	0.65
4052	0.69
4053	0.69
4054	1.30
4055	1.30
4056	1.35

4060	0.95
4063	1.15
4066	0.38
4067	4.30
4068	0.18
4069	0.18
4070	0.25
4071	0.22
4072	0.22
4073	0.22
4075	0.18
4076	0.60
4077	0.23
4078	0.25
4082	0.25
4093	0.45
4099	0.99
4175	1.15
4502	0.90
4503	0.55
4506	0.75
4507	0.45
4508	1.99
4510	0.70
4511	0.85
4512	0.70
4514	2.20
4515	2.50
4516	0.75
4518	0.75
4520	0.80
4521	2.36
4522	1.49
4527	0.95
4528	0.95
4529	1.40
4539	1.10
4549	3.50
4554	1.73
4555	0.72
4556	0.58
4560	2.18

4566	1.59
4568	2.18
4569	1.95
4572	0.30
4582	0.99
4584	0.49
4585	1.00
4702	4.50
4703	4.48
4704	4.24
4705	4.24
4706	4.50
4720	4.00
4723	0.95
4724	0.95
4725	2.24
40014	0.54
40085	0.99
40098	0.54
40106	0.54
40160	0.69
40161	0.69
40162	0.69
40163	0.69
40174	0.69
40175	0.69
40192	0.75
40193	0.75
40194	0.69
40195	0.69

TTL 'N'

7400	0.10
7401	0.10
7402	0.10
7403	0.11
7404	0.12
7405	0.12
7406	0.22
7407	0.22
7408	0.15

7448	0.56
7450	0.14
7451	0.14
7453	0.14
7454	0.14
7460	0.14
7470	0.28
7472	0.27
7473	0.28
7474	0.28
7475	0.35
7476	0.30
7480	0.26
7481	0.20
7482	0.75
7483	0.60
7485	0.75
7486	0.24
7489	1.05
7490	0.30
7491	0.55
7492	0.35
7493	0.35
7494	0.70
7495	0.60
7496	0.45
7497	1.40
74100	1.10
74104	0.62
74105	0.62
74107	0.26
74109	0.35
74110	0.54
74111	0.68
74112	1.70
74166	1.98
74118	0.85
74119	1.20
74120	0.95
74121	0.35
74122	0.34
74123	0.40

74125	0.40
74126	0.40
74128	0.65
74132	0.50
74136	0.65
74141	0.45
74142	1.85
74143	2.50
74144	2.50
74145	0.75
74147	1.50
74148	1.09
74150	0.79
74151	0.55
74153	0.55
74154	0.55
74155	0.55
74156	0.55
74157	0.55
74159	1.90
74160	0.55
74161	0.55
74162	0.55
74163	0.55
74164	0.55
74165	0.55
74166	0.70
74167	1.25
74170	1.25
74173	1.10
74174	0.75
74175	0.75
74176	0.75
74177	0.75
74178	0.90
74179	1.35
74180	0.75
74181	1.22
74182	0.70
74184	1.20
74185	1.20
74188	3.00

74190	0.55
74191	0.55
74192	0.55
74193	0.55
74194	0.55
74195	0.55
74196	0.55
74197	0.55
74198	0.85
74199	1.00
74221	1.00
74246	1.50
74247	1.51
74248	1.89
74249	1.89
74251	1.05
74265	0.66
74273	2.67
74278	2.49
74279	0.89
74283	1.30
74284	3.50
47285	3.50
74290	1.00
74293	1.05
74297	2.36
74298	1.85
74365	0.85
74366	0.85
74367	0.85
74368	0.85
74390	1.85
74393	1.85
74490	1.85

'LPSN'

7400	0.11
7401	0.11
7402	0.12
7403	0.12
7404	0.13

7405	0.14
7408	0.14
7409	0.14
7410	0.13
7411	0.14
7412	0.15
7413	0.28
7414	0.49
7415	0.14
7420	0.13
7421	0.15
7422	0.15
7426	0.18
7427	0.14
7428	0.35
7430	0.13
7432	0.14
7433	0.16
7437	0.17
7438	0.16
7440	0.13
7442	0.40
7447	0.42
7448	0.65
7449	0.61
7451	0.14
7454	0.15
7455	0.15
7463	1.50
7473	0.21
7474	0.18
7475	0.28
7476	0.22
7478	0.24
7483	0.50
7485	0.70
7486	0.18
7490	0.32
7491	1.25
7492	0.39
7493	0.38
7495	0.48

7496	1.20
74107	0.25
74109	0.25
74112	0.25
74113	0.25
74114	0.25
74122	0.40
74123	0.55
74124	1.80
74125	0.29
74126	0.29
74132	0.45
74133	0.30
74136	0.25
74138	0.40
74139	0.40
74145	1.20
74147	2.10
74148	1.60
74151	0.35
74153	0.35
74154	0.99
74155	0.50
74156	0.50
74157	0.36
74158	0.40
74160	0.40
74161	0.40
74162	0.40
74163	0.40
74164	0.50
74165	1.20
74166	1.75
74168	0.85
74169	0.85
74170	1.85
74173	0.75
74174	0.55
74175	0.55
74181	1.35
74183	2.96
74189	1.28

74190	0.60
74191	0.60
74192	0.68
74193	0.68
74194	0.42
74195	0.42
74196	0.65
74197	0.65
74200	3.45
74202	3.45
74221	0.60
74240	0.99
74241	0.99
74242	1.65
74243	1.65
74244	0.83
74245	1.50
74247	1.35
74248	1.35
74249	1.35
74251	0.46
74253	0.46
74257	0.55
74258	0.39
74259	0.39
74260	0.70
74266	0.24
74273	0.90
74275	3.20
74279	0.35
74280	2.50
74283	0.44
74290	0.58
74293	1.30
74295	1.50
74298	1.50
74365	0.35
74366	0.35
74367	0.35
74368	0.35
74373	0.78
74374	0.78
74375	1.15
74377	1.99
74378	1.40
74379	2.15
74384	2.50
74385	4.20
74386	0.29
74390	0.68
74393	0.61
74395	2.10
74396	1.99
74398	2.75
74399	2.30
74445	1.40
74447	1.95
74490	1.10
74668	1.05
74669	1.05
74670	1.70

74C CMOS

7400	0.20
7402	0.20
7404	0.20
7408	0.20
7410	0.20
7414	0.55
7420	0.20
7430	0.20
7432	0.20
7442	0.80
7448	1.03
7473	0.50
7474	0.50
7476	0.48
7483	0.98
7485	0.98
7486	0.26
7489	2.68
7490	0.80
7493	0.80
7495	0.94
74107	0.48
74151	1.52
74154	2.26
74157	1.52
74160	0.80
74161	0.80
74162	0.80
74163	0.80
74164	0.80
74165	0.84
74173	0.72
74174	0.72
74175	0.72
74192	0.80
74193	0.80
74195	0.80
74200	4.52
74221	1.06
74901	0.38
74902	0.38
74903	0.38
74904	0.38
74905	5.64
74906	0.38
74907	0.38
74908	0.84
74909	1.52
74910	3.62
74914	0.86
74918	0.98
74925	4.32
74926	4.32
74927	4.32

E&OE

Subject to availability

BF194	18p
BF195	18p
BF224	22p
BF241	18p
BF274	18p
BF440	21p
BF441	21p
BF362	49p
BF395	18p
BF479	66p
BF679S	55p
BFR91	1.33
BFW92	60
BFT95	99
BFY90	90
40238	85
BF256	38
2SK55	28p
2SK168	35p
J310	69p
J176	65
40823	65
40673	3SK5
3SK45	49
3SK51	54
3SK60	58
3SK88	1.24
MEM680	75
BF961	70
BC237	8p
BC238	8
BC239	8
BC307	8
BC308	8
BC309	8
BC413	10
BC414	11
BC415	10
BC416	11
BC546	12
BC556	12
BC550	12
BC560	12
BC639	22
BC640	22
2SC1775	18
2SA872A	14
2SD666A	30
2SB646A	30
2SD668A	40
2SB648A	40
2SD760	45
2SB720	45
2SC2547	19
2SA1085	20
2SB753	2.34
2SB723	2.34
2SK134	3.10
2SJ49	3.10
2SK135	4.25
2SJ50	4.25
2SK227	3.55
2SJ83	3.55

CRYSTALS

32.768kHz	2.70
100kHz	3.85
455kHz	5.00
1.000MHz	2.95
3.2768	2.70
4.000	2.00
4.1934	2.00
4.096	2.00
4.032	2.00
4.433619	2.00
4.800	2.00
5.000	2.00
6.5536	2.00
7.000	2.00
7.68	2.00
8.000	2.00
9.000	2.00
10.000	2.00
10.240	2.00

CRYSTALS

10.245	2.00
10.6985	2.50
10.700	2.00
10.7015	2.50
11.00	2.00
11.115	2.00
11.520	2.00
8.9985	2.00
9.0015	2.00
21.000	2.00
24.000	2.00
25.000	2.00
26.000	2.00
18.000	2.50

XTAL FILTERS
10M4B1; 10.7Mhz, 15Khz BW, 8 pole. 14.50
10M22D; 10.7Mhz, 2.4Khz BW, SSB, 8 pole. 17.20

RADIO CONTROL

RC XTALS
AM TX/RX
FM RX:
3rd ot/30pF
HC25U 1.65
FMTX: Fund
20pF HC25U
½ freq 1.85
PAIRS...AM 3.10
PAIRS...FM 3.25
CHANNELLING:
27MHz. 50kHz
35MHz: 20kHz

ALL PRICES EXCLUDE VAT – CURRENTLY AT 15%
POSTAGE 50p ORDERS UNDER £12 · FREE OVER £12

The lowest prices for prime, repeatable devices ? We think so, and wait to hear to the contrary. Ambit's new bigger, cheaper and complete range of parts is covered in our new 12 page A4 format short-form and price list: available free with an SAE, and supplied with all orders. You can order by ACCESS/BARCLAYCARD, cheque, PO with order - or come into our refurbished retail shop and use 'real' money! Our 3 catalogues (£1.85 inc. or 75p ea inc) cover the BIGGEST RANGE OF RF components in Europe as well as standard parts, so invest a set today. The saving you make on your first couple orders will soon repay th cost.

AMBIT international

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

200 North Service Road, Brentwood, Essex

NOW

DOUGLAS TRANSFORMERS FROM TITAN

NEW FRANCHISE AT FANTASTIC PRICES – EX STOCK

WE GUARANTEE THESE PRICES TO BE UNBEATABLE ANYWHERE !!

12/24V RANGE PRI 220/240V
SEC: 0 12V 0V 12V

TYPE	amps 12v	amps 24v	price £	p-p £
242	0.3	0.15	**1.70**	0.40
213	1	0.50	**2.32**	0.70
71	2	1	**2.51**	0.90
18	4	2	**3.24**	1.43
68	3	1.5	**3.15**	1.43
85	5	2.5	**5.52**	1.43
70	6	3	**6.26**	1.43
108	8	4	**7.36**	1.73
72	10	5	**8.05**	1.65
116	12	6	**8.57**	1.90
17	16	8	**10.53**	2.05
115	20	10	**13.69**	2.05
187	30	15	**17.62**	2.45
232	40	20	**25.16**	3.50
226	60	30	**35.35**	4.00

15/30V RANGE PRI 220/240V
SEC: 0V 12V 15V 0V 5V 9V 15V
VOLTS AVAILABLE 3 ⟹ 15—0—15

TYPE	amps 15v	amps 30v	price £	p-p £
112	1	0.50	**2.47**	0.95
79	2	1.0	**3.16**	0.95
3	4	2	**5.64**	1.43
20	6	3	**6.59**	1.73
21	8	4	**7.80**	1.73
51	10	5	**9.68**	1.90
117	12	6	**10.97**	2.05
88	16	8	**14.65**	2.20
89	20	10	**16.93**	2.35
90	24	12	**18.84**	2.55
91	30	15	**21.56**	2.65
92	40	20	**30.08**	3.50

25/50V RANGE PRI 120/220/240V
SEC: 0V 20V 25V 0V 8V 15V 25V
VOLTS OUT 5 ⟹ 25—0—25

TYPE	amps 25v	amps 50v	price £	p-p £
102	1	0.50	**2.88**	1.43
103	2	1.0	**3.60**	1.43
104	4	2	**7.04**	1.73
105	6	3	**8.33**	1.90
106	8	4	**11.18**	1.90
107	12	6	**14.79**	2.20
118	16	8	**20.49**	2.55
119	20	10	**24.52**	2.55
109	24	12	**29.39**	3.50

30/60V RANGE PRI 120/220/240V
SEC: 0V 24V 30V 0V 10V 18V 30V
VOLTS 6 ⟹ 30—0—30

TYPE	amps 30v	amps 60v	price £	p-p £
124	1	0.5	**2.92**	1.43
126	2	1	**5.78**	1.43
127	4	2	**7.13**	1.73
125	6	3	**10.73**	1.90
123	8	4	**12.28**	2.20
40	10	5	**15.55**	2.20
120	12	6	**17.72**	2.35
121	16	8	**25.09**	2.65
122	20	10	**29.07**	4.00
189	24	12	**33.51**	4.60

48/96V RANGE PRI 120/220/240V
SEC: 0V 36V 48V 0V 36V 48V
VOLTS 12 ⟹ 48—0—48

TYPE	amps 48v	amps 96v	price £	p-p £
430	1	0.5	**4.14**	1.43
431	2	1	**7.22**	1.73
432	4	2	**11.87**	2.05
433	6	3	**14.47**	2.20
434	8	4	**18.43**	2.45
435	10	5	**26.16**	2.65
436	12	6	**32.75**	4.00
437	16	6	**35.77**	4.60

AUTOTRANSFORMERS 240/220—115V
65VA — 10 KVA
0V 115V 220V 240V

TYPE	va	price £	p-p £
25	65	**3.82**	1.10
64	80	**4.40**	1.10
4	150	**5.64**	1.43
69	250	**7.13**	1.73
53	350	**8.97**	1.90
67	500	**11.09**	2.20
83	750	**12.42**	2.20
84	1000	**16.88**	2.65
95	2KVA	**31.26**	4.00
73	3	**61.27**	4.75
57	5	**87.42**	6.60
101	10	**159.45**	13.00

CASED AUTOTRANSFORMERS
240V LEAD IN:115V 2PIN SOCKET OUT

TYPE	va	price £	p-p £
56W	20	**5.52**	0.58
64W	80	**7.63**	1.43
4W	150	**9.63**	1.73
69W	250	**11.98**	1.90
67W	500	**18.67**	2.20
84W	1000	**26.90**	2.65
95W	2000	**48.45**	7.00
73W	3000	**69.18**	8.00

LINE ADJUSTMENT AUTOTRANSFORMERS
0 200 210 220 230 240 250

TYPE	va	price £	p-p £
415C	50	**2.13**	0.58
416C	100	**3.13**	1.10
417C	200	**3.65**	1.43
418F	350	**5.63**	1.43
419F	500	**6.13**	1.73
420E	750	**7.60**	1.90
421F	1000	**10.55**	2.05

MAINS ISOLATORS (SAFETY SCREEN)
PRI 120/220/240V SEC 60V 55V 0V 55V 60V 60V 55V 0V 55V 60V

TYPE	va	price £	p-p £
149F	60	**7.35**	1.73
150F	100	**8.61**	1.73
151F	200	**12.15**	2.05
152F	250	**14.75**	2.20
153F	350	**18.22**	2.55
154F	500	**22.70**	2.65
155F	750	**32.08**	7.00
156F	1000	**41.26**	7.00

MAINS ISOLATORS (SAFETY SCREEN)
PRI 380/415/460V SEC 60V 55V 0V 55V 60V 60V 55V 0V 55V 60V

TYPE	va	price £	p-p £
243F	60	**7.35**	1.43
244F	100	**8.61**	1.73
245F	200	**12.15**	2.05
246F	250	**14.75**	2.20
247F	350	**18.22**	2.55
248F	500	**27.70**	2.65
249F	750	**32.08**	7.00
250F	1000	**41.26**	8.00

Invertor ... In 12V DC Nom. Out 240V AC Square Wave 100 VA Con. 150 VA peak.
INV. 1 .. Cased, PVC covered steel case with BA 3 pin socket **£49.95** P&P £2.35.
INV. 2 .. Open frame for OEM **£39.95** P&P £2.35.

MAINS ADAPTORS
13 amp plug in type. Reversible spider jack lead.

TYPE	va	mA	price	p-p
100	6-7.5-9v	250	**3.85**	0.58
101	Regulated 6-7.5-9v	300	**4.70**	0.58

SEND TODAY 50p (REFUNDABLE WITH FIRST ORDER) FOR CATALOGUE

TITAN TRANSFORMERS AND COMPONENTS

Dept. P.E. CENTRAL HALL CHAMBERS GRIMSBY S.HUMBERSIDE
MAIL ORDER – PRICES INCLUDE 15% VAT

SPECIAL DPM OFFER

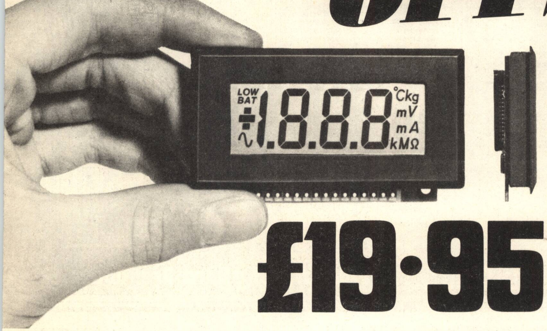

£19·95

INCLUDING V.A.T. POSTAGE AND PACKING

OUR free case has been designed to accept this special offer LE DPM 200 digital panel meter. By using this meter a wide range of accurate instruments can be constructed with the addition of only a few external components. The custom designed l.c.d. consumes only microwatts of power making it ideal for use in portable equipment.

Our offer price including VAT and postage etc., saves £3 on the normal 1 off price from Lascar.

SPECIFICATION

Input impedance:	>100M
Full scale reading:	199·9mV
Accuracy:	0·05% of reading ±1 digit
Power supply:	5–15V d.c.
Power consumption:	50μA (in low power mode), typically 8,000 hours PP3 life
Sample rate:	3 readings per sec.
Auto-zero:	No necessity to adjust for offsets
Auto-polarity:	Automatic polarity indication eliminates the need to reverse input leads to obtain correct reading.
Over-range warning:	1 in leading digit with other digits suppressed
Bandgap reference (50ppm/°C typ.)	incorporated for excellent stability of reading
Digit height:	15mm (0·6″) can be read at distances up to 10 metres
Low battery warning:	direct display, voltage threshold easily adjusted
Operating temperature:	0°C to 50°C
Overall dimensions:	72×36×12mm
Panel cut-out:	68×33mm
Display annunciators:	many useful legends are built into the custom l.c.d. which may be activated as required

To: Lascar Electronics Ltd., Unit 1, Thomasin Rd., Burnt Mills, Basildon, Essex SS13 1LH. Tel. 0268 727383

Complete both parts of the coupon in BLOCK CAPITALS

Please send me...... LE DPM 200(s) at £19·95 each inclusive

I enclose P.O./Cheque No ....Value............

Make cheques payable to Lascar Electronics Ltd.

Name ....

Address ....

....

....

Please allow 21 days for delivery

OFFER CLOSES FRIDAY 28th AUGUST 1981

Name ....

Address ....

....

....

From: Lascar Electronics Ltd., Unit 1, Thomasin Rd., Burnt Mills, Basildon, Essex SS13 1LH.

Please Note: Orders posted after the closing date cannot be accepted.

LIGHT METER

MARTIN KENT

FREE CASE PROJECT

THE measurement of light intensity is required in many applications areas, including photographic exposure meters, dust density meters for environmental control, fog density meters, flame monitoring in heating engineering, in addition to general photometry experiments.

The DP800 Lightmeter may be easily assembled using the LE DPM200 Panel Meter and very few additional components. Extensions of the basic circuit are also described to widen the possible applications.

OPTICAL SPECTRUM

The optical spectrum is characterised by radiation having wavelengths between 10nm and 1mm and may be divided into two invisible sections (infrared and ultraviolet) separated by a central visible section. Parameters defining the visible section are generally termed photometric units and the radiant energy is characterised by wavelengths of about 380nm to 780mm. The term 'light' only relates to that part of the optical spectrum capable of being detected by the human eye.

The rate of flow of visible radiant energy with respect to time is the luminous flux which is measured in lumens. For light measurements the standard unit is the lux which is a measure of the luminous flux density incident upon a surface or illuminance (Ev) and is defined as 1 lumen/m^2.

One of the traditional components used in light measurement is the cadmium sulphide light dependent resistor. The device is easy to apply but produces non-linear variations of resistance with respect to incident light. Phototransistors were a later development whereby light falling upon the exposed base causes variations in collector current. Operation of phototransistors is usually linear over small ranges.

Luminous fluxes should be measured with photodetectors which produce a linear output with special correction to the spectral sensitivity of the eye. Silicon photodiodes are available which act as variable current sources with output proportional to luminous flux and which also provide faster switching than phototransistors.

Fig. 1 shows the relative spectral response of the human eye and of the photodiode used in the DP800. When a photodiode is reverse-biased the leakage current is independent of the applied voltage but a condition is reached when the current cannot be further reduced by shielding from irradiation; the current then flowing is known as the dark current which is typically 1·4μA for the photodiode used (Fig. 2). The true photocurrent generated is the difference between the light current, when exposed to radiant energy, and the dark current.

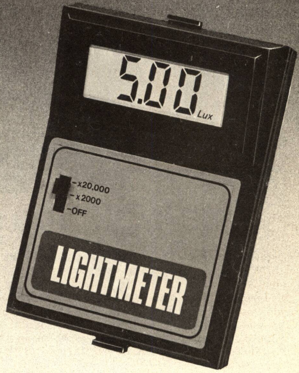

PE Digital Precision Lightmeter DP800

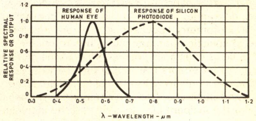

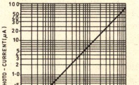

Fig. 1. Relative spectral characteristics

Fig. 2. (Left) Graph showing photocurrent vs irradiation for the photodiode used

CIRCUIT

The circuit diagram of the basic luxmeter is shown in Fig. 3. Photodiode D1 is reverse-biased by the stable 1·2V bandgap reference within the LE DPM200. The panel meter

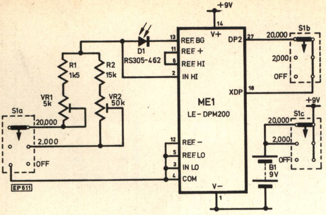

Fig. 3. Circuit of Lightmeter

operates with 200mV f.s.d. and the photocurrent is scaled to the correct voltage by R1 and VR1.

Typical responsivity of the photodiode is 0·7 µA/mW/cm². It is possible to obtain a direct reading of lux by using the fact that 1mW/cm² is equivalent to 200 lux, therefore 1 lux is equal to a photocurrent of typically 3·5nA.

The instrument may be easily scaled to provide ranges of varying sensitivity. For example, 2000 lux would produce 7µA photocurrent and to produce 200mV f.s.d. requires a resistance of approximately 28kΩ, similarly 20,000 lux requires a scaling resistor of 2·8kΩ. As a guide, the light energy in the UK on a sunny day can be in excess of 500W/m² or 10,000 lux. The wide tolerance in manufacturers' specification for the responsivity of the photodiode necessitates a wide range of adjustment on VR1. Devices with closer tolerance are available but are a great deal more expensive.

The p.c.b. track is shown in Fig. 4 and the component layout in Fig. 5. Ribbon cable is used to connect the p.c.b. to the panel meter.

APPLICATIONS

The circuit can be calibrated by comparison with another luxmeter and is capable of measuring light intensity over a very wide range, making it useful in photographic and general photometry applications. Lux readings may be converted to specific photographic values to enable the instrument to be used as an exposure meter. In the human eye the pupil of the iris adapts the area of the aperture, according to the effective luminance in the field of vision. The aperture area of the pupil acts like a variable stop, so that the solid angle for the incident luminous flux on the individual points of the retina is variable in the ratio of about 1:16. In photography, for a film of given sensitivity (ASA/DIN rating), the exposure required for a specific lux reading is dependent upon the camera aperture setting (f stop) and the shutter speed (since a fast shutter speed reduces the amount of light energy striking the film).

Shutter speeds on cameras are usually in steps of 2:1 (1/500 s, 1/250 s, 1/125 s etc.) and the aperture f stop numbers are also chosen to provide changes of aperture area in the range of 2:1 between adjacent f stop numbers, with higher numbers indicating smaller apertures. For a given lux reading, various combinations of shutter speed and aperture setting will produce the same overall exposure and the shutter speed may be selected according to subject movement etc. Examples of camera settings for ASA100/DIN21 type film are shown over.

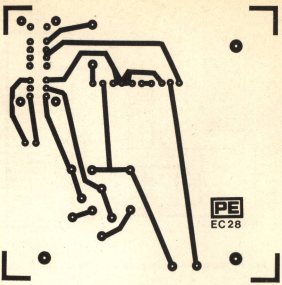

Fig. 4. Printed circuit board

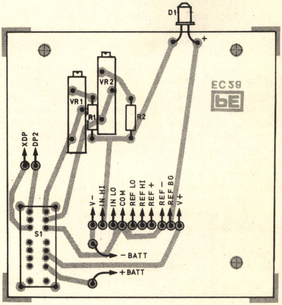

Fig. 5. Component layout

Bright Sunlight	f stop	22	16	11	8
	shutter speed	60	125	250	500

For reduced lux readings, combinations should be chosen to provide greater exposure.

Cloudy Conditions	f stop	8	5·6	4	2·8
	shutter speed	60	125	250	500

ALTERNATIVE CALIBRATION

An alternative method of calibrating the Lightmeter is to use an 18% grey scale test card which is used widely for calibration of photographic exposure meters. These meters are calibrated to read correctly when directed at the standard grey scale which is of density such that 18% of the incident light is reflected.

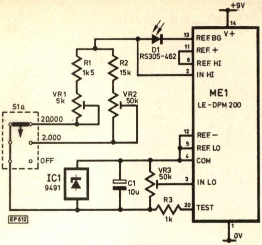

Fig. 6. Method of incorporating offset adjustment

OTHER CIRCUITS

When making low level lux measurements of luminous objects an adjustable offset control may be added to the basic circuit to remove the effects of ambient lighting or of the photodiode dark current at very low levels. Fig. 6 shows the method of incorporating an offset adjustment using a voltage divider across a bandgap reference integrated circuit.

For darkroom use the photodiode may be mounted remotely from the instrument, via screened cable, and used to measure the exposure required. The enlarger projects an image of the negative on to the photosensitive paper and the photodiode should be positioned to receive the radiation reflected from the paper. The photodiode should only evaluate the central picture content.

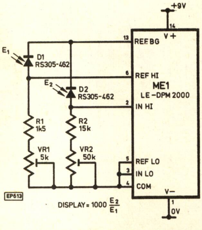

Fig. 7. Ratiometric method of measurement

RATIOMETRIC MEASUREMENTS

The versatile nature of the LE DPM200 may also be harnessed to provide ratiometric measurements, enabling the ratio of the most exposed to least exposed areas of negatives to be indicated, as shown in Fig. 7.

Ratiometric measurements are also useful in absorption experiments. Critical properties of materials, which are of particular interest in the fields of chemistry, medicine and pollution control, are characterised by absorbence. The general arrangement for absorbence measurements is

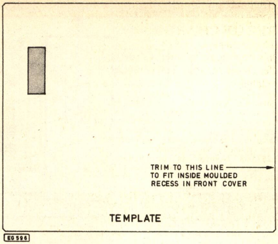
TRIM TO THIS LINE TO FIT INSIDE MOULDED RECESS IN FRONT COVER
TEMPLATE
EG596

Fig. 8. Front panel template

shown in Fig. 9. The relationship between absorbence, A, and light intensity, E, is:

$$A = \log \frac{E_I}{E_T}$$

where E_I = intensity of incident light
E_T = intensity of transmitted light

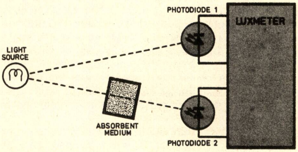

Fig. 9. Making absorbence measurement

The two photodiode inputs to the panel meter represent the intensity of light transmitted through space and through a medium that absorbs light. Relative absorption of the medium will be directly displayed and absolute absorption may be calculated if desired by taking the log of the displayed value.

COMPONENTS . . .

Resistors

R1	1k5	carbon film 5%
R2	15k	carbon film 5%
VR1	5k	multiturn preset
VR2	50k	multiturn preset

Semiconductors

D1 Photodiode RS305-462

Miscellaneous

ME1 LE DPM200 (see special offer)
Instrument case, front panel label, p.c.b., 4P3T slide switch.
Ribbon cable. PP3 battery connector

A kit of components required for the Lightmeter is available at £9.95 inc. VAT (**excluding** LE DPM200 and case) from **Lascar Electronics Ltd., Unit 1, Thomasin Road, Basildon SS13 1LH.**

HUNGARIAN MAGIC CUBE
The ultimate intellectual puzzle?

FREE OF CHARGE

With purchases over £18
(Only on request, at time of ordering)
Offer closes 31/8/81. Subject to availability.

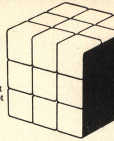

Invented by Prof. Rubik of the Budapest Academy of Design, this 3 × 3× 3 array of 27 cubes starts off with each external face of 9 unit cubes in one of six colours. Although it does not come apart, any single layer of 9 cubes can be rotated about its centre, quickly confusing the colour symmetry. Since there are 43,252,003,274,489,856,000 permutations, it may take a while to make just one face all the same colour again, and just a little longer to return it to its original pattern!

Sold separately
£3·50

CASIO VL-TONE. As featured in "TOMORROW'S WORLD" 23 April, 1981

BECOME AN INSTANT MUSICIAN – NO EXPERIENCE NECESSARY.
Create your own music with a VL-TONE. You combine the sound, rhythm and tempo and the VL-1 plays it back . . . beautifully!

VL-1 Electronic Musical Instrument and Calculator

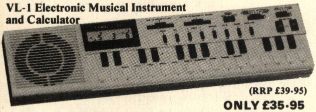

(RRP £39·95)

ONLY £35·95

VL-1: Utilizes Very Large Scale Integrated circuit advanced technology. This complete 29-note synthesiser records and plays back. The octave shift switch expands the range of the keyboard to almost 5 octaves.
Preset sounds: Piano, Violin, Flute, Guitar, Fantasy and ADSR (sound wave that can be varied in over 80 million ways).
One-key play: Record the notes of a melody. The notes are replayed in correct sequence simply by tapping the replay key and duration and tempo can be varied.
Auto play: Lets you re-listen to the melody you have played by the ONE-KEY PLAY. Manual play can also be recorded and played back. Notes are shown on the LC Display and individual notes can be added or deleted as required.
Auto rhythm: 10 built-in rhythms and a 19 step tempo control with digital readout. Can be incorporated in manual playing or added to your recording.
Facilities: LCD calculator display, note display and tempo display. Built-in amplifier and loudspeaker. Output jack. Pitch control. Battery power and light weight (438, 15·4 oz) allows playing anywhere. AC adaptor £5.
Dimensions: 30mm × 300mm × 75mm (1⅛ by 11¾ by 3″).

****** NEW CASIOTONE 202 ******

"Son of success . . . Even more impressive is the clav . . . The two harpsichords demonstrate the Casiotone's talent for sparkling, crystal clear tones". (Melody Maker). Polyphonic playing of 49 instruments over 4 octaves with 3 vibrato settings and sustain. 4 voice memory with button selection. Integral amp/speaker, pitch control. Output jacks. AC powered. RRP £325. **ONLY £275.**

OTHER CASIOTONE KEYBOARDS

MT-30 Polyphonic, 22 instruments over 3 octaves. Battery/mains (RRP £115) **£95.**
CT-301 Polyphonic, 14 instruments over 4 octaves. 8 × 2 rhythm accompaniments. Vibrato, delayed vibrato. Pitch control. Output jacks. AC only (RRP £285) **£245.**
CT-401 As CT-301 but with Casio Auto Chord for one finger or auto accompaniment. Plays major, minor and seventh chords with bass. Integral sustain and hold. (RRP £345) **£295.**

A CLASSIC IN ITS TIME

Battery powered, with integral stand. Ideal for car, caravan, boat, domestic or office use, or as a pocket watch (leatherette pouch with window included).

PQ-20 ALARM CLOCK

(RRP £14·95)
ONLY
£12·95

Large LC Display of full digital time. Symphonic alarm (Mozart, No. 40) or buzzer, with snooze facility. Hourly time signal option. Integral speaker and amplifier. Rapid setting. Accuracy ± 15 secs/month. One lithium battery lasts approx. 12 months. Dims: 9·3 × 108 × 48mm. (⅜ ×4¼ ×1⅞″). 53g (1·9oz).
MA-1 Battery Alarm Clock
Similar to PQ-20 but has blue LC Display, nightlight, 3 position volume control. 3 AA batteries last 15 months approx. Dims: 43 × 115 × 76mm (1¾ × 4½ × 3 inches). Ivory coloured case. (RRP £11·95) **ONLY £9·95**

PRICE includes VAT and P&P. Send cheques, P.O. or phone your ACCESS or BARCLAYCARD number to:

TEMPUS

Dept. PE, FREEPOST
3164-167 East Road
Cambridge CB1 1DB
Tel. 0223 312866

THESE SPACE INVADERS WILL ALARM YOU
The price won't

CASIO'S MOST AMAZING WATCHES EVER

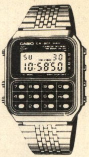

Display: Hours, minutes, seconds, am/pm, day and date. 12 or 24 hour format.
Auto Calendar: Day, date, month, year.
Alarm: 24 hour, with "On" symbol.
Hourly Chimes: Time signal every hour, on the hour. Easily switched on or off.
Professional Stopwatch: Lap times etc. from 1/100 second to 24 hours.
Dual Time: Second time zone.
Calculator: 8 digits, four functions, with constants and display symbols.
FINGER-TOUCH KEYBOARD.
DIGITAL SPACE INVADER GAME
with sound effects and scoring.
Water resistant case. Mineral glass.
CA-90: 46 × 36 × 10·55mm. Black resin (RRP £29·95) **ONLY £24·95**
CA-901: 40·5 × 35·2 × 10·5mm. Metal (RRP £34·95). **ONLY £29·95**

SUMMER TIME

Now is the time to buy a **Sports Watch** for your holidays and outdoor activities. These models (except HV027) are **WATER RESISTANT TO 100 METRES** and suitable for swimming, snorkelling, sailing and most other outdoor sports.
SEIKO DUAL DISPLAY
Analogue display of time with sweep second hand. Independent digital display of time (12 or 24 hour format); day/date calendar; 24 hour alarm function; hourly time signal; 1/100 second stopwatch. Instant setting. Luminous dial. 2 year battery life. Battery life indicator. Stainless steel case. HARDLEX glass. **JET 088.** Black outer bezel. 100 metre W/R case 36 × 40 × 9mm approx.

JET 088
100 METRE WATER RESISTANT

SAVE £35!

ONLY
£94·50

HV 027
WATER RESISTANT A BEAUTIFUL SPORTS WATCH

SAVE £17!

ONLY
£72·50

CASIO ALARM CHRONOS

W-100
Black resin case/strap
£19·95

W-150
All stainless steel
£32·50

W-150C
S/S case resin strap
£25·95

Full time (12 or 24 hour) and calendar display. Half-hourly time signal option. Alarm. 1/100 second stopwatch. Lap timing. Countdown alarm timer with repeater memory function. Time is always visible regardless of display mode. Nightlight. 9·65mm thick case. Mineral glass face. Amazing 5 year battery life.

OTHER CASIO WATCHES

Sports Chronograph: F-500, Resin £9·95. **Alarm Chrono:** F-81, Resin £15·95. **ALARM CHRONOGRAPHS: Melody A/C:** M-12, Resin £19·95. M-1200, S/S £29·95. **LCD Analogue/Digital A/C:** AA-81, Chrome £29·95. AA-82, S/S £39·95. AA-81G, Gold pl. £49·95. *** **NEW!** *** UC-50W, S/S 50 metre Water Resistant A/C with full month calendar display (forward/reverse stepping), chimes etc £19·95.

CASIO CALCULATORS

Digital space invader game: MG-880 £10·95. MG-770 £12·95. **With alarm/s calendar etc:** BQ-1100 Biolator £16·95. **With melody:** UC-360 £19·95. UC-365 £19·95. UC-3000 £27·95. ML-90 £19·95. ML-75 £17·95. MQ-1200 £19·95. ML-2000 £22·95. **SCIENTIFICS:** FX-81 £12·95. FX-100 £15·95. FX-510 £19·95. FX-2700P £19·95. FX-180P £19·95. FX-3500P £22·95. FX-502P with **FREE** MasterPack (RRP £17·95) £74·95. FA-1 Adaptor £19·95.
With clock, alarms, stopwatch etc: FX-6100 £18·95. FX-7100 £24·95. FX-8100 (also has calendar) £24·95.

SEND 20p FOR ILLUSTRATED CATALOGUE OF SELECTED CASIO AND SEIKO PRODUCTS

NOISE METER

FREE CASE PROJECT

MARTIN KENT

PE Digital Precision Sound Meter DP700

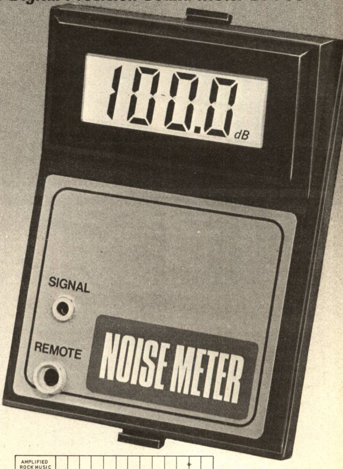

SPECIFICATION

Measurement Range	60–110dB
Resolution	0·1dB
Accuracy	0·5dB

ONE of the health hazards under constant attack by environmentalists is high sound level. In factories, offices, airports and indeed most situations where men and machines are placed together, the monitoring of sound levels is very important. If sound levels are high, then work rate can be impaired, pain may be induced and even permanent damage to hearing may be caused.

The DP700 Noisemeter is an extremely compact instrument, with very low power consumption, which measures between 60 and 110dB. True r.m.s. measurements are made by a new integrated circuit to achieve good accuracy from widely varying input waveforms. The instrument is simple to operate and will be found useful in checking sound levels at work or home. Many hobbies require the participants to be aware of sound levels including model aircraft and car rallying. Audiophiles can also use the instrument for checking sound systems and room accoustics.

SOUND MEASUREMENT

A graph of typical sound levels found in different environments is shown in Fig. 1. Intensity of sound covers an extremely wide range and if measurements are made with a conventional linear meter, then very large numbers are involved. Sound measurements are normally made on the dB scale to compress the readings and make the numbers more usable; also the human ear responds to sound logarithmically rather than linearly. It can be shown that if a certain sound level is taken as the 0dB reference, then a 120dB reading corresponds to an increase of 1,000,000:1 and long scale length instruments would be required to make such measurements.

The decibel (dB), or one-tenth of a bel (B), is defined as the logarithm of an electrical power ratio of 1.259:1. The number of dB corresponding to the ratio of two powers is given by 10 log (P_2/P_1), consequently the number of dB corresponding to the ratio of two voltages is given by 20 log (V_2/V_1) since power is proportional to the square of voltage.

The DP700 is designed to operate with an electret condenser microphone which converts sound pressure acting on a capacitive element into a voltage which is amplified by an integral i.c. amplifier.

The most accurate method of measuring alternating voltages is to determine the r.m.s. value. The majority of instruments which measure a.c. inputs employ averaging circuits which are scaled to provide r.m.s. indication provided the input waveform is sinusoidal. Sound waveforms are usually anything but sinusoidal and as the peak value moves further away from the mean (increasing crest factor) so the error in measurement using averaging circuits increases. Discrete r.m.s. measurement circuits are complex and difficult to set up due to the problem of requiring to calculate the square root of the mean sum of the input values squared.

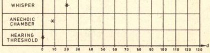

Fig. 1. Typical sound levels found in different environmental conditions.

The manner in which the corresponding dB scaling increases with voltage output from the microphone is shown in Table 1.

TABLE 1

Voltage Ratio	dB
1	0
10	20
100	40
1000	60
10,000	80
100,000	100
1,000,000	120

Table of dB scaling increases with output of microphone.

To achieve a wide span of readings a logarithmic amplifier is clearly required to convert the microphone voltage to a dB scaled voltage. Most sound level meters employ large numbers of ranges in order that approximations to the log value can be made over a narrow range. Such instruments normally employ centre-zero moving-pointer meters and can be awkward to use.

TRUE R.M.S. IC

The Noisemeter has been designed for ease of use and provides clear unambiguous indication from 60dB to 110dB without the need to change ranges. A new integrated circuit from Analog Devices, the AD636, is a laser-trimmed device which computes the true r.m.s. value of a complex input signal and produces a dB scaled output in addition to a linear output. The AD636 is designed specifically for interface with instruments such as the LE DPM200 panel meter and also requires low supply current to complement the ultra-low power of the panel meter.

The block diagram of the DP700 is shown in Fig. 2. A transistor amplifier interfaces the electret condenser microphone to the AD636 which converts the true r.m.s. value of the a.c. input to a d.c. value scaled in dB and is read directly by the LE DPM200.

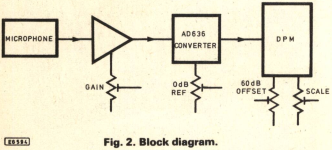

Fig. 2. Block diagram.

CIRCUIT DESCRIPTION

The circuit diagram of the Noisemeter is shown in Fig. 3. Transistor TR1 forms an input amplifier to permit a variety of microphones to be used and the input level is adjusted by VR1. The AD636, IC1, computes the root-mean-square relationship:

$$V_{RMS} = \sqrt{V_{IN}^2}$$

where V_{IN}^2 is the average of the squared instantaneous values of the input voltage over a nominal period. High crest factors of input waveform can be accepted without loss of accuracy.

The absolute value of the input signal is taken and converted to a current which is applied to a squarer circuit. The output current drives a current mirror through a low pass filter, the time constant of which is controlled by C4. The current mirror produces a current corresponding to the r.m.s. value of the input voltage and a voltage output of −3mV/dB.

The 0dB reference point is adjusted by VR2 which controls the internal reference current of the AD636. A range of 50dB is possible with the device and the panel meter reading is offset to provide a 60dB display with zero input voltage, such that the instrument is usable from 60dB to 110dB. The offset is adjusted by VR3.

Scaling of the panel meter is adjusted by VR4 which sets the reference voltage. The AD636 produces an output of −3mV/dB and the panel meter operates with a 300mV reference voltage instead of the usual 100mV. Operation of the panel meter is ratiometric such that:

$$\text{Display} = 1000\frac{V_{IN}}{V_{REF}}$$

The instrument is designed around a self-contained microphone with remote on/off switch and connected via two jack plugs. Easier access to machinery etc. is therefore provided than if the microphone element was mounted in the case. The remote on/off switch minimises the already very low current consumption of the instrument due to the use of the LE DPM200 panel meter. The microphone may, of course, be detached for use in recording or other sound systems.

ASSEMBLY AND TESTING

Very few components are required in addition to the LE DPM200 to complete the instrument. To ease the calibration, four wire links LKA-LKD are provided which should be

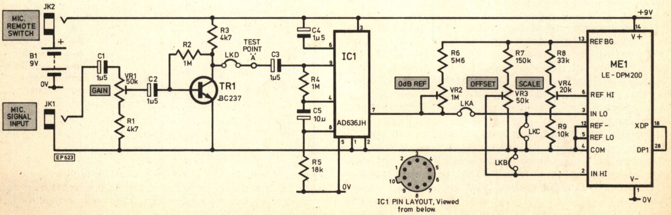

Fig. 3. Circuit of Noisemeter.

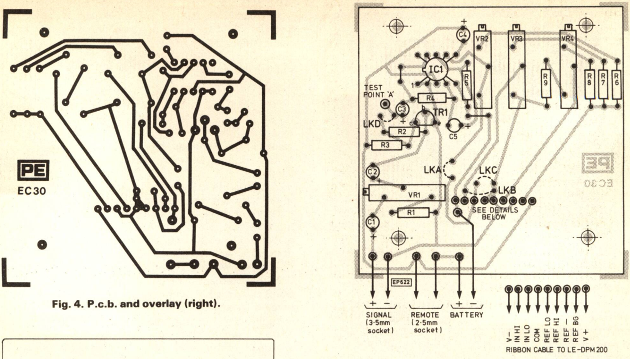

Fig. 4. P.c.b. and overlay (right).

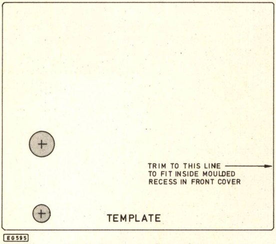
TRIM TO THIS LINE TO FIT INSIDE MOULDED RECESS IN FRONT COVER
TEMPLATE
EG595

Fig. 5. Front panel template.

omitted at this stage. When complete the pcb is connected to the panel meter by ribbon cable.

A 3·5mm jack socket mounted on the front case connects the input signal from the microphone and a 2·5mm jack socket connects the remote on/off switch. Connect the microphone to the sockets and a battery to the PP3 connector.

Testing and calibration should be carried out as follows: Ensure that link LKA connecting VR2 to IN LO is removed and then insert the link LKB to short IN HI to COM. The offset controls are now overriden, a 100mV d.c. reference voltage should be connected between IN LO and COM and VR4 should be adjusted to make the display read 33·3 to accommodate the 3mV/dB output of IC1. Disconnect the reference voltage.

Remove link LKB and add link LKC. VR3 should now be adjusted to provide a display of 60·0, corresponding to 60dB reading with zero input. Remove links LKC and LKD, add link LKA. Connect a 10mV r.m.s. sinewave of typically 1kHz between Test Point A and COM. Adjust VR2 to return the display to 60·0 to establish the 0dB reference point for the AD636. Disconnect the a.c. input and add link LKD.

Using a sound reference of typically 80dB, or comparing against another calibrated meter, VR1 should be adjusted to provide the correct reading for the particular microphone used. ★

COMPONENTS . . .

Resistors

R1	4k7	Carbon film 5%
R2	1M	
R3	4k7	
R4	1M	
R5	18k	
R6	5M6	
R7	150k	
R8	33k	
R9	10k	

Variable Resistors

VR1	50k	Multiturn presets
VR2	1M	
VR3	50k	
VR4	20k	

Capacitors

C1	1µ5	Tantalum Bead 16V
C2	1µ5	
C3	1µ5	
C4	1µ5	
C5	10µ	16V elect.

Semiconductors

TR1	BC237	
IC1	AD636JH	(Lascar Electronics)

Miscellaneous

ME1 LE-DPM200 (see special offer). JK1 3·5mm jack socket. JK2 2·5mm jack socket. PP3 battery connector, instrument case, p.c.b., ribbon cable. Microphone electret condenser with remote switch type and preamp YB, 33L. A complete kit of components for the Noisemeter is available at £29.95 inc VAT (excluding LE-DPM200 and case) from **Lascar Electronics Ltd, Unit 1, Thomasin Rd, Basildon, Essex, SS13 1LH.**

SAXON FOR ALL YOUR DISCO/P.A. NEEDS

STEREO DISCO SYSTEMS

100-600W COMPLETE WITH LIGHT SHOW

ABSOLUTELY COMPLETE

FEATURES:
- ★ MIC/TAPE INPUTS
- ★ CROSSFADE
- ★ SLAVE OUTPUT
- ★ FULL MONITORING/CUE LIGHT
- ★ WIDE RANGE BASS/TREBLE
- ★ FOUR CHANNEL SOUNDLIGHT

PLUS!! BUILT IN LIGHT DISPLAY – 2 YEAR WARRANTY
ONLY 20% DEPOSIT – TYPICAL APR 36%.

STANDARD CENTAUR 100W	**£345**	Dep. only £69
SUPER CENTAUR 200W	**£425**	Dep. only £85
GXL CENTAUR 200W	**£545**	Dep. only £109
CUSTOM CENTAUR 400/600W	**£945**	Dep. only £189

GXL CENTAUR

SEE OUR CATALOGUE for other exciting combinations of consoles and loudspeakers – **ONLY £1** – INCLUDES £30 WORTH FREE VOUCHERS – over 3000 systems now in use. Please telephone for details of carriage charges – area decides cost.

LIGHTING EQUIPMENT

PLUTO P140 projector C/W wheel **£57.50** carr. £1.50
PLUTO P250 projector C/W wheel **£94.90** carr. £1.50
PLUTO P500 projector C/W cassette **£115** carr. £2.50

FULL RANGE OF WHEELS, ADD ON ATTACHMENTS ETC IN OUR CATALOGUE

★ 22′ Rope Light **£39.50.** ★ Rope Controller with Sound/Lite **£19.75.** ★ The pair only **£55**
★ 4 CH Sound/Lite sequencer plus dimmers **£55** ★ 3 CH Sound/Lite **£39.50**
★ PLUTO Rhythmatic Super Rope Light Controller 4kW For/Rev/Auto functions **£69.50**
★ DJ ELECTRONICS 10 way chaser 32 programmes plus Sound/Lite plus Auto Bargain Price **£149**
★ DJ ELECTRONICS Auto Zoner 64 programme matrix unit. Similar to PE STARSPINNER **£225**

Carr. on all lighting controllers 90p.

Lightomation Freeze Flasher Strobe	**£64.75** carr. £1.50
Lightomation Super Freeze Flasher Strobe	**£99.75** carr. £1.50
Bulgin Plug/Socket 8 way	**£4.25** carr. 50p

Saxon Light Boxes. Match consoles & loudspeakers.

4 way 800 watt	**£55** carr. £4
3 way 600 watt	**£45** carr. £4
5 metre Multiway Lighting Lead	**£12.50** carr. £1

Boxes include lamps

FIRST CLASS CONSTRUCTIONAL PROJECTS – GLASS FIBRE PCB – FULL INSTRUCTIONS

LIGHTING KITS

Carr. on all kits 90p.

LK 1	**£9.90**	3cm 300W/ch 1V-100V input
LK 2	**£17.90**	3 channel 3kW zero voltage switched fully automatic level control 200mV-100V input.
LK 3	**£9.80**	2kW slider dimmer suitable for Pubs, Clubs etc. C/W face plate – suppressed – 15A triac.
LK 4	**£17.90**	4 channel 4kW sound-lite sequencer with for./rev./auto functions. Ideal for rope lights *or* spot banks.
LK 5	**£11.50**	4 channel rope light controller with sound-lite – Handles up to 20 ropes.
LK 6	**£7.50**	2 channel domestic automatic controller with built-in microphone – runs 4 or 6 bulbs.

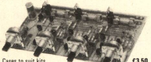

Cases to suit kits	**£3.50**
100W spots (state colour)	**£1.50**
Coloured pigmy lamps	**65p**
Rope lights 22′	**£39.50**

EFFECTS UNITS

'SAXON SMASH'
Connect between mic amp. – Press button for Alien Voice effect.
£9.75

'SAXON KLAXON'
4 siren effects for the price of 2
US Police UK Police
Hawaii 5-0 Destroyer
£19.75

'SAXON SIREN'
Single siren – State which required – US, UK or Hawaii Police or Destroyer
£9.75

MELOS MC350 Echo Chamber **£77.50** carr. £2.50 MELOS DE1 Digital Echo **£89.90** carr. £2.50

MIXER KITS

BUILD YOUR OWN DISCO!!

MONO DISCO MIXER **£19.75**
STEREO DISCO MIXER **£29.75**

EACH MIXER FEATURES:
★ Twin deck controls + Crossfade ★ Tape inputs ★ Mic input with Bass/Treble ★ Autofade circuitry & controls ★ Wide range tone controls ★ Ample monitor power front panel to suit **£3.50** – Supply for mains operation **£7.50.**

SPECIAL OFFER – LIMITED QUANTITY – DJ ELECTRONICS

'SUPREME' LIGHT UNIT

★ 3 channel 3kW ★ Individual bass/mid/treble ★Variable speed sequences
★ Additional effects of flowlight and override ★ Fully guaranteed.
Originally sold at **£89** we have a few of these great units at **ONLY £49.**
SEE THIS MARVELLOUS UNIT AT OUR SHOWROOM

MICROPHONES

ELECTRET

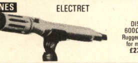

EM506
600 ohm/50k.
Top quality
Disco mic.
£24.30

ELECTRET

DI501
600Ω/50k.
Rugged. Value
for money.
£23.80

MIXERS

MX 680 STEREO

- ★ 5 channels, 2 phono, 2 tape, 1 mic.
- ★ Headphone monitor
- ★ All slider controls

£49.50
carr. £1.50

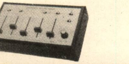

STEREO

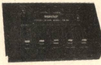

SM500 5 channel Disco Mixer
- ★ Magnetic cartridge inputs (2)
- ★ Mike plus 2 tape inputs
- ★ Twin VU meters plus record output
- ★ Switched headphone monitor
- ★ Mains powered

£54.50 plus carr. £1.50

P.A. GEAR

A FULL RANGE OF EQUIPMENT TO SUIT YOUR GROUP/PUB/CLUB ETC.

AP100 **£72** carr. £2.50
4 mixed inputs plus bass/treble master controls – 100W output.

AP200 **£119** carr. £3.50
6 mixed inputs on 3 channels – 3 sets bass/treble plus master plus presence 200W output plus slave output.

1×12 P.A. CAB. **£79** carr. £4
12″ 100W driver plus twin piezo horns – 100W handling.

2×12 P.A. CAB. **£116** carr. £5
2×12″ units plus twin piezos 200W RMS handling.

20% DEPOSIT TERMS AVAILABLE (See below)

LOUDSPEAKER CABINETS

THE AMAZING PDF BIN **£125** carr. £5.00
(illustrated opposite) 100W reflex CAB with twin horns – Very efficient and very loud and low distortion due to the cabinet design – Ideal for Discos.

WE HAVE A COMPLETE RANGE OF LOUDSPEAKERS IN CABINETS **FROM £30** – CALL IN AND SEE OR PHONE FOR DETAILS.

DRIVE UNITS

12″ 100W SAXON DRIVER 4/8/16 ohm
£24.50 carr. £1.50

★ Piezo Horns **£5.45** carr. 40p ★ 12″ Fane Crescendo 100W **£55** carr. £1.50 ★ 15″ Fane Crescendo **£69** carr. £2.50 ★ 12″ 50W Saxon Driver **£19.50** carr. £1.50 ★ 12″ 600 mans pro. 12 80W **£29** carr. £1.50 ★ 15″ Baker **£47.50** carr. £2.50 ★ Fane J104 50W horn **£15.50** carr. 50p ★ Fane 18″ 150W Crescendo – FEW ONLY AT **£89.50** carr. £3.

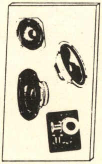

UNREPEATABLE HI-FI BARGAIN 3 WAY LOUDSPEAKER KIT C/W BAFFLE (pre-cut)

Comprises:
- ★ 25Hz-30KHz response
- ★ 6½″ linen surround bass unit
- ★ 5″ mid-range unit
- ★ 3″ tweeter
- ★ 3 way crossover, fixing screws and baffle
- ★ 20 watts handling capability – 8 ohm system

Full instructions provided
Must be heard to be believed!!

£10.50 or 2 for £20
Carr. £1.25 per kit.

ACCESSORIES

Carr. on accessories £1.50 unless otherwise stated

★ Disco Stand P&N Style	**£26.75** carr. £2.50
★ Stereo Headphones	**£7.50**
★ Flexilites	**£5.50**
★ Floor Mic. Stand	**£12.90**
★ Boom Arm	**£8.95**
★ Desk Stand	**£4.50**
★ Transformer to suit	**£3.50**
★ 12″ Goose Neck	**£5.65**
★ 6m Curly Lead	**£2.45**
★ 5m L/Speaker Lead	**£2.45**
★ Goose Neck Base	**£2.70**

★ DJ Electronic Jingle Machines reduced to **£95** with 16 Jingles – **SNIP!**

CABINET & KIT FITTINGS

★ ICI 'Hide' Vynide 50″ wide	**£4.75**/m
★ Kick Proof Grille 50″ wide	**£4.75**/m
★ ICI 'Vox' Vynide 50″ wide	**£4.75**/m
★ Aluminium Cabinet Trim	**35p**/St.
★ Blue or Black insert for Ali Trim	**7p**/St.
★ Plastic corners	**20p**
★ Strap handle	**70p**
★ IEC mains lead	**£1.20**
★ Heavy duty foot	**20p**
★ Metal corners	**30p**
★ H/duty strap	**£1.75**
★ IEC chassis plug	**50p**
★ L.S. cable	**20p**/m
★ Recess plates	**20p**
★ Mono jack plug	**30p**
★ Ventilation grille	**60p**
★ 6 way cable	**75p**/m
★ Pocket handle	**50p**
★ Stereo jack plug	**45p**
★ Mono/stereo jack skt	**35p**
★ Screened lead	**20p**/m

Carr. 50p min plus 5p in the £.

CREDIT TERMS AVAILABLE ON ORDERS OVER £100

20% deposit – Ring Sue on (01) 689 7826 and ask for a written quotation.
12-24 months to pay – typical APR 36%
or
INTEREST FREE OVER 3 MONTHS
(Discount vouchers invalid on interest free deals)

AMPLIFIER KITS

Well proven kits for a range of quality amplifier modules from 30W-240W.
- ★ Full short/open circuit proof
- ★ 4 or 8 ohm operation
- ★ High sensitivity – 240mV (—10dB)
- ★ 20Hz-30KHz response
- ★ Complete with heatsink and sockets
- ★ Match most mixer/preamps inc. our own make

BEAT THESE PRICES!!

240W AK1 **£19.75** carr. 90p
POWER SUPPLY PK1 **£14** carr. £1.50

120W AK2 **£12.75** carr. 70p
POWER SUPPLY PK2 **£9.90** carr. £1

60W AK3 **£7.90** carr. 70p
POWER SUPPLY PK3 **£6.90** carr. 90p

POWER SUPPLY KITS **INCLUDE** impregnated mains transformer – mains fuse – smoothing etc.

VISIT OUR SHOWROOMS AT CROYDON & SEE OUR WIDE RANGE OF EQUIPMENT

ONLY £1 GETS YOU OUR LATEST CATALOGUE OVER 250 LINES **PLUS** £30 WORTH DISCOUNT VOUCHERS

SAXON ENTERTAINMENTS (Dept PE)
327/333 Whitehorse Road,
Croydon, Surrey CR0 2HS.
Mon-Sat 9am-5pm
(LICENSED CREDIT BROKERS)

MAIL ORDER (01) 684 8007
CREDIT LINE (01) 689 7826
Send cheques or crossed PO's or ring (01) 684 8007
for COD, ACCESS or BARCLAYCARD
We deliver anywhere UK/N. IRELAND/W. EUROPE

ALL PRICES INC. VAT

Access VISA

MICRO PROMPT

The hardware and software exchange point for PE computer projects

IT DOES BOTH!

Sir—Without an assembler, the easiest way to store machine language programs is as a BASIC program of DATA statements, and poke them into the correct memory locations. Unfortunately this requires the conversion of hex instructions into decimal numbers and the writing of the BASIC program. The HECDEC program does both!

Simply enter the instructions as pairs of hex digits separated by Return and enter "X" to mark the end of the data. The BASIC program will then be sent to the cassette. Then LOAD the program back and add any necessary POKE instructions.

Comments on the program:
Line 30 set the dimension of B as required.
Line 40 two hex digits *must* be entered.
Line 70 X terminates the data entry.
Line 160 six DATA items per line.
Line 200 an option to retransmit the program. RETURN exits.

No check is made for illegal data entry, this could be added if thought necessary.

```
 10  REM HECDEC PROGRAM
 20  REM NOEL CAFFREY JAN
     1981
 30  K= 1: DIM B(200)
 40  INPUT "HEX DATA . . ."; A$
 50  I =1: N = 0
 60  S$ = MID$ (A$,1,1) : C =
     ASC(S$)
 70  IF S$ = "X" THEN GOTO 130
 75  IF LEN(A$)><2 THEN PRINT"
     ERROR . . . RE-ENTER":
     GOTO 40
 80  IF C< = 57 THEN N = N +
     C–48
 90  IF C>57 THEN N= N + C–55
100  IF I= 2 THEN GOTO 120
110  I= 2:  N=N*16: GOTO 60
120  B(K) = N: K = K + 1: GOTO 40
130  PRINT ":TURN ON TAPE
     RECORDER": SAVE
140  FOR I = 1TO 10000: NEXT
150  L = 1000: PRINT L; "DATA"; :
     FOR I = 1 TO K–1: PRINT B(I);
160  IF I/6 <>INT(I/6)THEN GOTO
     180
170  L = L + 100: PRINT: PRINT L;
     "DATA";: GOTO 190
180  PRINT ",";
190  NEXT
200  PRINT:  INPUT":ANOTHER
     COPY"; W$
210  GOTO 150
```

Noel Caffrey,
Castleknock,
Co. Dublin.

SCROLL CONTROL

Sir—While writing a program to convert hexadecimal to decimal and vice-versa for my UK101, it became apparent that it was not possible in BASIC to prevent the screen rolling up and leaving the input message on the screen. (At least, this could not be done within a reasonable time.) As this was required, I wrote the following program which enables one to leave the input message on the lowest line of the screen and only the resulting output is rolled up. It does however require a machine code routine. The accompanying program shows how the procedure works and uses the trivial (but short!) example of finding a square-root. Some of your readers may find this useful, especially for "conversion-type" programs; the output is very neat and uncluttered.

The routine as given works on an 8k machine, memory should be restricted to 8100 bytes at start up. The machine code is stored at 1FA4 to 1FC6. For a 4K machine lines 35 and 400 should be altered to read:—

```
35 POKE 11, 210: POKE 12, 15
400 DATA 4050, 35
```

The machine code then starts at 0FD2, memory should be restricted to 4050.

In passing it may be worth noting that in my hex. to dec. program I had to ensure that any input was valid by inputting it into a DIM field, this prevents any "REDO" messages being put out by the interpreter which would spoil the effect.

```
 10 REM NEAT OUTPUT ROUTINE
 20 REM BY S.F.J.

 30 GOTO 50
 35 POKE 11, 164: POKE 12, 31
 40 LET X = USR(X)
 45 RETURN

 50 READ SP, N1
 60 FOR I = 1 TO N1
 70 READ RE
 80 POKE SP, RE
 85 LET SP = SP + 1
 90 NEXT
100 FOR I = 1 TO 15: PRINT: NEXT
110 INPUT "INPUT NUMBER"; N
120 IF N < = 0 THEN 300
130 LET S = SQR(N)
140 GOSUB 35
150 PRINT TAB(10); N; TAB(25); S
160 PRINT TAB(10);
170 FOR I = 1 TO 25
180 PRINT CHR$(132);
190 NEXT
200 PRINT
210 GOTO 110
300 GOSUB 35
310 PRINT TAB(10); N; TAB(26);
    "INVALID!"
320 GOTO 160
400 DATA 8100, 35
410 DATA 169, 0, 170, 169, 64
420 DATA 168, 169, 191, 133, 225
430 DATA 169, 211, 133, 226, 161
440 DATA 225, 145, 225, 198, 225
450 DATA 169, 255, 197, 225, 208
460 DATA 244, 198, 226, 169, 207
470 DATA 197, 226, 208, 236, 96
```

Stephen Jaworski,
Walsall.

POOLS AID

On a light hearted note, here is a program which turns your UK101 into a punter's aid. Beats a blindfold and pin!

```
 10 INPUT "HOW MANY
    MATCHES ARE ON THE
    COUPON"; U
 20 INPUT "HOW MANY LINES DO
    YOU WISH TO ENTER"; V
 30 INPUT "HOW MANY
    MATCHES TO BE CHOSEN PER
    LINE"; W
 40 DIMA(W): L=INT
    (W*RND(1)+V)
 50 FOR T=1TOL: PRINTTAB(19)
    "THINKS": FORX=1TOW
 60 B=INT(U*RND(1)+1): FORY=
    1TOW: IFA(Y)=BTHEN60
 70 NEXT: A(X)=B: NEXT: FORZ=
    1TOW: FORQ=1TOW
 80 IFA(Q)<A(Q–1)THENS=
    A(Q): A(Q)=A(Q–1): A(Q–1)=S
 90 NEXT: NEXT: FORY=1TOW:
    1FT>L–VTHENPRINTA(Y);
100 IFY=WTHENPRINT
110 NEXT: NEXT: PRINTTAB(30)
    "GOOD LUCK": END
```

It will be noticed that an inefficient ranking method is used at 70–80. This adds to the suspense by slowing the execution considerably, so that a typical run may take about a minute.

The writer will be happy to accept 0·01% commission from winners of half-a-million or so.

R. J. Newman,
Chesham,
Bucks.

WARM START INTERRUPT

Sir—Concerning Mr. N. Climpson's Screen Editor on tape, from the July 1980 edition of Practical Electronics, I am sure I am not the only one who becomes infuriated when POKE 536, 45:POKE537,31 has to be typed in every time the machine is warm-started, to re-activate the editor. Hence I have designed a very simple machine code routine, which will re-activate the editor automatically after a warm start:

```
50076 DATA 169, 45, 141, 24, 2, 169, 31,
      141, 25, 2, 76, 116, 162
50078 FOR I=546 TO 558:READ
      A:POKEI, A:NEXT
50080 POKE01, 34: POKE 2,2
50082 NEW
```

(This should be added on to the end of the editor, and saved as a whole.)

All this does, is point the jump to warm start (addresses 0000–0002) to a simple routine to put 45 and 31 into addresses 536 and 537, respectively and then jump to address A274 to warm-start.

This method of interrupting the warm-start can incorporate any routine (for example to re-activate the error message program of D. J. Anderson, see September PE). I hope this will be useful.

Martin Stiby,
Dunstable.

TRACE PROBLEM WITH CEGMON

Sir—Mr. Beckett's TRACE program works very well on the standard UK101, and promises to be very useful. With the CEGMON, however, there seems to be a problem, and I wonder if anyone can help.

When the TRACE program is loaded and X = USR(X) entered one of three things happens:

1. TRACE operates as intended. This happens rarely, maybe due to some random store contents not under control.

2. The keyboard locks up, and nothing further can be done.

3. TRACE operates only while the space bar is held down, and single stepping (a potentially useful feature) can be achieved by pressing and releasing the space bar.

Occasionally both 1 and 3 are available. Pressing any key makes the subject program run continuously with TRACE, and pressing the space bar stops it.

The trace program given with the CEGMON is inferior, since it destroys the printing format, and especially with graphics one cannot follow what is going on.

R. J. Newman,
Chesham,
Bucks.

DYNAMIC CHANGEOVER

Sir—I refer to the letter "2MHz Conversion" in Microprompt, Practical Electronics, September, 1980. You note that the 1MHz/2MHz changeover switch cannot be used while the machine is working. The circuit below allows this frequency change to be performed while running. It is not infallible, but if the machine does hang up, Reset followed by Warm Start will usually restore the program.

The 7400 is wired as a pair of cross-coupled NAND gates, to debounce the frequency change switch. The output is used to drive the 74157, feeding either 1 or 2MHz to pin 9, wired to 00 (pin 37 of IC8, 6502).

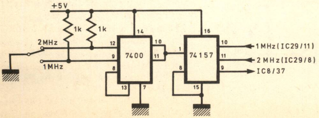

Break existing link between IC29/11 and IC8/37.

With reference to the new monitor for the UK101, I have found that programs recorded at 600 baud often show corruption when being loaded (the 50th character of a line repeats the 49th) if the machine is running at 1MHz. The problem disappears if 2MHz is used. Has anyone else noticed this? The original monitor does not show this problem.

D. P. Goulder,
Comberton,
Cambs.

PRINTER INTERFACE?

Sir—I wish to interface a Centronics printer to my UK101 and wondered if this could be done using the PE decoding module. If so, how? I would appreciate details on how to do this if it is possible.

N. Odell,
Sheffield.

PS: The printer requires seven data bits and Strobe, Acknowledge and Busy lines are provided.

REPLY

Yes there is nothing that cannot be done with the Decoding Module!

You could drive your printer from Port B of the PIA, though you may need to buffer each data line with something like 7407 gates.

To get it to print, you will need to take the strobe line low while data is on the output of the port. One way would be to connect bits 0-6 of the PIA directly to the 7 data lines of the printer (possibly via a buffer), and to connect bit 7 of the PIA to your strobe line.

Take the busy line to CB1, of the PIA and then all you need is some software. This will be a short program which picks up the SAVE vector and:

1) Configures the PIA for output on port 1
1a) Puts bits 7 high
2) Monitors the busy line (on CB1) until it is not busy
3) Outputs the character in the Accumulator to the port.
4) Takes bit 7 low, then high again to perform the strobe
5) Loops back to the UK101 output routine

This would be a fairly short machine code routine that could be located in the spare space at 0230 hex.

D. E. Graham.

IMMEDIATE ERROR BANISHED

Sir—One minor irritation on the UK101 Superboard is the OM error message after the first command in immediate mode having just returned to BASIC from the monitor. This is especially annoying whenever a long instruction has been used, such as

```
FOR X = 7000  TO  8191  :  PRINT
          CHR$(PEEK (X) ); : NEXT
```

Here is a patch of six bytes to avoid the OM error. The stack pointer is set to 255 (FF in hex) before the warm start.

```
0000   4C   FA        20JMP $02FA ;
                        TO THE PATCH
02FA   A2   FF          LDX # $FF
02FC   9A             A2TSX
02FD   4C   74          JMP $A274
```

The BASIC program pokes the patch into place.

```
5 REM TO AVOID OM ERROR MESSAGE
10 FOR X = 762 TO 767 : READ Z :
   POKE X,Z : NEXT
15 POKE 1,250 : POKE 2,2
20 DATA 162, 255, 154, 76, 116, 162
25 END
```

Robin H. Tracy,
Coventry.

STRING ANSWER

Sir—In response to R. J. Newman's query in the May 'Microprompt' the function STR$(X) is so designed that a leading blank (ASCII=32) will be inserted into the string from STR$(X) unless the number to be converted is negative—in which case the leading blank will be replaced by a minus sign (ASCII=45).

Eg.

```
100  X = –8 : X$ = STR$(X)
110 PRINT X$; ":" ;
120 PRINT ASC(X$) ; ASC (MID$(X$, 2,
     1))
RUN
–8 : 45 56
```

Christopher Davies,
Hove,
East Sussex.

TAPE VIEWER

Sir—Mr. Derry's letter (PE November 1980) was most welcome to one who has been making clumsy attempts to add auto-run to Basic programs. It would be useful to add that POKE 515,0 should be the first executable instruction in any auto-run program, so that other data on tape will not load and foul up the program.

His section on RAMless messages sent me to Edward H. Carlson's book "All About OSI BASIC in ROM" (Edward H. Carlson, 3872 Raleigh Dr, Okemos, Michigan 48864, USA) which inspired the following program for reading messages and programs without loading them into memory.

```
1 A=61440 : B=A+1
2 WAIT A,1 : ?CHR$ (PEEK(B)); :
GOTO 2
```

RUN the program, use CTRL/C to exit. (It may be necessary to stop the tape if unmodulated tone is playing through.) No error messages, no use of RAM (other than VDU RAM), and no waiting for ten minutes while EXMON loads! Any desired program line or message can be taken from the screen using one of the screen editors now available.

Mitch Park,
New Zealand.

E/MONITOR RELOCATED

Sir—In response to Mr. Walton's enquiry in the January 81 issue in Micro Prompt, I have successfully relocated the Extended Monitor to run at $1800–$1FFF leaving 6K below it.

The Extended Monitor uses an address table to select the function required. The ASCII value of the letter typed in is converted into an index which points to an address within the table. The 2 bytes of the address are fetched and pushed onto the stack, followed by the Processor Status Word. Control is then passed to the subroutine by executing an RTI (Return from Interrupt) instruction. The return address for the subroutine has been pushed onto the stack prior to this.

The address table is located at $0960–$0999 and is shown in Fig. 1. The procedure for successful relocation is as follows:

(1) Make a new copy of the program at the required location using the relocation facility.

(2) Determine the relocation constant (the amount by which the starting address has been increased), e.g. to locate at $1800, the relocation constant is $1000.

(3) Add the relocation constant to $0960 to give the base address of the new address table. Also, add the relocation constant to the addresses stored within the table.

(4) Step through the table starting at the base address you have calculated and change all the incorrect table entries (this will be most of them).

Character	Table Address	Contents
@	0960	0B53
A	0962	0BB3
B	0964	0C9A
C	0966	0CBF
D	0968	0CD2
E	096A	0C57
F	096C	0DA3
G	096E	0BC1
H	0970	0E33
I	0972	0C12
J	0974	0809
K	0976	0BAF
L	0978	0F43
M	097A	0D91
N	097C	0D35
O	097E	0F29
P	0980	0BB0
Q	0982	0D14
R	0984	0DB7
S	0986	0EC3
T	0988	0C6E
U	098A	084C
V	098C	0F3B
W	098E	0D7E
X	0990	0BB2
Y	0992	0BB1
Z	0994	0FB7
Return Address	0996	081E
Brkpt. Routine	0998	0BC7

Fig. 1 Extended Monitor Address Table

The new version of the Extended Monitor is now ready to run. If after jumping into the new version, all seems well, make sure by erasing the old version using "Fill".

Fig. 2 shows the table values required to run at $1800 and incorporates the following changes:

J transfers control to $0300

U Jumps to Cold Start Basic ($BD11)

Z jumps to the old monitor at $FE00

Having relocated the Extended Monitor, you now need to either burn it into EPROM or else make a new self-executing tape. As the procedure for making a new tape is rather long, I suggest that anyone wishing to know how to do this should write to me (via PE—Ed).

John Riley, B.Sc.,
Coventry.

Character	Table Address	Contents
@	1960	1B53
A	1962	1BB3
B	1964	1C9A
C	1966	1CBF
D	1968	1CD2
E	196A	1C57
F	196C	1DA3
G	196E	1BC1
H	1970	1E33
I	1972	1C12
J	1974	0300
K	1976	1BAF
L	1978	1F43
M	197A	1D91
N	197C	1D35
O	197E	1F29
P	1980	1BB0
Q	1982	1D14
R	1984	1DB7
S	1986	1EC3
T	1988	1C6E
U	198A	BD11
V	198C	1F3B
W	198E	1D7E
X	1990	1BB2
Y	1992	1BB1
Z	1994	FE00
Return Address	1996	181E
Brkpt. Routine	1998	1BC7

Fig. 2 Address Table for Extended Monitor at $1800

M/C FOR PSG

Sir—When using the programmable sound generator, it soon becomes apparent that machine code is much faster and more efficient on memory than BASIC. But even here, with several more complex sound effects, some sort of loader is required. The following program takes data from a table and loads it into the PSG registers. Put the starting address of the table in $E0, $E1 (lo byte first). The table should follow the format:

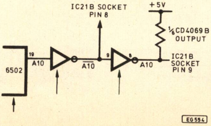

REGISTER
CONTENT
REGISTER
CONTENT
REGISTER
CONTENT
$FF

To execute .GO222

```
0222  A000        LDY#$00
0224  B1E0        LDA($E0),Y
0226  C9FF        CMP#$FF
0228  D001        BNE$022B
022A  60          RTS
022B  8DF0F1      STA$FIF0
022E  C8          INY
022F  B1E0        LDA($E0),Y
0231  8DF1F1      STA$F1F1
0234  C8          INY
0235  18          CLC
0236  90EC        BCC $0224
```

The addresses at $022C-D and $0232-3 will need altering for PSGs not located at $F1F0 and $F1F1.

T. D. Allen,
Poole.

OVERLOADED BUS

Sir—There is a fault in the UK101 circuit which may well have put a number of computers into cupboards gathering dust. It concerns the loading on the address bus line A10. This processor line is very heavily loaded with LSI integrated circuits (16 RAM inputs and 5 ROM inputs). It is also expected to drive one full t.t.l. load, namely IC21b – $\frac{1}{16}$ of a 7404.

I had rather a lot of problems getting my UK101 to work – 5 or 6 faulty t.t.l. circuits and a solder bridge which destroyed two 74123s. Since getting it working, one ROM and three RAMs have failed. My own preference for a Buffer, after giving considerable thought to the subject, is to use a 74LS output with a pull up resistor to the +5V line. This resistor should ideally be a constant current resistor and I've realised that $\frac{1}{16}$ of a CD40698 with input shorted to earth is the ideal sort of resistor – the gate output, of course.

The circuit I propose to use is shown below left, and I welcome comments on this.

On further consideration of the UK101 circuit I realize that the processor R/W line needs similar treatment. A8 and A9 also look poor, but I would guess that IC171, a 74LS139, has inputs which cause fewer problems.

There are some spare t.t.l. inverters available in IC18 so all one really needs is a CD40698 to make these changes, though I will have to open the case of my UK101 to check this.

J. D. Owen,
Pendine, Dyfed.

VARIABLE INTENSITY

The tone control occupies 1K of memory between D400 and D800 (just after the video refresh memory). To save space and money the unit uses the address decoding of the UK101. A $\overline{SEL}$ signal is derived from pin 9, IC20, which decodes A10, A11 and A12, A13, A14, and A15 (via IC23). The unit also uses the video address bus (VA0>VA9) and is therefore wired to the compukit board and not taken via the expansion sockets.

$\overline{SEL}$ takes the 2114s $\overline{WR}$ low, enabling data to be written into the 2114 through an LS243 (tristate buffer) which is enabled by SEL. $\overline{SEL}$ is also required to take control of the VA bus from the binary counters. This is also the function of $\overline{VA}$ (pin 6, IC56) for the video refresh memory. $\overline{VA}$ and $\overline{SEL}$ are therefore decoded and a new signal $\overline{VAS}$ (video address select) is formed. The p.c.b. track to pin 6, IC56 must be cut for this function.

In normal operation the binary counters address the 2114 through the VA bus. The data corresponding to the location's intensity then appear on the 2114's data bus. This bus is directly connected to the D-to-A converter (non latching). NB: The DAC 3851 used gives a current output, and so a trimpot is used to obtain the correct voltage. Some modification may be required for D/A converters with voltage outputs.

A point worth noting about the Compukit's video circuitry is that reverse characters, i.e. black on white, is available from pins 4 and 5 of IC70; this is much clearer for test than the standard white on black display. It is well worth having this feature switch-selectable or even programmable by 'POKEing'.

R. Mark Charles.

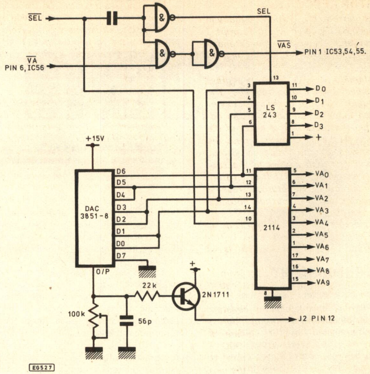

Extra Cases!

30p (plus postage) To Regular Readers.

FOLLOWING the Free Case gift with the May issue we have a quantity of cases available as extras to regular readers (at UK and BFPO addresses only) for 30p plus postage—the normal price from Lascar is £1.95 plus VAT and postage.

Extra cases—as used to house the Light, Noise and Capacitance Meters published in this issue—can be obtained from PE by sending in two correctly filled-in case coupons (name and address on both coupons please) **cut from PE,** a 30p postal order and a 15½p stamp (a case coupon is given here, another will be given next month). **We can only accept 30p postal or money orders** (NOT CURRENCY OR CHEQUES). Do not enclose any correspondence. **Incorrect or incomplete orders will not be accepted**—your stamp will be used to return them.

Send two completed case coupons cut from PE with your 30p postal order (payable to IPC Magazines Ltd), and a 15½p stamp to:

PE Instrument Case Offer, IPC Magazines Ltd., Westover House,
West Quay Road, Poole, Dorset. BH15 1JG.

Sorry we cannot undertake to send extra cases to overseas readers.

PLEASE ALLOW 28 DAYS FOR DELIVERY.

PE CASE COUPON

I enclose two completed case coupons cut from PE, a 30p postal order made payable to IPC MAGAZINES LTD., and a 15½p stamp. Please send me an extra instrument case.

NAME..............................

ADDRESS..........................

....

....

....

Only available to UK and BFPO addresses, allow 28 days for delivery. Incorrect or incomplete orders will be returned.

PATENTS REVIEW...

Copies of Patents can be obtained from:
the Patent Office Sales, St. Mary Cray, Orpington, Kent. Price £1·45 each.

SONIC HOLOGRAPHY

The second patent application from Robert Carver of the USA (WO 80/02219), filed under the Worldwide Patent Cooperation Treaty, gives hitherto undisclosed details of what the Carver Corporation sells in the USA as the "Sonic Hologram Generator". This exotic description has irritated some reviewers. But those who have heard the Carver sonic holography pre-amplifier in action confirm that it is capable of producing a surprising surround of sound from ordinary stereo recordings and just two loudspeakers fed from a stereo amplifier. The sonic holography patent, like the Carver amplifier patent referred to last month, is lengthy (nearly 150 pages including drawings) so also like the amplifier patent can cost up to £20 to buy. But it is, like all patents referred to in this column, available for free inspection at those libraries in the United Kingdom (e.g. the Science Library at the London Patent Office) which offer the public access to a full collection of British and foreign patent applications.

The holography patent postulates theories on audio reproduction which will not be accepted by all engineers. Essentially Carver argues that stereo reproduction through a pair of loudspeakers can be improved if the natural cross talk between loudspeakers is eliminated. It is of course inevitable that both ears of the listener will pick up sound from both loudspeakers, whereas anyone listening through headphones will hear the left channel only through the left ear and so on. It has previously been shown by various workers that binaural recordings made with a dummy head system (microphones set in the ears of a dummy head) and intended for replay through headphones, can be successfully reproduced through loudspeakers if there is electronic compensation for acoustic cross talk. Carver is in effect proposing a similar, but refined, technique to enhance the loudspeaker reproduction of recordings intended for *loudspeaker* reproduction. But it is clear that his thinking centres on recordings made in a typically transatlantic fashion.

Figure 1 shows how instruments 12a–g of an orchestra are recorded using a spaced pair of microphones M1, M2. Figure 2 shows how the recording is then replayed to a listener P through spaced loudspeakers LS, RS. It is here important to note that the use of the widely spaced pair of omnidirectional microphones is much less common in Europe than in the USA.

Here it is more normal to use a closely spaced or "coincident" pair of directional microphones. In the Carver example, sound from instrument of the orchestra 12f is picked up by microphone M2 and then, after a short delay and at reduced level, by microphone M1. When the recording is reproduced through loudspeakers LS, RS that sound is produced first by loudspeaker LS and then, after a short delay and at reduced level, by loudspeaker RS. Due to acoustic cross talk, when speaker LS reproduces the sound of instrument 12f it is heard first by the listener's left ear along the path Le and then, slightly later, by the listener's right ear, along slightly longer path Lr. When, soon after, the sound of instrument 12f is reproduced by speaker RS, it is heard first by the listener's right ear along path Rr and then, slightly later, by the left ear along slightly longer path Rl. Carver argues that stereo reproduction can be enhanced, to produce a nearly total dimensionalized effect whereby it appears that the music is in a sense surrounding the listener, if acoustic cross talk is cancelled so that the left ear hears only the left loudspeaker and so on. Instrument 12f is now heard first from the left loudspeaker by the left ear, and then, shortly afterwards, from the right loudspeaker by the right ear. In other words a spurious image of the sound follows the real image. This understandably confuses the ears and brain into believing that, as Carver puts it "the hearer somehow appears to be within the sound or in some manner surrounded by the various sources of the sound".

Figure 3 shows the basic circuit. The right channel input R(IN) is split and one signal fraction sent via frequency equalizer A(R) to a summing junction C(R). The remaining signal fraction is fed via phase inverter B(RL) to an array of four time delay frequency analysers b1(RL), b2(RL), b3(RL) and b4(RL). The phase inverter shifts the signal by 180° and splits it into four parts which are each delayed by a different period of time in the four delay devices. These devices also all modify the signal level as a function of frequency. The four, differently delayed, outputs are summed at C(L) with a fraction of the left channel input L(IN). This has been frequency equalized A(L) in mirror image circuitry which also feeds the summing junction C(R) with a left channel signal fraction processed at B(LR) and b1(LR) etc. So each of the two output channels contains an anti-phase, multiple-delay signal crossed over from the other channel. The crossover signals compensate for acoustic cross talk between

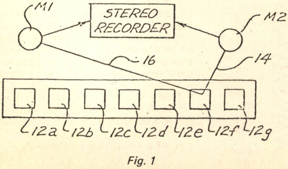

Fig. 1

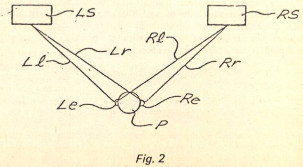

Fig. 2

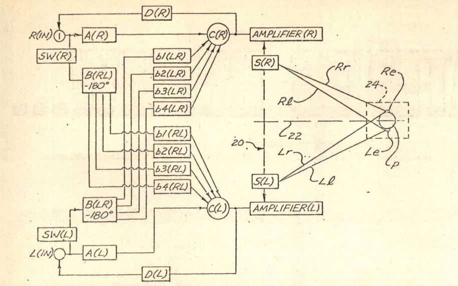

loudspeakers in the following manner. The listener's left ear first hears a sound direct from speaker LS along path Le. At the slightly later time when the listener's right ear would hear the same sound from loudspeaker LS along slightly longer path Lr, it also receives the delayed replica of that signal in anti-phase from speaker RS. There is thus cancellation at the right ear so the left ear hears only the left speaker.

An array of four different delay devices is used in each channel cross over to compensate for listener head movement. As the head and ears move to a different position so a different time delay in the compensating signal comes into play. So a compensating sound superimposed on one channel will still arrive at the same time as the main sound from the other channel. Carver suggests that in practice delay periods of 110, 180, 370 and 690 microseconds are suitable to create a comfortably large listening window.

Readout...

A selection from our Postbag

Readers requiring a reply to any letter must include a stamped addressed envelope.
Opinions expressed in Readout are not necessarily endorsed by the publishers of Practical Electronics.

CB: Learn from US mistakes

Sir—I've followed, as an observer, some of the developments in the UK concerning CB Radio, and I'm frankly amazed at the ridiculous claims being made for it.

As background, I witnessed the institution of CB on 27MHz in the US in 1958, and its various stages and problems through to the present (at least to October of 1979, when we came to Saudi Arabia for a two-year contract).

The basic errors made in the US (and I see the arguments being made to repeat the errors in Britain) were many. First, the band chosen was poorly suited for the stated objectives. Second, because the temptations for illegal operation were so great, and the controls so lax, even the stated objectives were forgotten to the point that those people who had a "legitimate" use according to the regulations were pushed out. The Federal Communications Commission has been notably incapable of doing more than putting a finger in the dike (part-time). Your policing agency will have the same problems, because the situation is identical.

Now, CB has some good points and good uses. But they are almost entirely related to individual use of the medium. Group activities and uses tend to be a waste of time and effort, because of the massive illegal use.

In the US at least (and the situation may be quite different in the UK), almost all the uses to which CB is put are duplications of things which are already available in other services; however, the use of CB is so easy that the other solutions are ignored. In short, 99% of what goes on on Stateside CB shouldn't even exist!

Let me list situations:

1. Emergency communications are quite often worthless on CB. Hoaxes are perpetrated daily. In Houston, Texas (our home), a "command centre" was set up in one of the downtown tall buildings to handle accident reports to the police from commuters on CB. Within a matter of months, the police began to ignore reports from even this well-planned and well-staffed operation, because of the numerous false calls. Additionally, legitimate emergency communications are deliberately disrupted a large majority of the time.
2. Profanity is rife on CB, and I don't mean "Hells" and "Damns". No subject of anatomy is too delicate to discuss in detail, no vulgar terms are taboo, and there is *no* way to protect your family. Anonymity works strange changes in the human animal.
3. After a short while, the frustrations of the whole thing cause the individual to either give up, or he decides to fight it. If he gives up, the remaining users gain (less interference) and he loses (he doesn't have the usage he desired). If he decides to fight it, everyone loses. First, he tries higher power. When that loses its splendour, or he finds that there are those who have more power than he does, he looks for something further. So he figures out a way to get away from the crowd (in the US they're called "Sliders"). Now he's got high power *and* he can move out of the band. Next facet: Most of the manufacturers of illegal equipment don't come anywhere near producing anything with any quality. The result is usually (and this can be documented) a 200 watt amplifier, for instance, that dumps 20 watts on channel 19, and the remaining 180 watts somewhere between 30 and 500MHz (Murphy's law says most of that will be on discrete TV channels).
4. Now, what happens next? Well, since he's illegal, there are few things in which he can legitimately engage, and eventually he decides that there's no fun in it, so he looks for new worlds to conquer. What's left? Well, he can move out and bootleg on the ham bands. This is a common occurrence is the US. He can have all sorts of fun creating havoc, and really disrupting things.
5. Many of the CB'ers in the US finally get disgusted and move up to legitimate Ham Radio via the licence route. Ham Radio is where they should have been in the first place.

Okay, for those who get disgusted and quit, and those who get disgusted and upgrade to ham radio, what purpose has CB served? With the illegality that is rampant (at least in the US), CB serves no purpose which justifies its existence, even for those who stay in it. And, Great Britain appears not to have learned the lessons from observing the mistakes of the other countries.

One last observation: I see in several of the magazines advertisements that suspiciously look like offers by UK commercial establishments to sell illegal equipment. CB is getting off to a *great* start! Why, some magazines print articles on how to build equipment that's illegal to use, and even tell you it's illegal to use it! Sounds slightly hypocritical to me.

I enjoy your magazine. The layout's good, the articles are interesting and it's easy to follow. Keep up the good work, and watch CB grow. I predict you'll find that the only winners will be the purveyors of equipment.

Kent Marshall,
Dhahran.

Get a great deal from Marshall's

A. MARSHALL (LONDON) LTD.
KINGSGATE HOUSE
KINGSGATE PLACE
LONDON NW6 4TA.
MAIL ORDER 01-624 8582 24HR SERVICE
INDUSTRIAL SALES 01-328 1009

ALSO RETAIL SHOPS AT
325 EDGWARE ROAD, LONDON W2 01-723 4242
40 CRICKLEWOOD BDY., LONDON NW2 01-452 0161
108A STOKES CROFT, BRISTOL. 0272 426801
85 WEST REGENT STREET, GLASGOW. 041-332 4133

WE TAKE ACCESS – AMERICAN EXPRESS – BARCLAYCARD CARD – DINERS

PLEASE ADD POSTAGE/PACKING 60p UNLESS STATED ALSO 15% VAT ON TOTAL – ALL ITEMS ON THIS ADVERTISEMENT SPECIALLY SELECTED FOR EX-STOCK DELIVERY. WATCH FOR SPECIAL REDUCTIONS ON STARRED ITEMS

RECHARGEABLE NICKEL CADMIUM BATTERIES & CHARGERS

TYPE	*VOLTS*	*AV. CAP.*	*PRICE*
S101 (HP7)	1.25	0.5AH	£0.98
Sub C (HP11)	1.25	1.2AH	£1.75
Sub D (HP2)	1.25	1.2AH	£1.95
S104 (HP11)	1.25	1.8AH	£2.00
S103 (HP2)	1.25	4.0AH	£3.75

Penlight 4 Charger for 1-4 HP7 ....£5.25
Combibox FW611 Charger for HP7, HP11, HP2 ....£13.25
Combibox FW610 Charger for HP7, HP11, HP2 ....£19.95

CAPACITORS

SIEMENS LAYER B32560 7mm

.001	to	.015/400v	£0.08
.0082	to	.027/250v	£0.08
.033	to	.1/250v	£0.10
0.15/250	£0.12		
0.22/250	£0.14		
0.1/100	£0.12	0.15/100	£0.13
0.22/100	£0.45	33/100	£0.20
0.47/100	£0.26	0.68/100	£0.34

SIEMENS LAYER B32561 10mm

.01 – .022/400v			£0.08
.033/400v	£0.09	.047/400v	£0.10
.022/250v	£0.08	.047/250v	£0.09
.068/250v	£0.10	.1/250v	£0.13
.22/250v	£0.16	.47/250v	£0.26
.22/100v	£0.16	.47/100v	£0.25
.68/100v	£0.30	1.0/100v	£0.40

Other values stocked prices or reduced.

SIEMENS ELECTROLYTIC AXIAL

4.7/100	13	22/40	16
10/63	16	22/63	18
10/100	16	22/100	20
47/25	16	47/40	19
47/63	20	47/100	24
100/25	20	100/40	19
100/63	21	100/100	44
220/16	19	220/25	22
220/40	24	220/63	45
220/100	67	470/16	23
470/40	47	470/63	72
470/100	1.16	1000/16	45
1000/40	75	1000/25	60
2200/16	1.50	2200/25	95
2200/40	1.23	4700/16	1.20
4700/25	1.50		

MANY OTHER RANGES CAPACITORS INCLUDE MULLARD C280 MULLARD/SIEMENS CERAMIC. SIEMENS B41070 RADIAL. HIGH VOLTAGE DISC CERAMIC, ETC.

LINEAR INTEGRATED CIRCUITS

LF 1331N	2.70	SAA 5000	3.04
LF 13741H	2.70	SAA 5010	7.11
* LM 301-8	0.26	SAA 5012	7.11
LM 308N	0.48	SAA 5020	5.33
LM 348	0.90	SAA 5030	8.26
* LM 380 N14	0.50	SAA 5040	15.14
LM 383	1.56	SAA 5050	8.51
* LM 386N	0.75	SAS 560	1.60
LM 389N	0.92	SAS 570	1.60
LM 340T5	0.50	SAS 580	1.80
LM 710-14	0.42	SAS 590	1.80
LM 723 CH	0.60	* SFF 96800A	6.25
LM 723 C14	0.40	SFF 96810A	4.28
LM 741 C14	0.58	SFF 96821A	5.19
LM 923	0.44	* SN 76115	0.70
LM 1303	1.00	* SN 76228	1.00
LM 1458	0.40	* SN 76116	1.25
LM 1801	2.04	* SN 76666	0.70
LM 1871	1.95	* TAA 263	1.00
LM 1872	1.95	TAA 521	0.75
* LM 3900	0.50	TAA 621	2.49
LM 3909	0.67	TAA 700	1.50
* LM 3914	2.20	TAD 100	1.55
* LM 3915	2.20	TBA 120	0.75
LM 4250	1.42	TBA 500	0.45
NE 531	0.95	TBA 550	3.50
NE 543K	1.55	TBA 570Q	2.20
NE 544	1.60	* TBA 810S	1.00
* NE 555	0.21	TBA 920	2.75
* NE 556	0.73	* TBA 990Q	2.65
NE 558	3.12	TCA 270S	3.15
NE 562	3.12	TDA 2540	3.85
NE 565	1.05	TDA 2611	1.58
NE 566	1.53	* TLO 81CP	0.32
NE 567	1.10	* TLO 82CP	0.56
NE 570	3.50	* TLO 84CN	1.00

SINCLAIR INSTRUMENTS

			p/p
Digital Multimeter			
	PDM35	£34.50	£0.60
" "	DM235	£52.50	£1.30
" "	DM350	£72.50	£1.30
" "	DM450	£119.00	£1.30
Digital Frequency Meter			
	PFM200	£49.80	£0.60
Low Power Osilloscope			
	SC110	£139.00	£1.30
TF200 Frequency Meter		£145.00	£1.30
TGF 105 Pulse Generator		£85.00	£1.30

NEW

LCD Multimeter	TM353	£84.00	£1.30
LCD Multimeter	TM351	£99.00	£2.50
LCD Multimeter	TM352	£49.95	£1.30
Prescaler	TP600	£37.50	£0.60

LEADER INSTRUMENTS

Just a selection

Singletrace Osicilloscope 510A 5"	£127.00	£3.00
Doubletrace Osicilloscope 308S 3"	£419.00	£2.50
Coubletrace Oscilloscope 508A 5"	£299.00	£3.00
LSG 16 Sig. Gen. TV/Radio	£55.00	£2.00
LDM 815 Dip Meter	£45.00	£1.00

TRANSISTORS/DIODES STOCK CLEARANCE

2N 697	.10	AD 161	.25	BC 184L	.05	BF 195	.10
2N 914	.10	AF 106	.10	BC 212A	.05	BF 196	.10
2N 929	.05	AF 109	.10	BC 213B	.05	BF 199	.05
2N 3133	.10	AF 126	.10	BC 213L	.05	BSY 28	.10
2N 3566	.50	BC 115	.05	BC 214	.05	MJE 371	.30
2N 3638	.05	BC 118	.05	BC 214B	.05	MPSA 05	.05
2N 3642	.10	BC 154	.10	BC 214L	.05	ZTX 500	.05
2N 3708	.05	BC 157A	.05	BC 238B	.05	AA 119	.05
2N 3711	.05	BC 157B	.05	BC 239C	.05	BA 102	.05
2N 3794	.05	BC 158	.05	BC 251B	.05	BA 142	.05
2N 3771	.75	BC 159	.05	BC 253	.08	BA 144	.05
2N 3905	.08	BC 167B	.05	BC 308B	.08	BA 154	.05
2N 3962	.10	BC 168B	.05	BC 350	.05	BA 316	.05
2N 4286	.05	BC 169B	.05	BC 347	.05	BA 317	.05
2N 4400	.05	BC 170B	.05	BC 414	.05	BA 318	.05
2N 5220	.05	BC 171B	.05	BC 415A	.05	BAW 49	.05
2N 5222	.10	BC 172	.06	BC 416A	.05	BAX 13	.05
AC 126	.15	BC 172C	.06	BC 517	.12	BAY 93	.02
AC 127	.15	BC 173	.05	BCY 71	.05	BB 105B	.10
AC 132	.05	BC 174B	.05	BCY 72	.09	BY 126	.14
AC 152	.15	BC 178B	.14	BD 138	.10	CV 7641	.05
AC 188	.15	BC 182A	.05	BF 161	.08	GEX 23A	.03
AC 188K	.15	BC 183	.05	BF 177	.05	ITT 44	.05
AC 187K	.15	BC 183B	.06	BF 180	.08	ITT 921	.05
ACY 22	.05	BC 183L	.05	BF 181	.05	OA 47	.10
ACY 30	.05	BC 183 LA	.05	BF 194	.05	OA 90	.05

CRIMSON ELEKTRIK HI FI MODULES

CE 608	Power Amp	£20.09
CE 1004	Power Amp	£23.43
CE 1008	Power Amp	£26.30
CE 1704	Power Amp	£33.48
CE 1708	Power Amp	£33.48
CPS 1	Power Unit	£19.52
CPS 3	Power Unit	£23.52
CPS 6	Power Unit	£30.00
CPR 1	Pre Amp	£32.17
CPR 1S	Pre Amp	£42.52

U.K. Postage and Packing + 10%

ILP HI FI MODULES

Power Amplifiers		*Pre Amplifiers*	
HY30	£7.29	HY6	£6.44
HY60	£8.33	HY66	£12.19
HY120	£17.48	*Power Supplies*	
HY200	£21.21	PSU30	£4.50
HY400	£31.83	PSU36	£8.10
		PSU60	£13.04
MOS120	£25.88	PSU70	£15.92
MOS200	£33.46	PSU180	£21.34

Postage & Packing to U.K. included.

* CD4000	£0.17	* CD4013B	£0.44	* CD4024B	£0.60	CD4049	£0.33	* CD4069	£0.14	* CD4095	£1.00
CD4001B	£0.20	CD4014	£0.72	CD4028B	£0.60	CD4050B	£0.33	* CD4071B	£0.16	* CD4096	£1.00
CD4002	£0.20	CD4015	£0.72	* CD4029B	£1.05	CD4051B	£0.70	* CD4072	£0.20	CD4099B	£1.40
CD4007	£0.20	CD4016	£0.36	CD4034B	£2.20	CD4052B	£0.70	* CD4073B	£0.16	CD4507	£0.44
CD4008B	£0.74	* CD4017B	£0.70	* CD4035B	£1.05	* CD4060B	£1.10	* CD4075B	£0.16	CD4510B	£0.90
CD4009	£0.40	CD4018B	£0.75	CD4040	£0.90	* CD4063	£1.10	* CD4081B	£0.16	CD4511	£1.02
CD4010	£0.40	CD4019B	£0.44	* CD4041B	£0.80	CD4066B	£0.45	* CD4082	£0.20	CD4514	£2.20
CD4011B	£0.20	CD4020B	£0.90	CD4042B	£0.64	* CD4067	£4.20	* CD4085	£0.90	CD4520B	£0.90
CD4012	£0.20	CD4022B	£0.78	CD4047B	£1.02	CD4068	£0.30	* CD4086	£0.90	CD4522	£1.10

SN7400	£0.19	* SN7420	£0.15	SN7445	£0.91	* SN7460	£0.15	* SN7496	£0.20	SN74164	£0.91
SN7401	£0.19	SN7423	£0.19	* SN7446	£0.24	* SN7472	£0.20	* SN74107	£0.20	SN74165	£0.91
SN7403	£0.19	SN7426	£0.21	* SN7447	£0.24	* SN7484	£0.51	* SN74121	£0.20	* SN74174	£0.60
* SN7404	£0.15	SN7432	£0.21	* SN7448	£0.30	* SN7490	£0.25	* SN74141	£0.24	* SN74182	£0.60
SN7410	£0.19	* SN7440	£0.15	SN7450	£0.19	* SN7491	£0.35	SN74145	£0.77	* SN74190	£0.60
* SN7412	£0.15	* SN7441	£0.30	* SN7453	£0.15	* SN7492	£0.20	* SN74155	£0.50	SN74192	£0.91
SN7414	£0.55	* SN7442	£0.20	* SN7454	£0.15	* SN7493	£0.20	SN74157	£0.70	* SN74197	£0.60

SIEMENS LEDS

5.8mm Red Yellow Green	£0.14	TIL 209	£0.18
3.2mm Red	£0.12	TIL 228	£0.35
3.2mm Green/Yellow	£0.14	TIL 78	£0.54
Flashing Diodes (3Hz)	£0.90	BPW 34	£1.18
Rect Leds 2.5 x 5.0mm Red	£0.12	SFH 205	£0.80
Rect Leds 2.5 x 5.0mm Green/Yellow	£0.18	ORP 12	£1.20
		4N25	£0.90

MA 1032 Digital LCD Clock Module £11.50
.5" 12 or 24hr mode, 24 alarm with on/off control, sleep timer, snore timer etc. 1.5v batt. low consumption

MA 1026 Alarm/Thermometer Module £11.50

MA 1003 12v Car Clock Module, Special Price £12.50 whilst stocks last

NSN3914, 3915, 3916 End Stackable Led Bar

Graphs Arrays with Driver All @ £4.95 each.

DIGITAL FUEL STRETCHER SYSTEM GIVES ACTUAL Mpg. OR L/100Km
EASILY FITTED – SUITABLE FOR MOST CARS. £58.50 p/p £1.30
FLOW SENSOR S8011 £14.75
SPEED SENSOR S8010 £11.95

SEND LARGE SAE FOR DETAILS OF SENSORS & PARTS TO BUILD OWN FUEL STRETCHER SYSTEM.
MINI METAL DETECTOR FOR LOCATING PIPES/CABLES UNDER PLASTIC – A MUST FOR EVERY HANDYMAN £9.95

PRESENSITISED POSITIVE FOTO RESIST PC BOARDS 1.6mm THICK

SIZE	*SINGLE SIDE*	*DOUBLE SIDE*
100 x 160mm	£1.40	£1.65
100 x 220mm	£1.95	£2.05
203 x 114mm	£1.70	£2.10
233.4 x 220mm	£3.75	£4.50

KIT FOR UV EXPOSURE UNIT FOR DEVELOPING FOTO BOARDS COMPLETE WITH BOX & GLASS SCREEN 228 x 152mm £34.50 OR WITHOUT BOX £19.50

ALL PRICES EXCLUSIVE OF VAT

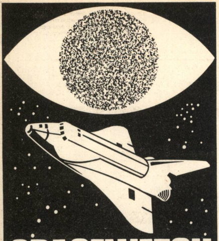

SPACEWATCH

FRANK W. HYDE

WILLIAM HERSCHEL

In 1781 on the 16th of April, William Herschel, using his telescope which he had built with his own hands, discovered the planet Uranus. This musician from Germany became one of the world's greatest astronomers. He lived at a time in British history which saw the beginning of a new surge forward in technology over wide horizons. His discovery of the planet named after him and now called Uranus, marked more than a mere observational feat, opening up new wonders and extending the solar system with the first discovery of an additional planet. It marked also a new development in technology. Herschel added to the astronomical scene an advanced technology in practical optics.

The story of his entry into the study of astronomy is interesting and instructive. During the time that he lived in Bath he was given the opportunity to use a small telescope. So struck was he by the increased richness of the number of stars which could be seen with the naked eye, that he sought to purchase a telescope of his own. Eventually he was offered one at a cost of something like £100. This he could not afford so he set about making his own. Many of these activities have been recorded, but it is worth noting that he decided to make a larger telescope on the assumption that this would enable him to see more. The materials to hand that could be used for the tube, the stand and controls were plentiful. It was the 'mirror' that posed the main difficulty. He recognised that the material, an alloy called 'speculum' metal, had limits. So expert did he become in the manipulation and polishing techniques that the 'mirror' was of such quality that it surpassed any then known.

Here then was one of startling new events of science history, for had it not been for Herschel's production of a so well figured 'mirror' Uranus might not have been discovered for a long time. This was why the planet had not been discovered previously though others had described a possible body without confirmation. The simple fact was that the telescope was so good that Herschel recognised that he was looking at a planet because it *appeared as a disc* and therefore could not be a star.

It is a fitting tribute to this man that the new 4·2m telescope being built for the observatory on the island of La Palma, was named the William Herschel Telescope by the Director of the Royal Greenwich Observatory, Professor F. Graham Smith, during the National Astronomy Week which began on April 25, 1981. The 4·2m telescope has an altazimuth mounting, the system that Herschel used for all his telescopes. The 4·2m telescope is the largest of the three telescopes to be set up at the Roque de los Muchachos, La Palma. There is a connection between Spain and Herschel because the King of Spain purchased one of his best telescopes (with a 24in. mirror) and installed it in Madrid in 1804.

THE NEW FRONTIER

The successful first flight of the shuttle Columbia marks a point in space history that must touch the hearts of even the most blasé of citizens anywhere. The vistas that open will affect every walk of life and invade every area of human endeavour. The capability of the new technology will result in the extension of benefits to the whole world. For some of the plans, already past the drawing board, there will be the requirement for the extensive use of engineering which calls for a vast amount of raw materials and the processing of millions of components of all kinds. For some of the commercial activities a number of thermo electric items such as solar cells will require an increase in the winning of items like gallium, arsenide and silicon, far beyond the present consumption. Material for the assembly of large structures is another item which will consume raw materials for platforms such as would never be contemplated on earth—structures which will be measured in hectares and miles as continuous units. Operational personnel in space could well be getting toward the 1,000 mark by the end of the century, that is to say the personnel aloft as distinct from the back-up teams. The continuous servicing of the existing individual spacecraft and satellites means increased life with fewer launches. Units can be standarised as the pallets that are already operational.

It will indeed be a brave new world extension. Progress is now in a logarithmic mode and looking back over 200 years it is clear that these modes increase in frequency and there are new clichés such as 'we have learned more in the three days of this mission than in the last three years'. At a recent conference on Saturn and Uranus these were the constant remarks—and so it will go on.

A look back at the Columbia mission and the technical details of the launch is instructive. One point that emerges is that in most sections of the operations the results were beyond target so that the normal planned programme was well within the capability of the possible activities. For example the 7·5 million pounds of thrust at lift-off took the vehicle aloft at a steeper angle than was planned. This 5% steeper climb lifted the vehicle (the Americans call it 'lofting'), and this of course used more fuel than was planned, but because the greater height was attained it helped to restore the propulsion requirement and the astronauts were notified that they were ahead of time, and instructions might be advanced. However, because of the balancing of the two conditions the original timing was restored. No adverse conditions arose when it came to the time of separation of the boosters.

It was a tribute to the planning that the crew were warned that the main engine cut-off would be at 8min 34sec. This was exactly correct. At this cut-off point the velocity was 25,670ft/sec, only 2ft/sec higher than the target. Altitude and the rate of climb was exact. All moves went smoothly to the point when the 130nau.m by 130nau.m orbit was reached. More details will be available later when the official reports are released.

The re-entry part of the mission was an unqualified success and started when the speed of the vehicle was at mach 25. At mach 5 the mission commander John F. Young took manual control. The height was then 115,000 feet and Young continued control through the reversal stage till 35,000 feet. The vehicle's tile protection was safe through the 2,300 to 3,000 deg.F period of blackout. This was at a height of 188,000 feet at mach 10·3.

It may be possible in the next issue of *Spacewatch* to have more details of the moment to moment sequence, outward and return.

The Columbia will go back for refurbishing and it is expected that the next mission will be in September or early October this year. As has already been stated, the first period of shuttle operations will be used to fulfil the time already booked for scientific and defence activities. This is expected to continue on present contracts to 1985. By that time the other shuttles will be operational and open for business. The goal of the enterprise is to 'carry into space anyone who needs to operate equipment, experiments or machinery'. There will be available NASA trained pilots, engineers, doctors, physicists and other scientists. Normally healthy people from 25 to 65 will be able to go into space with safety. It is expected that the upper limit will be increased to 80 in the next decade. Each vehicle can be used 100 times and there will be four of them in the initial programme.

It is perhaps not unreal to look at the facilities of the shuttle and see a picture of a unit having attached to it all kinds of units each doing some job or other and the whole looking as though there was a fiesta with everything 'dressed overall'.

JOBLESS BUILD A GATEWAY TO THE STARS

Astronomer Patrick Moore officially opened a new visitor centre which has been created at the Royal Observatory, Blackford Hill, Edinburgh, by a team of unemployed adults and teenagers. It traces developments and the international role of the Royal Observatory and houses the nucleus of a national collection of Scottish astronomical telescopes dating from about 1710. It also gives the latest information on the exploration of space. A model of the Space Shuttle is on view.

The Manpower Services Commission paid the wages of the unemployed persons.

Interfacing COMPUKIT

Part 7 D.E.Graham

THIS MONTH we conclude the series with discussion of an Interrupt Driven Clock, and with applications of the Analogue to Digital Converter section of the *P.E.* Analogue Board. These include voltage, temperature, light and sound measurement with v.d.u. bar chart displays, plus a data logger and sampling oscilloscope. But first we continue the discussion of the use of interrupts, begun last month.

6522 INTERRUPTS

The interrupt lines of the 6821 on the Decoding Module and the 6522 on the Analogue Board have both been connected to the UK101's $\overline{IRQ}$ line so that interrupts from both these devices may be readily handled. Unfortunately space has not allowed a discussion of the use of 6821 interrupts during this series. The principles involved however are similar to those for 6522 interrupts, and for further information on the 6821 the reader is referred to the data sheets.

6522 interrupts are handled through two sets of registers, the Interrupt Flag Register or IFR (register 13 at 61357) and the Interrupt Enable Register or IER (register 14 at 61358). These are represented in Table 6.3 of part 6 of the series. From this it will be seen that one bit of the IFR and one bit of the IER are associated with each of the control lines CA1, CA2, CB1 and CB2, and one with each timer and the shift register.

The various bits of the IFR are automatically set by the 6522 when events such as the timing out of the timers, or particular transitions on the peripheral control lines occur, and these flags may be inspected periodically by the CPU. If the interrupt is used however, such continual polling is not necessary, and the CPU need only inspect the IFR once an interrupt has been sensed and accepted. The IFR will then tell the CPU which one of the 7 possible functions caused the interrupt.

To condition the 6522 to cause an interrupt request (ie by taking $\overline{IRQ}$ low) when any of its flags are set is achieved by previously setting the corresponding bit in the Interrupt Enable Register. This register uses bit 7 to indicate whether specified bits are to be set or unset. If bit 7 is a one, then writing to any other bit of the register will set that bit. Thus, placing 130 (=128+2) into the IER codes bit 7 with a one, so that the remaining data (2) will cause bit 1 to be set. No other bit positions will be affected. Unsetting bits in the IER is accomplished with bit 7 at zero, so that writing 65 to the IER will unset bits 6 and 0, again leaving the remainder unchanged. To clear the register completely the IER should be loaded with 127. Pressing the Reset button on the Decoding Module will also zero this register.

INTERRUPT DRIVEN CLOCK

As an example of the use of interrupts with the 6522 we will look at the implementation of an interrupt driven clock on the UK101.

This will employ timer T1 on the 6522 to produce an interrupt every 50ms, and the UK101 will be conditioned to respond to this by updating a series of memory locations in which it holds the current time in hours, minutes, seconds, and twentieths of a second.

Table 7.1 gives the assembler listing of a program which accomplishes this. It resides at 0230 hex in an unused area of RAM below the UK101's BASIC file space. The program falls into two parts: the interrupt service routine itself, from 0230 to 0278 hex; and the initialisation routine from 027D to 02A6 hex. This latter is executed only once at the outset, and we will look at this first.

The first five lines set a jump to 0230 instruction at the UK101's IRQ vector. Line 780 initialises the memory location TWENT that is used to count twentieths of a second. The next sequence is used to configure the 6522. Lines 790 and 800 set timer T1 in the continuous mode by placing 64 into the ACR. Lines 810 and 820 enable the T1 interrupt by loading the IER with 192 (=128+64), thus setting bit 6. The instruction CLI at line 830 clears the interrupt mask, while lines 840 to 870 load the low and high order bytes of the T1 latches with the values 78 and 195, so initiating the count. The count total is thus 195 x 256 + 78 (=49998). The 2 micro-secs delay inherent in the counter make this up to 50000, so giving a 50ms interrupt repetition rate. The final command executes a return from subroutine.

The interrupt service routine starting at 0230 first places the accumulator on the stack, and executes a read from the low byte of T1's count registers. This latter has the effect of automatically clearing the T1 interrupt flag, so taking $\overline{IRQ}$ high again in preparation for the reception of further interrupt requests. The program then decrements the location TWENT (at 022A hex), and checks to see whether it has reached zero. If not it restores the accumulator from the stack, and exits the interrupt routine. If zero has been reached on the other hand, it increments the location SECS (at 022B hex), checking to see whether 60 seconds have been counted, in which case it increments MINS, and so on.

To start the clock once the program has been entered, it is only necessary to execute the subroutine at 027D. This may be accomplished from BASIC using a USR(X) call, or from a machine code routine with a JSR command. We will access it from BASIC.

RUNNING THE INTERRUPT CLOCK FROM BASIC

The BASIC program listed in Table 7.2 consists of two parts. The first loads the clock program of Table 7.1. The second allows the current time to be inserted in the three locations SECS, MINS and HRS, and uses a USR(X) call to enter the clock initialisation routine, thus starting the clock. Lines 3000 onwards then cause the time to be POKEd to the centre of the screen. Line 2100 determines the screen position of the display, and this should be altered for Superboard use.

The clock display program may be exited by pressing the space bar at any time, and as long as the UK101 Reset is not pressed, the interrupt clock will continue to operate. Other programs may then be loaded, run and saved as required without disrupting the clock, and these may if desired access the continually updated time by PEEKing locations 555, 556 and 557 for seconds, minutes and hours respectively. There seems to be just one proviso to this: programs which use more than the simplest configuration of GOSUB commands must be avoided, since due to an error in the UK101's firmware the IRQ vector has been located within the stack. As a result, subroutine calls can corrupt the interrupt vector at 01CO, and are in turn corrupted by it. It is for this reason that the program of Table 7.2 avoids subroutine calls, and makes use of flags F and F1 to get around the problems which this creates.

Once the clock has been started, the whole program may be erased with a NEW command, if desired, so as to save memory space, again without affecting the running of the clock.

As with other applications of the 6522, the accuracy of the interrupt clock is tied to that of the UK101's 8 MHz crystal. In my machine this caused the clock to run slow by about 2 secs every hour. This could of course be corrected by using a closer tolerance crystal. But a much simpler way is to alter the value loaded into the low byte of T1's latch register—this is the last data item (78) on line 210 of the program of Table 7.2. With this method it should be possible to achieve accuracies of the order of 1 sec in 16 hours, which should be sufficient for most foreseeable applications.

MACHINE CODE TO BASIC TRANSLATOR

Lines 100 to 340 of the program on Table 7.2, which enter the interrupt clock program in 6502 code using BASIC, were themselves produced by a translator program written for the purpose. Since this program can translate the contents of any section of memory into BASIC POKE statements, it can be used for saving data or programs stored anywhere in the machine. The program is listed in Table 7.3. It first requests the start and end address of the memory block to be recorded. These may be in hex or decimal, since a hex to decimal conversion routine is included in the program. Next it requests the line number that the BASIC program which it will write is to start from, and the title of the program. It then instructs the cassette recorder to be set to record, and writes the program directly on to it. The machine may then be cleared, and the cassette loaded and run as if it were a normal program.

ANALOGUE TO DIGITAL CONVERTER

The fourth section of the Analogue Board consists of a multiplexed 8 channel analogue to digital converter. The heart of this unit is a ZN427 monolithic A/D converter i.c. See Fig. 7.1. This uses the so-called successive approximation technique to achieve conversion times of some 20µs or less. This is a far more efficient means of conversion than the other commonly used method which simply causes a D/A converter to sequence its output from zero to 255, using a comparator to stop it when the output matches the analogue signal to be measured. In this case conversion may take as long as 255 clock cycles.

Fig. 7.2 gives the circuit of the A/D section of the Analogue Board. The 8 analogue inputs are taken through SK6, whose full pinout is given in Fig. 7.3. From here they are applied to IC8, a 4051 8 way analogue switch. This selects one of the 8 channels according to the logic states of its pins 6, 9, 10 and 11. These in turn are determined by the

```
.80 0000               ;INTERRUPT CLOCK AT 022B, C & D
 90 0000               START=$0230
100 0230               *=START
110 0230               TWENT=START-6
120 0230               SECS=START-5
130 0230               MINS=START-4
140 0230               HRS=START-3
150 0230               ACR=61355
160 0230               IER=61358
170 0230               TL=61348
180 0230               TH=61349
200 0230 48     BEGIN PHA ;INTERRUPT SERVICE ROUTINE
220 0231 ADA4EF LDA TL
230 0234 CE2A02 DEC TWENT
240 0237 D03B   BNE OUT
250 0239 A914   LDA #20
260 023B 8D2A02 STA TWENT
270 023E A901   LDA #1
280 0240 18     CLC
290 0241 6D2B02 ADC SECS
300 0244 8D2B02 STA SECS
310 0247 C93C   CMP #60
320 0249 D029   BNE OUT
330 024B A900   LDA #0
340 024D 8D2B02 STA SECS
350 0250 A901   LDA #1
360 0252 18     CLC
370 0253 6D2C02 ADC MINS
380 0256 8D2C02 STA MINS
390 0259 C93C   CMP #60
400 025B D017   BNE OUT
410 025D A900   LDA #0
420 025F 8D2C02 STA MINS
430 0262 A901   LDA #1
440 0264 18     CLC
450 0265 6D2D02 ADC HRS
460 0268 8D2D02 STA HRS
470 026B C918   CMP #24
480 026D D005   BNE OUT
490 026F A900   LDA #0
500 0271 8D2D02 STA HRS
510 0274 EA     OUT NOP
520 0275 EA     NOP
530 0276 EA     NOP
540 0277 68     PLA
550 0278 40     RTI
```

Table 7.1. Assembler Listing of Interrupt Clock

```
560 0279 00     BRK
570 027A 00     BRK
580 027B 00     BRK
590 027C 00     BRK
700 027D          ;INITIALISE CLOCK
710 027D A94C   LDA #$4C
720 027F 8DC001 STA $01C0
730 0282 A930   LDA #$30
740 0284 8DC101 STA $01C1
750 0287 A902   LDA #$02
760 0289 8DC201 STA $01C2
770 028C A914   LDA #20
780 028E 8D2A02 STA TWENT
790 0291 A940   LDA #64
800 0293 8DABEF STA ACR
810 0296 A9C0   LDA #192
820 0298 8DAEEF STA IER
830 029B 58     CLI
840 029C A94E   LDA #$4E
850 029E 8DA4EF STA TL
860 02A1 A9C3   LDA #$C3
870 02A3 8DA5EF STA TH
880 02A6 60     RTS
```

```
OK
LIST

 90 REM INTERFACING UK101 PROGRAM 19
 100 REM 6522 INTERRUPT CLOCK AT 0230 HEX
 105 REM LOCATIONS  560  TO  678
 110 DATA 72 , 173 , 164 , 239 , 206 , 42 , 2 , 208 , 59 , 169
 120 DATA 20 , 141 , 42 , 2 , 169 , 1 , 24 , 109 , 43 , 2
 130 DATA 141 , 43 , 2 , 201 , 60 , 208 , 41 , 169 , 0 , 141
 140 DATA 43 , 2 , 169 , 1 , 24 , 109 , 44 , 2 , 141 , 44
 150 DATA 2 , 201 , 60 , 208 , 23 , 169 , 0 , 141 , 44 , 2
 160 DATA 169 , 1 , 24 , 109 , 45 , 2 , 141 , 45 , 2 , 201
 170 DATA 24 , 208 , 5 , 169 , 0 , 141 , 45 , 2 , 234 , 234
 180 DATA 234 , 104 , 64 , 0 , 0 , 0 , 0 , 169 , 76 , 141
 190 DATA 192 , 1 , 169 , 48 , 141 , 193 , 1 , 169 , 2 , 141
 200 DATA 194 , 1 , 169 , 20 , 141 , 42 , 2 , 169 , 64 , 141
 210 DATA 171 , 239 , 169 , 192 , 141 , 174 , 239 , 88 , 169 , 78
 220 DATA 141 , 164 , 239 , 169 , 195 , 141 , 165 , 239 , 96
 310 FORC=0 TO  118
 320 READ I
 330 POKE  560 +C, I
 340 NEXT
 2000 PRINT:PRINT:PRINT:PRINT:PRINT
 2005 PRINT:PRINT,"INTERRUPT CLOCK"
 2007 PRINT:PRINT:PRINT"  ENTER PRESENT TIME"
 2010 INPUT"    HOURS";H
 2020 INPUT"    MINUTES";M
 2030 INPUT"    SECS";S
 2035 POKE557,H
 2040 POKE556,M
 2045 POKE555,S
 2050 POKE11,125
 2060 POKE12,2
 2070 X=USR(X)
 2100 Z=53660
 2110 FORQ2=1TO16:PRINT:NEXT
 2200 REM MAIN CLOCK LOOP
 2230 IFF1=0THEN3000
 2240 F1=0
 2250 IFF=2THEN6000
 2260 GOTO4000
 3000 REM CLOCK DISPLAY
 3020 H=PEEK(557)
 3030 M=PEEK(556)
 3040 S=PEEK(555)
 3100 H$=STR$(H)
 3120 M$=STR$(M)
 3140 S$=STR$(S)
 3160 T$="  "+H$+":"+M$+":"+S$+"    "
 3200 REM POKE ROUTINE
 3210 FORI=1TOLEN(T$)
 3220 Q=ASC(MID$(T$,I,1))
 3230 POKEZ+I,Q
 3240 NEXT
 3500 REM SPACE BAR SCAN
 3510 POKE530,1
 3520 POKE57088,253
 3530 IFPEEK(57088)=239THENF1=1
 3540 POKE530,0
 3545 IFF=2THEN5550
 3550 GOTO2200
 4000 PRINT:PRINT:PRINT"  DISPLAY ROUTINE EXITED"
 4010 PRINT"  CLOCK CONTINUES"
 4020 PRINT"  TO RESUME DISPLAY, RUN 2100
 4030 POKE530,0
OK
```

Table 7.2. Interrupt Clock in BASIC

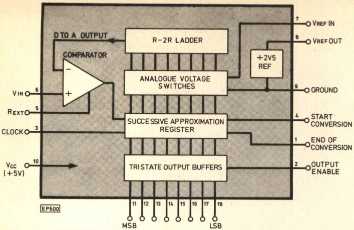

Fig. 7.1. ZN427 Block Diagram

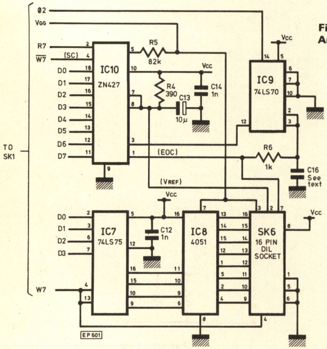

quad latch IC7. This is enabled by line W7 from the Decoding Module. The 8 channels are selected by POKEing the channel number (0-7) to address 61319. Thus the command POKE 61319, 6 will connect channel 6 (at pin 10 of SK6) to the input of the converter.

The converter itself requires a low-enable Start Conversion pulse, and this is supplied by $\overline{W7}$ from the Decoding Module. This means that each time the multiplexer at 61319 is addressed, a new conversion sequence is initiated.

The clock input of the converter at pin 3 requires a frequency less than 600 kHz. In order to satisfy this condition, IC9 is used to divide the UK101 Ø2 clock by two, giving a clocking frequency of 500 kHz. Other timing conditions of the ZN427 are satisfied by delaying the operation of the divide by two counter until the ZN427 End of Conversion signal (EOC) goes negative. This is achieved by taking pin 1 of IC10 to pins 2 and 3 of IC9. In the prototype, this was further delayed by the insertion of C16 (50nF); and this capacitor was included in the component overlay diagram published in part 4 of the series. This extra delay time is not necessary for any of the applications described below, and it is recommended that C16 be removed from the board, so greatly enhancing conversion times.

The EOC signal produced by the ZN427 to indicate the completion of conversion has been taken to pin 7 of SK6, and may be monitored by the CPU if required, although conversion is so fast that there is barely time to monitor it in machine code (and certainly not in BASIC) before conversion is completed. Once conversion has taken place, the converter may be read at 61319. Thus the following two commands will print the value of the analogue input on channel 4.

POKE 61319, 4
PRINT PEEK(61319)

The POKE and PEEK statements may of course be put within a FOR loop to sequence through each of the 8 channels:

FOR A = 0 TO 7
POKE 61319, A
PRINT PEEK(61319)
NEXT

Fig. 7.2. A/D section of Analogue Board

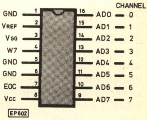

Fig. 7.3. Connections to SK6 on Analogue Board

```
50 REM INTERFACING UK101 PROGRAM 20
60 REM MACHINE CODE TO BASIC TRANSLATOR
70 PRINT:PRINT:PRINT:PRINT
72 PRINTTAB(6)"MACHINE CODE TO BASIC TRANSLATOR"
74 PRINT:PRINT
75 PRINT"    THIS PROGRAM PRODUCES A TAPED PROGRAM"
76 PRINT"    IN BASIC FOR REPRODUCING ANY BLOCK OF"
77 PRINT"    MEMORY LOCATIONS"
90 PRINT:PRINT:PRINT
92 PRINT"    ARE START AND END ADDRESSES OF MEMORY"
93 PRINT"    BLOCK IN HEX"
95 INPUTY$
96 IFLEFT$(Y$,1)="Y"THEN600
98 PRINT
100 INPUT"   START ADDRESS IN MEMORY";AS
105 PRINT
110 INPUT"   END ADDRESS IN MEMORY";AE
120 INPUT"   FIRST LINE NO OF BASIC PROG";NB
130 PRINT"   TITLE OF BASIC PROGRAM"
135 INPUTA$
140 SAVE
150 PRINT"   START RECORDER"
160 INPUT"   ENTER S TO START";B$
200 PRINTNB; "REM ";A$
205 PRINTNB+5; "REM LOCATIONS ";AS;" TO ";AE
210 FORA=0TO(AE-AS)STEP10
220 PRINTNB+10+A;" DATA";
230 FORB=0TO9
240 PRINTPEEK(AS+A+B);
250 IFAS+A+B=AETHENB=10
254 IFB<9THENPRINT",";
260 NEXT
270 PRINT
280 NEXT
400 Z=NB+100+10*INT((AE-AS)/10)
410 PRINTZ;" FORC=0 TO ";AE-AS
420 PRINTZ+10;" READ I"
430 PRINTZ+20;" POKE ";AS;"+C, I"
440 PRINTZ+30;" NEXT"
450 FORZX=1TO5000:NEXT
500 POKE517,0
510 FORA=1TO16:PRINT:NEXT
520 PRINT,"RECORDING COMPLETE"
550 END
600 PRINT"   START ADDRESS (HEX) IN MEMORY"
620 GOSUB900
630 AS=N
635 PRINT
640 PRINT"   END ADDRESS (HEX) IN MEMORY"
650 GOSUB900
660 AE=N
670 GOTO120
900 REM HEX CONVERSION
910 INPUTQ$
920 IFLEN(Q$)<>4THENPRINT:PRINT"  4 DIGIT FORMAT ONLY":GOTO900
930 N=0
940 X$="0123456789ABCDEF"
950 FORJ=1TO4
960 FORI=1TO16
970 IFMID$(Q$,J,1)=MID$(X$,I,1)THEN1010
980 NEXTI
990 PRINT:PRINT"  CHARACTER NOT IDENTIFIED - REDO"
1000 GOTO900
1010 N=N+(I-1)*16^(4-J)
1020 NEXTJ
1030 PRINT"   DECIMAL EQUIVALENT = ";N
1050 RETURN
OK
```

Table 7.3. Machine Code to Basic Translator Program

The conversion scale of the ZN427 is determined by the voltage applied to its pin 7. On the Analogue Board this is connected to the ZN427's precision 2·55 volt reference source, which results in a very convenient conversion scale of 10 mV per digit, so that an input of 2·17 volts for example will produce a digital value of 217, and so on.

EIGHT CHANNEL DISPLAY PROGRAM

The program in Table 7·4 may be used to monitor the input levels on all 8 channels of the converter. Analogue to digital conversion is carried out in lines 220 and 230, and the updated conversion result POKEd to the screen, after suitable processing. As may be seen from the photograph, a horizontal bar graph representation is also produced for each channel. This latter is only altered in subsequent passes if a change in input voltage is detected. The program may be exited by depressing the space bar.

VOLTAGE MEASURING

As it stands, the converter will measure voltages from 0 to 2·55 volts presented to the input pins of its 8 channels (ie pins 16 to 9 of SK6, corresponding to channels 0 to 7 respectively). For accurate conversion, each input should be loaded with an impedance of 10k or less. This is necessary to ensure an impedance match with the input circuitry of the ZN427, and also in order to avoid charge carry-over from one channel to the next as the multiplexer sequences through the channels. If for example a voltage is applied to channel 0, and the input of channel 1 is left floating, channel 1 will read a non-zero voltage as measured in the display program of Table 7.4. This is avoided by keeping input loads below 10k and by earthing unused inputs.

If it is required to increase the voltage range of any channel of the converter, this may be accomplished by using a resistor network. That shown in Fig. 7.4 gives a scale factor of two so that 5 volts will give a reading of 250. The resistors used should be 1% types or better, although if these are not available, lower tolerance resistors could be trimmed (by constructing series/parallel combinations) so as to give a reading of 127 or 128 when point X is connected to pin 2 of SK6. This is the ZN427's own 2·55 volt reference source. The function of C in the dropper network is to keep the input impedance low enough to match the ZN427. Similar techniques may be used to extend the range further.

ANALOGUE JOYSTICK

Each of the 8 channels of the converter may be used with a virtually infinite variety of sensors. We will give circuits for use with some of the more obvious. Fig. 7.5 gives a circuit for a two-direction joystick. Each joystick potentiometer is supplied by the 2·55 volt reference source, and 100nF capacitors are again used to keep the input impedance low. As the circuit stands the two joysticks are connected to channels 0 and 1, and very straightforward software could be used to move a cursor or other character to any point of the screen in response to the position of the joystick. With the analogue use of the joystick, as opposed to the digital applications discussed in parts 3 and 5 of the series, the cursor could immediately move to the selected spot without having to traverse all intermediate screen positions first.

LIGHT SENSOR

Fig. 7.6 gives the circuit for an l.d.r. light sensor. With R1 at 1k this produces a good range of output, from very dim conditions (a v.d.u. screen at 1 metre) to brightly lit interiors. Higher precision in dark conditions may be achieved by increasing the value of R1, while improving the range in very bright conditions will be limited by the current drawn.

Table 7.4. Eight Channel A/D Converter Display

```
100 REM INTERFACING UK101 PROGRAM 21
110 REM 8 CHANNEL A/D CONVERTER DISPLAY
120 FORA=1TO8:PRINT:NEXT
130 PRINTTAB(10)"8 CHANNEL A/D CONVERTER"
140 PRINT:PRINTTAB(13)"(SPACE BAR EXITS)"
150 PRINT:PRINT:PRINT:PRINT:PRINT:PRINT
160 FORA=1TO3000:NEXT
170 FORA=1TO16:PRINT:NEXT
180 GOSUB 470
190 Z=53335
200 B=61319
210 FORA=0TO7
220 POKEB,A
230 N=PEEK(B)
240 S=Z+A*128
250 GOSUB 300
260 GOSUB 560
270 NEXT
280 GOSUB 410
290 GOTO210
300 REM NUMERICAL DISPLAY ENTRY POINT
310 REM SCREEN POKE ROUTINE
320 N$=STR$(N)
330 L=LEN(N$):REM STRING DISPLAY ENTRY POINT
340 FORM=1TOL
350 Q=ASC(MID$(N$,M,1))
360 POKES+M,Q
370 NEXT
380 IFPEEK(S+M)=32THEN 400
390 POKES+M,32:M=M+1:GOTO 380
400 RETURN
410 REM SPACE BAR MONITOR
420 POKE530,1
430 POKE57088,253
440 IFPEEK(57088)=239THENPOKE530,0:END
450 POKE530,0
460 RETURN
470 REM TEXT HANDLING
480 B$="CHANNEL"
490 Z=53323
500 FORA=0TO7
510 N$=B$+STR$(A)
520 S=Z+A*128
530 GOSUB 330
540 NEXT
550 RETURN
560 REM BAR DISPLAY CALCULATION
570 N1=INT(N/10+.5)
580 N2=N1-N(A)
590 IFN2=0THENN(A)=N1:RETURN
600 IFN2<0THEN 650
610 FORQ1=N(A)TON1-1
620 POKES+6+Q1,161
630 NEXT
640 GOTO 680
650 FORQ1=N(A)TON1STEP-1
660 POKES+6+Q1,32
670 NEXT
680 N(A)=N1
690 RETURN
OK
```

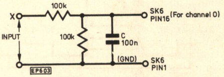

Fig. 7.4. Divide by two network

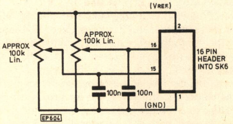

Fig. 7.5. Connection of 2 axis joystick to A/D converter

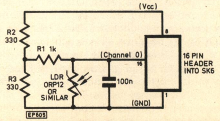

Fig. 7.6. Connection of light sensor to A/D converter

The left hand end of R1 could have been connected to the 2·55 volt reference source at pin 2 of SK6, but this is easily overloaded (maximum loading about 1k), and it is more prudent to use the pair of dropper resistors shown; or alternatively a 2·5 volt zener could be used. With the circuit of Fig. 7.6, quite small changes in light level may be discerned; and by using an l.d.r. on each channel, pattern recognition experiments may be undertaken. For such an application nine (or better still, sixteen) would be a more appropriate number of light sensors to use, in which case a second multiplexer could be added, either driven by one port of the PIA or VIA, or using a second 74LS75 latch, for which purpose the decoded line W7 has been taken out to pin 4 of SK6 on the Analogue Board. In such an application it should be noted that POKEing a one to bit 3 at 61319 renders the analogue switch IC8 open circuit.

TEMPERATURE SENSOR

Thermistors may be used for temperature measurement using a simple dropper resistor in the same manner as described for the l.d.r. application, although only fairly high resistance types are suitable, in order to avoid self-heating effects.

Far more precise measurement may be achieved for little extra outlay by using a temperature sensing diode such as the LM335Z. This is essentially a diode whose forward voltage is dependent on its temperature in a very linear manner, at the rate of 10mV per degree Kelvin. This means that its voltage increases by 10mV for every degree Centigrade above absolute zero (−273°C). Thus at 20°C its forward voltage will be 2·93. This voltage is unfortunately beyond the direct range of the A/D converter. But it is easily reduced with a resistor network such as that shown in Fig. 7.7. This will produce a reading of about 146 at 20°C.

To improve the reading precision, a d.c. amplifier with offset facility can be used between the sensor and the converter. Fig. 7.8 gives a circuit for such an arrangement. With this the voltage gain of the amplifier can be altered from unity to about 50 by adjusting VR1, and an offset of ±3 volts at maximum gain can be achieved by altering VR2. It should be noted however, that even at quite modest gain settings, the earth loop caused by using the UK101's mains transformer to drive the Decoding Module produces hum problems, and a small fluctuation appears on the reading. To avoid this, a separate 9-0-9 volt transformer should be used to power the Decoding Module.

To obtain the highest precision with the LM335Z (1°C error at room temperature) it should be used in conjunction with a 10k potentiometer as in Fig. 7.9, and the potentiometer adjusted to give an output as close to 2·982 volts as possible at 25°C.

The d.c. amplifier of Fig. 7.8 may also be used for increasing the sensitivity of the converter for use in other applications, such as d.c. voltage measurement etc.

AUDIO DETECTION

The circuit of Fig. 7.10 allows sound levels to be measured with the A/D converter. Like the temperature sensor amplifier of Fig. 7.8, it uses a 741 op. amp., but no earth loop hum problems arise in this case because no offset is required, and pin 2 can be taken down to earth. The values of R1 and C1 in the integrator following the diode detector circuit should be selected to give a time constant appropriate to the use to which the unit is to be put. Generally speaking this should be somewhat greater than the sample repetition time of the program driving the converter. In the case of the 8 channel display program of Table 7.4, a time constant of about one tenth of a second is appropriate, and may be achieved using 10k for R1 and 10μ for C1. For much higher sample repetition rates, such as those achievable with the sample 'scope program below, C1 may be removed completely for certain applications.

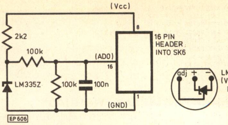

Fig. 7.7. Connection of Temperature Sensor to A/D converte

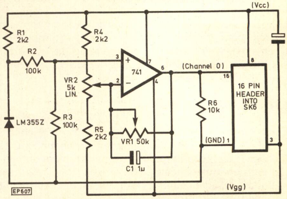

Fig. 7.8. Temperature Sensor with voltage amplifier

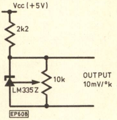

Fig. 7.9. Calibration of LM335Z temperature sensor

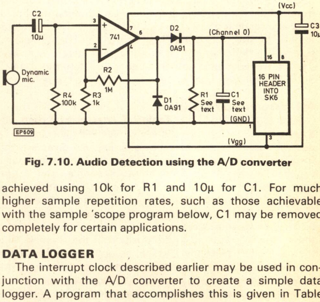

Fig. 7.10. Audio Detection using the A/D converter

DATA LOGGER

The interrupt clock described earlier may be used in conjunction with the A/D converter to create a simple data logger. A program that accomplishes this is given in Table 7.5. To use it, load the interrupt clock program in BASIC of Table 7.2, then load the data logger supplement of Table 7.5. The latter makes use of routines in the former, including the interrupt clock itself, to implement the data logging function. When RUN is executed, the interrupt clock will operate as before, but now pressing the space bar will cause a transfer to the data logger. This requests a start time for logging in hours, minutes and seconds; then a repetition

```
4090 REM INTERFACING UK101 PROGRAM 22
4100 REM DATA LOGGER SUPPLEMENT
4110 REM TO BE LOADED ON TOP OF
4120 REM PROGRAM 19 (THE INTERRUPT
4130 REM CLOCK)
5000 REM DATA LOGGER
5020 F=2:Z=53276:NA=0
5100 FORQ2=1TO16:PRINT:NEXT
5110 PRINT,"DATA LOGGER"
5130 PRINT:PRINT:PRINT"   START TIME OF RECORDING"
5140 INPUT"   HOURS";SH
5142 INPUT"   MINUTES";SM
5144 INPUT"   SECONDS";SS
5150 PRINT:PRINT"   REPETITION PERIOD OF READINGS"
5160 INPUT"   HOURS";RH
5170 INPUT"   MINUTES";RM
5180 INPUT"   SECONDS";RS
5190 PRINT:PRINT"   NUMBER OF READINGS"
5200 INPUTNR
5210 DIMA(NR,8):DIMA$(NR)
5220 FORQ4=1TO16:PRINT:NEXT
5230 PRINT"  NO";TAB(11)"TIME";TAB(33)"DATA"
5500 GOTO2200
5550 REM ENTRY POINT
5560 IFS=SSANDM=SMANDH=SHTHEN5600
5570 GOTO2200
5600 REM DATA AQUISITION
5605 PRINT" ";NA+1;"..";
5610 PRINTT$;
5620 FORQ2=0TO7
5625 IFQ2=4THENQ3=-24:PRINT
5630 POKE61319,Q2
5640 A(NA,Q2)=PEEK(61319)
5650 PRINTTAB(23+6*Q2+Q3);
5660 PRINTA(NA,Q2);
5670 NEXT
5680 Q3=0
5690 PRINT:PRINT
5695 NA=NA+1:IFNA=NRTHEN6100
5700 CS=0:CM=0
5710 SS=SS+RS
5720 IFSS>59THENSS=SS-60:CS=1
5730 SM=SM+RM+CS
5740 IFSM>59THENSM=SM-60:CM=1
5750 SH=SH+RH+CM
5760 IFSH>=24THENSH=SH-24
5800 GOTO2200
6000 PRINT,"EXIT FROM DATA LOGGER"
6010 GOTO6110
6100 PRINT,"DATA LOGGING COMPLETE"
6110 PRINT,NA;"READINGS TAKEN"
6120 PRINTTAB(15)"TIME";T$
6125 PRINT:PRINT
6130 PRINT"TO DISPLAY CLOCK, RUN 2100"
6140 PRINT"TO RESTART LOGGER, RUN 5000"
```

Table 7.5. Data Logger Supplement

```
100 0000          ;SAMPLE SCOPE
110 0000          START=$0230
120 0230          *=START
130 0230          ;INPUT ROUTINE
140 0230 AE2E02 LDX START-2
150 0233 AD2F02 BB LDA START-1
160 0236 8D87EF STA 61319
170 0239 AC2D02 LDY START-3
180 023C 88     AA DEY
190 023D EA     NOP
200 023E EA     NOP
210 023F EA     NOP
220 0240 D0FA   BNE AA
230 0242 AD87EF LDA 61319
240 0245 9D9002 STA $0290,X
250 0248 CA     DEX
260 0249 D0E8   BNE BB
270 024B 60     RTS
280 024C 00     BRK
290 024D 00     BRK
300 024E 00     BRK
310 024F 00     BRK
400 0250          ;OUTPUT ROUTINE
410 0250 AE2E02 CC LDX START-2
420 0253 BD9002 DD LDA $0290,X
430 0256 8D88EF STA 61320
440 0259 AC2C02 LDY START-4
450 025C 88     EE DEY
460 025D EA     NOP
470 025E EA     NOP
480 025F EA     NOP
490 0260 D0FA   BNE EE
500 0262 CA     DEX
510 0263 D0EE   BNE DD
520 0265 4C5002 JMP CC
```

Table 7.6. Assembler Listing of Sample 'Scope

period in hours, minutes and seconds; and lastly the number of loggings required. This latter number sets the dimension of two arrays A$(I), which records the time of each reading, and A(I,J), which contains the 8 data values recorded at each reading.

The program then initiates the continued POKEing of the time to the centre of the top line of the screen, at the same time continually checking to see whether the start time has been reached. When it has, the A/D converter sequences through its 8 channels, and the resultant data is stored in the array for later use. The number of the reading, the time and the 8 data values are also printed on to the screen. See accompanying photograph. The program then waits for the duration of the repetition period, and again stores and prints the data measured. If hard copy or cassette recording of the data is required, an appropriate routine may be added at 6200 to be executed after data logging has been completed. And as with the interrupt clock itself, the space bar may be used to exit the data logger.

The logger program is highly flexible, and can take readings at intervals as short as 1 second, or as long as 24 hours, and the number of readings allowed is limited only by the memory size of the machine. A 4k machine will allow some 15 or 16 readings, while with 8k this rises to somewhere above 110. If memory size is a problem, a considerable saving could be made by storing the measured data individually in RAM by means of POKE statements to a protected area. Alternatively the program could be modified so as to print out, but not to store, the data, in which case there is no limit to the number of readings taken.

The uses to which the data logger may be put are legion. It could for example be used to monitor the temperature, noise, light and humidity levels in a given locality; and checks could be made on the effectiveness of thermal insulation by recording inside and outside temperature over a 24 hour period. It could also be used to gather data on the temperature dependence of a resistance, or to record the voltage decay curve of a CR combination of sufficiently long time constant. Additionally, the logger could be used in conjunction with the event recorder using T2 of the VIA described last month, to log the number of events of a given kind occurring within any period. Those events could variously be counts from a Geiger-Muller tube, passages across a photocell, the occurrence of sound levels above a given threshold etc. Once the data has been collected from whatever source, the UK101 can then be used to analyse it in any appropriate manner, and to present the results graphically if so desired.

WAVEFORM SAMPLING

The very fast conversion rate attainable with the ZN427 A/D converter—around 50,000 per second—allows the sampling and digital storage of waveforms at frequencies up to a few kHz. Using the converter a series of samples may be taken in very rapid succession, and stored in RAM, from where they may be analysed at leisure. For example, Fourier analysis might be performed on the data, or the sampled waveform could be replayed continuously through the D/A converter for steady display on an oscilloscope screen. Alternatively the UK101 VDU screen could be used to display the sampled waveform.

For such applications it is obviously essential to use machine code, since using BASIC would only allow some 100 or so samples to be taken every second. Table 7.6 gives an assembler listing of a two-part program which has a sampling and replay facility. The first part, which is located at 0230 hex, causes a series of samples to be taken and stored in RAM above 0290 hex. The sampling rate, the number of samples, and the channel number from which the samples are taken are determined by the contents of locations 022D, 022E and 022F respectively, and these may be set up before the program is run. The second part of the program, which begins at 0250 hex, allows the replay of the stored data in a continuous loop to the D/A converter located at 61320 dec. The number of samples to be replayed, and the replay rate, are determined by the contents of locations 022E and 022C respectively, and again these parameters may be set up before the routine is run.

A program in BASIC is given in Table 7.7 which loads the above program, and then controls the sampling and replay parameters with a series of INPUT statements. The program sets the channel number to 0, and the number of samples to 100 in lines 280 and 290. These may be altered if required, though 100 is the maximum number of samples allowed. It then requests a sample rate from 1 (fast) to 255 (slow), and after making the sample, requests a replay rate. It then replays through the D/A converter in a continuous mode, which can only be exited through a reset and warm-start.

The accompanying photographs show a 'scope trace of a 100Hz waveform that was sampled and replayed using this program. The original waveform is also shown. As may be seen from this, fidelity of reproduction is very good, even though no sample-and-hold circuitry has been used in the A/D conversion.

Sampling with this arrangement is fast enough for the lower end of the audio spectrum, and the circuit of Fig. 7.10 may be used in conjunction with the sampler to allow sampling of parts of speech signals and other audio waveforms.

As suggested above, the 100 data samples produced by the sampler may be analysed at leisure, or modified before replaying them through the D/A converter. If it is required to work on more than one set of samples, for comparison purposes for example, the 100 bytes of data may be transferred to another location using PEEK and POKE commands. The 100 bytes from 0290 hex would then be used simply as a temporary input buffer for the incoming data.

VDU SAMPLE SCOPE

If no suitable oscilloscope is available, or a larger display is required, the add-on program of Table 7.8 will allow for any 40 byte wide part of the sampled waveform to be displayed on the UK101 screen. When this program is loaded on top of the sample scope program of Table 7.7, it requests an offset factor to be entered (0-60) after the sampling routine has been executed, and POKEs up a display on the screen, using the characters 128-135 to achieve a vertical resolution of 128. The offset factor determines whereabouts along the 100-wide sample the display is taken from, and altering this moves the 40-byte wide sample window to left or right through the 100 bytes of data. If the space bar is depressed during the display, a new offset factor may be entered to change the position of the window. If a number greater than 60 is entered here, the program re-enters the sampling routine so that a new sample may be taken. The accompanying photograph shows the screen representation of the 100 Hz signal shown in the oscilloscope trace photographs referred to earlier. As may be seen, reproduction quality is quite good given the constraints imposed by the UK101's low resolution graphics.

CUSTOMISED WAVEFORM GENERATOR

The D/A section of the machine code routine referred to above may also be used on its own for the creation of customised waveforms. The 100 bytes of memory space above 0290 hex can be filled from BASIC using SIN, COS, LOG, RND, power or other functions of the user's choice. The replay routine in machine code may then be executed to generate the waveform repeatedly, and at speed, through the D/A converter at 61320.

The number of bytes of digitised waveform sent to the D/A converter before the sequence is repeated is determined by the data held in location 558 dec. This may be POKEd with any value from 1 to 100 so as to achieve a smooth follow on from the end of one displayed cycle of the waveform to the next.

Table 7.7. Sample Oscilloscope in BASIC

```
100 REM INTERFACING UK101 PROGRAM 23
110 REM SAMPLE SCOPE PROGRAM
120 GOSUB 360
130 REM
140 FORA=1TO16:PRINT:NEXT
150 PRINT,"SAMPLE SCOPE"
160 PRINT,"ON CHANNEL 0"
170 PRINT:PRINTQQ$
180 GOSUB270
190 POKE11,48:POKE12,2:X=USR(X)
200 PRINT:PRINT:PRINT"    SAMPLE MADE"
210 PRINT:PRINT
220 INPUT"    REPLAY RATE (1-255)";RR
230 PRINT:PRINT"    REPLAY IN PROGRESS"
240 PRINT"    USE RESET KEYS TO EXIT"
250 POKE556,RR
260 POKE11,80:POKE12,2:X=USR(X)
270 REM INITIALISATION
280 C=0:REM SET CHANNEL
290 N=100:REM SET NO OF SAMPLES (100 = MAX)
300 INPUT"    SAMPLE RATE 1 (HIGH) TO 255 (LOW)";R
310 IFR<1ORR>255THEN300
320 POKE559,C
330 POKE558,N
340 POKE557,R
350 RETURN
360 REM MACHINE CODE PROGRAM
370 REM LOCATIONS  560  TO  615
380 DATA 174 , 46 , 2 , 173 , 47 , 2 , 141 , 135 , 239 , 172
390 DATA 45 , 2 , 136 , 234 , 234 , 234 , 208 , 250 , 173 , 135
400 DATA 239 , 157 , 144 , 2 , 202 , 208 , 232 , 96 , 0 , 0
410 DATA 0 , 0 , 174 , 46 , 2 , 189 , 144 , 2 , 141 , 136
420 DATA 239 , 172 , 44 , 2 , 136 , 234 , 234 , 234 , 208 , 250
430 DATA 202 , 208 , 238 , 76 , 80 , 2
440 FORC=0 TO  55
450 READ I
460 POKE  560 +C, I
470 NEXT
480 RESTORE
490 RETURN
```

Table 7.8. Supplement to Sample Oscilloscope for Screen Display of Waveform

```
205 REM INTERFACING UK101 PROGRAM 24
206 REM GIVES SCREEN DISPLAY OF
207 REM SAMPLED WAVEFORM
208 REM LOAD ON TOP OF PROGRAM 23
210 GOTO7000
7000 REM SCREEN DISPLAY ROUTINE
7050 INPUTZZ
7060 IFZZ<0 OR ZZ>60THEN110
7070 ZZ=60-ZZ
7100 X=54222
7110 FORQ=1TO16:PRINT:NEXT
7120 S=656 +ZZ+40
7130 FORN=0TO40
7140 H=INT((PEEK(S-N))/2)
7150 H1=INT(H/8)
7160 H2=INT((H-H1*8))
7170 POKEN+X-64*H1,H2+128
7200 NEXT
7250 POKE530,1
7260 POKE57088,253
7270 IFPEEK(57088)<>239THEN7260
7280 POKE530,0
7290 GOTO7000
```

A NOTE ON THE USE OF NEW MONITORS

All programs in this series are fully compatible with the UK101's original monitor, and with Technomatic's CE1 monitor. But difficulties may arise with other new monitors when using the 3 or 4 programs that contain machine code routines located at 0230 hex, such as the Interrupt Clock and the Sample Scope program. The reason for this is that monitors such as Cegmon, Wemon and Compshop's new monitor use some of the space above 022A hex for scratchpad purposes. With Cegmon this space can be kept free by disabling the screen editor, and using the original screen handling routines. But to get around the problem more generally, an alternative set of programs have been prepared for the Interrupt Clock and Data Logger, and the Sample Scope, which relocate the machine code routines at the top of memory. There is no space to list these programs here, but they are included in the cassette containing the 24 numbered programs from this series, available from *Technomatic Ltd.*

On Wemon and Compshop's new monitor, but not on the CE1 or Cegmon, the IRQ vector has also been relocated, and this must be accounted for in programs such as the Interrupt Clock and Data Logger, which make use of IRQ, by modifying lines 720, 740 and 760 of the assembler listing in Table 7.1. Further details on this modification are given in the data supplied with the cassette, since the shifted version of these programs must in any case be used with these two monitors.

INTERFACING COMPUKIT

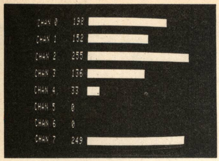

```
CHAN 0   198
CHAN 1   152
CHAN 2   255
CHAN 3   136
CHAN 4,  33
CHAN 5   0
CHAN 6   0
CHAN 7   249
```

Screen Photograph of Eight Channel Display Program

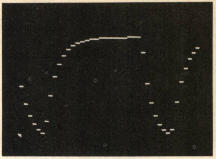

Screen display of sampled 100Hz waveform

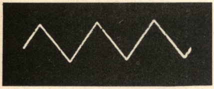

Triangular Waveform generated by the Customised Waveform Generator, and output through the D/A Converter

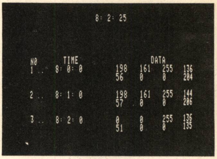

```
            8: 2: 25



NO      TIME                      DATA
1 ..    8: 0: 0         198   161   255   136
                        56    0     0     204

2 ..    8: 1: 0         198   161   255   144
                        57    0     0     206

3 ..    8: 2: 0         0     0     255   136
                        51    0     0     135
```

Screen Photograph of Data Logger

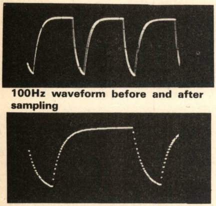

100Hz waveform before and after sampling

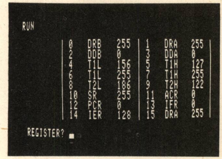

```
RUN

        | 0   DRB   255 | 1   DRA   255 |
        | 2   DDB   0   | 3   DDA   0   |
        | 4   T1L   156 | 5   T1H   127 |
        | 6   T1L   255 | 7   T1H   255 |
        | 8   T2L   186 | 9   T2H   122 |
        | 10  SR    255 | 11  ACR   0   |
        | 12  PCR   0   | 13  IFR   0   |
        | 14  IER   128 | 15  DRA   255 |

 REGISTER? ■
```

Screen photograph taken during the running of the 6522 Handling Program (Program 12) described last month

NEXT MONTH . . . we shall be publishing an **EPROM PROGRAMMER** which may be driven from this interface system.

Additionally, we will be taking a look at **Chromosonic's Colour Board** in use with the UK101

Constructor's Note

In order to improve stability in the offset adjustment on the D/A converter op amp IC11, R10 on the Analogue Board should be increased to 47k.

Filling the data space using the program below will produce an even triangular wave made up of exactly 100 samples:

```
2000 FORA=0TO99
2010 B=4×A
2020 IFA>49THENB=4×(99−A)
2030 POKE656+A,B
2040 NEXT
2050 GOTO300
```

The accompanying photograph shows the waveform produced using this program. As may be seen, its shape is good, and since it is constructed of a relatively large number of samples, its true step nature is not apparent in the photograph. It should be noted when creating other waveforms using the machine code replay sequence, that although the storage space for the waveform begins at 0290 hex, this location is the *last* rather than the *first* to be accessed, so that the *last* byte of waveforms placed into these locations for subsequent replay should be at 0290 hex, the first being at 0290+N-1, where N is the number of samples to be replayed.

CONCLUSION

Although this is the final article of the present series, it by no means exhausts the possible applications of the UK101 Decoding Module and Analogue Board. Further applications are planned for future issues of P.E., and it is hoped that ideas will also be contributed by UK101 and Superboard users through the columns of P.E.'s MicroPrompt. ★

D.I.Y. KITS FOR SYNTHESISERS, SOUND EFFEC

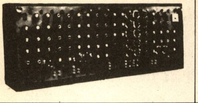

BASIC COMPONENTS SETS include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits PCBs and parts are shown in our lists.

LAYOUT DIAGRAMS are supplied free with all PCBs unless "as published".

AMERICAN EXPRESS · Buy it with Access · BARCLAYCARD VISA

PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

P.E. MINISONIC MK2 SYNTHESISER

A portable mains operated miniature sound synthesiser with keyboard circuits. Although having slightly fewer facilities than the large Formant synthesiser the functions offered by this design give it great scope and versatility. 3 Oct KBD & GJ contacts needed.

Set of basic component kits (excl.KBD R's & tuning pots – see list for options available) and PCBs (incl. layout charts)	KIT 38-25	**£80.14**
"Sound Design" booklet		**£1.00**
Knobs, skts, sw's		See our list

P.E. 128-NOTE SEQUENCER

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable. 4 Oct KBD and GJ contacts needed.

Set of basic comps, PCBs and charts	KIT 76-7	**£35.56**
Set of text photocopies	TEXT 76	**£1.36**
Knobs, skts, sw's	HW 76	**£6.62**

P.E. 16-NOTE SEQUENCER

Sequences of up to 16 notes may be programmed by the panel controls and fed into most voltage controlled synthesisers.

Set of basic comps, PCBs and charts	KIT 86-5	**£32.10**
Set text photocopies	TEXT 86	**£1.84**
Knobs, sets, sw's	HW 86	**£11.15**

P.E. STRING ENSEMBLE

A multivoiced polyphonic string instrument synthesiser.

Set of basic comps, PCBs & charts	KIT 77-8	**£109.72**

ELEKTOR CHOROSYNTH

A 2½-octave Chorus synthesiser with an amazing variety of sounds ranging from violin to cello and flute to clarinet amongst many others. Experienced constructors can readily extend the octave coverage. 3 Oct KBD and GJ contacts needed.

Basic comps, PCBs and charts	KIT 100-8	**£44.39**
Text photocopy	TEXT 100	**70p**
Knobs, skts, sw's	HW 100	**£11.55**

ELEKTOR FORMANT SYNTHESISER

A very sophisticated synthesiser for the advanced constructor who puts performance before price.

Set of basic comps, PCBs (as publ.)	KIT 66-14	**£255.45**
Set of text photocopies	TEXT 66	**£7.83**
Knobs, skts, sw's		See our list

ELEKTOR DIGITAL REVERB UNIT

A very advanced unit using sophisticated i.c. techniques instead of mechanical spring lines. The basic delay range of 24 to 90mS can be extended up to 450mS using the extension unit. Further delays can be obtained using more extensions.

Main unit basic comps and PCB (as publ.)	KIT 78-3	**£49.95**
Extension unit comps and PCB	KIT 78-4	**£39.95**
Text photocopy	TEXT 78	**86p**
Knobs, skts, sw's	HW 78	**£2.94**

ELEKTOR ANALOGUE REVERB

Using i.c.s instead of spring-lines the main unit has a maximum delay of up to 100mS, and the additional set extends this up to 200mS. May be used in either mono or stereo mode.

Main unit basic component set	KIT 83-4	**£29.23**
Additional Delay basic components	KIT 83-2	**£20.07**
PCB (as publ.) to hold both kits included in Kit 83-4		
Text photocopy	TEXT 83	**67p**
Knobs, skts, switch	HW 83	**£2.84**

ELEKTOR SEWAR

For use with Elektor Analogue Reverb to give greater flexibility to the reverb effects.

Basic comps, PCB (as publ.)	KIT 101-1	**£18.19**
Text photocopy	TEXT 101	**60p**
Knobs, skts, switch	HW 101	**£2.44**

NEW KITS

EE 3-CHAN STEREO MIXER

Full level control on left and right of each channel, and with master output control and headphone monitor.

Basic comps, PCB & chart	KIT 107-1	**£8.61**
Text photocopy	TEXT 108	**65p**
Knobs, skts & sw's	HW 107	**£3.19**

3-MICROPHONE STEREO MIXER

Enables stereo live recordings to be made without the 'hole in the middle' effect. Independent control of each microphone.

Basic comps, PCB & chart	KIT 108-1	**£5.41**
Text photocopy	TEXT 108	**55p**
Knobs, skts, & sw's	HW-108	**£2.55**

E.E. HEADPHONE AMPLIFIER

For use with magnetic, ceramic or crystal pick-ups, tapedeck or tuner, and for most headphones. Designed with RIAA equalisation.

Basic comps, PCB & chart	KIT 104-1	**£9.79**
Text photocopy	TEXT 104	**85p**
Knobs, & sockets	HW 104	**£2.50**

E.E. AUDIO EFFECTS UNIT

A variable siren generator that can produce British & American police sirens, Star Trek, Red Alert, heart-beat monitor sounds, etc.

Basic comps, PCB & chart	KIT 105-1	**£4.87**
Text photocopy	TEXT 105	**65p**
Knobs, skts & switch	HW 105	**£1.91**

GUITAR PRACTISE AMPLIFIER

A 3 watt mains powered amplifier suitable for instrument practise or as a test gear monitor. Drives 8 or 15 ohm loudspeaker.

Basic comps, PCB & chart	KIT 106-1	**£9.81**
Text photocopy	TEXT 106	**65p**
Knobs, skts, switch	HW 106	**£2.02**

SIGNAL TRACER & GENERATOR

Allows audio signals to be injected into circuits under test, and for tracing their continuity. Includes frequency & level controls.

Basic comps, PCB & chart	KIT 109-1	**£5.80**
Text photocopy	TEXT 109	**55p**
Knobs, skts, sw's & probes	HW 109	**£3.17**

P.E. GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration.

Basic comps, PCB & chart	KIT 75-1	**£6.99**
Text photocopy	TEXT 75	**38p**
Knobs & sets	HW75	**91p**

P.E. AUTO-WAH UNIT

Automatically give Wah or Swell sounds with each note played.

Basic comps, PCB & chart	KIT 58-1	**£10.11**
Text photocopy	TEXT 58	**58p**
Knobs & skts	HW58	**£1.26**

ELEKTOR WAVEFORM CONVERTER

Converts a saw-tooth waveform into sinewave, mark-space saw-tooth, regular triangle, or square-wave with variable mark-space.

Basic comps, PCB & chart, but excl. sw's	KIT 67-1	**£9.24**
Knobs, skts, sw's	HW 67	**£4.23**

P.E. SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses.

Basic comps, PCB & chart	KIT 89-1	**£4.34**
Text photocopy	TEXT 89	**78p**
Knobs, skts, sw's	HW 89	**£1.89**

ELEKTOR RING MODULATOR

Compatible with the Formant & most other synthesisers.

Set of basic comps & PCB (as publ.)	KIT 87-2	**£6.84**
Text photocopy	TEXT 87	**38p**
Knob, skt	HW 87	**75p**

ELEKTOR FUNNY TALKER

Incorporates a ring modulator, chopper & frequency modulator to produce fascinating sounds when used with speech & music.

Basic comps, PCB (as publ.)	KIT 99-1	**£9.60**
Text photocopy	TEXT 99	**40p**
Knobs & skts	HW 99	**£1.22**

ELEKTOR FREQUENCY DOUBLER

For use with guitars & other electronic instruments to produce an output one octave higher than the input. Inputs and outputs may be mixed to give greater depth.

Basic comps, PCB (as publ.)	KIT 98-1	**£5.48**
Text photocopy	TEXT 98	**20p**
Knobs & skts	HW 98	**£1.24**

P.E. SPLIT-PHASE TREMOLO

A simple but effective substitute for a rotary cabinet. The output of an internal generator is phase-split and modulated by an input signal from an electronic guitar or other instrument. Output amplitudes, depth & rate are variable. May be fed to one or two amplifiers.

Basic comps, PCB & chart	KIT 101-3	**£17.68**
Text photocopy	TEXT 102	**65p**
Knobs & skts	HW 102	**£2.53**

P.E. MINISONIC WAVEFORM CONVERTER

A simple converter that modifies the Minisonic sawtooth waveform to produce triangle and sine outputs. Ideally one should be used with each Minisonic VCO.

Basic comps, PCB & chart	KIT 96-1	**£3.98**
Knob, skts, switch	HW 96	**99p**

P.E. GUITAR MULTIPROCESSOR

An extremely versatile sound processing unit capable of producing, for example, flanging, vibrato, reverb, fuzz and tremolo as well as other fascinating sounds. May be used with most electronic instruments.

Basic comps, PCB & charts (excl. SWs)	KIT 85-5	**£49.23**
Set of text photocopies	TEXT 85	**£2.52**
Knobs, skts, sw's		See our list

P.E. PHASER

An automatically controlled 6-stage phasing unit with integral oscillator.

Basic comps, PCB & chart	KIT 88-1	**£10.91**
2-Notch extension, PCB & chart	KIT 88-2	**£6.36**
Text photocopy	TEXT 88	**68p**
Knobs, skts, switch	HW 88	**£1.63**

ELEKTOR PHASING & VIBRATO

Includes manual and automatic control over the rate of phasing & vibrato. Slightly modified to also include a 2-input mixer stage.

Set of basic comps, PCB & chart	KIT 70-2	**£21.67**
Text photocopy	TEXT 70	**67p**
Knobs, skts, sw's	HW 70	**£3.27**

P.E. GUITAR EFFECTS UNIT

Modulates the attack, decay and filter characteristics of a signal from most audio sources, producing 8 different switchable effects that can be further modified by manual controls.

Basic comps, PCB & chart	KIT 42-4	**£7.68**
Text photocopy	TEXT 42	**28p**
Knobs & skts	HW 42	**£1.85**

P.E. GUITAR OVERDRIVE

Sophisticated versatile fuzz unit incl. variable controls affecting the fuzz quality whilst retaining attack and decay, and also providing filtering. Usable with most electronic instruments.

Basic comps, PCB & chart	KIT 56-3	**£11.22**
Text photocopy	TEXT 56	**68p**
Knobs & skts	HW 56	**£2.29**

P.E. SMOOTH FUZZ

Basic comps, PCB & chart	KIT 91-1	**£6.52**
Text photocopy	TEXT 91	**55p**
Knobs & skts	HW 91	**£1.22**

WE ALSO SELL COMPONENTS ASK FOR OUR LIST

ADD: POST & HANDLING
U.K. orders: Keyboards add £2.70 each. Other goods: Under £5 add 50p. under £20 add 75p. over £20 add £1. Recommended insurance against postal mishaps: add 50p for cover up to £50, £1 for £100 cover, etc., pro-rata Insurance must be added for credit card orders.
N. B. Eire, C.I., B.F.P.O and other countries are subject to higher export postage rates.

ADD 15% VAT
(or current rate if changed). Must be added to full total of kits, discount post & handling on all U.K. orders. Does not apply to Exports, or photocopies.

EXPORT ORDERS ARE WELCOME but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list – Europe send 50p, other countries send £1.00.
Note that we do not offer a C.O.D. service and that our terms are payment in advance.

PHONOSONICS · DEPT PE16 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

TERMS: C.W.O., MAIL ORDER OR COLLECTION
BY APPOINTMENT (TEL 01-302 6184)

ND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

LIST–Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

OVERSEAS enquiries for list Europe—send 50p: other countries—send £1.00.

KIMBER-ALLEN KEYBOARDS AND CONTACTS

IMBER-ALLEN KEYBOARDS as required for many published projects. The manufacturers laim that these are the finest moulded plastic keyboards available. All octaves are C to C, the eys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

Octave (37 notes) **£25.50** 4 Octave (49 notes) **£32.25** 5 Octave (61 notes) **£39.75**

ONTACT ASSEMBLIES (gold-clad wire) – 1 required for each KBD note:
Type GJ – SPCO **33p** ea. Type GB – 2 pr N/O **37½p** ea.

. 6-CHANNEL MIXER

h specification stereo mixer with variable impedances

sic comps & PCB's	KIT 90-8	**£56.43**
ra 2-channel set with PCB	KIT 90-9	**£10.21**
t of Text photocopies	TEXT 90	**£1.50**
ob, skts, sw's		See our list

YTHM GENERATORS

al available, including programmable 16 64000 pattern, and pre-programmed 15 rn using either M252 or M253 rhythm chips. ection of effects instruments circuits is also ble.

ND & RAIN EFFECTS IT

htly modified version of the original P.E. unit.

sic comps, PCB & chart	KIT 28-1	**£4.84**
xt photocopy	TEXT 28	**28p**
obs, skts, sw's	HW 28	**£1.65**

E. ENVELOPE SHAPER ITH VCA

an integral Voltage Controlled Amplifier, and full manual control over the A.D.S.R. ions.

asic comps, PCB & chart	KIT 50-1	**£8.03**
xt photocopy	TEXT 50	**58p**
nobs, skts	HW50	**£1.32**

E. TRANSIENT ENERATOR

ADSR envelope shaper without VCA, and tionally providing Repeat-triggering enabling nthesiser to be programmed for mandolin of o effects.

asic comps, PCB & chart	KIT 63-2	**£7.62**
ext photocopy	TEXT 63	**58p**
nobs, skts	HW63	**£1.82**

E. EXTERNAL-INPUT YNTHESISER-INTERFACE

ws external inputs such as guitars, ophone etc., to be processed by synthesiser uits.

asic comps, PCB & chart	KIT 81-1	**£3.90**
nobs, sets	HW 81	**£1.18**

E. TUNING FORK

duces 84 switch-selected frequency-accurate s with an LED monitor clearly displaying beat- adjustments.

et of basic comps, incl. power supply.

CBs & charts	KIT 46-3	**£23.32**
ext photocopy	TEXT 46	**97p**
nobs, skts, sw's	HW 46	**£2.89**

E. TUNING INDICATOR

mple octave frequency comparitor for use with thesisers and other instruments where the full satility of KIT 46 is not required.

asic comps, PCB & chart	KIT 69-1	**£8.19**
ext photocopy	TEXT 69	**58p**
nobs, skts, sw's	HW 69	**£1.56**

DIGITAL EXPOSURE UNIT

Controls up to 750 watts in ½ second steps up to 10 minutes, with built-in audio alarm.

Basic comps, PCBs	KIT 93-3	**£23.45**
Text photocopy	TEXT 93	**£1.20**
Knobs, skts	HW 93	**£2.48**

P.E. DISCOSTROBE

A 4-channel light show controller giving a choice of sequential, random, or full strobe mode of operation.

Basic comps, PCB & chart	KIT 57-3	**£19.37**
Text photocopy	TEXT 57	**78p**
Knobs, skts, sw's	HW 57	**£7.30**

P.E. CONSTANT DISPLAY FREQUENCY COUNTER

A 4-digit counter for 1Hz to 99kHz with 1Hz sampling rate. Readout does not count visibly or flicker due to blanking.

Basic comps, PCB & chart	KIT 79-4	**£31.61**
Text photocopy	TEXT 79	**78p**
Knobs, skts, sw's	HW 79	**£4.67**

P.E. VOICE OPERATED FADER

For automatically reducing music volume during talkover – particularly useful for discos.

Basic comps, PCB & chart	KIT 30-1	**£4.37**
Text photocopy	TEXT 30	**28p**
Skts	HW 30	**32p**

P.E. DYNAMIC NOISE LIMITER

Very effective stereo circuit for reducing the hiss found in most tape recordings.

Basic comps, PCB & chart	KIT 97-1	**£8.07**
Text photocopy	TEXT 97	**75p**

P.E. DYNAMIC RANGE LIMITER

Preset to automatically control sound output levels.

Basic comps, PCB & chart	KIT 62-1	**£5.31**
Skts	HW 62	**44p**

ALL KITS INCLUDE SPECIALLY DESIGNED PRINTED CIRCUIT BOARDS

MORE KITS AND COMPONENTS ARE IN OUR LISTS

RICES ARE CORRECT AT TIME OF PRESS.
. & O. E. DELIVERY SUBJECT TO AVAILABILITY.

PHONOSONICS

ELECTROVALUE

BEST SELLERS . . .

RECHARGEABLE CELLS by SANYO-CADNICA. Size AA 99p, C 2.27, D 3.76, PP3 4.10 with tags: AA 1.06, C 2.43, D 3.99.
CHARGERS PP3 4.75, AA 4.95, A, C, D 7.60.
PLASTIC BOXES PB1 116 x 77 x 35mm 62p.
Breadboards Euro 5.70N, Veroblock 3.63.
Bimboard 8.03, Buzzer 6-15V 80p.
CAPACITORS polystyrene 47-4700pF ea 7p. C280 .01 6p, .1 7p, .22 9p (full range).
Polyester (PCM 7.5mm) .001 6p, .0047 7p, .056 8p, .1 9p, (PCM 10mm) 1uF 26p.
(Many more values in this range).
Variable Dilecon 100pF 2.08, 500pF 3.21.
ELECTROLYTICS full range.
CONNECTORS ¼'' jack plug 32p, skt 12p. 3.5mm jack plug 17p, skt 14p, 2.5mm 12p.
DIP header 14 pin 38p, 16 pin 43p.
Quick test mains block 5.25.
Fuse holders 20mm panel 22p, chassis 6p.
HALL-EFFECT devices from 1.89N.
Heat sinks Power 1.25° C/W 2.85; finger type TO3 25p, TO220 25p.
INTEGRATED CIRCUITS – hundreds of types: 741 18p, 555 23p, CA3140E 40p, LM380N 99p, LM3914N 2.68, S566B 2.14, TCA965 1.20.
IC holders 8 pin 9p, 14-40 pin 1p per pin.
KNOBS, screw fittings ¼'' from 16p.
Loudspeakers 2.1/2'' 8 or 64 ohms 93p.
Magneto resistors from 1.60N.
Meters, panel 60 x 45mm 50uA-1A ea 4.80.
Opto LEDS red 7p, yellow 9p, green 11p; ultrabright 21p all colours.
LED drivers UAA170/UAA180 ea 1.52.
POTENTIOMETERS carbon 20mm dia. 100R-2M2 lin, 220R-4M7 log single 29p. 1K-2M2 lin, 4K7-2M2 log duals, ea 81p. Add 51p if required with switch.
Sliders mono 72p, stereo 1.18, bezel 34p.
Wirewound 25R-10K, 3 watt ea 1.50.
PRINTED CIRCUIT MATERIALS. 300 x 150mm S/S SRBP 1.25, f/gl 1.90. 500gm ferric chloride lab grade 3.40. Positiv 20 photo resist 75ml 1.65. Etch resist pen 1.05, silver paint 3g 4.14N. Relays 12v coil 3P2W 10A contacts 2.90. Resistors ⅓W, ½W, ¾W 5% ea 2p. Metal oxide TR5 2% 5p, film MR25 5p.
SEMICONDUCTORS 1N4007 6p, 1N4148 3p, RCA2N3055 70p, BC107-9 family 14p, BC182/212 family 9p, BFR34A 63p, BFT65 1.19, C106D1 45p, TIP31A/32A ea 44p, TIP41A/42A ea 45p, TIP2955/TIP3055 ea 55p.
Solder 500gm 60/40 20SWG 7.30N.
IRONS Antex C, CCN, CX or X25 ea 4.40N. Oryx 50 temperature controlled 11.50N.
ISO-TIP cordless with charger 24.00N.
SWITCHES slider DPDT min 18p, std 20p. Wavechange 1P12W, 2P6W, 3P4W, 4P3W ea 40p. Time switch 13A 3 on/3 off per day 14.68N. Min toggles silver contacts SPDT 57p. DPDT 80p, 3PDT 1.64, 4PDT 2.75. DIL gold plated 4PST 95p, 10PST 2.10.
Miniature drills, 12V dc TITAN 10.28N. TITAN kit 17.06N, Stand 12.00N.
Tools CK pliers 4.70, cutters 6.10, strippers 4.95.
Vero wiring system kit 4.42, wire 1.17.
Computers Nascom 1 built £140.00N.
NASCOM 2 kit £295.00 complete (less 8 x 4118's £225.00N). P/S kit, 3 amp 32.50N, 16K RAM kit 110.00N.

BEST SERVICE

★

KEEN BUYERS! A S.A.E. BRINGS COMPREHENSIVE PRICE LIST (Valid 3 mths.) COVERING CATALOGUE '81.

ACCESS AND BARCLAYCARDS ACCEPTED

EVERYTHING BRAND NEW & GUARANTEED

HARD TO FIND ITEMS

KEEN PRICES & DISCOUNTS

SPECIAL QUANTITY DISCOUNTS

SPEEDY TURN ROUND ON ORDERS

NO P/P CHARGES ON U.K. C.W.O. ORDERS OVER £5.75. (Add handling charge of 40p if under).

★

PLEASE ADD 15% V.A.T. TO TOTAL VALUE OF ALL ORDERS.

★

Shop Hours – 9–5.30: Sats. 9–1 pm.

ELECTROVALUE LTD. **DEPT. PE/7, 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB.**
Phone Egham 33603 (STD 0784 . London 87). Telex 264475
Northern Branch (Personal Shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

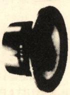

Wilmslow Audio

THE firm for speakers!

SEND 50p FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

AUDAX ● AUDIOMASTER ● BAKER ● BOWER & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMANS ● HARBETH ● ISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● McKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANNOY ● VIDEOTONE ● WHARFEDALE ●

WILMSLOW AUDIO (Dept. P.E.)
35/39 CHURCH STREET, WILMSLOW, CHESHIRE

Tel: 0625 529599
FOR MAIL ORDER & EXPORT OF DRIVE UNITS, KITS ETC.
Tel: 0625 526213
(SWIFT OF WILMSLOW) FOR HI-FI & COMPLETE SPEAKERS

ILP

SIMPLY AHEAD and staying there

The range grows bigger...better...

New Profile Amplifiers - Two New Series

MOS200

HY60

MOSFET

CHOOSE AN I.L.P MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P's exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETS, and are easier to mount. Connection is via five pins on the underside. **I.L.P MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLIEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.**

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02

BIPOLAR

STANDARD O/P TRANSISTORS

CHOOSE AN I.L.P BIPOLAR POWER AMP where power and price are first consideration while maintaining optimum performance with hi-fi quality and wide choice of models. From domestic hi-fi to disco and P.A., for instrument amplification, there is an I.L.P Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shoulders. Connections are simple, via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.29 + £1.09
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£8.33 + £1.25
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£17.48 + £2.62
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£21.21 + £3.18

ILP POWER AMPS ARE ENCAPSULATED FOR THERMAL STABILITY AND LONGER LIFE

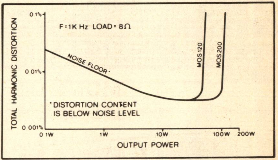

Load impedance both models 4Ω - ∞ Input sensitivity both models 500mV

Input impedance both models 100KΩ Frequency response both models 15Hz-100KHz – 3dB

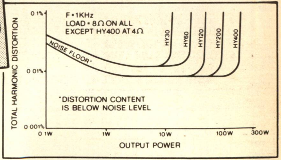

Load impedance all models 4Ω - ∞ Input sensitivity all models 500mV

Input impedance all models 100KΩ Frequency response all models 15Hz-50KHz – 3dB

THE NEW PROFILE EXTRUSIONS

The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages: – Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow easy mounting; standardisation enables us to keep our

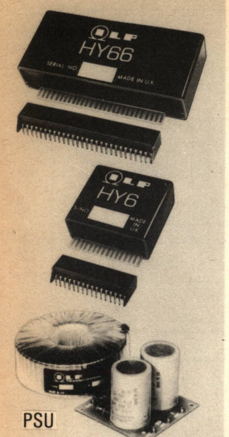

PSU

I L P PRE-AMPS

HY6 (mono) and **HY66** (stereo) are new to I.L.P's range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.
Sizes – **HY6** – 45 x 20 x 40 mm. **HY66** – 90 x 20 x 40 mm.
Active Tone Control circuits provide ±12dB cut and boost.
Inputs Sensitivity – Mag. PU. –3mV: Mic – selectable 1-12mV: All others 100mV. **Tape O/P** – 100mV: **Main O/P** – 500mV: **Frequency response** – D.C. to 100KHz – 3dB.

HY6 mono £6.44 + 97p VAT Connectors included
HY66 stereo £12.19 + £1.83 VAT Connectors included

B6 Mounting Board for one HY6 78p + 12p VAT
B66 Mounting Board for one HY66 99p + 15p VAT

WITH ALL
ILP MODULES

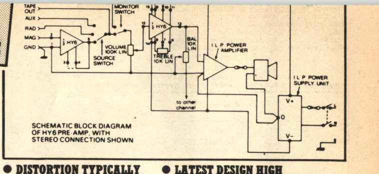

SCHEMATIC BLOCK DIAGRAM OF HY6 PRE-AMP, WITH STEREO CONNECTION SHOWN

- **DISTORTION TYPICALLY 0.005%**
- **S/N RATIO – 90dB (Mag. P.U. – 68 dB)**
- **38 dB overload margin on Mag. P.U.**
- **LATEST DESIGN HIGH QUALITY CONNECTORS**
- **ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING**
- **NEEDS ONLY UNREGULATED POWER SUPPLY ±15 to ±60v**

I L P POWER SUPPLY UNITS

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P power supply units are space-saving, more efficient and their better overall design helps enormously when assembly building. All models in the range are compatible with all I.L.P amps and pre-amps with types to match whatever I.L.P power amps you choose.

PSU30 ± 15V at 100mA to drive up to 12 x HY6 or 6 x HY66 **£4.50** + 0.68p VAT
- *THE FOLLOWING WILL ALSO DRIVE I.L.P PRE-AMPS*

PSU36 for use with 1 or 2 HY30's **£8.10** + £1.22 VAT
- *ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS*

PSU50	for use with 1 or 2 HY60's	£10.94+£1.64 VAT
PSU60	for use with 1 HY120	£13.04+£1.96 VAT
PSU65	for use with 1 MOS120	£13.32+£2.00 VAT
PSU70	for use with 1 or 2 HY120's	£15.92+£2.39 VAT
PSU75	for use with 1 or 2 **MOS120**	£16.20+£2.43 VAT
PSU90	for use with 1 HY200	£16.20+£2.43 VAT
PSU95	for use with 1 **MOS200**	£16.32+£2.45 VAT
PSU180	for use with 1 HY400 or 2 HY200	£21.34+£3.20 VAT
PSU185	for use with 1 or 2 **MOS200**	£21.46+£3.22 VAT

WE WANT TO KNOW

We have always maintained good working relations with our customers, and therein lies a large measure of the company's success and growth. Now that we are running our most exciting programme yet, we would like to have your comments about our current products and any others you would like to see coming from I.L.P. Send us your letter (with your age, job, etc. if you don't mind) to Customer Liaison, I.L.P. Electronics Ltd., FREEPOST, – Roper Close, Canterbury CT2 7EP. (No stamp required).

NO QUIBBLE 5 YEAR GUARANTEE
7-DAY DESPATCH ON ALL ORDERS
BRITISH DESIGN AND MANUFACTURE
FREEPOST SERVICE

★ **Freepost facility**
When ordering or writing about I.L.P products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.

★ **TO ORDER** Send cheque or money order payable to I.L.P Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.

NOW TURN TO OUR AD ON PAGE 81

BRITAIN'S LEADING QUALITY MODULE SUPPLIERS

To: I.L.P ELECTRONICS LTD. CANTERBURY CT2 7EP
Please supply ....
.... Total purchase price £..........
I enclose Cheque ☐ Postal Orders ☐ International Money Order ☐
Please debit my Access/Barclaycard Account No. ....
....
NAME ....
ADDRESS ....
....
Signature ....

ALL U.K. ORDERS DESPATCHED POST FREE

ILP ELECTRONICS LTD.
FREEPOST 2 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.
Telephone (0227) 54778 [Technical (0227) 64723] Telex 965780
Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

MICRO TIMES

19 Mill St. Bideford, North Devon EX39 2JR
Telephone Bideford (023 72) 79798 (Dept. PE3)

★ ★ ★ THIS MONTH'S SUPER SAVERS ★ ★ ★

MEMORIES	1+	25+
2114 450ns.	**£1.45**	**£1.40**
2114 300ns.	**£1.55**	**£1.50**
FROM TOSHIBA TC5515P		**£3.65 each.**
4K CMOS RAM (1k × 4) 450ns.	**£3.65.**	**£3.45**
CMOS RAM 5101		**each £3.45**
	1+	25+
4116 200ns.	**£1.45**	**£1.40**
4116 150ns	**£1.90**	**£1.85**
HM6116P-3. (16k 150ns).		**Special £19.95 each.**

EPROMS	1+	25+
2708 450ns.	**£2.95**	**£2.75**
2716 450ns.	**£3.25**	**£3.15**
2732 Intel type		**£9.90 each.**
Buy 5 off for		**£49.00.**

6809 single Board Computer •kit•
IEEE S-100 Standard
Complete kit **£160** plus 15% VAT. £1 P&P. Uses Motorolas powerful MC6809 CPU. 4K/8K/16K ROM 2K RAM, ACIA, PIA, 8080 simulated I/O, RS-232 Handshake, 8 sel Baud Rates, Manual includes: 11×17in. Schematic parts list. User notes. Software listings and more!

Bare Board	**£48••**
Uses 6809: 6850: 6821 – buy set for	**£18.50**
ADMONS (2716)	**£24.00**

Data available. S.a.e. please.

AY-3-8910
GI SOUND COMPUTER CHIP
Features:
–Full software control of sound generation.
–Interfaces with most 8-bit and 16-bit microprocessors.
–3 independently programmed analog outputs.
–Two 8-bit general purpose I/O ports.
–Single +5 volt supply.
••SPECIAL PRICE £6.95••
Data 50p. Large S.a.e. please.

Low Profile D/Face Wipe DIL Sockets.	
40 pin	**39p**
28 pin	**29p**
24 pin	**25p**
22 pin	**24p**
18 pin	**20p**
16 pin	**18p**
14 pin	**16p**
8 pin	**12p**

Quantities 100+
Discount 5%

LINEAR IC'S	
NE555	**18p**
NE556	50p
RC4136	**65p**
LM301AN	**26p**
LM311P	**48p**
LM318	**£1.50**
LM324N	**43p**
LM339N	**43p**
LM348N	**80p**
LM358P	**40p**
LM380	**65p**
LM3900N	**48p**
LM3914	**£2.10**
LM3915	**£2.10**
LM13600	**£1.20**
SN76477N	**£1.70**
UA709	**30p**
LM741	**15p**
UA733	**75p**
UA747	**60p**
UA748	**30p**
TL074CN	**£1.25**
TL081CP	**40p**
TL082CP	**70p**
TL084CN	**£1.00**
LM3302	**95p**
TL490	**£1.10**
1488	**75p**
1489	**75p**
8T26	**£1.50**
8T28	**£1.50**
8T95	**£1.50**

ENCODER/ TRANSMITTER	
LM1871	**£1.90**

RECEIVER/ DECODER	
LM1872	**£1.90**

VOLTAGE REGULATORS		
	1A	
7805	5V	**55p**
7812	12V	**55p**
7905	5V	**60p**
7912	12V	**60p**
	100mA	
78L05	5V	**29p**
78L12	12V	**29p**
	500mA	
79M12	12V	**64p**
79M05	5V	**64p**
723		**32p**

THYRISTORS	
C106D	**28p**
TIL's	
TIL 32	**45p**
TIL209	**10p** red
TIL232	**18p** green
TIL212	**16p** Yell
TIL216	**18p** red
TIL228	**20p** red
TIL220	**12p** red
TIL224	**18p**
TIL311	**£5.50**
TIL312/3	**£1.00**
TIL321/A	**£1.15**
TIL330A	**£1.15**

CPU's	
6502	**£5.45**
6504	**£7.25**
6802	**£5.85**
6809	**£15.00**
8080A	**£4.15**
8085A	**£6.45**
Z80	**£5.45**
Z80A	**£6.45**

SUPPORT DEVICES	
6520	**£3.15**
6522	**£5.60**
6532	**£7.75**
6810	**£2.50**
6821	**£1.90**
6845	**£15.00**
6850	**£1.95**
6852	**£3.30**
8212	**£1.75**
8216	**£1.75**
8228	**£3.95**
8255	**£4.10**
Z80 CTC.	**£4.25**
Z80 PIO	**£4.25**
Z80ACTC	**£5.40**
Z80APIO	**£5.40**
Z80 DMA	**£16.00**
Z80ADMA	**£18.00**
Z80S10/0	**£18.00**
Z80AS10/0	**£24.00**
Z80 S10/1	**£18.00**
Z80AS10/1	**£24.00**
Z80 S10/2	**£18.00**
Z80AS10/2	**£24.00**
SN76477N, SOUND CHIP	**£1.70**

A single chip versatile SOUND EFFECTS GENERATOR SN76477N is ideally suited for applications such as arcade or home video games,alarms, sound effects boxes and toys.
DATA **£1.25**
50p Large S.a.e.

INTERSIL ICL 7660 **£2.25**
Voltage Converter. Now ex-stock.
★ Simple conversion of +5V Logic supply to ±5V supplies.
★ Simple voltages multiplication (V out =(–)n.Vin).
★ 99.9% typical open circuit voltage conversion efficiency.
★ 98% typical power efficiency.
★ Wide operating voltage range 1.5V to 10.0V.
★ Easy to use, requires only 2 external non-critical components.
DATA AVAILABLE 50p. Large S.a.e. please.

JUST ARRIVED FROM VERO
S100 Prototyping Boards.

Microboard Pattern 06-2175L	**£16.40•**
Square Pad Universal Pattern 06-2338F	**£16.40**
Prototyping Board for your APPLE/IT2020	**£8.37•**

FLOPPY DISC CONTROLLERS	
FD1771	**£19.50**
FD1791-2	**£32.00**
WD1691D	**£14.50**
WD2143-01	**£5.00**
•SPECIAL Complete Pkg.	**£50**

includes FD1791-2+WD1691D +WD2143-01.
Individual Data available 50p per copy.
Large 50p S.a.e. please

COMBO CHIPS
Intended for Z80 Usage.
Z80 Combo Chip (MK3886) 2½ meg. **£25.00**
Z80A Combo Chip (MK3886N-4) 4 meg. **£29.95**

VEROBLOC SOLDERLESS BREADBOARD
360 reliable contacts.
Will accommodate any size of IC.
Can be fully interlocked one with another.
SPECIAL PRICE £3.55 each.

KITS FOR BEGINNERS

AROUSE THE MICRO CHIP INTEREST IN THE YOUNGSTERS STARTER KITS.

ULTRONIC FLY REPELLER
A must for campers.
Features:
–LED indication.
–Pocket size case.
–Low Power consumption.
Kit + all parts + case with instructions for easy asssembly. Battery not included.
•£4.75•

LIGHT ACTIVATED SWITCH
Used for automatic lighting control, elec. appliance control, electronic gun burglar alarm and auto-open door system.
Switch on/off 200W elec. appliances.
Kit + parts + instructions for easy assembly.
•£3.75•

ELECTRONIC WHEEL OF FORTUNE
Fun Kit.
Easy to assemble.
Case included.
Wonderful game.
SPECIAL •£5.45

ORDERING INFORMATION
Please add 50p P&P.
Plus 15% VAT to all orders.
EXPORT ORDERS ACCEPTED.
Add 15% P&P on total order. VAT not applicable.
ACCESS/BARCLAY CARD WELCOME.

VISA

It is our policy to offer you brand new, full spec. devices.

Prices subject to change without notice.

CROFTON ★ STAR ★ OFFER

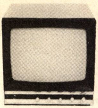

9″ Crofton Monitors

P4 White **£64.97** P31 Green **£78.20**

STOCKISTS IN ALL AREAS WANTED

Shugart Floppy Disk Drive

No case, no power supply
5¼"S.S.S.D. SA400 **£146.05**
5¼" D.S.S.D. SA 450 **£280.31**
8"S.S.S.D. SA800 **£337.52**

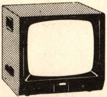

Ikegami 12″ Monitors

P4 White **£166.50** P31 Green **£179.97**

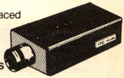

2/3″ fully interlaced CCTV Camera only **£103.50**
Lens extra.

REFURBISHED VIDEO CAMERAS ALWAYS AVAILABLE

The above prices include VAT. Carriage extra.

Buy it with Access

All major credit cards accepted. Small surcharge.

BARCLAYCARD

Phone or write to

CROFTON ELECTRONICS LIMITED

35 Grosvenor Road, Twickenham, Middlesex TW1 4AD. Tel: 01.891 1923/1513

PARNDON ELECTRONICS LTD.

Dept. No. 21 44 Paddock Mead, Harlow, Essex, CM18 7RR. Tel: 0279 32700

RESISTORS: ¼ Watt Carbon Film E24 range ± 5% tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Bandoliered and colour coded.
£1·00 per hundred mixed. (Min 10 per value)
£8·50 per thousand mixed. (Min 50 per value)
Special stock pack. 60 values, 10 off each **£5·50**

DIODES: **IN4148** 3p each. Min order quantity – 15 items.
£1·60 per hundred

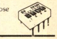

DIL SWITCHES: Gold plated contact in fully sealed base – solve those programming problems.
4 Way **86p** each. 6 Way **£1·00** each. 8 Way **£1·20** each.

DIL SOCKETS: High quality, low profile sockets.
8 pin – **10p.** 14 pin – **11p.** 16 pin – **12p.** 18 pin – **19p.** 20 pin – **21p.**
22 pin – **23p.** 24 pin – **25p.** 28 pin – **27p.** 40 pin – **42p.**

ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS
MIN. ORDER – U.K. £1·00. OVERSEAS £5 · CASH WITH ORDER PLEASE

STORAGE CABINETS

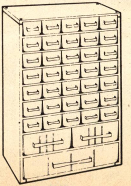

Type 1838

Metal Cabinets 12″ wide x 5¾″ deep, finished blue with transparent plastic drawers.

Type	H (ins)	No. of Drawers Sm	Med	Lge	Price
1118	11	15	2	1	**£10·75**
1633	16	30	2	1	**£13·95**
1838	18	35	2	1	**£15·95**
2236	22	30	4	2	**£18·55**
2260	22	60	–	–	**£18·55**

Access/Barclaycard welcome
Prices include VAT and Post. Cheque/P.O. to:
Millhill Supplies (Tools),
35 Preston Crowmarsh, Benson,
Oxon OX9 6SL.

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics – now it can be your turn. Whether you are a newcomer to the field or already working in the industry. ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personel guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians
Radio, T.V. Electronics Technicians
Radio Amateurs
Electrical Installation Work

Diploma Courses

Colour T.V. Servicing
CCTV Engineering
Electronic Engineering & Maintenance
Computer Engineering and Programming
Radio, T.V. and Audio, Engineering & Servicing
Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free Electronics careers guide.

Name ______________________

Address ______________________

____

______________________ Age ________

ICS

To ICS, Dept 273J, Intertext House,
London SW8 4UJ
or telephone 01-622 9911 (all hours)

All these advantages...

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1–2 hours and installation even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light, systems function light, and security changeover switch. Will work all rev counters.

Fits all 12 v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED
Die pressed case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.

Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."

Sparkrite
HIGH PERFORMANCE
ELECTRONIC IGNITION

Electronics Design Associates, Dept. PE1179, 82 Bath St., Walsall, WS1 3DE

Electronics Design Associates, Dept. PE/7/81
82 Bath Street, Walsall, SW1 3DE. Phone: (0922) 614791

Name ______________________

Address ______________________

____

____

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.	QUANTITY REQ'D.
X5 KIT £16·95	
ACCESS OR BARCLAY CARD No.	

I enclose cheque/PO's for
£
Cheque No.
Send SAE if brochure only required.

SMALL ADS

The prepaid rate for classified advertisements is 28 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £9.50 per single column centimetre (minimum 2·5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

RECEIVERS AND COMPONENTS

BLACKPOOL AND THE FYLDE. For components come to ETESON ELECTRONICS, 15b, Lower Green, Poulton-le-Fylde. Tel. 885107. Mail order too – S.A.E. lists.

BRAND NEW COMPONENTS BY RETURN

Electolytic Capacitors 16V, 25V, 50V.
0·47, 1·0, 2·2, 4·7 & 10 Mfds. — **5p.** **22 & 47—6p** 100—**7p.** (50V—**8p**). 220—**8p.** (50V—**10p**), 470—**11p.** (40V—**16p**), 1000/15V—**15p.** 1000/25V—**18p.** 1000/40V—**35p.**

Subminiature bead Tantalum electrolytics.
0·1, 0·22, 0·47, 1·0 @ 35V, 4·7 @ 6·3V — **14p.** 2·2/35V, 4·7/25V—**15p.** 10/25V, 15/16V—**20p.** 22/16V, 33/10V, 47/6V, 68/3V & 100/3V—**30p.** 15/25V, 22/25V, 47/10V—**35p.** 47/16V—**80p.**

Subminiature Ceramic Caps. E12 Series 100V.
2% 10 pf. to 47 pf.—**3p.** 56 pf. to 330 pf.—**4p.** 10% 390 pf. to 4700 pf.—**4p.**

Vertical Mounting Ceramic Plate Caps. 50V.
E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf.—**2p.**

Polystyrene E12 Series 63V. Horizontal Mntg
10 pf. to 820 pf.—**3p.** 1000 pf. to 10,000 pf.—**4p.**

Miniature Polyester 250V Vert. Mtg. E6 Series.
·01 to ·068—**4p.** ·1—**5p.** 15, 22—**6p.** ·33, ·47—**10p.** ·68 — **12p.** 1·0 — **15p.** 1·5 — **22p.** 2·2 — **24p.**

Mylar (Polyester) Film 100V. Vertical Mounting.
·001, ·0022, ·0047—**3p.** ·01, ·022—**4p.** ·04, ·05, 0·1—**5p.**

Miniature Film Resistors Highstab. E12 Ser. 5%.
0·125W mixed carbon/metal 10Ω to 1MΩ—**1p.** 0·25W Carbon 1Ω to 10MΩ (10% over 1M0Ω)—**1p.** (E24 Series av. in ¼W C. Film 1Ω to 5M6Ω). 0·25W, 0·5W & 1·0W Metal Film 10Ω to 2M2Ω—**2p.**
1N4148—**2p.** 1N4002—**4p.** 1N4006—**6p.** 1N4007—**7p.**
BC107/8/9, BC147/8/9, BC157/8/9, BF195 & 7—**10p.**
8 Pin i.c's. 741 Op. amp.—**18p.** 555 Timer—**24p.**
Dil Holders 8 pin—**9p.** 14 pin—**12p.** 16 pin—**14p.**
LED's. 3 & 5mm. Red—**10p.** Green & Yellow—**14p.**
Grommets for 3mm.—**1½p.** 2 pce. holders 5mm.—**2½p.**
20mm. Q.B. Fuses ·15, ·25, ·5, 1, 2, 3 & 5A—**3p.**
20mm. Anti Surge 100mA. to 5·0A—**5p.**
20mm. Fuseholders P.C. or Chassis Mtg.—**5p.**
Solid A1. knobs 15mm.—**25p.** 25mm.—**35p.** 30mm.—**50p.**
400mW Zener diodes E24 series 2V7 to 33V—**8p.**

Prices VAT inclusive Post 15p. (Free over £5.00).

THE C. R. SUPPLY CO.
127, Chesterfield Rd., Sheffield S8 0RN.

TURN YOUR SURPLUS Capacitors, transistors, etc., into cash. Contact COLES-HARDING CO., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement.

VLF DETECTOR KITS
PROFESSIONAL AUTOMATIC METAL LOCATOR

The printed circuit Board & Search Head are ready built & aligned for easy assembly. Discrimination is by a rising tone for non ferrous & a falling tone ferrous. Complete kit inc. meter **£27.**

Discriminating Pulse Induction Kit **£48**

C.D.I. SYSTEMS LTD.,
Storrington 4830 (Anytime)

BALLARD'S OF TUNBRIDGE WELLS have moved to 54, Grosvenor Road, no lists. S.A.E. all enquiries phone Tunbridge Wells 31803.

BOURNEMOUTH/BOSCOMBE. Electronic components specialists for 33 years. Foresters (National Radio Supplies), Late Holdenhurst Road. Now at 36, Ashley Road, Boscombe. Tel. 302204. Closed Weds.

T & J ELECTRONIC COMPONENTS – Quality components, competitive prices, catalogue **45p.** 98 Burrow Road, Chigwell, Essex.

1920's ONWARD VALVES, WIRELESS. SAE. Sole Electronics, PE, 37, Stanley Street, Ormskirk, Lancs. L39 2DH.

SOFTWARE

ZX81 AND ZX80 SOFTWARE on cassette. Games, educational and household programs available, including GCE "O" level maths, household manager and telephone index-/address list. Prices from **£2.00.** Send S.A.E. for catalogue to: ROSE CASSETTES, 148, Widney Lane, Solihull, West Midlands B91 3LH.

Superboard/UK101
Low Cost Add-Ons
ALL PRICES INCLUDE VAT & POST

8K RAM + 16K EPROM board, fully buffered and decoded. Top quality PCB – 40 pin DIP connector. All memory bank selectable in 4K blocks anywhere in memory. Includes 4K 300ns RAM (2114). Full instructions etc. supplied.
Kit £48.99 built and tested £56.99

High speed cassette interface kit, 300/2400/ 4800/ switchable to suit recorder.
Easy to fit kit £16.90.

Enhanced Video Display. True 48×32 Display
Full kit and instructions **£15.95.**

Software for all Superboard/UK101 screen formats.
Chess 1.9 **£7.90,** *Draughts* **£3.50.**

Superboard II Series II fully built tested and guaranteed. **£169.99.**

NORTHERN MICRO Tel. Holmfirth (048489) 2062
29 Moorcroft Park
New Mill
HUDDERSFIELD
S.A.E. for list please
Callers welcome by appt.

CARDBOARD COMPUTOR. Learn Assembly Language Programming and Computor Architecture. £8.97 inc. VAT. Also Solar Cells, Science Kits, Energy Books, Stirling Engines, Space Blankets etc. Send 25p for lists. Edencombe Ltd., Dept. PM34, Nathans Road, North Wembley, Middlesex HA0 3RX.

Marick
Computer Products

Dept PEc
1, Branksome Close,
Paignton,
DEVON TQ3 1EA

UK 101 Software on Tape

- 8K Asteroid Runner
- 8K Nuclear Holocaust
- 4K Alien Invaders
- 4K Snakes and Ladders
- 4K The My-my Game
- 8K Home Finance
- 5K Space Defender
- 4K UK 101 Breakout
- 4K Drawing Machine
- 4K Fruit Machine

Only £3.50 each. Each game comes on individual cassettes.

8K Quest for the Golden Crown
The Adventure game you've been waiting for!
Search through the Labyrinth in the Mountains in the West for the Golden Crown of the late King Triaric.
The game comes with a manual giving the History of the Golden Crown, and instructions for playing the game. **£5.50**

Balloon Race 8K
Manoeuver your balloon through the Gorse Bush Tracks without mishap. An original game that we think you will find very challenging and quite frustrating. **Only £4.50**

Programmable Sound Generator
We supply the P.C.B. (and manual describing software, hardware, construction details with a tape containing a demonstration and experiment program) – you supply the components and you can build yourself a sound unit to bring your programs to life in a way you never imagined! **£9.50**

ZX81, ZX80, Acorn Atom, Sharp PC1211 software available – Wide range, low price, fast delivery. Send S.A.E. for details (state computer) to: BUG-BYTE, (Dept PE), 251, Henley Road, Coventry.

SIX GAMES (1K) for the ZX80 Pontoon, Guess the Number, Battleships, Slot Machines (1 & 11), Maths Quiz, Maze (1 & 11). Cassette with full instructions for **£3.00** from: P. Bramwell, 87, Anderson Crescent, Great Barr, Birmingham B43 7ST.

COMPUKIT 4K game 'Seek and Destroy' with running score etc. Cassette **£2.50** including circuit for optional low cost sound. Alan Stott, 29, Hounds Road, Chipping Sodbury, Bristol.

BOOKS AND PUBLICATIONS

BOOKS BOOKS BOOKS. Large range of radio and electronic books in stock. Send SAE for lists. Servio Radio, Dept. PE7 156-158, Merton Road, Wimbledon, London SW19 1EG.

OUT OF PRINT Book Service, 17, Fairwater Grove (E), Cardiff. Send SAE for details.

ANY SINGLE SERVICE SHEET £1 L.S.A.E. Thousands different repair/service manuals/sheets in stock. Repair data your named T.V. £6 (with circuits £8). S.A.E. Newsletter, pricelists, quotations. AUS (PE), 76 Church Street, Larkhall, Lanarkshire. (0698 883334).

EDUCATIONAL

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 272J Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers: also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 272J Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 272J Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

TELEVISION COMPUTER COMMUNICATION & RADAR SERVICING

TWO YEAR full-time Modular Diploma course to include a *high percentage of practical work.*

- ELECTRONIC PRINCIPLES
- MONO TV & CCTV
- COLOUR TV & VCR
- MICROELECTRONICS & DIGITAL TECHNIQUES
- COMPUTERS & MICROPROCESSORS
- COMMUNICATIONS & RADAR

Each of the above Modules are 13 weeks in duration. Individual Modules can be arranged for applicants with suitable electronics background.

Tuition fees (UK & Overseas) £1500 per year (i.e. £500 per Module).

Next session starts September 14th.

Prospectus from:

LONDON ELECTRONICS COLLEGE

**Dept: AA, 20 Penywern Road,
London SW5 9SU. Tel: 01-373 8721.**

CAREERS in Marine Electronics. Courses commencing September and January. Further details, the Nautical College, Fleetwood FY7 8JZ. Tel. 03917 79123.

TUITION

PAY AS YOU LEARN, postal mathematics tuition. 23, St. Lukes Close, Middlestown, Wakefield.

SERVICE SHEETS

BELL'S TELEVISION SERVICES for Service Sheets on Radio, Tv, etc **£1.00** plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

FOR SALE

MAPLIN CABINET and extras for Disco Project. Cost £90, want £60 o.n.o. All V.& C. Will deliver. Phone Inverness 32897.

ZX80 SINCLAIR built with manual, mains adaptor, leads. **£55.** Telephone (0407) 810 689.

PRINTER, PRINTER, PRINTER. Data Dynamics plain paper printer with supplies. Ideal for UK101 or similar. **£130.** Tel. 01-959 1844.

NEW BACK ISSUES OF 'PRACTICAL ELECTRONICS' available **90p.** each Post Free. Cheque or uncrossed P/O returned if not in stock. Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

MINISONIC £180, String ensemble **£150,** perfect. Complete sound system, 12 channel mixer. Will separate. 01-866 2721.

KIMBER ALLEN KEYBOARD, 49 notes, with contacts plus tape decks, record decks, speakers, scope. Back issues of P.E. and more. Any takers? Phone 01-237 2828

SUPERBOARD with Cegmon, good P.S.G. Many extras, metal cased **£250.** Phone East Kilbride (03552) 37384.

ELECTRONICS MAGAZINES over 100 magazines, mostly P.Es 1964-1977 **£20** buyer collects. Aylesbury 21736 evenings.

MISCELLANEOUS

PRACTICAL ELECTRONICS P.C.B's

Drilled, 1·5mm Glass fibre Fry's Roller Tinned

MAR 81 27/28 MHz converter EA236 **£1.44**
Digital counter timer EG505/7/9 set **£5.29**
APR 81 Speech processor EP502 **97p.** Intruder alarm EG513 **£1.82**
MAY 81 Digi Sounder EG518-20 set of two **£4.39**
Multimeter EC 21/2 **£2.29** Thermometer EC 20 **98p**

For full list and current pcb's send SAE. Pcb's also produced to customers own masters. Trade enquiries welcomed. Write for quote. CWO Please. **Postage** – add 35p postage and packing to complete order. Europe 70p.

PROTO DESIGN
14 Downham Road, Ramsden Heath,
Billericay, Essex CM11 1PU. Telephone 0268-710722

SEEN MY CAT? 5,000 odds and ends. Mechanical. Electrical. Cat Free. Whiston Dept. PRE, New Mills, Stockport.

RYDER ORGAN SYSTEM

The WW classical design for full-size keyboards, including couplers. Expanded range of p.c. boards & data available includes chorus, vibrato, combination stop control.
Reverberation. A new compact solid-state unit gives smooth natural sound. Demo cassette, on loan, deposit £1.50, refund £1.00. (Prices UK only).

**HIYKON LTD. (P), Woodside Croft,
Ladybridge Lane, Bolton BL1 5ED.**

ULTRASONIC TRANDUCERS. £2.85 per pair + 25p P. & P. Dataplus Developments, 81 Cholmeley Road, Reading, Berks.

ENAMELLED COPPER WIRE

SWG	1 lb	½ lb	¼ lb
10-19	2.95	1.70	0.85
20-29	3.05	1.75	0.95
30-34	3.45	1.90	1.00
35-39	3.75	2.10	1.15
40-43	4.95	2.75	2.15
44-46	5.90	3.50	2.40

FREE WIRE TABLES WITH EACH ORDER.

INDUSTRIAL SUPPLIES,
**102 Parrswood Road, Withington,
Manchester 20.**
Prices include P & P in UK.

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolak Light Sensitive Lacquer – now greatly improved and very much faster. Aerosol cans with full instructions **£2.25.** Developer **35p.** Ferric Chloride **55p.** Clear Acetate sheet for master **14p.** Copper-clad Fibre-glass. Board approx. 1mm thick **£1.70** sq. ft. Post/packing **75p.** WHITE HOUSE ELECTRONICS, P.O. BOX 19, Castle Drive, Penzance, Cornwall.

DIGITAL WATCH BATTERY REPLACEMENT KIT

These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener, also one doz. assort. push pieces, full instructions and battery identification chart. We then supply replacement batteries—you fit them. Begin now. Send **£9.00** for complete kit and get into a fast growing business. Prompt despatch.

**BOLSTER INSTRUMENT CO.
(PE26)**
11 Percy Avenue, Ashford, Middx. TW15 2PB.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for ....

insertions. I enclose Cheque/P.O. for £ ....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics).

NAME ....

ADDRESS..

....

Send to: Classified Advertisement Manager
PRACTICAL ELECTRONICS
**GMG, Classified Advertisements Dept., Room 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-261 5846**
Rate:
28p per word, minimum 12 words. Box No. **60p** extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

BURGLAR ALARM EQUIPMENT. Latest Discount Catalogue out now! Phone C.W.A.S. Alarm 0274 682674.

BIG EARS

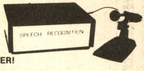

**SPEECH
INPUT
FOR
YOUR
COMPUTER!**

BIG EARS opens the door to direct man-machine communication. The system comprises analogue frequency separation filters, preamps and signal conversion, together with a quality microphone and extensive software.

Words, in any language, are stored as "voice-prints" by simply repeating them a few times in "learn" mode. Using keyword selection techniques, large vocabularies can be constructed.

Use **BIG EARS** as a front end for any application: data enquiry, robot control, starwars — the possibilities are unlimited...

BUILT, TESTED & GUARANTEED ONLY £49!

PRICE INCLUDES POSTAGE & PACKING PLEASE ADD VAT AT 15%

PLEASE STATE COMPUTER: UK101, SUPERBOARD, NASCOM2, PET, TRS80, ETC.

MICROGRAPHICS

Colour Conversion for
UK101/NASCOM 1 & 2/ Superboard. **KIT £45**
(Modulator included) **BUILT £60**

COLOUR MODULATOR **KIT £12**
RGB in, PAL/UHF out **BUILT £18**

Please add VAT at 15% to all prices
Barclay/Access orders accepted on telephone

WILLIAM STUART SYSTEMS Ltd
Dower House, Billericay Road,
Herongate, Brentwood,
Essex CM13 3SD.
Telephone: Brentwood (0277) 810244

VISA

BRAND NEW, NOT SURPLUS, BARGAIN PACKS! 10 7400 £1, 10 BC 183L £1, 10 BC 213L £1, 2 7805 £1. Prices include VAT. Postage 25p. CWO to: MICRO MUSICAL LTD., The Old Vicarage, 37, Wood Lane, Shilton, Coventry CV7 9LA.

MAKE YOUR OWN PRINTED CIRCUITS

Etch Resist Transfers – Starter pack (5 sheets, lines, pads, I.C. pads) **£2.00.** Large range of single sheets in stock at **43p** per sheet.

Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. Full instructions supplied. 2 sheets (20 x 25cm) negative paper and 2 sheets (18 x 24cm) positive film **£1.80.**

20p stamp for lists and information. P&P **35p**/order

Closed for holidays July 20th to August 15th

**P.K.G. ELECTRONICS
OAK LODGE, TANSLEY, DERBYSHIRE**

SECONDHAND ELECTRONIC TEST EQUIPMENT including oscilloscopes, generators, PSU's. Norfab, Telephone Potter Heigham (069-27) 721.

WRONG TIME?

MSF CLOCK is ALWAYS CORRECT – never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, also parallel BCD output for computer etc, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, ACCURACY, **£54.80.**

60KHZ RUGBY RECEIVER, as in MSF Clock, serial data and audio outputs, **£15.70.**

Each fun-to-build kit includes all parts, printed circuit, case, postage etc, money back assurance so GET yours NOW. Assembled to order.

**CAMBRIDGE KITS
45 (FU) Old School Lane, Milton, Cambridge.**

DIGITAL WATCH BATTERIES. Any sort **75p** each + p.p. Send S.A.E. or 15p with number or old battery to Disclec, Y, 511 Fulbridge Road, Werrington, Peterborough PE4 6SB.

Cabinet and Flightcase Fittings

Fretcloths, Coverings, Handles, Castors etc., Jacks and Sockets, Cannons, Bulgins, Reverb Trays, Emilar Compression-Drivers, AKG Mics, Celestion Speakers, ASS, Glassfibre Horns.

Send 30p Postal Order for illustrated catalogues to:–

ADAM HALL (P. E. SUPPLIES)
**Unit G, Carlton Court, Grainger Road,
Southend-on-Sea, Essex SS2 5BZ.**

SUPERB INSTRUMENT CASES BY BAZELLI, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a Low **£1.05.** Chassis punching facilities at very competitive prices, 400 models to choose from. Suppliers only to Industry & The Trade. BAZELLI (Dept. No. 23), St. Wilfrids, Foundry Lane, Halton, Lancaster, LA1 6LT.

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4. 01-531 1568.

ENAMELLED COPPER WIRE				
SWG	1lb	8oz	4oz	2oz
8 to 29	2.76	1.50	0.80	0.60
30 to 34	3.20	1.80	0.90	0.70
35 to 39	3.40	2.00	1.10	0.80
40 to 43	4.75	2.60	2.00	1.42
44 to 47	5.90	3.40	2.39	2.00
48 to 49	15.96	9.58	6.38	3.69
SILVER PLATED COPPER WIRE				
14 to 30	6.50	3.75	2.20	1.40
TINNED COPPER WIRE				
14 to 30	3.85	2.36	1.34	0.90

Prices incl P&P, VAT.
Orders under £2 please add 20p.
SAE for List of Copper/Resistance Wire. Dealer enquiries welcome.
Reg. Office, 22 Coningsby Gardens.

PSYCHOTRONIC GENERATORS, gravity lazers, electrokinesis, electroptography, skinvision, SAE 4″×9″. PARALAB, Downton, Wilts.

NEW 32.7KHz ULTRASONIC ALARM QUARTZ LOCKED + PANIC FACILITY

No alignment – No interaction between units. KITS INC F/G PCB ABS BOX HARDWARE ALL COMPS. Single unit construction – screw connections. 240V operation with battery back up option. 15ft. detection range internally preset. Delay on leaving and entry. Invalid movement delay, self cancelling alarm, approx 2 mins. Latching alarm for panic – ext. resetable with keyswitch. Solid state drive 12VDC @ 25mA and Relay Contact 240VAC 3A ALARM KIT UAQ+P **£21.65.** Built and Tested **£29.65.** Keyswitch in Box **£5.95.** Multitone Sounder 12VDC @ 25mA 95db **£9.20.** All prices inclusive – CWO – UK.

**GJD ELECTRONICS, 105 Harper Fold Road,
Radcliffe, Manchester M26 0RQ.**

CLEARING LABORATORY: scopes, generators, P.S.U.'s bridges, analysers, meters, recorders, etc. 0403-76236.

UK101 – SUPERBOARD

Two really great additions to the UK101 from Computer User Aids.

1. PROGRAMMABLE GRAPHICS

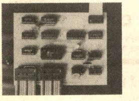

128 User defineable graphics for any UK101. No cuts are made to the board. Simply connect using cables supplied.

HI RES Graphs, 3D drawings, technical graphics, maths, chess. Almost any imaginable symbol may be created.

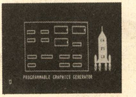

COMPLETE KIT – No extras needed – Includes PCB, chips, sockets, jumpers and even demo tape. **£67.85** inc. VAT P&P or add £4.50 for ready built.

2. PROGRAMMERS AID

Extra fast renumber, trace, find, delete and many more. All on EPROM. No eprom board required. Simply plug onto existing board and go. Suitable for Cegmon, Newmon, Synmon etc.
ALL THESE ROUTINES IN EPROM – **£21.00** inc VAT P&P.

Write or phone now for details of the UK101 User Group and of our other products. These prices apply to members of the User Group only. Membership just £4.60 per 6 months.

**COMPUTER USER AIDS
9 Moss Lane, Romford, Essex.
Telephone Romford 64954.**

Inner London Education Authority

**LONDON COLLEGE OF FURNITURE
41/71 Commercial Road, London E1 1LA**

Department of Musical Instrument Technology

COURSES IN ELECTRONICS FOR THE MUSIC INDUSTRY

T.E.C. DIPLOMA IN MUSICAL INSTRUMENT STUDIES
(2 year full time specializing in Electronics)
T.E.C. HIGHER DIPLOMA IN MUSICAL INSTRUMENT TECHNOLOGY
(2 year full time specializing in Electronics)

The Electronics options of these T.E.C. courses allow the student to specialize in music industry application.

Suitable students would be interested in both music and electronics and wish to combine them within this course.

Application forms and further details are obtainable from the Senior Administrative Officer at the College.

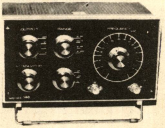

LOW COST

**AUDIO SIGNAL GENERATORS
MODEL 146-9**
(Sine & Square Waves)
10Hz-100kHz
Very low distortion (×0015%)
£41.40 (or in kit form £35.65)
p.p. and ins. £2
With frequency meter **£57.50.**

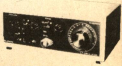

ALSO economical model 113
Sine/Square. 1 volt into 600. Dist .02%.
£31.60 (Kit version **£26.50**) p.p. £1.

**TELERADIO ELECTRONICS
325 Fore Street, Edmonton, London N9 0PE**
S.A.E. for leaflets . . . Closed all day Thursdays . . . 01-807 3719

CALLERS BY APPOINTMENT ONLY

DELTA TECH

62 NAYLOR ROAD, LONDON, N20 0HN
Tel: 01-445 8224
Prices include VAT. Add 35p P&P

Minimum Access Order £4
Discounts on items marked *
10 off 5%, 20 of 10%, 40 off 20%

We welcome Access

CERAMIC CAP (50V)
33pF to 50nF **4p**

POLYSTYRENE CAP (50V)
10pF to 1000pF **5p**

POLYESTER CAP (100V)*
1nF to 68nF **6p,** 100nF **7p,** 150nF **8p,** 220nF **9p,** 330nF **10p,** 470nF **11p,** 680nF **12p,** 1uF **14p,** 1u5 **16p,** 2u2 **20p,** 3u3 **20p,** 4u7 **20p.**

ELECTROLYTIC CAP (uF/V)*
1/25 to 47/25 **6p,** 68/25 **7p,** 100/25 **8p,** 150/25 **9p,** 160/25 **8p,** 200/12 **6p,** 250/12 **7p,** 220/25 **10p,** 470/25 **13p,** 500/30 **12p,** 470/40 **15p,** 640/16 **8p,** 1000/10 **10p,** 1000/40 **30p,** 1500/40 **35p,** 2200/6V3 **12p.**

SWITCHES*

Toggle 3A/250V DPDT	**35p**
Rotary 2A/250V DPST	**30p**
Slide DP 3 Way	**15p**
DIL SWITCH 3 Way SPDT	**80p**
3 Way SPST	**55p**
7 Way SPST	**80p**

RESISTORS (¼W 5%)*
10 Ohms to 10 Mohms **2p**

PRESETS (·15W Hrztal)*
100 Ohms to 2 Mohms **7p**

POTENTIOMETERS (¼W)
Linear & Log Scale
4K7 to 2M2 **35p**

VERO BOARDS (·1″ copper)

2·5″ × 5″	**70p**
3·75″ × 5″	**80p**

ZENER DIODES (400mW)*
2V7 to 33V **8p**

DIL SOCKETS*

8 pin	**9p**	18 pin	**16p**
14 pin	**10p**	22 pin	**20p**
16 pin	**11p**	24 pin	**21p**
		28 pin	**25p**
		40 pin	**35p**

DIODES

OA47	**8p**
OA91*	**8p**
OA200	**5p**
OA202	**6p**
1N916	**4p**
1N4148	**4p**
1N4001/2	**4p**
1N4003	**5p**
1N4004/5*	**6p**
1N4006/7	**8p**
1N5400	**11p**
1N5401	**12p**
1N5402	**13p**
1N5404*	**14p**

OPTO ELECTRONICS

2N5777	**40p**
LD271	**40p**
OCP71	**65p**
ORP12	**80p**
SFH205	**100p**
DL704	**110p**
DL707	**110p**
FND500*	**80p**

LEDs*

3mm & 5mm Clips	**3p**
Red	**12p**
Green	**16p**
Yellow	**16p**
Rect. Green	**25p**

BRIDGE RECTIFIERS

WO2M	**18p**
WO6M	**20p**
1A/50V*	**20p**
1A/200V	**23p**
1A/400V	**28p**
1A/600V*	**29p**
2A/50V	**30p**
2A/100V*	**32p**
3A/100V	**60p**
3A/600V	**75p**

VOLTAGE REGULATORS

500mA: LM320H-5	**40p**
LM320H-24	**30p**
200mA: LM342P-12*	**30p**
500mA: LM79M12*	**40p**
1Amp: 7805*	**70p**
7812/15	**70p**
7818/24	**70p**
7905	**80p**
7912/15	**80p**
7918/24	**80p**

THYRISTORS

4A/300V* (MCR106-5)	**23p**
4A/400V (C106D)	**40p**
12A/100V* (TIC126F)	**40p**
8A/400V* (MOTOROLA)	**75p**

TRIACS

3A/400V (C206D)	**60p**
10A/600Vm*	**75p**
15A/600Vm*	**95p**
30A/600Vm*	**130p**

*THYROTEK
3 pin press fit
Data Supplied.

DIAC

ST2	**24p**

LINEAR CIRCUITS

709-8	**33p**
710-14	**50p**
741-8	**22p**
747-14	**75p**
748-8	**35p**
AY-1-0212	**685p**
AY-1-1313	**750p**
AY-1-1320	**345p**
AY-1-5050	**140p**
AY-3-1270	**965p**
AY-3-8912	**748p**
AY-5-1224A	**275p**
AY-5-1317A	**725p**
AY-5-4007D	**520p**
CA3018H	**70p**
CA3019	**80p**
CA3028AH	**85p**
CA3046N	**70p**
CA3048	**245p**
CA3054N	**40p**
CA3080E	**78p**
CA3089E	**250p**
CA3090AQ*	**350p**
CA3130E	**95p**
CA3140E*	**50p**
CA3160E	**110p**
ICL7106	**920p**
ICL8038CC	**350p**
ICM7555	**92p**
LF351N	**52p**
LF356N	**95p**
LM10C	**460p**
LM301AN	**30p**
LM308N	**45p**
LM311	**80p**
LM318H	**180p**
LM318N	**200p**
LM324N	**55p**
LM339N	**70p**
LM348N	**95p**
LM377N	**200p**
LM380N	**90p**
LM381N	**140p**
LM382N	**130p**
LM386N	**90p**
LM733	**110p**
LM1310N	**140p**
LM1458N*	**45p**
LM1830	**172p**
LM2917	**220p**
LM3900N	**55p**
LM3909N	**75p**
LM3911	**138p**
LM3914	**240p**
LM3915	**254p**
LM13600	**144p**
MC1495L	**405p**
MC1496P	**80p**
MC3340P	**138p**
MK50398	**730p**
ML922	**485p**
ML926	**160p**
ML928	**160p**
ML929	**160p**
NE531	**150p**
NE555	**26p**
NE556*	**50p**
NE562	**400p**
NE564	**485p**
NE565	**138p**
NE566	**160p**
NE567	**160p**
NE571	**485p**
RC4136	**92p**
S566B	**310p**
SL480	**195p**
SL490	**275p**
SN76023N	**170p**
SN76115AN*	**100p**
SN76477	**185p**
TAA621	**290p**
TBA641B	**250p**
TBA651	**220p**
TBA800	**90p**
TBA810S	**110p**
TBA820	**80p**
TDA1004	**335p**
TDA1008	**355p**
TDA1022	**660p**
TDA1024	**120p**
TDA2020	**335p**
TL071	**52p**
TL072	**97p**
TL074	**150p**
TL081	**45p**
TL082	**80p**
TL084	**125p**
TL170	**57p**
UAA170	**190p**
XR2206	**340p**
ZN414	**100p**
ZN424E	**150p**
ZN425E	**460p**
ZN1034E	**220p**

TRANSISTORS

AC126	**22p**
AC127	**22p**
AC128	**20p**
LS12	**28p**
LS13	**45p**
AC141	**15p**
AC142	**15p**
AC151	**17p**
AC153	**25p**
AC176	**22p**
AC187	**22p**
AC187K	**30p**
AC188	**22p**
AD149	**40p**
AF114	**30p**
AF124	**60p**
AF125	**35p**
AF126	**55p**
AF127	**35p**
BC107	**11p**
BC108	**11p**
BC109	**11p**
BC113	**8p**
BC117	**23p**
BC119	**10p**
BC140	**20p**
BC142	**30p**
BC143	**30p**
BC147	**10p**
BC148	**10p**
BC149	**10p**
BC157	**12p**
BC158	**12p**
BC170	**6p**
BC171	**10p**
BC172	**6p**
BC173	**8p**
BC177	**16p**
BC178	**16p**
BC179	**16p**
BC182	**10p**
BC182L*	**10p**
BC183	**10p**
BC184	**10p**
BC186	**25p**
BC207	**13p**
BC209	**13p**
BC212	**10p**
BC212L*	**10p**
BC213L	**10p**
BC214	**10p**
BC214L*	**10p**
BC261B	**23p**
BC301	**32p**
BC303	**32p**
BC328	**17p**
BC477	**35p**
BC478	**20p**
BC547	**12p**
BC548	**12p**
BC549	**12p**
BC557	**14p**
BC558	**14p**
BC559	**14p**
BCY70	**18p**
BCY71	**18p**
BD115	**35p**
BD131	**40p**
BD132	**40p**
BD135	**25p**
BD136	**25p**
BD137	**25p**
BD138	**25p**
BD139	**40p**
BD140	**40p**
BF181	**8p**
BF184	**25p**
BF185	**25p**
BF194	**12p**
BF195	**12p**
BF196	**12p**
BF197	**12p**
BF224B	**14p**
BF244C*	**30p**
BF258	**28p**
BF259	**40p**
BFR39	**30p**
BFR40	**20p**
BFR79	**32p**
BFR80	**20p**
BFX29	**25p**
BFX84	**25p**
BFX87	**25p**
BFX88	**25p**
BFY50*	**25p**
BFY51	**25p**
BFY52	**25p**
BRY39	**50p**
BSX19	**12p**
BSX20	**22p**
BU205	**200p**
BU208	**210p**
MJ2955	**110p**
MJE340	**52p**
MJE3055	**80p**
MPF102	**45p**
MPF104	**40p**
MPF105	**40p**
MPF106	**45p**
OC28	**50p**
OC35	**50p**
OC72	**20p**
TIP29	**40p**
TIP29B	**42p**
TIP30	**40p**
TIP30B	**42p**
TIP31	**30p**
TIP31A*	**31p**
TIP32	**40p**
TIP33	**65p**
TIP33C	**70p**
TIP34A	**75p**
TIP35B	**200p**
TIP36A	**200p**
TIP36B	**210p**
TIP41A	**60p**
TIP42A	**60p**
TIP2955	**70p**
TIP3055*	**40p**
ZTX108	**12p**
ZTX109	**12p**
ZTX300	**14p**
ZTX301	**18p**
ZTX303	**18p**
ZTX304	**23p**
ZTX311	**18p**
ZTX341	**22p**
ZTX500	**15p**
ZTX501	**15p**
ZTX502	**20p**
ZTX503	**17p**
ZTX504	**24p**
2N696	**20p**
2N697	**20p**
2N698	**20p**
2N706	**14p**
2N914	**20p**
2N918	**35p**
2N1131	**20p**
2N1132	**13p**
2N1302	**35p**
2N1304	**35p**
2N1306	**30p**
2N1308	**35p**
2N1613	**25p**
2N2217	**18p**
2N2219	**23p**
2N2222A	**23p**
2N2369	**17p**
2N2484	**25p**
2N2646	**50p**
2N2904	**21p**
2N2905	**21p**
2N2906	**21p**
2N2907	**21p**
2N2926G	**10p**
2N3053	**20p**
2N3054	**30p**
2N3055	**45p**
2N3442	**140p**
2N3702	**11p**
2N3703	**11p**
2N3704	**11p**
2N3705	**11p**
2N3706	**11p**
2N3707	**11p**
2N3708	**11p**
2N3709	**11p**
2N3710	**11p**
2N3711	**11p**
2N3772	**50p**
2N3773	**250p**
2N3819	**21p**
2N3820	**40p**
2N3823	**70p**
2N3866*	**65p**
2N3903	**15p**
2N3904	**15p**
2N3906	**15p**
2N4037	**45p**
2N4058	**10p**
2N4059	**10p**
2N4060	**10p**
2N4061	**10p**
2N5458	**40p**
2N5459	**40p**
2N6027	**30p**
3N128	**100p**

CMOS 40XX

00	**16p**
01B*	**17p**
02	**16p**
06B	**90p**
07*	**16p**
08	**85p**
09	**42p**
10	**50p**
11B*	**20p**
12	**25p**
13B	**45p**
14	**80p**
15B	**80p**
16	**44p**
17	**75p**
18	**85p**
19	**50p**
20B	**100p**
21	**95p**
22*	**95p**
23	**25p**
24B	**55p**
25	**20p**
27	**50p**
28	**85p**
29	**100p**
30	**55p**
35	**110p**
41	**85p**
42	**80p**
43	**95p**
44	**95p**
47	**105p**
48	**60p**
49	**40p**
50B	**50p**
66	**55p**
68	**25p**
69*	**22p**
70B	**30p**
71	**25p**
72	**25p**
73	**25p**
81	**28p**
82	**28p**
86	**80p**

45XX

10	**99p**
11B	**99p**
16	**105p**
18	**105p**
20	**105p**
28	**105p**

TTL 74XX

00	**16p**
01	**16p**
02	**16p**
03	**16p**
04	**16p**
05	**18p**
06	**35p**
07	**35p**
08	**20p**
09	**20p**
10	**16p**
11	**25p**
12	**20p**
13	**30p**
14	**44p**
16	**30p**
17	**28p**
20*	**15p**
21	**40p**
22	**26p**
23	**33p**
25	**33p**
26	**45p**
27	**33p**
28	**40p**
30	**18p**
32	**30p**
33	**38p**
37	**35p**
38	**32p**
40	**18p**
41	**70p**
42	**60p**
43	**115p**
44	**110p**
45	**105p**
46	**100p**
47A	**75p**
48	**75p**
50	**16p**
51	**16p**
53	**16p**
54	**16p**
60	**16p**
70	**35p**
72	**30p**
73*	**33p**
74	**33p**
75	**40p**
76	**33p**
80	**50p**
82	**88p**
83	**103p**
85	**140p**
86	**35p**
89	**240p**
90*	**33p**
91	**85p**
92	**50p**
93	**36p**
94	**85p**
95	**75p**
96	**66p**
97	**200p**
100	**130p**
105	**60p**
107	**35p**
109	**60p**
110	**55p**
118	**90p**
121	**35p**
122	**50p**
123	**65p**
125	**50p**
126	**48p**
132	**65p**
141	**52p**
145	**90p**
147	**170p**
150	**130p**
151	**70p**
153	**70p**
154	**120p**
155	**80p**
156	**80p**
157	**75p**
160	**100p**
161	**99p**
162	**99p**
163	**99p**
164	**120p**
165	**120p**
166	**120p**
167	**225p**
173	**110p**
174	**99p**
175	**90p**
177	**90p**
178	**150p**
179	**177p**
180	**90p**
181	**170p**
182	**90p**
184	**150p**
185	**150p**
190	**120p**
191	**120p**
192	**110p**
193	**110p**
194	**100p**
195	**80p**
196	**99p**
197	**80p**
198	**150p**
199	**160p**

TTL 74LSxx

LS00	**15p**
LS01	**15p**
LS02	**16p**
LS03	**16p**
LS04	**17p**
LS05	**26p**
LS08	**25p**
LS10	**23p**
LS11	**26p**
LS12	**28p**
LS13	**45p**
LS14	**57p**
LS20	**20p**
LS21	**26p**
LS27	**35p**
LS30	**22p**
LS32	**28p**
LS42	**75p**
LS47	**85p**
LS48	**110p**
LS73	**50p**
LS74	**30p**
LS75	**42p**
LS76	**50p**
LS78	**50p**
LS86	**40p**
LS90	**46p**
LS92	**80p**
LS93	**70p**
LS95	**130p**
LS96	**125p**
LS109	**85p**
LS113	**70p**
LS114	**46p**
LS122	**80p**
LS123	**70p**
LS132	**70p**
LS154	**194p**
LS157	**70p**
LS163	**108p**
LS221	**120p**
LS251	**150p**
LS253	**102p**
LS279	**100p**

TD 500

This supurb power amplifier module is a dual mode output configuration. i.e. Class AB low power primary power output stage, dumping power into a rugged class B 6 transistor output stage with inbuilt protection against open and short circuits and thermal overload. 500w into 2 ohms. Input sensitivity .775v RMS (odb) at 25K omhs. Freq. res. 30Hz-25KHz-1dB at full power. Size 7″x6½″x1¾″. T.H.D. .1% max.

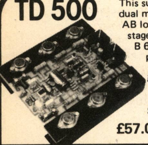

£57.00.inc VAT. 300w version **£47.00**

1Kw DIMMER PAK

* Full wave control using 8A triacs * Moulded plastic case — completely insulated * 1Kw max load filament lamps or inductive loads * Easy clip-in fixing * Compact size: 4¾″ x 1 3/16″ x 2 3/8″ (120 x 30 x 60mm). Cut out size: 4 1/8″ x 7/8″ (105 x 23mm).

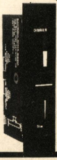

INCREDIBLE VALUE AT ONLY **£16.95**

Four way and eight way facing panels available as optional extras. **Conforms to B.S.800.**

TP 125 AMP

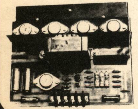

The TP125 power amplifier module will suit all applications where high power, quality and reliability are of utmost importance. Output power ratings using PS125 supply: 125w RMS cont. sine wave, 235w RMS square wave, both into 7.5 ohms. 79w RMS cont. and 145w RMS square wave into 15 ohms. Peak power greater than 300w. T.H.D. 2% @ 125w, 1% @ 50w ref. 1kHz. Size: 6¾″x6½″x3″.

EXCELLENT VALUE **£30.00.**

£22.95

4 CHANNEL SOUND SEQUENCE TO LIGHT CHASER - 4LSM1

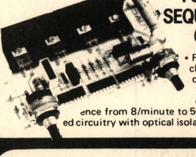

* RCA 8a Triacs * 1000w per channel * Switched master control for sound operation from ½w to 125w * Speed control for fixed rate sequence from 8/minute to 50/sec * Full logic integrated circuitry with optical isolation for amp protection.

TUAC

TUAC Ltd., 119 Charlmont Road, SW17.
Tel 01 672 3137 9080
PRICE INCLUDES VAT. P+P FREE

TO ORDER BY POST. Make cheques/P.O.s payable to TUAC LTD. or quote Access/Barclaycard No. and post to TUAC LTD. 119 Charlmont Road, London SW17 9AB. We accept telephone orders from Access/Barclaycard Holders.

TUAC MAIN DISTRIBUTORS

Birmingham, George Matthews, 85/87 Hurst St, (Tel: 622 1941).
Buckinghamshire, Disco Barn Iver, 20 Thorney Lane South, (Tel: 653171).
Canterbury, Socodi Music, 9 The Friars, (Tel: 60948).
Cheshire, Cookies Disco Centre, 126 West St, Crewe, (Tel: 0270 214739).
Edinburgh, Cruiser Sound Supplies, 13 Ferry Rd, Leith, (Tel: 554993).
Exeter, Electrosure Ltd, Fore St, (Tel: 56687).
Glasgow, Rock Electronics, 149 Glasgow Rd, Dumbarton, (Tel: 32588).
London, Session Music, 163 Mitcham Rd, Tooting SW17, (Tel: 672 3413).
London, Garland Brothers, Chesham House, Deptford Broadway, SE8. (Tel: 01-692 4412)
Kingston, ABC Music, 56 Surbiton Rd, (Tel: 01-546 9877).
Luton, Luton Disco Centre, 88 Wellington St, (Tel: 411733).
Manchester, A1 Music, 88 Oxford St, (Tel: 236 0340).
Middlesborough, Salcoglen, 43 Borough Rd, (Tel: 242851).
Swansea, Burns Electronic Amplification, 63 Ridgeway, Killay, (Tel: 27915).

AITKEN BROS.

35, HIGHBRIDGE, NEWCASTLE ON TYNE
TEL. 0632 26729

Thandar Digital Multimeters

HANDHELD

PDM35 3½ digit LED	£39.68
Carrying Case	£1.73
AC Adaptor	£4.03
TM354 3½ digit LCD	£45.94
Carrying Case	£1.73
TM352 3½ digit LCD	£57.44
Carrying Case	£2.01

Post 75p

BENCH PORTABLE

DM235 3½ digit LED	£60.38
Carrying Case	£8.86
AC Adaptor	£8.69
DM350 3½ digit LED	£83.38
Carrying Case	£8.86
AC Adaptor	£5.69
DM450 4½ digit LED	£113.85
Carrying Case	£8.86
AC Adaptor	£4.03
TM351 3½ digit LCD	£113.85
Carrying Case	£6.84
TM353 3½ digit LCD	£96.60
Carrying case	£6.84

Send SAE for full spec.
All prices include leads.

Extra accessories

Universal test leads	£11.27
Nicads for LED bench models	£8.63
40 Kv probe all models	£34.44

Postage £1.00.

Oscilloscopes

CALSCOPE SUPER 6 6 MHz bandwidth	£186.30
CALSCOPE SUPER 10 10 MHz bandwidth dual trace	£251.85
THANDAR SC110 10 MHz bandwidth portable	£159.85

Carriage included in price.
Send SAE for full spec.

Multimeters

KRT100 1K o.p.v. 10 ranges	£5.50
Y7206EN 20K o.p.v. 19 ranges	£11.95
YN360TR 20K o.p.v. 19 ranges plus transistor tester	£13.95
7081GND 50K o.p.v. 36 ranges	£19.95
EM20 20K o.p.v. 17 ranges mic case	£19.50
AT1020 20K o.p.v. 19 ranges plus transistor checker	£15.95
EM30 30K o.p.v. 17 ranges inc. case	£23.95
MM20 20K o.p.v. 22 ranges inc case, AC current	£25.95
MM50 50K o.p.v. 19 ranges inc case	£32.50
360TR 100K o.p.v. 23 ranges	£34.50
MM100 100K o.p.v. 22 ranges	£42.50
EM1500 20K o.p.v. 21 ranges	£49.95
Carrying Cases	
MM100	£14.95
EM1500	£10.30

Postage £1.00.

Frequency Counters

HANDHELD

Thandar PFM200. LED. 20Hz-200MHz	£57.27
GSC MAX 50 LED. 100Hz-50MHz	£56.35
GSC MAX 550 LED. 500Hz-550MHz	£97.75
GSC PS500 Prescaler. Extends range by ten times. For max 50	£34.50

Postage 75p.

BENCH PORTABLE

GSC 5001 Counter-timer	£212.75
GSC 6001 5Hz-650MHz	£224.25
Thandar TF200. LCD. 10Hz-200MHz	£166.75
Thandar TP600 Pre-scaler 600MHz	£43.13

Postage £1.50.
Send SAE for full spec.

Capacitance Meter

GSC 3001 1pf-199, 900uf	£178.25
Tri-Mode Comparitor	£178.25

Send SAE for full spec.
Postage £1.50.

Generators

GSC 2001 Function 1Hz-100kHz. Sine Square Triangle	£89.70
GSC 4000 Pulse 0.5Hz-5.0MHz	£109.25
Thandar TG105 Pulse 5Hz-5MHz	£97.75
Thandar TG100 Function 1Hz-100kHz	£90.85
GSC DP1 Hand held digital pulser	£58.65

Post + Packing £1.00.

Logic Probes

GSC LP1 10MHz	£35.65
GSC LP2 1.5MHz	£20.70
GSC LP3 50MHz	£56.35
GSC LPK1 Kit 1.5MHz	£13.70

Post + Packing 50p.
Send SAE for full spec.

Solderless Breadboards

GSC EXP 325 **£1.84**, EXP350 **£3.62**, EXP650 **£4.14** EXP48B **£2.64**, EXP 300 **£6.61**, EXP600 **£6.95**.

Postage 25p.

PB6 **£9.95**, PB100 **£13.57**, PB101 **£19.78**, PB102 **£26.39**, PB103 **£41.34**, PB104 **£55.14.**

Powered Boards
PB203 **£68.94**, PB203A **£97.75**, PB203AK Kit **£79.35.**

Postage £1.00.

Soldering Irons by Antex

TEMPERATURE CONTROLLED

TCSU1 Station with CTC iron + 2 bits	**£43.96** *Post £1.75*
Model CX – 17 watt	£4.98
Model C – 15 watt	£4.83
Model X25 – 25 watt	£4.98
ST3 Iron Stand	£1.84

Post 40p.
All spares available.
Send SAE for list and full spec.

Education Establishment order accepted.
Phone or send your ACCESS or BARCLAYCARD number.
All prices include VAT.

VISA

DISCO BARGAIN

22′ ROPE LIGHT
AND CONTROLLER
with SOUND to LIGHT

ONLY £59.50 P&P £1.50

COMPLETE & READY TO WORK – JUST PLUG IN!
ROPE ONLY **£45.50** CONTROLLER ONLY **£19.50**
P&P £1.00 EACH

10 WAY CHASER – 10KW – 64 PROGRAMMES
Includes AUTOMATIC & SOUND TO LIGHT

KIT **£49.50** CASE **£11.50**

P.E. STAR SPINNER

FULL KIT PRICE OF £109.95 SAVING £16.60 OVER INDIVIDUAL PRICES.

PRICES INCLUDE VAT – ADD POST & PACKING 60p ON INDIVIDUAL ITEMS – COMPLETE KIT P&P FREE

Send Cheque or Crossed P.O.'s or Write/Phone your Card No.

Access

FELTGLOW LTD.
105B LONDON ROAD,
BEXHILL, E. SUSSEX.
(0424) 221686.

BARCLAYCAR
VISA

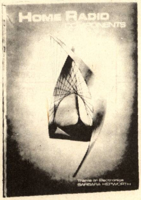

Top Priority for every constructor– HOME RADIO CATALOGUE

- About 2,000 items clearly listed.
- Profusely illustrated throughout.
- Large A-4 size pages.
- Bargain list, order form and coupons each worth 25p if used a directed, all supplied free.

Price £1, plus 50p for post, packin and insurance.

Send cheque or P.O. for £1.50

HOME RADIO Components LTD
Dept. PE, P.O. Box 92, 215 London Roa
Mitcham, Surrey. 01-543 565

CELESTION

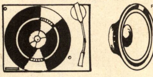

RICHARD ALLAN

WE SELL
FANE, GOODMAN
High quality power speakers
12 in 50W 8 ohms
12 in 50W 16 ohms
12 in 80W 8 ohms
12 in 80W 16 ohms
15 in 150W 8 ohms
15 in 150W 16 ohms

PIEZO HORN TWEETERS
Up to 100 watts each. No x-over required. Flared Horns. Mid range Flared Horns. In stock now. Large range of speakers, public address equipment, microphones, mixers, ham equipment.

Heavy chromed Floor Stand.	£9.95
Boom Arm	£8.50
Echo Chamber	£59.95
Analogue Echo Chamber	£69.95

CB Antenna & Accessories in stock now!!

Special offer Disco Driver 80 **£27.95**
Stockists of leading makes of Disco Units & Lighting Equipment.
CITRONIC, FAL, TK, ICE, OPTIKINETICS, PLUTO.

Give your cabinets the professional finish.
Send 2 × 14p stamps for illustrated catalogue.

CROSSOVERS

100W	8 ohm	2 way
100W	8 ohm	3 way
80W	8 ohm	4 way
60W	8 ohm	2 way

All prices include VAT at 15%. *Mail Orders welcome.*

MUSICRAFT
303 EDGWARE ROAD,
LONDON W.2. ENGLAND
TELEPHONE: 01-402 9729 / 01-402 2898

NICKEL CADMIUM BATTERIES

	AA (HP7) 0.5AHr	SUB 'C' 1.2AHr	'C' (HP11) 1.65AHr	'C' (HP11) 2.0AHr	'D' (HP2) 4.0AHr	PP3 0.1AHr
1–24	£0.85	£1.38	£1.69	£2.25	£2.97	£3.79
25–49	£0.82	£1.28	£1.58	£2.10	£2.77	
50–99	£0.80	£1.24	£1.52	£2.02	£2.67	
100 up	£0.70	£1.15	£1.41	£1.87	£2.47	

All cells are brand new full spec devices from reputable mnfrs. All Nickel Cadmium cells (except PP3) are supplied complete with solder tags and are **'VENTED' devices** suitable for fast charge.

CHARGERS – single or dual O/P to charge PP3, AA or SUB 'C' cells in 12-14 hrs (chargers will charge 'C' and 'D' cells but with longer charging time). Units-supplied complete in plug top case with flying leads. Number of cells (10 max) in series and type must be specified for each required O/P when ordering.

SINGLE O/P CHARGER **£5.04**
DUAL O/P CHARGER **£5.72**

TRANSFORMERS – as used in chargers, 2 × 12 volt 0.25 amp secondarys 240v primary, tag connections **£1.57** each.

Data and charging circuits free with orders over £10 otherwise 30p post. P&P 10% if order less than £10, 5% if order over £10. Prices *DO NOT INCLUDE VAT* and this should be added to the total order.

Cheques, P.O.'s Mail Order to:–

SOLID STATE SECURITY,
Dept. (PE), Bradshaw Lane,
Parbold, Wigan, Lancs.
Telephone 02576-3018.

PROGRESSIVE RADIO

31, CHEAPSIDE, LIVERPOOL L2 2DY

SEMICONDUCTORS. Texas R1038 TO3 power trans. **50p.** 741 8 pin **22p.** NE555 **24p.** TAG4443 SCR **45p.** 723 14 PIN REGS. **35p.** AD 161/2 MATCHED PAIRS **70p.** 2N5062 SCR **18p.** TIL209 RED LEDS 10 for **75p.** BD238 **28p.** BD438 **28p.** MPU131 P.U.T.'s 40V, 200mA, 375M/W **15p** each. 2N3733 **£1.75.** Infra Red 0.2" LEDs **30p.**
RECTANGULAR LED's, red, green or yellow **12p** each. BY223 **20p.**

MINIATURE MAINS TRANSFORMERS. ALL 240VAC PRIMARY, 6-0-6 100mA, 3-0-3 100mA, 12-0-12 50mA, all **75p** each. 12V 200mA **75p.** 12V 500mA **£1.20.** 0-6V-0-6V 280mA **£1.30.**

PULSE TRANSFORMERS. 1:1 (GPO type) **30p.** 1:1 plus 1 min. P. C. mounting **60p.**

MINIATURE SOLID STATE BUZZER. 33×17×15mm. output at 3 feet 70db, only 15mA drain, operating voltage 2 types 6 or 12VDC **75p each.**

LOUD BUZZER. 6-12 volts **63p.** Rotary Alarm siren, 12VDC., Red plastic body and mounting bracket 68×75mm **£4.50p. 6" ALARM BELLS,** motorised aluminium gong, output 88db at 3 mtrs., 12V DC 65mA, **£7.95p.**

POCKET MULTIMETER. MODEL NH55 2,000 ohms per volt. 1,000 volts AC/DC, 100mA DC current, 2 resistance ranges to 1 meg **£5.50p.**

SOLDER SUCKER. High suction/teflon nozzle, **£4.65p.**

TRANSDUCERS. 40KHz. REC/SENDER **£3.50** pair.

HIGH IMPEDENCE HEADPHONES, mono 2,000 ohms imp. transducer type, adjustable band and padded earpiece **£2.75.**

SPECIAL OFFER STEREO HEADPHONES. 8 ohms, adjustable, standard stereo plug only **£2.95p**

INTERCOM UNITS (can be used as baby alarm) supplied with approx. 60' cable, call button, 2 was **£5.25** pair, 3 way **£7.25p. WIRELESS INTERCOM,** 2 units both operate on 240VAC and mains connected. AM frequency 180KHz., **£29.95p.**

MINIATURE TIE PIN MICROPHONE. Omni, 1K imp., uses deaf aid battery (supplied) **£4.95p. LOW COST CONDENSER MIKE.** Stick type. Omni, 600 ohms, on/off switch, standard jack plug only **£2.95p. EM607 CONDENSER MICROPHONE.** Highly polished metal stick mike, uni directional, 600 ohms. 30-18KHz., on/off switch only **£7.95p.**

JACKSONS C280 **50p. 50PF VARIABLE CAPS. 50p each. MERCURY (TILT) SWITCH** 1"×⅜". **35p.**

Special clearance offer of tools, (1) Side Cutters, (2) Long nosed Pliers, (3) Heavy duty pliers, insulated handles, all at **£1.00 each.**

CRIMPING TOOL. for standard terminals also 6 gauge stripper and wire cutter, insulated handles only **£2.30.**

40 CHANNEL AM CB RECEIVER, for car use, operates on 12V DC **£7.95p.**

CB HAND HELD PA MICROPHONES with Pressil switch, curly lead, noise cancelling type « **£7.25p** or power type « **£7.95p.**

POWER SUPPLY. 240V AC input, 13.8V DC out at 3/5 amp **£14.75p** (+ 75p P&P).

FM MICROPHONE, Electret condenser type, tuneable 85-95MHz, arrival distance 50 mtr outdoors (approx.), size 163×35mm **£10.25p.** (Not licenseable in U.K.).

Cash with order please, official orders welcome from schools etc., please add 30p post and packing. VAT inclusive.
SAE for latest illustrated stock list. *ALL ORDERS DESPATCHED BY RETURN POST*

I L P TRANSFORMERS

INCREASED PRODUCTION CAPACITY BRINGS LOWER PRICES

TOROIDAL
IN A RANGE OF 76 TYPES FROM 30VA TO 500VA AND IN CHOICES OF THREE PRIMARIES 110V, 220V or 240V

TYPE	SERIES No.	SECONDARY RMS Volts	SECONDARY RMS Current	PRICE
30VA *0x30mm* *0.45 Kg*	1X010	6+6	2.50	**£4.48** *+0.87p P/P* *+0.80p VAT*
	1X011	9+9	1.66	
	1X012	12+12	1.25	
	1X013	15+15	1.00	
	1X014	18+18	0.83	
	1X015	22+22	0.68	
	1X016	25+25	0.60	
	1X017	30+30	0.50	
50VA *0x35mm* *0.9 Kg*	2X010	6+6	4.16	**£4.93** *+£1.10 P/P* *+0.90p VAT*
	2X011	9+9	2.77	
	2X012	12+12	2.08	
	2X013	15+15	1.66	
	2X014	18+18	1.38	
	2X015	22+22	1.13	
	2X016	25+25	1.00	
	2X017	30+30	0.83	
	2X028	110	0.45	
	2X029	220	0.22	
	2X030	240	0.20	
80VA *90x30mm* *1 Kg*	3X010	6+6	6.64	**£5.47** *+£1.43 P/P* *+£1.04 VAT*
	3X011	9+9	4.44	
	3X012	12+12	3.33	
	3X013	15+15	2.66	
	3X014	18+18	2.22	
	3X015	22+22	1.81	
	3X016	25+25	1.60	
	3X017	30+30	1.33	
	3X028	110	0.72	
	3X029	220	0.36	
	3X030	240	0.33	
120VA *90x40mm* *1.2 Kg*	4X010	6+6	10.00	**£6.38** *+£1.43 P/P* *+£1.17 VAT*
	4X011	9+9	6.66	
	4X012	12+12	5.00	
	4X013	15+15	4.00	
	4X014	18+18	3.33	
	4X015	22+22	2.72	
	4X016	25+25	2.40	
	4X017	30+30	2.00	
	4X028	110	1.09	
	4X029	220	0.54	
	4X030	240	0.50	

TYPE	SERIES No.	SECONDARY RMS Volts	SECONDARY RMS Current	PRICE
160VA *110x40mm* *1.8 Kg*	5X012	12+12	6.66	**£8.44** *+£1.43 P/P* *+£1.48 VAT*
	5X013	15+15	5.33	
	5X014	18+18	4.44	
	5X015	22+22	3.63	
	5X016	25+25	3.20	
	5X017	30+30	2.66	
	5X018	35+35	2.28	
	5X028	110	1.45	
	5X029	220	0.72	
	5X030	240	0.66	
225VA *110x45mm* *2.2 Kg*	6X014	18+18	6.25	**£10.06** *+£1.73 P/P* *+£1.77 VAT*
	6X015	22+22	5.11	
	6X016	25+25	4.50	
	6X017	30+30	3.75	
	6X018	35+35	3.21	
	6X026	40+40	2.81	
	6X028	110	2.04	
	6X029	220	1.02	
	6X030	240	0.93	
300VA *110x50mm* *2.6 Kg*	7X016	25+25	6.00	**£11.66** *+£1.73 P/P* *+£2.01 VAT*
	7X017	30+30	5.00	
	7X018	35+35	4.28	
	7X026	40+40	3.75	
	7X025	45+45	3.33	
	7X028	110	2.72	
	7X029	220	1.36	
	7X030	240	1.25	
500VA *140x60mm* *4 Kg*	8X017	30+30	8.33	**£15.53** *+£2.05 P/P* *+£2.64*
	8X018	35+35	7.14	
	8X026	40+40	6.25	
	8X025	45+45	5.55	
	8X033	50+50	5.00	
	8X028	110	4.54	
	8X029	220	2.27	
	8X030	240	2.08	

I.L.P. TOROIDALS
Only half the weight and height of their laminated equivalents. in choice of 110V, 220V, 240V primaries coded as follows: (Secondaries can be connected in series or parallel)
For 110V Primary insert 0 in place of "X" in type number.
For 220V Primary (Europe) insert 1 in place of "X" in type number.
For 240V Primary (U.K.) insert 2 in place of "X" in type number.
Example – 120VA 240V 15+15V. 4A=42013.

+ A NEW SERIES OF P.C.B MOUNTING LAMINATED TYPES

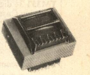

TYPE	SERIES No.	SECONDARY RMS Volts	SECONDARY RMS Current	PRICE
3VA	P2401	3+3	0.50	**0.92p** *+24p P/P* *+17p VAT*
	P2402	4.5+4.5	0.33	
	P2403	6+6	0.25	
	P2404	7.5+7.5	0.20	
	P2405	9+9	0.17	
	P2406	12+12	0.12	
	P2407	15+15	0.10	
	P2409	20+20	0.07	
6VA	P3401	3+3	1.00	**£1.91** *+£30p P/P* *+33p VAT*
	P3402	4.5+4.5	0.67	
	P3403	6+6	0.50	
	P3404	7.5+7.5	0.40	
	P3405	9+9	0.33	
	P3406	12+12	0.25	
	P3407	15+15	0.20	
	P3408	17.5+17.5	0.17	
	P3409	20+20	0.15	
	P3410	25+25	0.12	
12VA	P4401	3+3	2.00	**£2.09** *+58p P/P* *+40p VAT*
	P4402	4.5+4.5	1.33	
	P4403	6+6	1.00	
	P4404	7.5+7.5	0.80	
	P4405	9+9	0.66	
	P4406	12+12	0.50	
	P4407	15+15	0.40	
	P4408	17.5+17.5	0.34	
	P4409	20+20	0.30	
	P4410	25+25	0.24	

ABOUT THE NEW LAMINATES

I.L.P. LAMINATED
I.L.P. printed circuit mounted mains transformers have two independent primary windings which can be connected in series for 240V or parallel for 120V operation. The two independent secondaries can also be connected in series or parallel to give a wide range of output voltage/current configurations. All are wound on split bobbins, eliminating need for a inter-winding screen. Breakdown tested to 2000 VAC minimum.
Regulation – 3VA typically 21%; 6VA typically 15%;
12VA typically 10%

GOODS DESPATCHED WITHIN 7 DAYS OF RECEIPT OF ORDER ·
OR SINGLE AND SMALL QUANTITY ORDERS.

SEE OUR ADS
ALSO ON PAGES 72 & 73

- ★ **CUSTOMER DESIGN ENQUIRIES INVITED. QUANTITY PRICE LIST AVAILABLE.**
- ★ **FREEPOST FACILITY** (U.K. only). Simply send your order in envelope to **FREEPOST** to address below. **NO STAMP REQUIRED.**
- ★ **TO ORDER** *Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £1 extra to TOTAL value of order.*
- ★ **Also available from ELECTROVALUE and MARSHALLS.**

I L P TRANSFORMERS (A division of I.L.P. ELECTRONICS LTD.)

FREE POST T2 GRAHAM BELL HOUSE ROPER CLOSE
CANTERBURY CT2 7EP. Phone (0227) 54778 Technical (0227) 64723 Telex 965 780

To: I.L.P. ELECTRONICS LTD. CANTERBURY CT2 7EP
Please supply Transformer(s)................ No.(s)................
.... Total purchase price £..........
I enclose Cheque ☐ Postal Orders ☐ International Money Order ☐
Debit my Access/Barclaycard Account No......................
....
NAME...
ADDRESS..
....
Signature..
P.E.

CLEF ELECTRONIC MUSIC

FIRST

FOR **PIANOS**
FOR **STRINGS**
FOR **ROTORS**
FOR **RHYTHM**

IF MUSIC IS YOUR INTEREST

Since 1972 Clef Products have consistently produced leading designs in the field of Electronic Musical Instruments, many of which have been published under the authorship of A. J. Boothman. With musical quality of paramount importance new techniques have been evolved and the latest musically valid technology has been incorporated into projects which have been successfully completed by constructors over a wide range of technical capability.

PIANOS

Kits or Manufactured
SPECIALISTS SINCE 1972

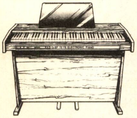

The most advanced form of Touch Sensitive action simulating piano key inertia by patented technique.

SIX OCTAVES £207

(component kits include keyboard and may be purchased in four stages)

7½ OCTAVES £232

Four mixable voices for serious tone variation plus electronic chorus and flanger effects. See lists for Cabinets, P.A. & Manufactured Pianos.

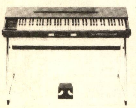

Back up **TELEPHONE** advice to our customers is available direct from the Designer of all kits advertised.

STRINGS

P.E. STRING ENSEMBLE

Versatile String Synthesizer with split keyboard facility and impressive voices. 49 note organ diode keyswitch system with four pitches plus two phase Chorus generator. Kit includes Swell Pedal.

COMPONENT KIT £174

ROTOR-CHORUS

Comprehensive two speed organ rotor simulator plus a three phase chorus generator on a single 8″ × 5″ p.c.b. The kit includes all components for mains operation and a stereo headphone driver p.c.b. Easily integrated with existing organ/amplifier system.

COMPONENT KIT £89.00

KEYBOARDS

Our Square Front Keyboards are chosen for their superior feel to the discerning musician whilst giving adequate physical strength for the high impact playing present in the Piano application.

49 NOTE C-C	**£25.00**	**QUANTITY**
73 NOTE F-F	**£41.00**	**ENQUIRIES**
88 NOTE A-C	**£49.50**	**WELCOME**

MASTER RHYTHM

As published in Practical Electronics

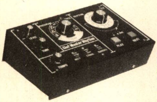

FULLY PROGRAMMABLE
TWENTY-FOUR PATTERNS
EIGHT PARALLEL TRACKS
TWELVE INSTRUMENTS
SEQUENCE OPERATION

Kit includes all components to build this comprehensive User Programmable Rhythm Generator in an attractive metal case with finished case, hardware and wire.

KIT – £79.00 BUILT – £114.00

OUR PRICES INCLUDE V.A.T., CARRIAGE & INSURANCE

Please send S.A.E. for complete lists or use our telephone BARCLAYCARD service. Very competitive **EXPORT** rates – in Australia please contact JAYCAR in Sydney.

ALL INSTRUMENTS MAY BE SEEN IN OUR SHOW ROOM.

CLEF PRODUCTS (ELECTRONICS) LIMITED
(Dept. P.E.) 44A Bramhall Lane South, Bramhall,
Stockport, Cheshire SK7 1AH 061-439-3297

INTERESTED IN

ELECTRONICS?

TRY A ZEDPACK!

COMPONENTS AT A PRICE EVERYONE CAN AFFORD

Z1	300 mixed ½ and ¼ **watt resistors**	**£1·95**
Z2	150 mixed 1 **and** 2 **watt resistors**	**£1·50**
Z3	300 mixed **capacitors,** most types	**£3·95**
Z4	100 mixed **electrolytics**	**£2·20**
Z5	100 mixed **polystyrene caps**	**£2·20**
Z6	300 mixed **printed circuit components**	**£1·95**
Z7	300 mixed **printed circuit resistors**	**£1·45**
Z9	100 mixed miniature ceramic and **plate caps**	**£1·20**
Z10	25 **assorted pots.**	**£1·50**
Z11	25 assorted **presets,** skeleton etc.	**£1**
Z12	20 assorted **vdr's** and **thermistors**	**£1·20**
Z13	1lb **mixed hardware.** Nuts, bolts self-tappers, sleeving, etc.	**£1·20**
Z14	100 mixed, new and marked, full spec. **transistors.** Pack includes:— BC148, BF154, BF274, BC212L, BC238, BC184L, PBC108 and, or lots of similar types	**£4·95**
Z15	100 mixed **diodes** including:—zener, power, bridge, signal, germanium, silicon etc. All full spec.	**£4·95**
Z16	20 1N4148	**£1**
Z17	20 1N4003/10D2	**£1**
Z18	20 assorted zeners, 1 watt and 400mw	**£1·50**
Z19	12 ·125″ TIL 209 RED. LED'S	**£1**
Z20	10 Assorted **switches,** including push button, slide, multipole, miniature etc.	**Fantastic value. £1·20.**

UHF MODULATORS

Video in UHF out. Calibrated to channel *36* (625 line UHF) housed in metal box 2½″ × 2″ × ½″ with 9′ coaxial lead, TV plug and connection data. **£2·50** ea. **3 for £6.**

Aluminium finish *slider knobs*, standard fitting. **10** for **£1**

200μA Miniature level/batt. **meters,** as fitted to many cassette recorders. **90p**

Deluxe FIBREGLASS printed circuit etching kits.

Includes 100 sq ins. of copperclad F/G board. 1lb ferric chloride, (made for U.S. army to MIL, SPEC.), 1 dalo etch resist pen, abrasive cleaner, tweezers, etch resist dish and instructions. **OUR PRICE £5·95**

1lb of FeCl. **£2·25.**

150 sq. ins. single sided board.	**£2·20**
150 sq. ins. double sided board.	**£3·30**
100 Miniature **reed switches.**	**£2·30**
100 **Subminiature** Reed Switches.	**£4·20**

SMALL MAGNETS

With hole in 6 for **£1**

P/B SWITCH BANKS

These cost a fortune! Were made for various music centres. Includes independent and interdependent latching types multi pole c/o etc. Can be modified. Can't be repeated. **3 Banks for £1.**

KNOBS for Switch Banks **10 for £1.** Chrome or spun aluminium finish.

MINIATURE MAINS TRANSFORMERS

Top quality. Split bobbin construction will give 4·5V-0-4·5V at 250MA. 1¾″ × 1½″ × 1½″, all sorts of uses. **ONLY £1** 3 for **£2·50.**

PP3 Battery Connectors 10 for 50p.

Miniature Press to Make Switches, Red knob. **3 for 50p.**

Subminiature S.P.C.O. Slide Switches. **6 for 50p.**

Miniature D.P.C.O. Slide Switches. **6 for 50p.**

Standard **2P. 3 Position** Slide Switch. **4 for 50p.**

4 × **HP11** Battery Holders (2 × 2 Flat type) with leads. **2 for 50p.**

Assorted Fuse Holders including 20mm, P.C., Panel and chassis types. **Pack of 7 for 50p.**

3·5mm Jack Sockets, switched. **Enclosed type.** P.C. or panel mounting. With nuts and washers. **4 for 50p.**

9 Section, **Chrome on Brass Telescopic Aerial.** Plugs into any 3·5mm socket. Approx 25″ extended **£1** each. 3 for **£2·50.**

Hi Power **Infra Red Transmitter** 5mm LED. **TIL 38** 60p ea. **3** for **£1·50.**

Crystal Clear 3mm **LEDS very pretty** Red, Green, Yellow. 10 of one colour **£1.** 10 of each **£2·50.**

ALTERNATOR RECTIFIERS

Make lovely **60 amp** bridges. Ideal for **High Power Battery Chargers.** Type 4AFI. **Set of 4** (2 neg. case + 2 pos. case) **£2.**

Special Purchase enables us to offer **Mullard C280 Polyester Capacitors** (Liquorice Allsorts) at the unbeatable price of **£2 for 100 mixed. £15 for 1000.** These consist of factory clearance lots i.e. spillages, floor sweepings, cosmetic rejects etc.

To: "GEMINI ELECTRONIC COMPONENTS" DEPT PE
"THE WAREHOUSE" SPEEDWELL ST. LONDON S.E.8.
Where shown. Send Cheque* or Postal Order. Plus 60p P&P. and 15% VAT.
Please Quote ZED Code. *Schools etc. SEND OFFICIAL ORDER
ZED PACKS now available for **Callers** at 50 Deptford Broadway, London, S.E.8.

RADIATION DETECTORS

BE PREPARED WITH THIS DETECTOR

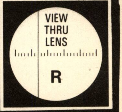

Recommended for General use.
CIVIL DEFENCE ● FIRE SERVICES ● MEDICAL

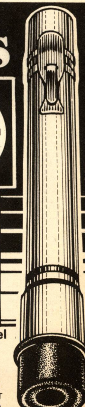

- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS.
- UNIT IS SIZE OF FOUNTAIN PEN AND WILL CLIP IN TOP POCKET.
- PRECISION INSTRUMENT, METAL CASED, WEIGHT 2oz.
- CONTAINS 3 LENSES. ■ RUGGED CONSTRUCTION.
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH.

COMPLETE WITH DATA

FREE RECHARGE AFTER PURCHASE

British design and manufacture. Tested, calibrated and guaranteed. Ex-stock delivery by return.

Be prepared, buy whilst available.

Standard model
0-5 or 0-50R
ONLY
£6.95 inc.VAT
Post & Packing 60p

HENRY'S
404 EDGWARE ROAD,
LONDON W2 1ED

Buy it with Access   VISA

Index to Advertisers

Acorn ... Cover II
Adam Hall (P.E. Supplies) ... 78
Aitken Bros. ... 80
Ambit ... 44

Barrie Electronics ... 7
B.I.E.T. ... 4
Bi Pak ... 13
Bolster Instruments ... 77
Boss Industrial Mouldings ... 14
British National Radio & Electronics School ... 8

Cambridge Kits ... 78
C.D.I. Electronics Systems ... 76
Chromasonic Electronics ... 6, 7
Clef Products ... 82
Computer Components (Teleplay) ... Cover III
Crofton Electronics ... 74
C.R. Supply ... 76
C.U.A. ... 78

Delta Tech ... 79
Doram ... 12
Dziubas M. ... 14

E.D.A. ... 75
Electrovalue ... 71
Electroware (O.K. Machine & Tool) ... 37

Feltglow ... 80

Gemini ... 82
GJD Electronics ... 78
Global Specialties Corporation ... 5

Hameg Ltd ... 22
Heathkit ... 4
Henry's Radio ... 14, 82
Hiykon Ltd. ... 77
Home Radio ... 80

ICS Intertext ... 75, 76
ILP Electronics ... 72, 73, 81
Industrial Supplies ... 77

L & B Electronics ... 12
London College of Furniture ... 78
London Electronics College ... 77

Maplin Electronics ... Cover IV
Marick ... 76
Marshall A. ... 60
Microcircuits ... 15
Micro Peripherals (Mighty Micro) ... 41
Micro Times ... 74
Midwich Computers ... 22
Millhill ... 74
Modern Book Co. ... 83
Musicraft ... 80

Northern Micro ... 76

Parndon ... 74
Phonosonics ... 70, 71
P.K.G. Electronics ... 78
Progressive Radio ... 81
Proto Design ... 77

Radio Component Specialists ... 83
Radio & T.V. Components ... 16
Rapid Electronics ... 8

Saxon Entertainments ... 53
Science of Cambridge ... 10, 11
Scientific Wire Co. ... 78
Solid State Security ... 81
Swanley Electronics ... 4

Technomatic ... 84
Teleradio ... 78
Tempus ... 49
Titan ... 44
T.K. Electronics ... 9
T.U.A.C. ... 79

Videotone ... 33

Watford Electronics ... 2, 3
West London Direct Supplies ... 83
William Stuart Systems ... 78
Wilmslow Audio ... 71

NEW 1981
MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL
by Markus Price: £32.50

RADIO AMATEUR HANDBOOK
by ARRL 1981 ed. Price: £8.00

THE ART OF ELECTRONICS
P. Horowitz Price: £13.50

WORLD RADIO T.V. HANDBOOK
1981 edition Price: £10.50

ELECTRONIC PRINCIPLES 2nd ed.
A. P. Malvino Price: £4.35

MANUAL OF ELECTRONIC SERVICING TESTS & MEASUREMENTS
by R. Genn Price: £10.00

INTRO. TO DIGITAL FILTERS
by T. Terrell Price: £6.95

MICROPROCESSORS & MICRO-COMPUTERS FOR ENG. STUDENTS & TECHNICIANS
by B. Wollard Price: £5.65

USING CP/M A SELF TEACHING GUIDE
by J. Fernandez Price: £6.75

★ALL PRICES INCLUDE POSTAGE★

THE MODERN BOOK CO.
BRITAIN'S LARGEST STOCKIST
of British and American Technical Books
19-21 PRAED STREET
LONDON W2 1NP
Phone 01-402 9176
Closed Saturday 1 p.m.

MAINS INTERCOM

NO BATTERIES NO WIRES
ONLY £37.99 PER PAIR
+ VAT £5·70
+ P & P £2·15

The modern way of instant 2-way communications. Just plug into power socket. Ready to use. Crystal clear communications from room to room. Range ½-mile on the same mains phase. On/off switch. Volume control, with 'buzzer' call and light indicator. Useful as inter-office intercom, between office and warehouse, in surgery and in homes. Also F.M. 2 channel "touch" model **£55·95** + VAT £8·40 + P & P £2·15

NEW AMERICAN TYPE CRADLE
TELEPHONE AMPLIFIER

£18.95
+ VAT £2·85
+ P & P £1·65

Latest transistorised Telephone Amplifier, with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control, conversation recording, model at **£20·95** + VAT £3·15. P & P £1·65.

DOOR ENTRY SYSTEM

No house/business/surgery should be without a DOOR ENTRY SYSTEM in this day and age. The modern way to answer the door in safety to unwanted callers. Talk to the caller and admit him only if satisfied by pressing a remote control button which will open the door electronically. A boon for the invalid, the aged, and busy housewife. Supplied complete d.i.y. kit with one internal Telephone, outside Speaker panel, electric door lock release (for Yale type surface latch lock); mains power unit, cable (4 pairs) 50 ft. and wiring diagram. Price **£59·95** + VAT £9·00 + P & P £2·25. Kit with two Telephone's **£69·95** + VAT £10·50 + P & P £2·45.

10-day price refund guarantee on all items
WEST LONDON DIRECT SUPPLIES (PE7)
169 KENSINGTON HIGH STREET,
LONDON, W8. 01-937-5548.

BAKER 50 WATT AMPLIFIER £69 Post £2

Superior quality ideal for Halls/PA systems. Disco's and Groups. Two inputs with Mixer Volume Controls. Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm. AC 240V (120V available). Blue wording on black cabinet.

BAKER 150 Watt AMPLIFIER 4 Inputs £89

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains. Printed Circuit, £3
DELUXE MODEL Ready Built. 800 watts £4

STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. £2·95

SOUND TO LIGHT CONTROL KIT MK II

Complete kit of parts, printed circuit. Mains transformer. 3 channels. Up to 1,000 watts each. Will operate from 200MV to 100 watts signal source. Suitable for home Hi-Fi and all Disco Amplifiers. Cabinet extra £4·50. £15 Post 95p

200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Screw 75p each or 6 for £4, or 12 for £7.50.

MAINS TRANSFORMERS Primary 240V A.C.		POST
250-0-250V 70mA, 6·5V, 2A	£4.50	£2
250-0-250V 80mA, 6·3V 3·5A, 6·3V 1A	£5.00	£2
350-0-350V 250mA, 6·3V 4A C.T. 5V/6·3V 2A	£14.50	£2
300-0-300V 120mA, 2×6·3V 2A C.T.; 5V 2A	£10.00	£2
220V 45mA, 6·3V 2A	£2.50	£1

GENERAL PURPOSE LOW VOLTAGE
Tapped outputs available

2 amp 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V	£6.00	£2
1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£6.00	£2
2 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£9.50	£2
3 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£12.50	£2
5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£16.00	£2

		POST			POST
6V, 500mA	£2.00	80p	6-0-6V, 100mA	£1.50	80p
12V, 100mA	£1.30	80p	20V, 40V, 60V, 1a	£4.00	£2
12V, 750mA	£2.00	80p	12V, 3a	£3.50	£1
10-0-10V 2a	£3.00	£1.	10V, 30V, 40V, 2a	£3.50	£2
30V, 5a and 17V-0-17V, 2a	£4.00	£2	12V, 2a	£3.25	£1
			20V, 1a	£3.00	£1
0·5, 8, 10, 16V, ½a	£2.50	£1	20-0-20V, 1a	£3.50	£1
9V, 3a	£3.50	£1	25-0-25V, 2a	£8.00	£2
15-0-15V 2a	£3.75	£1	2 of 18V, 6a	£11.00	£2
30V, 2a	£3.50	£1	12-0-12V, 2a	£3.50	£1
30V, 1½a	£3.30	£1	9V, ¼a	£1.50	80p

AUTO TRANSFORMERS 115V to 240V 500W £12.00 £2
CHARGER TRANSFORMERS – RECTIFIERS

6-12V-3a	£4.00	£2	6-12V-2a	£1.00	80p
6-12V-4a	£6.50	£2	6-12V-4a	£2.00	80p

R.C.S. LOUDSPEAKER BARGAINS
3 ohm. 6 × 4in., 5in., 7 × 4in. £1·50. 8 × 5in. £3·00. 6½in. £3·00 8in. £3·50 10in. £4·00. 12in. £4·50.
8 ohm. 2¾in. £1·50. 3in. £1·50. 5in. £1·50. 8in. £3·50. 12in. £4·50
16 ohm. 6 × 4in. £1·50. 5in. £1·50. 8in. £3·50. 12in. £4·50. 10 × 6in. £3·50. 25 ohm 3½in, 35 ohm 3in. £1·50.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS 90-100 mA Post 75p £2·95
All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer input 200-240 a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA. State voltage.

PP BATTERY ELIMINATOR. BRITISH MADE Post 75p £4·50
Mains power pack 9 volt 400 ma stabilised, with overload cutout. Plastic case size 5 × 5¼ × 2¼. Suitable Radio/Cassettes. DELUXE Switched Model 3-6-7½-9V. 400ma **£7·50.**

THE "INSTANT" BULK TAPE ERASER
Suitable for cassettes, and all sizes of tape reels.
A.C. mains 200/240V.
Leaflet S.A.E. £8 Post 95p
HEAD DEMAGNETISER PROBE **£5·00**

A.C. ELECTRIC MOTORS POST 75p.
2 Pole, 240V, ·2 Amp. Spindle – 1·43 × 0·212in. £1·75. 2 pole, 240V, ·15 Amp. Double spindle – 1·75 × 0·16in. Each £1. 2 Pole, 120V. ·5 Amp. Spindle – 0·75 × 0·2in. Two in series=240V. 50p each. Brush Motor. From a Food Mixer 240V, ·3 Amp. High Speed and Powerful. Spindle – 0·5 × 0.25in. £2·95

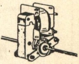

ALUMINIUM CHASSIS 18 s.w.g. Undrilled, 4 sides, riveted corners: 6 × 4 × 2½in. £1·20; 8 × 6 × 2½in. £1·50; 10 × 7 × 2½in. £1·90; 14 × 9 × 2½in. £2·50; 16 × 6 × 2½in. £2·40; 12 × 3 × 2½in. £1·50; 12 × 8 × 2½in. £2·20; 16 × 10 × 2½in. £2·70.
ALI ANGLE BRACKET 6 × ¾ × ¾in. 25p.
ALUMINIUM PANELS 18 s.w.g. 12 × 12in. £1·30; 14 × 9in. £1·20; 6 × 4in. 36p; 12 × 8in. 90p; 10 × 7in. 80p; 8 × 6in. 60p; 14 × 3in. 60p; 12 × 5in. 60p; 16 × 10in. £1·40; 16 × 6in. 90p.
ALUMINIUM BOXES, MANY SIZES IN STOCK.
4 × 2½ × 2in. £1.00; 3 × 2 × 1in. 80p; 6 × 4 × 2in. £1.30; 8 × 6 × 3in. £2.10 12 × 5 × 3in. £2.30; 6 × 4 × 3in. £1.60; 10 × 7 × 3in. £2.50.

HIGH VOLTAGE ELECTROLYTICS

8/800V	£1·20	50/500V	£1·20	32+32/350V	50p
16/500V	75p	220/450V	95p	32+32/500V	£1·80
32/500V	75p	8+16/450	75p	40+80/500V	£2
				16+32+32/500V	£2

DE LUXE BSR HI-FI AUTOCHANGER
Stereo Ceramic Cartridge
Plays 12in., 10in., or 7in records Auto or Manual. A high quality unit 240V AC.
Size 13½ × 11¼in.
Above motor board 3¼in.
Below motor board 2¼in.
£20 Post on All Decks £2.

BSR Single Player P207 cueing device, ceramic cartridge. £17 post £2
Garrard Single Player 730 SP metal turntable, cueing device, Snake arm, Magnetic cartridge. £27.50 post £2
BSR. C172. Slim arm. Metal Turntable Ceramic Head. Cueing Device Auto Stop £20 post £2
BSR Auto Changer. 11in. Turntable. Budget price. Stereo ceramic, reliable unit, 3-speed. £17·50 post £2
ISKRA. Disco Deck 3 speed stereo £9·95 or £18 pair post free

Rapid Mail Order 65p minimum postage. Callers Welcome.
Barclay – Access – Visa. Lists 30p. Closed Wed.
Radio Components Specialists
337, WHITEHORSE ROAD
CROYDON, SURREY, U.K. TEL: 01-684 1665.

TTLs by TEXAS

7400	11p
7401	12p
7402	12p
7403	12p
7404	14p
74S04	60p
7405	18p
7406	30p
7407	30p
7408	17p
7409	19p
7410	15p
7411	24p
7412	20p
7413	30p
7414	40p
74C14	60p
7416	27p
7417	27p
7420	17p
7421	30p
7422	22p
7423	34p
7425	30p
7426	30p
7427	30p
7428	30p
7430	17p
74L30	50p
7432	30p
7433	30p
7437	30p
7438	30p
7440	17p
7441	70p
7442A	60p
7443	112p
7444	112p
7445	75p
7446A	93p
7447A	60p
7448	80p
7450	17p
7451	17p
7453	17p
7454	17p
7460	17p
7470	36p
7472	30p
7473	30p
7474	24p
7475	30p
74L75	150p
7476	35p
7480	50p
7481	100p
7482	84p
7483A	70p
7484	100p
7485	100p
7486	30p
7489	210p
7490A	30p
7491	80p
7492A	46p
7493A	30p
7494	84p
7495A	60p
7496	60p
7497	180p
74100	100p
74104	65p
74105	65p
74107	34p
74109	55p
74110	55p
74111	70p
74116	100p
74118	100p
74119	120p
74120	100p
74121	28p
74122	48p
74123	48p
74125	55p
74126	60p
74128	75p
74132	60p
74136	60p
74141	50p
74142	200p
74145	90p
74147	120p
74148	100p
74150	100p
74151A	60p
74153	60p
74154	90p
74156	90p
74157	50p
74159	120p
74160	70p
74161	70p
74162	70p
74163	70p
74164	90p
74165	90p
74166	90p
74167	180p
74170	200p
74172	300p
74173	120p
74174	90p
74175	85p
74176	90p
74177	90p
74178	160p
74180	93p
74181	160p
74182	90p
74184A	150p
74185	150p
74186	500p
74190	90p
74191	90p
74192	90p
74193	90p
74194	90p
74195	95p
74196	95p
74197	80p
74198	150p
74199	150p
74221	100p
74C221	120p
74251	100p
74259	200p
74265	75p
74278	250p
74279	100p
74283	140p
74284	250p
74285	250p
74290p	150p
74293	150p
74294	200p
74298	200p
74365	60p
74366	60p
74367	60p
74368	60p
74390	140p
74393	140p
74490	225p

74LS SERIES

74LS00	14p
74LS02	14p
74LS04	14p
74LS05	22p
74LS08	22p
74LS10	20p
74LS11	25p
74LS13	30p
74LS14	50p
74LS20	20p
74LS21	25p
74LS27	30p
74LS30	20p
74LS32	27p
74LS33	30p
74LS38	30p
74LS42	60p
74LS47	60p
74LS55	30p
74LS73	30p
74LS74	27p
74LS75	40p
74LS76	45p
74LS83	70p
74LS85	80p
74LS86	40p
74LS90	50p
74LS93	50p
74LS107	45p
74LS112	100p
74LS123	60p
74LS124	180p
74LS125	45p
74LS126	45p
74LS132	60p
74LS133	60p
74LS136	50p
74LS138	55p
74LS139	55p
74LS151	100p
74LS153	60p
74LS154	200p
74LS155	90p
74LS157	50p
74LS158	90p
74LS160	90p
74LS161	75p
74LS162	90p
74LS163	60p
74LS164	75p
74LS165	120p
74LS166	150p
74LS173	110p
74LS174	100p
74LS175	90p
74LS181	320p
74LS190	80p
74LS191	80p
74LS192	80p
74LS193	80p
74LS195	90p
74LS196	90p
74LS221	90p
74LS240	140p
74LS241	120p
74LS242	120p
74LS243	120p
74LS244	120p
74LS245	150p
74LS251	90p
74LS253	75p
74LS257	90p
74LS259	120p
74LS266	90p
74LS273	130p
74LS367	50p
74LS373	120p
74LS374	120p
74LS378	100p
74LS393	120p

4000 SERIES

4000	18p
4001	22p
4002	20p
4006	95p
4007	25p
4008	80p
4009	40p
4010	50p
4011	22p
4012	18p
4013	40p
4014	84p
4015	84p
4016	45p
4017	60p
4018	89p
4019	45p
4020	90p
4021	110p
4022	100p
4023	20p
4024	50p
4025	20p
4026	130p
4027	50p
4028	84p
4029	100p
4030	55p
4031	200p
4033	180p
4034	200p
4035	110p
4040	100p
4041	80p
4042	80p
4043	90p
4044	90p
4046	110p
4047	100p
4048	55p
4049	45p
4050	45p
4051	80p
4052	80p
4053	80p
4054	150p
s4055	125p
4056	160p
4059	600p
4060	115p
4063	120p
4066	55p
4067	450p
4068	22p
4069	25p
4070	30p
4071	22p
4072	22p
4073	22p
4075	22p
4076	107p
4081	25p
4082	22p
4093	60p
4094	175p
4098	100p
4099	130p
4412	1100p
4502	120p
4503	70p
4507	55p
4510	90p
4511	90p
4514	250p
4516	110p
4518	90p
4520	100p
4521	250p
4528	100p
4532	140p
4534	550p
4536	375p
4538	140p
4543	180p
4553	320p
4560	250p
4569	180p
4583	120p
4584	75p
40097	90p
14433	1100p
14500	700p
14599	290p

INTERFACE ICs

DP8304	450p
MC1488	75p
MC1489	75p
58174	£14
75107	160p
75182	230p
75324	375p
74325	375p
75361	300p
75363	225p
75362	350p
75451	72p
75491/2	96p
8T26	160p
8T28	160p
8T95	160p
8T97	160p
81LS95	120p
81LS96	140p
81LS97	140p
81LS98	140p
9601	120p
9602	220p

★ SPECIALS ★

2114L (450ns)	£1.40
2716 (+5V)	£3.00
4116 (200ns)	£1.40

93 SERIES

9301	160p
9302	175p
9308	316p
9310	275p
8311	275p
9312	160p
9314	165p
9316	225p
9321	225p
9322	150p
9334	340p

LINEAR I.Cs

*AY1-0212	600p
*AY1-1313	668p
*AY1-1320	320p
*AY1-5050	140p
AY-3-8910	700p
AY3-8912	650p
AYS-1224A	240p
*CA3019	80p
CA3028A	90p
*CA3046	70p
*CA3048	225p
CA3080E	72p
RC4136	90p
*CA3089E	225p
*CA3090AQ	375p
CA3130E	100p
CA3140E	50p
CA3160E	100p
CA3161E	140p
CA3162E	450p
CA3189E	300p
FX209	750p
HA1388	260p
ICL7106	850p
ICL8038	300p
ICM7555	80p
LF351	45p
LF356	95p
LM301A	27p
LM311	70p
LM318	200p
LM319	200p
LM324	45p
LM339	75p
LM348	95p
*LM377	175p
*LM380	75p
*LM381AN	180p
LM386	95p
LM709	36p
LM710	50p
LM725	350p
LM733	100p
LM741	20p
LM747	70p
LM748	35p
LM2917	250p
LM3900	60p
LM3909	70p
LM3911	130p
LM3914	225p
LM3915	225p
LM3916	225p
LM4136	120p
LM13600	120p
MB3712	200p
*MC1310P	150p
MC1458	48p
MC1495L	350p
*MC1496	70p
*MC3340P	120p
MK50398	750p
MM57160	620p
NE531	150p
NE555	20p
NE555	20p
NE556	60p
NE564	420p
NE565	130p
NE566	155p
NE567	140p
*NE571	425p
NE5534A	250p
PLL02A	600p
RC4151	400p
S566B	270p
*SAD1024A	1250p
SFF96364	800p
SN76477	175p
TA7120	200p
TA7204	250p
TA7205	250p
TA7222	200p
TA7310	250p
*TAA621	275p
*TBA641B11	300p
*TBA651	200p
*TBA800	90p
*TBA810	100p
*TBA820	90p
*TCA940	175p
TC4500A	250p
*TDA1004A	300p
TDA1008	320p
TDA1010	225p
*TDA1022	600p
TDA1024	120p
TDA1034B	250p
TDA1170	300p
TDA2002V	325p
*TDA2020	320p
TL064	150p
TL071/81	45p
TL072/82	75p
TL074	130p
TL084	110p
TL170	50p
UAA170	175p
ULN2003	100p
UPC1156H	300p
XR2206	300p
*ZN414	90p
ZN419	225p
ZN424E	135p
ZN425E	400p
ZN427E-8	750p
ZN1034E	200p
95H90	800p

VEROBOARD

0.1
(copper clad)

2½ × 3¾	75p
2½ × 5	85p
3¾ × 3¾	85p
3¾ × 5	95p
3¾ × 17	380p
4¾ × 17	420p
Pkt of 100 pins	50p
Spot face cutter	85p
Pin insertion tool	99p

VERO WIRING PEN

Plus spool	325p
Spare spool (wire)	80p
Combes	7p each

VOLTAGE REGULATORS

Fixed Plastic TO-220

1A	+ve		−ve	
5V	7805	60p	7905	60p
12V	7812	60p	7912	60p
15V	7815	60p	7915	60p
18V	7818	60p	7918	70p
24V	7824	60p	7924	70p
100mA		TO-92		
5V	78L05	30p	79L05	70p
12V	78L12	30p	79L12	70p
15V	78L15	30p	79L15	70p

OTHER REGULATORS

LM309K	135p	TBA625B	120pp
LM317T	200p	TL430	65p
LM323K	500p	78H05KC	550p
LM723	37p	78MGT2C	140p

OPTO-ELECTRONICS

2N5777	45p	OCP71	130p
ORP12	90p	ORP60	90p
ORP61	90p	TIL78	55p
LEDS			
0.125"		0.2"	
TIL32	55p	TIL220 Red	16p
TIL209 Red	13p	TIL222 Gr	18p
TIL211 Gr	20p	TIL228 Red	22p
TIL212 Ye	25p	MV5491 TS	120p
TIL216 Red	18p	Clips	3p
DISPLAYS		FND500	120p
3015F	200p	FND507	120p
DL704	140p	MAN3640	175p
DL707 Red	140p	MAN4640A	200p
DL707 Gr	140p	TIL31	600p
DL747 Red	225p	TIL312/3	110p
DL747 Gr	225p	TIL321/2	130p
FND357	120p	TIL330	140p
DRIVERS		7750	200p
9368	250p	7760	200p
9370	250p	NSB5881CC	570p

COMPUTER BOOKS (NO VAT)

Introduction to Microcomputers Vol 0	595p
Introduction to Microcomputers Vol 1	630p
Micros-Interfacing Techniques	995p
TTI Cookbook	715p
C-MOS Cookbook	750p

Please add 70p p & p per book.

TRANSISTORS

AC126	25p
AC127/8	20p
AC176	25p
AC187/8	25p
AF116/7	50p
AD149	70p
AD161/2	45p
AU107	250p
BC107/8	11p
BC109	11p
*BC117	20p
*BC147/8	9p
*BC149	10p
*BC157/8	10p
*BC159	11p
*BC169C	12p
*BC172	12p
BC177/8	17p
BC179	18p
*BC182/3	10p
*BC184	11p
BC187	30p
*BC212/3	11p
*BC214	12p
BC461	36p
BC477/8	30p
*BC516/7	50p
*BC547B	16p
*BC549C	18p
*BC557B	16p
*BC559C	18p
BCY70	18p
BCY71/2	22p
BD131/2	50p
BD135/6	54p
BD139	56p
BD140	60p
BD189	60p
BD242	70p
BDY56	200p
BF115	36p
BF167	30p
BF173	30p
BF178	36p
BF200	32p
*BF244B	35p
*BF256B	70p
BF257/8	32p
BF259	36p
*BFR39	25p
*BFR40	25p
BFR41	25p
*BFR79	25p
*BFR80	25p
*BFR81	25p
BFX29	30p
BFX30	34p
BFX84/5	30p
BFX86/7	30p
BFX88	30p
BFW10	90p
BFY50	30p
BFY51/2	30p
BFY56	33p
BFY90	90p
BRY39	45p
BSX19/20	25p
BU104	225p
*BU105	190p
*BU108	250p
BU109	225p
*BU205	200p
*BU208	200p
*BU406	145p
*E300	50p
*E308	50p
J310	50p
MJ2501	225p
MJ2955	90p
MJ3001	225p
*MJE340	65p
MJE2955	100p
MJE3055	70p
*MPF102	45p
*MPF103/4	40p
*MPF105/6	40p
MPSA06	30p
*MPSA12	50p
*MPSA13	50p
MPSA43	50p
*MPSA20	50p
*MPSA56	32p
MPSA70	50p
*MPSU06	63p
MPSU65	78p
OC28	130p
OC35	130p
*R2008B	200p
*R20108	200p
*TIP29A	40p
*TIP29C	55p
*TIP30A	48p
*TIP30C	60p
*TIP31A	58p
TIP31C	62p
TIP32A	68p
TIP32C	82p
TIP33A	90p
TIP33C	114p
TIP34A	115p
TIP34C	160p
TIP35A	225p
TIP35C	290p
TIP36A	270p
TIP36C	340p
TIP41A	65p
TIP41C	78p
TIP42A	70p
TIP42C	82p
TIP2955	78p
TIP3055	70p
*TIS43	40p
TIP54	150p
*TIS93	30p
*ZTX108	12p
ZTX300	13p
ZTX500	15p
*ZTX502	18p
*ZTX504	30p
2N457A	250p
2N696	35p
2N697	25p
2N698	45p
2N706A	20p
2N918	35p
2N930	18p
2N1131	50p
2N1132	30p
2N1613	30p
N1711	30p
2N2102	60p
2N2160	300p
2N2219A	30p
2N2222A	30p
2N2369A	25p
2N2484	30p
2N2646	50p
2N2904/5	30p
2N2906A	24p
2N907A	30p
*2N2926	9p
2N3053	30p
2N3054	65p
2N3055	48p
2N3442	140p
2N3553	240p
*2N3565	30p
*2N3643/4	48p
*2N3663	20p
*2N3702/3	12p
*2N3704/5	12p
*2N3706/7	14p
*2N3708/9	12p
*2N3773	300p
*2N3819	25p
*2N3820	50p
2N3823	70p
2N3866	90p
*2N3903/4	18p
*2N3905/6	20p
2N4037	65p
2N4058/9	12p
*2N4060	12p
*2N4061/2	18p
*2N4123/4	27p
*2N4125/6	27p
*2N4401/3	27p
2N4427	90p
*2N4871	60p
*2N5087	27p
*2N5089	27p
2N5172	27p
2N5179	90p
2N5191	83p
2N5194	90p
*2N5245	40p
*2N5294	55p
*2N5401	50p
*2N5457/8	40p
*2N5459	40p
*2N5460	60p
2N5485	44p
*2N6027	48p
2N6247	190p
2N6254	130p
2N6292	65p
2SC1306	200p
2SC1939	300p
2SC2028	150p
2SC2029	300p
2SC2078	200p
3N128	120p
3N140	100p
3N141	110p
3N201	110p
3N204	120p
40290	250p
40361/2	45p
40409	100p
40410	100p
40411	300p
40594	120p
40595	120p
40673	75p
40871/2	100p

MEMORIES

2102-2L	120p
2107B	500p
2111-3	400p
2112-4	300p
2114 (25ons)	300p
2114 (45ons)	200p
4027	375p
4044	900p
4116	200p
5101	320p
6810	200p

ROM/PROMs

71301	700p
74S188	225p
74S287	350p
74S387	350p
74S471	700p
745571	650p
93427	400p
93436	650p
93446	650p
93448	900p

CPUs

CP1610	930p
1802	750p
2650A	£16
6502	550p
6800	400p
6802	650p
8080A	450p
8085A	650p
INS8060	£10
Z80	550p
Z80A	650p

EPROMs

1702A	650p
2708	300p
2716	400p

CRYSTALS

32.768KHz	250p
100KHz	300p
1.00MHz	320p
1.8432MHz	325p
2.00MHz	325p
2.476MHz	325p
3.2768MHz	300p
3.6864MHz	325p
4.00MHz	290p
4.1943MHz	300p
4.4336MHz	125p
5.00MHz	325p
6.00MHz	300p
6.144MHz	300p
8.00MHz	300p
8.867MHz	300p
10.00MHz	310p
10.70MHz	300p
16.00MHz	350p
18.00MHz	300p
18.432MHz	350p
19.968MHz	390p
27.145MHz	325p
38.6667MHz	350p

UART

AY 3 1015P	400p
AY 5 1013A	400p
IM6402	450p

CHARACTER GENERATORS

RO-3-2513UC	600p
RO-3-2513LC	650p
SN 74S262AN	£10

KEYBOARD ENCODER

AY-5 2376	£7

SUPPORT DEVICES

3242	800p
3245	450p
6522	600p
6532	800p
6821	200p
6850	200p
6852	325p
6875	600p
8154	990p
8155	850p
8205	320p
8212	200p
8216	200p
8224	250p
8226	275p
8228	300p
8251	450p
8253	800p
8255	450p
8257	800p
8259	800p
8279	950p
Z80P10	500p
Z80AP10	600p
Z80CTC	500p
Z80ACTC	600p
Z80DART	1200p
Z80ADART	1500p
Z80ADMA	1200p
Z80-510-1	2200p
MC14411	700p
MC14412	800p

SOFTY

Ideal hardware/software development tool. Kit **£100** + £1.50 P&P. Expansion board for programming +5V EPROMS. Ready built **£40.**

MINI FLOPPY DISC DRIVE

FD-50A 40 Track DOUBLE/SINGLE DENSITY 5¼" **£140**

EPROM ERASER

UV140 – Erasers up to 14 EPROMS in approx. 20 mins. Slide in tray for safety. Mains and Erase indicators. **£61.50**

ACORN ATOM

Full size Qwerty Keyboard, 2K Ram, 8K HYPER-ROM,

UHF TV output kit	£120
Ready-built	£150
Floating Point Rom.	£20

POWER SUPPLY UNIT

3 Amp, 5 Volts, Ready-built **£18**
(Suitable for fully loaded Acorn Atom and many other applications.)

EXPANSION PCB

Low price versatile system for UK101 and superboard. Compact memory expansion PCB. 8K RAM(2114) plus 4 Eprom sockets for 2708, 2716, 2732 Eproms. Plated thru holes. Fully bufferred and decoded lay-out. PCB **£17.50**
Interfacing instructions supplied.

LOW PROFILE DIL SOCKETS BY TEXAS

8 pin	9p	18 pin	16p	24 pin	20p
14 pin	10p	20 pin	18p	28 pin	26p
16 pin	11p	22 pin	20p	40 pin	30p

HEADER PLUGS

16 pin	60p
24 pin	90p
40 pin	275p

WIRE WRAP SOCKETS BY TEXAS

8 pin	25p	18 pin	50p	24 pin	70p
14 pin	35p	20 pin	60p	28 pin	80p
16 pin	40p	22 pin	65p	40 pin	100p

SUBMINIATURE SWITCHES

TOGGLE	
SPST	55p
SPDT	58p
DPDT	60p
DPDT (Centre off)	85p
Push to make	15p
break	25p
*SLIDE DPDT	18p
*ROCKER SPST	28p
***WAFER**	
1P/12W	45p
3P/4W	45p
4P/3W	45p
2P/6W	45p

DIL SWITCHES

4 way SPST	90p
8 way SPST	120p

ZERO FORCE INSERTION SOCKET

24 pin	£7

ANTEX SOLDERING IRONS

C-15W	415p
CX-17W	425p
CCN-15W	425p
X25	440p

SPARE BITS

C/CCN/CX	50pp
X25	50p

SPARE ELEMENTS

C/CX/X25	180p
CCN	200p
IRON STAND	160p

VEROBOARDS

DIP Breadboard
4·15" × 6·15" **325p**
(Suitable for 20 × 14 pin or 16 × 16 pin DIL ICs) DIP Breadboard as above with tracks for 31 way connector **375p**

CONNECTOR PLUGS

31 way Plug	120p
31 way Socket	120p
S-100 Busboard	£15

EDGEBOARD CONNECTORS 0.156" PITCH

2 × 10 way	85p	2 × 22 way	135p
2 × 15 way	100p	2 × 25 way	160p
2 × 18 way	120p		

COUNTERS

74C925	550p
ICM7217A	850p
ICM7216B	£20
ZN1040E	700p

CRT CONTROLLER

96364	£8
6845	£10
6847	£9.50
5027	£15

UK101: INTERFACING COMPUKIT
(Current PE)

HARDWARE:

Decoding Module Kit + PCB	£27.50 + VAT
Display Board Kit + PCB	£9.50 + VAT
Analogue Board Kit + PCB	£47.00 + VAT

The analogue Board kit includes D/A Converter, 8 Channel A/D Converter, AY-3-8910 Prog. Sound Generator, 6522 VIA giving timing and counting functions plus extra 16 bit port.

SOFTWARE:
C60 CASSETTE TAPE containing all the numbered programs of the series **£3.50** + VAT

FIRMWARE:
NEW LOW PRICED MONITOR
The CE1 Monitor in EPROM for the UK 101.
Contains Nigel Climpson's versatile Screen Editor described in PE plus Rapid Screen Clear, Checksum Load, Checksum Save and Audio Routines. **£9.95** + VAT

NEW RETAIL SHOP AT

**305 Edgware Rd.,
London W2**

VAT: Please add VAT at 15% on total order value. Access & Barclaycards Accepted.

Please add 30p p&p & VAT.

Government, Colleges, etc, Orders accepted.

CALLERS WELCOME Mon. Fri 9.30-5.30
Saturday 10.30-4.30

TECHNOMATIC LTD.

17 BURNLEY ROAD, LONDON NW10
(2 minutes Dollis Hill tube station) (ample street parking)
Tel: 01-452 1500 **Telex: 922800**

Published approximately on the 15th of each month by IPC Magazines Ltd., Westover House, West Quay Road, Poole, Dorset BH15 1JG. Printed in England by Chapel River Press, Andover, Hant
Sole Agents for Australia and New Zealand – Gordon & Gotch (A/sia) Ltd; South Africa – Central News Agency Ltd.
Subscriptions INLAND and OVERSEAS £11.80 payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex.

Practical Electronics is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at mo than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to VAT, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in an unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

THE VIDEO GENIE SYSTEM

deal for small businesses, schools, colleges, homes, etc. Suitable for the experienced, inexperienced, hobbyist, teacher, etc.

EG3000 Series

WITH NEW EXTRA KEYS!

6K
279
VAT

● 16K user RAM plus extended 12K Microsoft BASIC in ROM ● Fully TRS-80 Level II software compatible ● Huge ange of software already available ● Self contained, PSU, HF modulator, and cassette ● Simply plugs into video onitor or UHF TV ● Full expansion to disks and printer ● Absolutely complete — just fit into mains plug.

YOUR ZX80 IS NOW NO LONGER REDUNDANT

pgrade your ZX80 to the full animated graphics of the X81. (No screen flicker). **For only £12.95** + VAT, **in kit orm.** Works only in conjunction with **new** 8K ROM from inclair (not included).

WE ARE NOW STOCKING THE *AUTOSTART* APPLE II AT REDUCED PRICES

16K **£549**
32K **£579**
48K **£599**
+ VAT

etting Started APPLE II is faster, smaller, and more owerful than its predecessors. And it's more fun to use too ecause of built-in features like:
● BASIC — The Language that Makes Programming Fun. ● High-Resolution Graphics (in a 54,000-Point Array) for inely-Detailed Displays. ● Sound Capability that Brings rograms to Life. ● Hand Controls for Games and Other uman-Input Applications. ● Internal Memory Capacity of 8K Bytes of RAM, 12K Bytes of ROM; for Big-System Perormance in a Small Package. ● Eight Accessory Expansion lots to let the System Grow With Your Needs.

You don't need to be an expert to enjoy APPLE II. It is a omplete, ready-to-run computer. Just connect it to a video isplay and start using programs (or writing your own) the irst day. You'll find that its tutorial manuals help you make it our own personal problem solver.

NTRODUCING

THE NEW & *EXCITING* TRS80 MODEL III

16K **£559** + VAT 32K **£589** + VAT 48K **£619** + VAT

he Radio Shack TRS-80™ Model III is a ROM-based omputer system consisting of:
● A 12-inch screen to display results and other information ● A 65-key console keyboard for inputting programs and data o the Computer ● A Z-80 Microprocessor, the "brains" of he system ● A Real-Time Clock ● Read Only Memory ROM) containing the Model III BASIC Language (fully ompatible with most Model I BASIC programs) ● Random ccess Memory (RAM) for storage of programs and data hile the Computer is on (amount is expandable from "16K" o "48K", optional extra) ● A Cassette Interface for long-term torage of programs and data (requires a separate cassette ecorder, optional/extra) ● A Printer Interface for hard-copy utput of programs and data (requires a separate line printer, ptional/extra) ● Expansion area for upgrading to a diskased system (optional/extra) ● Expansion area for an RS-32-C serial communications interface (optional/extra)
ll these components are contained in a single moulded case, nd all are powered via one power cord.

EUROPE'S FASTEST SELLING ONE BOARD COMPUTER

COMPUKIT UK101

★6502 based system — best value for money on the market. ★Powerful 8K Basic — Fastest around ★Full Qwerty Keyboard ★4K RAM Expandable to 8K on board. ★Power supply and RF Modulator on board. ★No Extras needed — Plug-in and go ★Kansas City Tape Interface on board. ★Free Sampler Tape including powerful Dissassembler and Monitor with each Kit. ★If you want to learn about Micros, but didn't know which machine to buy then this is the machine for you.

Build, Understand and Program your own Computer for only a small outlay.

NEW ISSUE COMPUKIT WITH ALL THE FEATURES THAT MADE IT THE MOST PROFESSIONAL COMPUTER KIT ON THE MARKET. Now WITH FREE NEW EXTENDED MONITOR (a saving of £22), which includes Flashing Cursor, Screen Editing, & Save Data on Tape.

KIT ONLY **£149** + VAT

Fully Assembled — **£199** + VAT

DEALER ENQUIRIES INVITED

4K Upgrade Kit **£15.90** + VAT

NEW MONITOR IN ROM available separately **£22** + VAT
Revised BASIC 3 ROM — contains cure for GARBAGE collection routine — allows correct use of STRING ARRAYS. Suitable for Compukit or Superboard **£7.50** + VAT.

FOR THE COMPUKIT — Assembler Editor **£14.90** Screen Editor Tape **£1.90**
GAME PACKS — 1). Four Games **£5.00** 2). Four Games **£5.00** 3). Three Games 8K only **£5.00**
Super Space Invaders (8K) **£6.50** Space Invaders **£5.00** Chequers **£3.00** Realtime Clock **£3.00**
Case for Compukit **£29.50** 40 pin Expansion Jumper Cable **£8.50** All Prices exclusive VAT

NEW REDUCED PRICES

8K **£399**
16K **£449**
32K **£499**
+ VAT
RRP £795 for 32K

The PEDIGREE PETS

Very popular for home & business

use 8K Microsoft Basic in ROM 8K Pet 32K & 16K with new improved keyboard All with green screen

Cassette Deck **£55** extra Full range of software available

Interface PET IEEE — Centronics Parallel
Decoded **£77.00** + VAT

HITACHI PROFESSIONAL MONITORS

9" — ~~£129~~ **£99.95**
12" — ~~£199~~ **£149**

● **Reliability** Solid state circuitry using an IC and silicon transistors ensures high reliability. ● **500 lines horizontal resolution** Horizontal resolution in excess of 500 lines is achieved in picture center. ● **Stable picture** Even played back pictures of VTR can be displayed without jittering. ● **Looping video input** Video input can be looped through with built-in termination switch. ● **External sync operation** (available as option for U and C types) ● **Compact construction** Two monitors are mountable side by side in a standard 19-inch rack.

SPECIAL SCOOP

GET YOURSELF A NEW MX80 PRINTER AND SAVE A FORTUNE

only **£299** + VAT

Interface Cards for Apple, Pet, TRS80, Nascom and Compukit — RS232 Interface Cards not necessary for parallel. **£49** + VAT

Full TRS80/Genie Graphics including cables. Ready to go. **EX-STOCK.**

Now Available Fiction Feed Option **£49** + VAT

TEAC DISK DRIVES

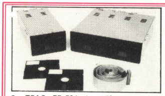

- TEAC FD-50A has 40 tracks giving 125K Bytes unformatted single density capacity.
- The FD-50A can be used in double density recording mode.
- The FD-50A is Shugart SA400 interface compatible.
- Directly compatible with Tandy TRS80 expansion interface.
- Also interfaces with Video Genie, SWTP, Heathkit, North Star Horizon, Superbrain, Nascom, etc, etc.
- Address selection for Daisy chaining up to 4 Disks.
- Disks plus power supply housed in an attractive grey case.

40 TRACK			
Single Disk Drive	**£225** + VAT	Double Disk Drive	**£389** + VAT
77 TRACK			
Single Disk Drive	**£299** + VAT	Double Disk Drive	**£499** + VAT

NOW AVAILABLE
PANASONIC KX-T1520 AUTOMATIC ANSWERING SYSTEM
£190 + VAT

LOW COST TELEPHONE ANSWERING MACHINE

only **£99.95** + VAT

Microprocessor controlled answering machine. Plug into your phone line. Records any phone call messages. Remote bleeper enables you to listen to your messages from anywhere in the world. Uses standard cassettes. Comes complete with mains adaptor, microphone, remote bleeper, base unit, cassette with 30 sample pre-recorded messages.

SHARP PC1211

£79.90 + VAT

COMPUTER POWER THAT ONCE FILLED A ROOM CAN NOW BE CARRIED IN YOUR POCKET!

● Programs in BASIC ● "QWERTY" Alphabetic Keyboard ● 1.9K Random Access Memory ● Long Battery Life.

Delivery is added at cost. Please make cheques and postal orders payable to **COMPSHOP LTD.**, or phone your order quoting **BARCLAYCARD, ACCESS, DINERS CLUB** or **AMERICAN EXPRESS** number.

MAIL ORDER AND SHOP: **CREDIT FACILITIES ARRANGED** — send S.A.E. for application form.

14 Station Road, New Barnet, Hertfordshire, EN5 1QW *(Close to New Barnet BR Station — Moorgate Line).*
Telephone: 01-441 2922 (Sales) 01-449 6596 Telex: 298755 TELCOM G
OPEN (BARNET) — 10am - 7pm — Monday to Saturday

NEW WEST END SHOWROOM:
311 Edgware Road, London W2. Telephone: 01-262 0387
OPEN (LONDON) — 10am - 6pm — Monday to Saturday

IRELAND: 80 Marlborough Street, Dublin 1. Telephone: Dublin 749933
COMPSHOP USA, 1348 East Edinger, Santa Ana, California, Zip Code 92705.
Telephone: 0101 714 5472526

TELEPHONE SALES
OPEN 24 hrs. 7 days a week
01-449 6596

"Europes Largest Discount Personal Computer Stores"

PE NOV 1981

MAPLIN make it easy...

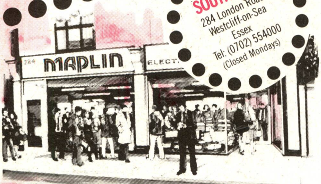

in
SOUTHEND
284 London Road
Westcliff-on-Sea
Essex
Tel: (0702) 554000
(Closed Mondays)

in
HAMMERSMITH
159-161 King Street
Hammersmith
London W6
Tel: 01-748 0926
(Closed Mondays)

For personal service visit one of our stores.
Our new store at Hammersmith is conveniently situated near the end of the M4 and the North and South Circular Roads.
There is excellent street parking on meters a few steps away and Hammersmith Underground Station is nearby. Call in and see us soon

in our
CATALOGUE
320 big pages packed with data and pictures of over 5,500 items

Over 100,000 copies sold already!
Don't miss out on your copy.
On sale now in all branches WH Smith price £1.
In case of difficulty check the coupon below.

by
MAIL ORDER
A fast service
You can rely on

- ✲ Same day service on in-stock lines
- ✲ Very large percentage of our stock lines in stock
- ✲ All prices include VAT
- ✲ Large range of all the most useful components
- ✲ First class reply paid envelope with every order
- ✲ Quality components—no rejects—no re-marks
- ✲ Competitive prices
- ✲ Your money is safe with a reputable company

On price, service, stock, quality and security it makes sense now more than ever to make MAPLIN your first choice for components every time!

make it easy... with MAPLIN

The
Maplin Matinée
Amazing value for only £299.95 plus £99.50 for cabinet if required

Easy to build, superb specification.
Comparable with organs selling for up to £1,000. Full construction details

Post this coupon now.
Please send me a copy of your 320 page catalogue. I enclose £1.25 (incl. 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name ____________________

Address ____________________

____

____

PE-7-81

MAPLIN ELECTRONIC SUPPLIES LTD.
All mail to: **P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 554155 Sales: (0702) 552911**